

# ECE 3040 Microelectronic Circuits

*Exam 3*

*April 18, 2002*

*Dr. W. Alan Doolittle*

Print your name clearly and largely:

*Solutions*

---

**Instructions:**

Read all the problems carefully and thoroughly before you begin working. You are allowed to use 1 new sheet of notes (1 page front and back), your note sheets from the previous exams as well as a calculator. There are 100 total points in this exam. Observe the point value of each problem and allocate your time accordingly. **SHOW ALL WORK AND CIRCLE YOUR FINAL ANSWER WITH THE PROPER UNITS INDICATED.** Write legibly. If I cannot read it, it will be considered a wrong answer. Do all work on the paper provided. Turn in all scratch paper, even if it did not lead to an answer. Report any and all ethics violations to the instructor. Good luck!

Sign your name on **ONE** of the two following cases:

---

I DID NOT observe any ethical violations during this exam:

---


I observed an ethical violation during this exam:

**First 25% Multiple Choice, True/False (Select the most correct answer)**

- 1.) (3-points) The gate current in the MOSFET is
- Highest under large positive gate bias
  - Highest under large negative gate bias
  - Is determined by the change in fermi level position at the semiconductor-oxide interface
  - Is always zero
  - Is zero except in inversion


- 2.) (3-points) A depletion mode PMOS transistor has a...
- ...p-type substrate.
  - ...n-type substrate
  - n-type channel when biased into cutoff (either depletion or accumulation)
  - huge gate current.

 - 3.) (4-points each, 12-points total) For the three transistor cross-sections I, II and III shown below, answer each of the three questions a-c:



- For  $V_{GS} > V_{DS} > 0$  which cross-sectional view (I, II or III) is correct. II
- For  $0 < V_{GS} < V_{GS} - V_t < V_{DS}$  which cross-sectional view (I, II or III) is correct. I
- For  $V_{GS} < 0$  and  $V_{DS} > 0$  which cross-sectional view (I, II or III) is correct. III

 - 4.) (4-points) Which energy band diagram corresponds to a PMOS capacitor biased into accumulation.



- 5.) (3-points) For a Transresistance amplifier designed for maximum gain (circle all that apply):
- You should have a high input impedance?
  - You should have a low input impedance?
  - You should have a high output impedance?
  - You should have a low output impedance?
  - The output is a voltage

Second 10% Short Answer:

p-type substrate

6.) (10 points) An NMOS transistor at room temperature has an oxide thickness of 1000 angstroms (1 angstrom =  $10^{-8}$  cm), determine the doping required to make the transistor begin conducting at 0.75 V. Use the following:

Substrate relative Dielectric Constant,  $\epsilon_{r\text{-semiconductor}} = K_S = 11.7$

Oxide relative Dielectric Constant,  $\epsilon_{r\text{-oxide}} = K_{ox} = 3.9$

Dielectric Constant of free space,  $\epsilon_0 = 8.854 \times 10^{-14}$  F/cm

Substrate intrinsic concentration,  $n_i = 1 \times 10^{10}$  cm $^{-3}$

Also recall that the total dielectric constant of the semiconductor is:  $\epsilon_s = \epsilon_{r\text{-semiconductor}} \epsilon_0$  while the total dielectric constant for the oxide is:  $\epsilon_{ox} = \epsilon_{r\text{-oxide}} \epsilon_0$

$$C_{ox} = \frac{\epsilon_{ox}}{x_{ox}} = \frac{3.9(8.854 \times 10^{-14})}{1000 \times 10^{-8} \text{ cm}} = \frac{1}{q} \ln \left( \frac{N_A}{n_i} \right)$$

$$= 3.45 \times 10^{-8} \text{ F/cm}^2 \Rightarrow 0.0259 \ln \left( \frac{N_A}{1 \times 10^{10}} \right)$$

$$V_T = 2\phi_F + \frac{\epsilon_{si}}{C_{ox}} \sqrt{\frac{2qN_A}{\epsilon_s} (2\phi_F)}$$

$$0.75 = 2\phi_F + \frac{11.7(8.854 \times 10^{-14}) \text{ F/cm}}{3.45 \times 10^{-8} \text{ F/cm}^2} \sqrt{\frac{2(1.6 \times 10^{-19}) N_A (2)\phi_F}{(11.7)(8.854 \times 10^{-14}) \text{ F/cm}}}$$

$$0.75 = 2\phi_F + 3 \times 10^{-5} \sqrt{(6.178 \times 10^{-7}) \phi_F N_A}$$


$V_T$	$\phi_F$	$N_A$
1.003	0.298	$1 \times 10^{15}$
0.592	0.239	$1 \times 10^{14}$
0.839	0.280	$5 \times 10^{14}$
0.716	0.262	$2.5 \times 10^{14}$
0.745	0.267	$3 \times 10^{14}$
0.750	0.268	$3.1 \times 10^{14}$

$$N_A \sim 3.1 \times 10^{14} \text{ cm}^{-3}$$


**Problems (3<sup>rd</sup> 20%)**

 7.) You may assume that the Op-Amps are ideal.

- a.) (15-points) Determine an equation relating the output voltage,  $V_{out}$  in terms of the three input voltages,  $V_{in1}$ ,  $V_{in2}$ ,  $V_{in3}$ .
- b.) (5-points) Determine the input impedance seen by the source  $V_{in3}$ .




 Extra work can be done here, but clearly indicate with problem you are solving.



Using Superposition:

step 1: Let  $v_{in2} = v_{in3} = 0$

 


voltage divider on + input

$$v_{out} = v_{in1} \left( \frac{R_2}{R_1 + R_2} \right) \left( 1 + \frac{R_F}{R_3} \right)$$

Non-inverting stage


step 2: Let  $v_{in1} = v_{in3} = 0$

 

$$v_{out} = v_{in2} \left( \frac{R_1}{R_1 + R_2} \right) \left( 1 + \frac{R_F}{R_3} \right)$$

step 3:

(let  $v_{in2} = v_{in1} = 0$ )

 

$$v_{out} = v_{in3} \left( -\frac{R_F}{R_3} \right)$$

$$v_{out} = v_{in1} \left( \frac{R_2}{R_1 + R_2} \right) \left( 1 + \frac{R_F}{R_3} \right) + \dots$$

$$\dots v_{in2} \left( \frac{R_1}{R_1 + R_2} \right) \left( 1 + \frac{R_F}{R_3} \right) + \dots$$


$$\dots \left( -v_{in3} \frac{R_F}{R_3} \right)$$

Extra work can be done here, but clearly indicate with problem you are solving.

$$v_{out} = v_{in_1} \left( \frac{3}{5} \right) (10) + v_{in_2} \left( \frac{2}{5} \right) (10) - v_{in_3} \cdot 9$$

$$v_{out} = 6v_{in_1} + 4v_{in_2} - 9v_{in_3}$$

R<sub>in3</sub>

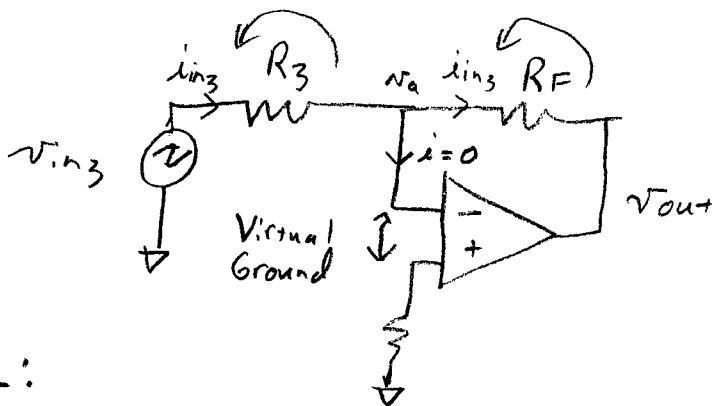

Method 1:

Since the virtual ground assures  $v_a = 0$ ,  $R_{in3} = R_3$  or

Method 2: 
$$v_{out} + i_{in3}(R_F + R_3) = v_{in3}$$

$$+ v_{out} = - \frac{R_F}{R_3} v_{in3}$$

$$\Rightarrow - \frac{v_{in3} R_F}{R_3} + (R_F + R_3) i_{in3} = v_{in3}$$

$$v_{in3} \left( 1 + \frac{R_F}{R_3} \right) = i_{in3} (R_F + R_3)$$


$$R_{in3} = \frac{v_{in3}}{i_{in3}} = \frac{R_3}{R_F + R_3} (R_F + R_3)$$

$$R_{in3} = R_3$$

Pulling all the concepts together for a useful purpose: (4<sup>th</sup> portion)

 8.) **(45-points)** Given the following circuit, what is the AC voltage gain,  $V_{out}/V_{inAC}$ ? You may assume all capacitors have infinite capacitance and are thus, AC shorts. Additionally consider the circuit to be operated at low frequencies where you can neglect all small signal capacitances. Grading will be based as such: 20 points for DC solution ( $V_{GS}$ ,  $V_{DS}$  along with  $I_{DS}$  for both transistors), 5 points for the conversion to the small signal model and 20 points for the small signal analysis.

Hint: Assume and then verify that both transistors are saturated. If M2 is saturated, identify its functionality (i.e. what is M2 being used for) in the DC circuit. Do not panic! Performing this identification will make the AC solution easier but is not necessary to get the correct answer.



Use the following parameters:

For NMOS Depletion Transistors:

$M2 \rightarrow K_n' = 20 \mu A/V^2$   $V_T = -1.0V$   $\lambda = 0.0 V^{-1}$  Length (L) = 1  $\mu m$  Width (W) = 100  $\mu m$

For NMOS Enhancement Transistors:

$M1 \rightarrow K_n' = 20 \mu A/V^2$   $V_T = 1.0V$   $\lambda = 0.0 V^{-1}$  Length (L) = 1  $\mu m$  Width (W) = 100  $\mu m$

For PMOS Depletion Transistors:

$K_p' = 40 \mu A/V^2$   $V_T = +3.0V$   $\lambda = 0.1 V^{-1}$  Length (L) = 10  $\mu m$  Width (W) = 10  $\mu m$

For PMOS Enhancement Transistors:

$K_p' = 40 \mu A/V^2$   $V_T = -3.0V$   $\lambda = 0.1 V^{-1}$  Length (L) = 10  $\mu m$  Width (W) = 10  $\mu m$

Extra work can be done here, but clearly indicate with problem you are solving.

DC solution:

M1  $\Rightarrow$  NMOS Enhancement  $\lambda = 0, \mu_n = 200 \text{ cm}^2/\text{Vs}, V_{TN} = 1$

M2 = NMOS Depletion  $\lambda = 0, \mu_n = 200 \text{ cm}^2/\text{Vs}, V_{TN} = -1$

M2 is always saturated, (Note  $V_{DS} > V_{GS} - V_T$    
  $> 0 - (-1)$    
  $\rightarrow$  always positive)


$$\underline{I_{D_{S2}} = I_{D_{S1}} = \frac{\mu_n}{2} \left(\frac{W}{L}\right) (V_{GS} - V_T)^2 (1 + \lambda V_{DS})}$$

$$= \frac{200 \text{ cm}^2/\text{Vs}}{2} \left(\frac{100 \mu\text{m}}{1 \mu\text{m}}\right) (0 - (-1))^2 (1 + 0)$$

$$\boxed{I_{D_{S2}} = I_{D_{S1}} = 1 \text{ mA}}$$

$$1 \text{ mA} = I_{D_{S1}} = \left(\frac{200 \text{ cm}^2/\text{Vs}}{2}\right) \left(\frac{100 \mu\text{m}}{1 \mu\text{m}}\right) (V_{GS} - 1)^2 (1 + 0)$$

$$1 = (V_{GS} - 1)^2$$

 

$$V_{GS} - 1 = 1$$

$$V_{GS} = 2 \text{ V}$$

$$V_{DS} = 12 - (-2 \text{ V}) = 14 \text{ V}$$

M1 Saturation assumption is verified:

$$(V_{DS} > V_{GS} - V_{TN}) \Rightarrow (14 > (2 \text{ V} - 1 \text{ V}))$$

M2:

$$V_{DS} = 10 \text{ V}$$

$$V_{GS} = 0$$

$$I_{DS} = 1 \text{ mA}$$

$$V_{D2} = -2 \text{ V} \quad V_{S2} = -12 \text{ V}$$

$$V_{DS} = -2 \text{ V} - (-12) = 10 \text{ V}$$

$$V_{DS} > V_{GS} - V_{TN}$$


$$10 \text{ V} > 0 - (-1)$$

$10 \text{ V} > 1 \Rightarrow$  Assumption Verified




Extra work can be done here, but clearly indicate with problem you are solving.

## AC Solution:

 


M2  
Makes a DC  
Current source and thus  
is an AC open circuit

 Saturated  
with  $V_{GS} = \text{constant}$   
 $I_{DS} = \text{constant}$



 If you did not recognize  
M2 forms a current source



reduces to

current through  $R_L$

$$v_{in} = v_{gs1} + (g_{m1} v_{gs1}) R_L$$

$$= v_{gs1} (1 + g_{m1} R_L)$$


$$\frac{v_{gs1}}{v_{in}} = \frac{1}{1 + g_{m1} R_L} = \frac{1}{1+2} = \frac{1}{3}$$

$$v_{out} = g_{m1} v_{gs1} R_L$$

$$\frac{v_{out}}{v_{gs1}} = g_{m1} R_L = 2$$

$$A_v = \left( \frac{v_{out}}{v_{gs1}} \right) \left( \frac{v_{gs1}}{v_{in}} \right) = \frac{g_{m1} R_L}{1 + g_{m1} R_L} = \frac{2}{3} \text{ V/V}$$

 Bonus: (10-points - Absolutely no partial credit) Determine an expression for ~~and sketch the frequency~~  
the transfer voltage gain,  $V_o/V_i$ .



By superposition,

$$v_{out} = \left( \frac{R}{R + \frac{1}{Cs}} \right) \left( 1 + \frac{R_1}{R_1} \right) v_{in} - \frac{R_1}{R_1} v_{in}$$

Voltage divider  
on + input

$$\begin{aligned} \frac{v_{out}}{v_{in}} &= \frac{2RCs}{1+RCs} - 1 \\ &= \frac{2RCs - (RCs+1)}{1+RCs} \end{aligned}$$

$$\frac{v_{out}}{v_{in}} = \frac{RCs - 1}{RCs + 1} \quad v/v$$