

10:13
10:10

ECE 3040 Microelectronic Circuits

Exam 3

April 19, 2006

Dr. W. Alan Doolittle

Print your name clearly and largely:

Solutions

Instructions:

DO NOT TAKE APART ANY PAGES OF THIS EXAM AND SHOW ALL WORK ON THE PROVIDED PAGES. Read all the problems carefully and thoroughly before you begin working. You are allowed to use 1 new sheet of notes (1 page front and back), your note sheet from the previous exams as well as a calculator. There are 100 total points in this exam. Observe the point value of each problem and allocate your time accordingly. **SHOW ALL WORK AND CIRCLE YOUR FINAL ANSWER WITH THE PROPER UNITS INDICATED.** Write legibly. If I cannot read it, it will be considered a wrong answer. Do all work on the paper provided. Turn in all scratch paper, even if it did not lead to an answer. Report any and all ethics violations to the instructor. Good luck!


Sign your name on **ONE** of the two following cases:

I DID NOT observe any ethical violations during this exam:

I observed an ethical violation during this exam:

First 20% Multiple Choice and True/False (Select the most correct answer)

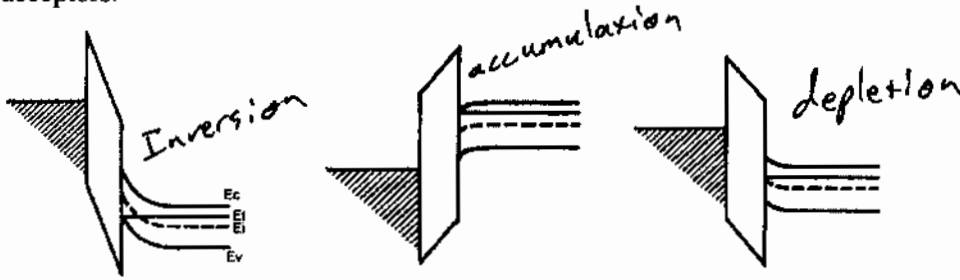1.) (3-points total) In each of the three cases shown below indicate whether the charge at the oxide/semiconductor interface is predominately p-type, n-type, ionized donors or ionized acceptors.




- (A) p-type (B) n-type (C) ionized donors

2.) (2-points) True/False: The Gate-Source overlap capacitance (not the gate input capacitance) results in an increase in gain at high frequencies.

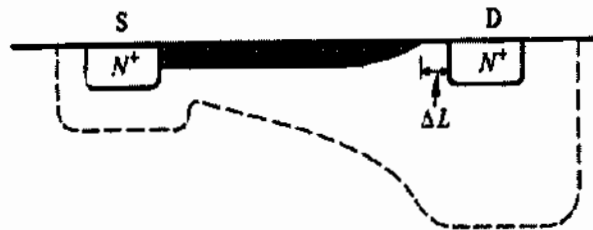* 3.) (2-points) In the MOSFET transistor to the right, what is the voltage across the pinched off region?

- a.) $V_G - V_T$
- b.) V_{DS}
- c.) V_{D-sat}
- d.) $V_G - V_{Sat}$
- e.) Not enough information given to solve



4.) (2-points) True/False: A well designed transresistance amplifier should have a very high input resistance.

$\rightarrow \frac{V_{out}}{I_{in}} \rightarrow \text{Low } R_{in}$

5.) (3-points) Which of the following is true of feedback circuits.

- a.) Feedback in a voltage amplifier can increase the input resistance
- b.) Feedback in a voltage amplifier can decrease the output resistance
- c.) Feedback in a voltage amplifier can decrease the input resistance
- d.) Feedback in a voltage amplifier can increase the output resistance
- e.) Feedback in a voltage amplifier can increase the amplifier bandwidth if the open loop gain is larger than the closed loop gain
- f.) Feedback in a voltage amplifier can decrease the amplifier bandwidth if the open loop gain is larger than the closed loop gain
- g.) There are too many answers here for a measly 3 point problem

Short Answer

6.) (4-points) Your brilliant professor has developed a new device that has a DC IV characteristic of:

$$I_{\text{lan}} = 3 V_{\text{doo}} - 4 V_{\text{little}} \quad \text{and} \quad I_{\text{dr}} = 5 V_{\text{doo}} - 6 V_{\text{little}}$$

The bias voltages of the new device are $V_{\text{doo}} = 7 \text{ V}$ and $V_{\text{little}} = 8 \text{ V}$. Determine all four y-parameters for the small signal model of this new device. Be sure to show your work.

~~Handwritten scribbles~~

~~Handwritten scribbles~~


$$y_{11} = \left. \frac{\partial I_{\text{lan}}}{\partial V_{\text{doo}}} \right|_Q = 3$$

$$y_{12} = \left. \frac{\partial I_{\text{lan}}}{\partial V_{\text{little}}} \right|_Q = -4$$

$$y_{21} = \left. \frac{\partial I_{\text{dr}}}{\partial V_{\text{doo}}} \right|_Q = 5$$

$$y_{22} = \left. \frac{\partial I_{\text{dr}}}{\partial V_{\text{little}}} \right|_Q = -6$$

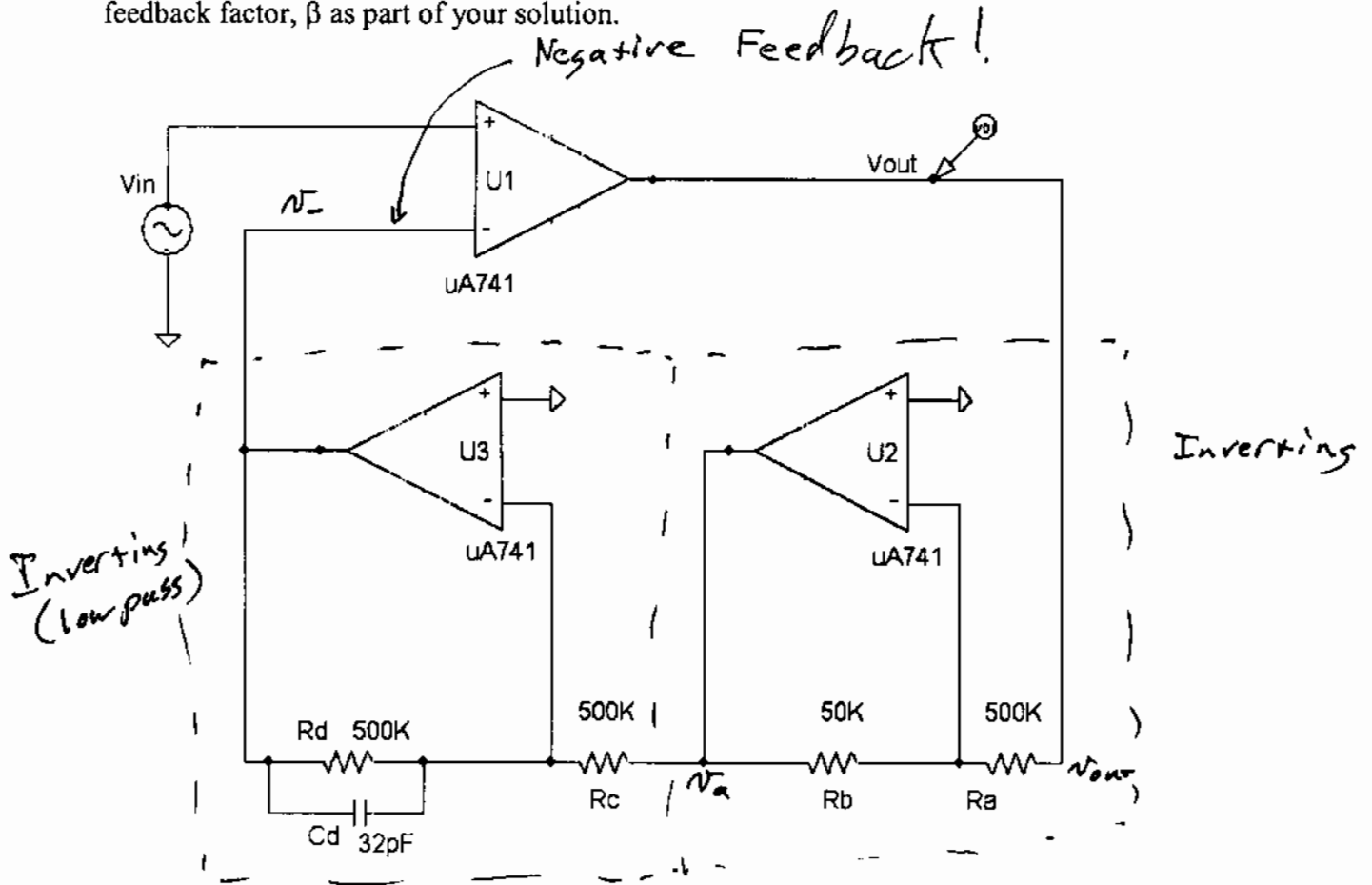7.) (20-points) Sketch and label all break frequencies, the voltage gain in flat regions in a Bode plot (gain in dB vs Log(frequency)). You may assume that the Op-Amps are ideal. To receive full credit the asymptotes and an estimate of the actual gain curve should BOTH be sketched on the same plot. Hint: you may find it helpful to determine the feedback factor, β as part of your solution.



$$\beta = \frac{v_-}{v_{out}} \quad \text{and} \quad \frac{v_{out}}{v_{in}} = \frac{A_{openloop}}{(1 + \beta A_{openloop})}$$

Determine β

$$\frac{v_a}{v_{out}} = -\frac{R_b}{R_a} = -\frac{50k}{500k} = -0.1 \text{ V/V}$$

$$= \frac{1}{\beta} \quad (\text{since } A_{openloop} = \infty)$$


$$\frac{v_-}{v_a} = -\frac{R_d \parallel \frac{1}{Cs}}{R_c} = -\frac{R_d \frac{1}{Cs}}{R_d + \frac{1}{Cs}} = \frac{-1}{R_c} \left(\frac{1}{1 + R_d Cs} \right)$$

$$\therefore \frac{1}{\beta} = \left(\frac{v_{out}}{v_a} \right) \left(\frac{v_a}{v_-} \right) = (-0.1) \left(\frac{1 + R_d Cs}{-1} \right)$$

$$\frac{v_{out}}{v_{in}} = \frac{1}{\beta} = +10 (1 + R_d Cs)$$

Low pass

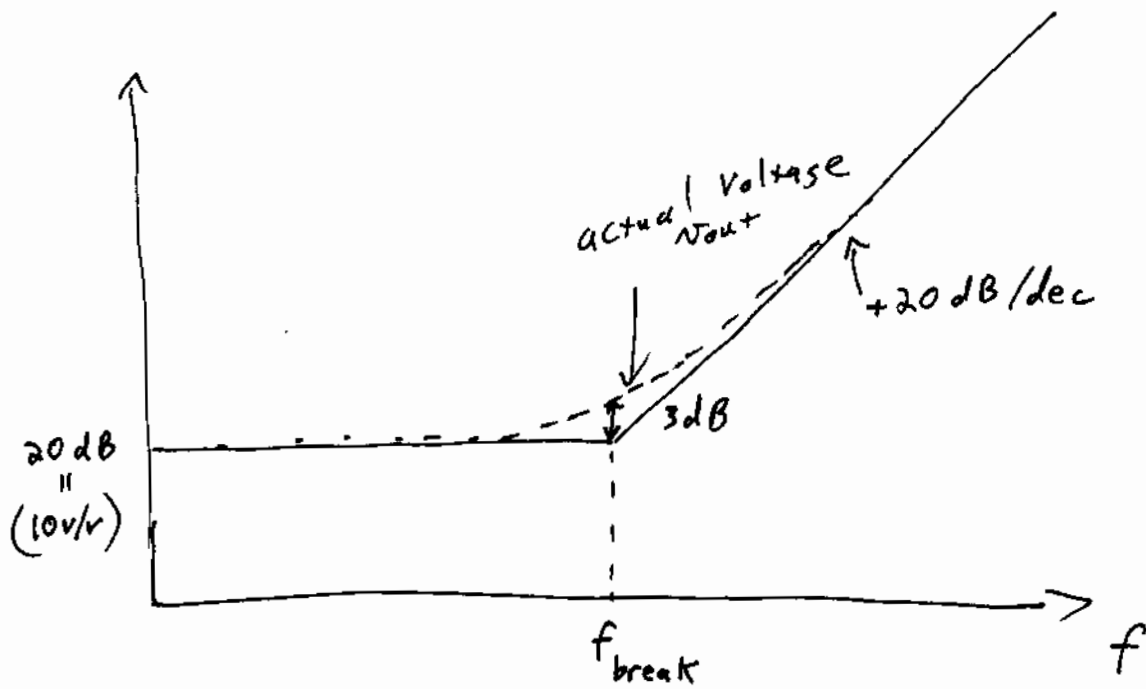
Extra work can be done here, but clearly indicate with problem you are solving.



$$f_{\text{break}} = \frac{1}{2\pi R_0 C_d} = 9,947\text{ Hz}$$

7.) (20-points) Sketch and label all break frequencies, the voltage gain in flat regions in a Bode plot (gain in dB vs Log(frequency)). You may assume that the Op-Amps are ideal. To receive full credit the asymptotes and an estimate of the actual gain curve should BOTH be sketched on the same plot. Hint: you may find it helpful to determine the feedback factor, β as part of your solution.

Alternative Solution 1

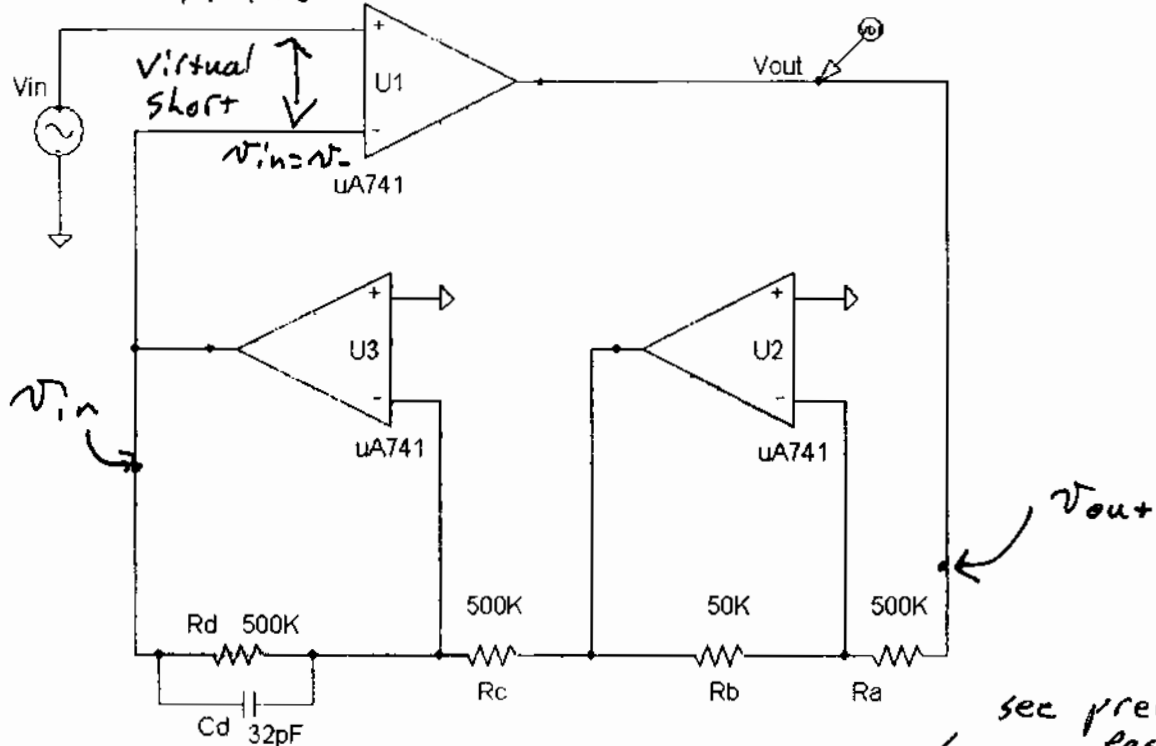

$$v'_{in} = v'_{out}$$

$$\left(\frac{R_b}{R_a} \right) \left[\left(\frac{1}{1 + R_d C_d s} \right) \left(\frac{-R_d}{R_c} \right) \right]$$


see previous page for more detail

$$\frac{v_{out}}{v_{in}} = 10 (1 + R_d C_d s)$$

Note: The virtual short exists because β is positive ^{thus} feedback overall is negative.

7.) (20-points) Sketch and label all break frequencies, the voltage gain in flat regions in a Bode plot (gain in dB vs Log(frequency)). You may assume that the Op-Amps are ideal. To receive full credit the asymptotes and an estimate of the actual gain curve should BOTH be sketched on the same plot. Hint: you may find it helpful to determine the feedback factor, β as part of your solution.

Alternative solution 2

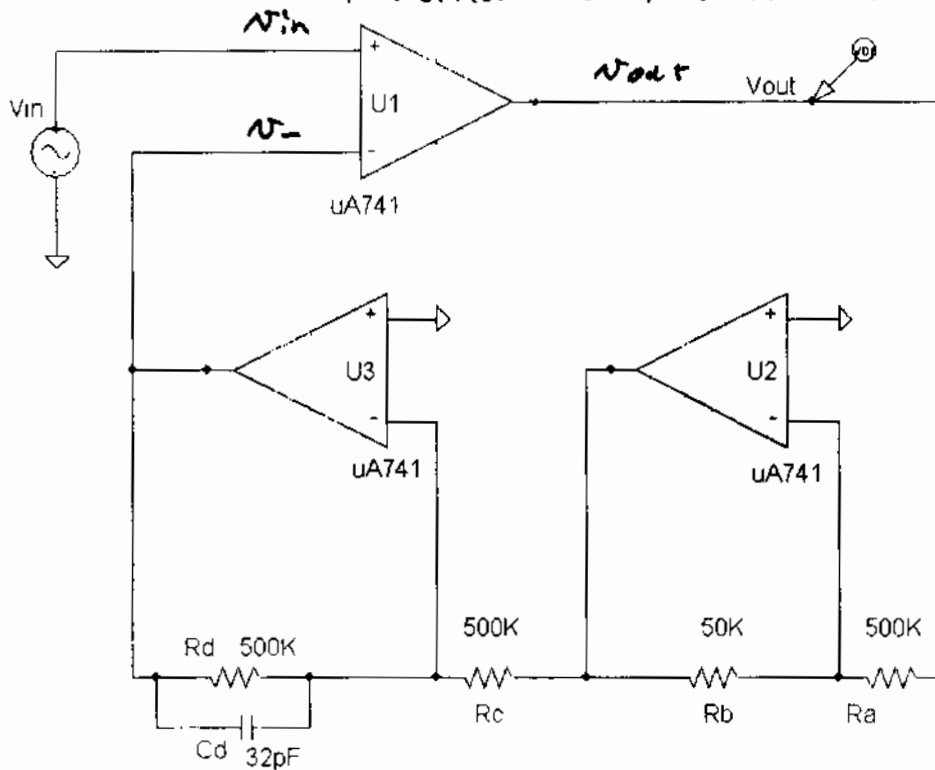

$$v_{out} = A (v_{in} - v_{-})$$

$$\text{but, } v_{-} = v_{out} \left(\frac{-R_b}{R_a} \right) \left(\frac{-R_d \parallel \frac{1}{Cs}}{R_c} \right)$$

$$= v_{out} (-0.1) \left(\frac{-R_d}{R_c (1 + R_d C_d s)} \right)$$

$$v_{-} = v_{out} (0.1) \left(\frac{1}{1 + R_d C_d s} \right)$$


$$v_{out} = A v_{in} - A \frac{0.1}{1 + R_d C_d s} v_{out}$$

$$v_{out} \left(1 + \frac{0.1 A}{1 + R_d C_d s} \right) = A v_{in}$$

$$\frac{v_{out}}{v_{in}} = \frac{A}{1 + \frac{0.1 A}{1 + R_d C_d s}} \Rightarrow A \rightarrow \infty \Rightarrow \frac{v_{out}}{v_{in}} = (1 + R_d C_d s)$$

Pulling all the concepts together for a useful purpose:

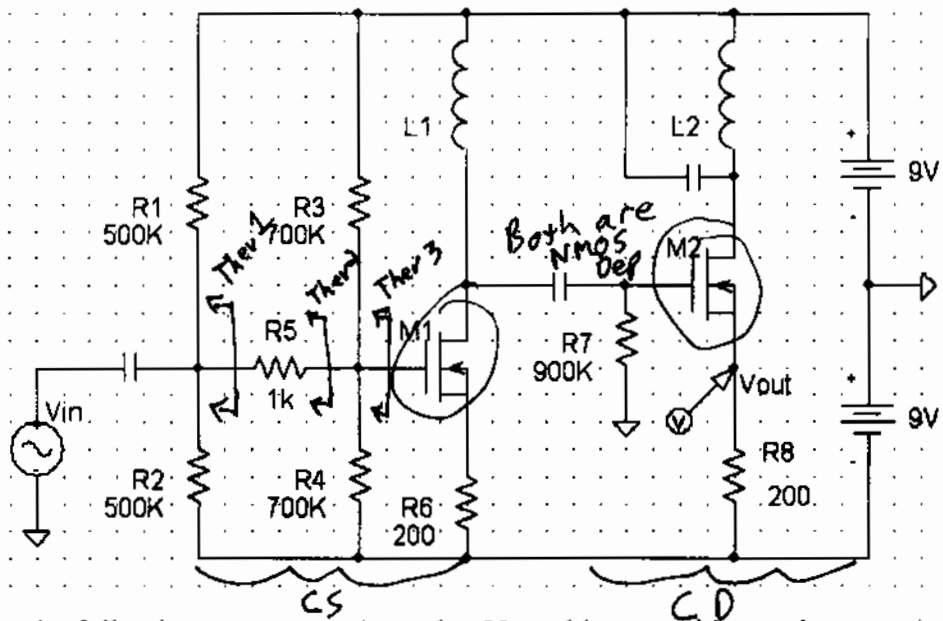8.) (50-points) Given the following circuit, (a) Identify the configuration of the two stages (common ____). (b) What is the AC voltage gain, V_{out}/V_{in} ? You may assume all capacitors have infinite capacitance. You may assume all inductors have infinite inductance. Additionally consider the circuit to be operated at low frequencies where you can neglect all small signal capacitances. Grading will be based as such: part a=5 points, part b=18 points for DC solution (gate, source and drain voltages along with drain current), 9 points for the conversion to the small signal model and 18 points for small signal analysis.



Use the following parameters (note that V_T and λ vary with transistor type):

For NMOS Depletion Transistors:

$K_n' = 20 \mu\text{A}/\text{V}^2$ $V_T = -4.0\text{V}$ $\lambda = 0.0 \text{V}^{-1}$ Length (L)=10 μm Width (W)=10 μm $K_n = 20 \mu\text{A}/\text{V}^2$

For NMOS Enhancement Transistors:

$K_n' = 30 \mu\text{A}/\text{V}^2$ $V_T = +0.75\text{V}$ $\lambda = 0.1 \text{V}^{-1}$ Length (L)=10 μm Width (W)=10 μm

For PMOS Depletion Transistors:

$K_n' = 40 \mu\text{A}/\text{V}^2$ $V_T = +3.0\text{V}$ $\lambda = 0.0 \text{V}^{-1}$ Length (L)=10 μm Width (W)=10 μm

For PMOS Enhancement Transistors:

$K_n' = 50 \mu\text{A}/\text{V}^2$ $V_T = -1.75\text{V}$ $\lambda = 0.1 \text{V}^{-1}$ Length (L)=10 μm Width (W)=10 μm

Extra work can be done here, but clearly indicate with problem you are solving.


DC Solution
Stage 1

Should notice that $R_1 + R_3$ are symmetric with $R_2 + R_4 \Rightarrow V_{G_{M1}} = 0$ but assuming you did not.


Thevenin 1 (see drawings):

$$V_{th} = 0V \quad R_{th} = 250k$$

Thevenin 2:

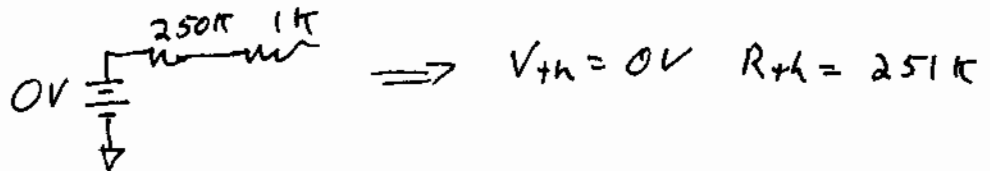


Thevenin 3:

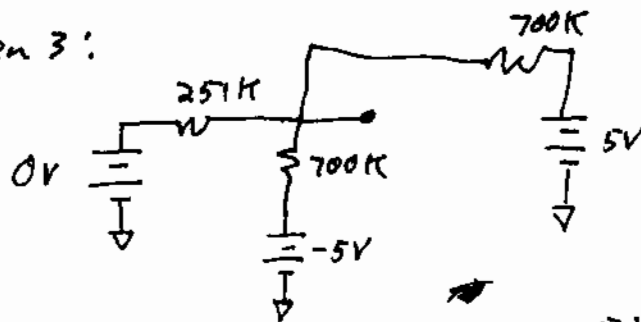

$$V_{th} = (5) \frac{251k \parallel 700k}{251k \parallel 700k + 700k} + (-5) \frac{251k \parallel 700k}{251k \parallel 700k + 700k} = 0$$
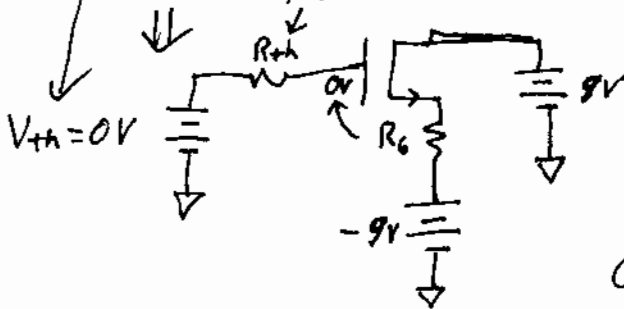
$$R_{th} = 700k \parallel 700k \parallel 251k$$



Assume Saturation

$$I_{os} = \frac{1}{2} k_n (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$0 = V_{GS} - 9V + I_{os} R_6$$

$$V_{GS} = 9 - I_{os} R_6$$

$$\Rightarrow I_{os} = \frac{1}{2} k_n (9 - I_{os} R_6 - V_{TH})^2$$

$$= \frac{1}{2} k_n (9 - I_{os} R_6)^2$$

$$= \frac{1}{2} k_n (81 - 18 I_{os} R_6 + I_{os}^2 (R_6)^2)$$

Extra work can be done here, but clearly indicate with problem you are solving.

$$I_{D5} = \frac{1}{2} K_n (169 - 26 I_{D5} R_6 + I_{D5}^2 (R_6)^2)$$

$$0 = \frac{1}{2} K_n 169 - \left(1 + \frac{1}{2} K_n (26) R_6\right) I_{D5} + \frac{1}{2} K_n R_6^2 I_{D5}^2$$

$$= 0.00169 - I_{D5} (1.052) + 0.4 I_{D5}^2$$

$$= c + b I_{D5} + a I_{D5}^2$$

$$I_{D5} = \frac{1.052 \pm \sqrt{(1.052)^2 - 4(0.4)(0.00169)}}{2(0.4)}$$

$$= \frac{1.052 \pm (1.0507)}{0.8}$$

$$I_{D5} = 2.6 \text{ Amps or } 1.607 \text{ mA}$$

Check assumption:

$$-9 + I_{D5} R_6 + V_{D5} = 9V \quad \text{and } V_{G5} = 9 - I_{D5} R_6$$


$$V_{D5} = 18 - I_{D5} 200$$

$$\rightarrow 17.67V \rightarrow V_{G5} - V_T = 8.67 + 4 = 12.67V$$

$$\text{or } V_{D5} = -502V$$

Assumption Verified

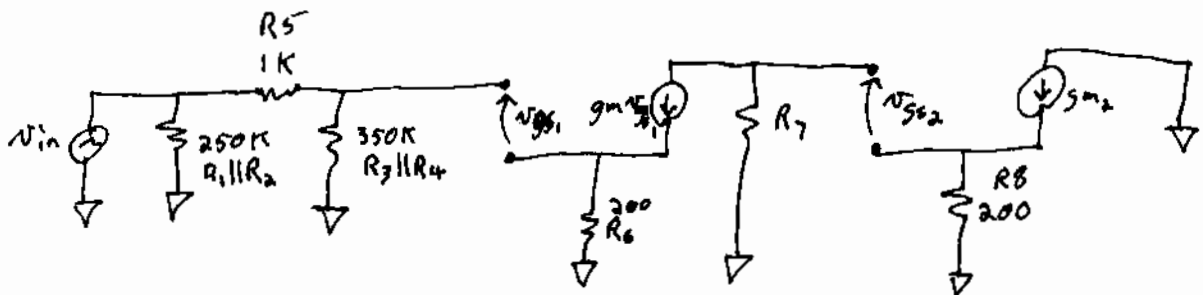Note: Stage 2 DC solution is impossible
Conversion: Identical!!




$$g_{m1} = g_{m2} = \frac{I_{D5}}{\left(\frac{V_{G5} - V_T}{2}\right)} = \frac{1.607 \text{ mA}}{\frac{1}{2}(12.67)} = 0.000253$$

$$r_{o1} = r_{o2} = \infty$$

Extra work can be done here, but clearly indicate with problem you are solving.
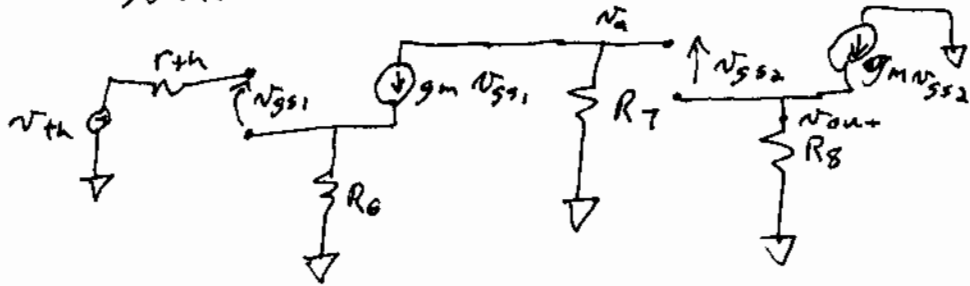
$$v_{th} = \frac{350K}{351K} v_{in} \quad r_{th} = 1K \parallel 350K$$



$$1) \quad v_{zh} = v_{gs1} + g_m v_{gs1} R_6$$

$$\frac{v_{zh}}{v_{gs1}} = (1 + g_m R_6)$$

$$2) \quad v_a = -g_m v_{gs1} R_7$$

$$\frac{v_a}{v_{gs1}} = -g_m R_7$$

$$3) \quad v_a = v_{gs2} + R_8 g_m v_{gs2}$$

$$\frac{v_a}{v_{gs2}} = (1 + g_m R_8)$$

$$4) \quad v_{out} = g_m v_{gs2} R_8$$

$$\frac{v_{out}}{v_{gs2}} = g_m R_8$$

$$\begin{aligned} \frac{v_{out}}{v_{in}} &= \left(\frac{v_{gs1}}{v_{th}} \right) \left(\frac{v_{zh}}{v_{gs1}} \right) \left(\frac{v_a}{v_{gs1}} \right) \left(\frac{v_{gs2}}{v_a} \right) \left(\frac{v_{out}}{v_{gs2}} \right) \\ &= \left(\frac{350}{351} \right) \left(\frac{1}{1 + g_m R_6} \right) \left(-g_m R_7 \right) \left(\frac{1}{1 + g_m R_8} \right) \left(g_m R_8 \right) \\ &= (2) \left(\frac{0.9517}{0.9517} \right) \left(-228.3 \right) \left(\frac{0.9517}{0.9517} \right) \left(0.0507 \right) \\ \frac{v_{out}}{v_{in}} &= -10.46 \text{ V/V} \end{aligned}$$