
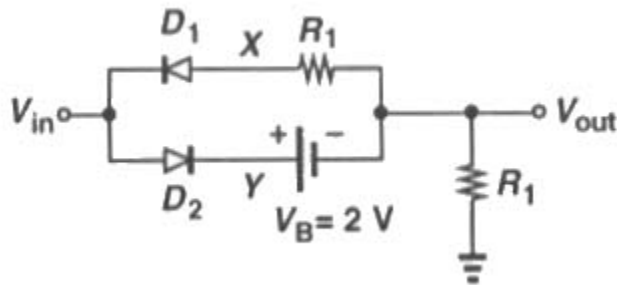


## Homework 4

A silicon p-n diode maintained at 300K has a doping of  $N_a=3 \times 10^{18} \text{ cm}^{-3}$  and  $N_d=1.0 \times 10^{16} \text{ cm}^{-3}$  and mobilities in the two regions of  $\mu_n=1000 \text{ cm}^2/\text{V}\cdot\text{Sec}$ ,  $\mu_p=200 \text{ cm}^2/\text{V}\cdot\text{Sec}$ , minority carrier lifetimes in the two regions of  $\tau_n=10 \mu\text{s}$   $\tau_p=1.2 \mu\text{s}$ .

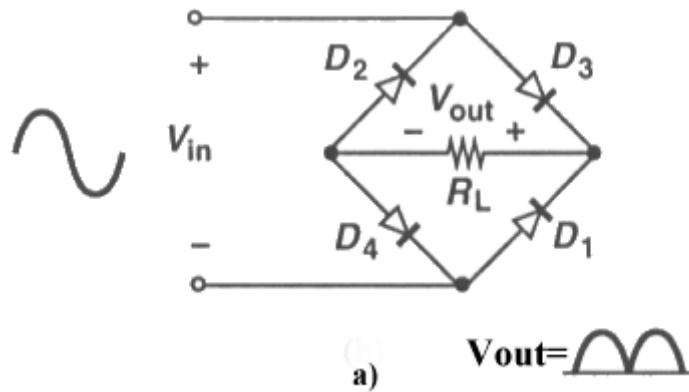- 1) What is the built in voltage?
- 2) What is the depletion width (total,  $W$ ) and width on each side of the junction ( $x_n$  and  $x_p$ )?
- 3) Why is the value of  $x_p$  different from  $x_n$  (i.e. why is the depletion region asymmetric)?
- 4) What is the leakage current density,  $J_0$  (not  $I_0$ )?
- 5) Write out the J-V equation of the diode explaining which part is due to diffusion current and which part is due to drift current.
- 6) What is the capacitance per unit area and the small signal diode resistance at 0 volts? (Assuming the diode area is  $2.0 \times 10^{-5} \text{ cm}^2$  when solving problems 6-8)
- 7) What is the capacitance per unit area and the small signal diode resistance at -3 volts (i.e. reverse bias)?
- 8) What is the capacitance per unit area and the small signal diode resistance at +0.5 volts (i.e. forward bias)?
- 9) The diode is to be used in a 3GHz oscillator circuit for a cell phone and thus is placed in parallel with a 12 nH inductor. If the device is intended to be biased at -3 V (see results from problem above), what diode area is required?
- 10) If the bias voltage is changed to -1V, what is the shift in frequency that results?
- 11) Using the Ideal Diode Model for the circuit below, draw a graph of the Output voltage (y- axis) vs Input voltage (x-axis) for all voltage inputs between -10 and +10 V. Repeat with the CVD model using a turn on voltage of 0.6 V.





12) The circuit above is called a full wave bridge rectifier and is so common in power supply applications that you can buy the diode sets as one single part. The resistor  $R_L$  is not part of the rectifier but instead is the load you are trying to deliver power to (it could represent a computer or any other appliance that consumes DC power). The input voltage is a sin wave (120 Volts, 60 Hz voltage for our example here but in general can have any amplitude or frequency). The output is the absolute value of the input or a “Fully Rectified” waveform as shown in the figure.

- Using the Ideal diode model, draw the equivalent circuit for the positive  $\frac{1}{2}$  cycle of the input waveform (i.e. 1<sup>st</sup>  $\frac{1}{2}$  cycle) indicating the direction of current flow through the load resistor,  $R_L$ .
- Using the Ideal diode model, draw the equivalent circuit for the negative  $\frac{1}{2}$  cycle of the input waveform (i.e. 2<sup>nd</sup>  $\frac{1}{2}$  cycle) indicating the direction of current flow through the load resistor,  $R_L$ .
- Explain the advantage this circuit offers in terms of efficiency of the power used compared to our  $\frac{1}{2}$  wave rectifier we discussed in class.
- Discuss the advantage this circuit offers in regards to the direction of current flow delivered to the load.
- How could we “smooth out” the voltage waveform to make it look more like a DC voltage?

13) Shown below is the voltage regulator with  $V_i=27V$ , the breakdown voltage of the zener diode is  $V_z=9V$ ,  $R_1=15 K\Omega$ . Assume the zener diode is perfect.

- What is the minimum value of our load resistor,  $R$ , that can be used and still have a regulated output voltage?
- What is the maximum load current that can be drawn from the regulator?
- What is the output voltage for  $R=5 K\Omega$ ?

