

Bring this homework to class on Friday Jan. 16, but do not turn it in until the end of class. Note that A' is a notation for NOT(A).

#1. Fill in the truth table below for the logic function  $Out = A+BC$

A	B	C	Out
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

#2. Simplify the Boolean expression so that it has only three parameters (out of A, A', B, B', C, C'):

$$A'C + ABC = \underline{\hspace{10em}}$$

$$= \underline{\hspace{10em}}$$

$$= \underline{\hspace{10em}}$$

#3. Fill in the truth table for the Output of the function in problem #2.

A	B	C	Out
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

#4. Using DeMorgan's Theorem, express the function below as indicated.

$$F(A,B,C) = AC' + A'C' + BC'$$

---

---

a. With only OR and Complement operations: \_\_\_\_\_

---

---

b. With only AND and Complement operations: \_\_\_\_\_

#5. In order to design a single stage logic circuit, we need to express the logic function so that only single literals are complemented [ no complemented parentheses like  $(A+B)'$  ]. Express the following logic functions that way (use DeMorgan's theorem):

$$(A' + B)'C + ((D + E')F)' = \underline{\hspace{15em}}$$
$$= \underline{\hspace{15em}}$$
$$= \underline{\hspace{15em}}$$
$$= \underline{\hspace{15em}}$$

$$(AB(C + D))' = \underline{\hspace{15em}}$$
$$= \underline{\hspace{15em}}$$
$$= \underline{\hspace{15em}}$$
$$= \underline{\hspace{15em}}$$
$$= \underline{\hspace{15em}}$$