 


**HW-7. Finite State Machine - Circuit Design**

**Design the logic to implement the following FSM.** This is the state diagram for a Mealy machine with 3 states that outputs a "1" on every third "1" received as input, no matter how many "0"s are intermingled. For example:

Input: 010110100101110110110  
 Output: 000010000001000100010



This is the truth table for the logic that is needed. P1,P0 is the present state, Number the states such that 2\*P1 + P0 is the number of 1's seen in the present sequence of 3. N1,N0 the next state.

P1	P0	Input	N1	N0	Output
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	0	0	1

Answer \_\_\_\_\_

$N1 = P1 \cdot I' + P0 \cdot I$

Input (I) - P1,P0	00	01	11	10
0	0	0	x	1
1	0	1	x	0

$N0 = P0 \cdot I' + P1' \cdot P0' \cdot I$

Input (I) - P1,P0	00	01	11	10
0	0	1	x	0
1	1	0	x	0



$Output = P1 \cdot P0' \cdot I$

Input (I) - P1,P0	00	01	11	10
0	0	0	x	0
1	0	0	x	1


$$N1 = P1 \cdot I' + P0 \cdot I$$

$$N0 = P0 \cdot I' + P1' \cdot P0' \cdot I$$

$$\text{Output} = P1 \cdot P0' \cdot I$$

  

Not-Connected Lines

 

Connected Lines