

Problem 1:

$$Y(x, t) = 1.5 \cos\left(2\pi \cdot 10^8 t - \frac{2\pi}{3} x + \frac{\pi}{3}\right) e^{-.0005x} \text{ (Volts)}$$

- (a) The Amplitude is 1.5 Volts at spatial position $x = 0\text{m}$. It has an attenuation of $e^{-.0005x}$.
The Period, $T = \frac{2\pi}{2\pi \cdot 10^8} \text{ s} = 10^{-8} \text{ s}$
The frequency is $1/T = 10^8 \text{ Hz} = 100 \text{ MHz}$
The wavelength, $\lambda = c/f = 3\text{m}$
The phase, $\phi = \pi/3 \text{ rad}$
The attenuation factor, $\alpha = .0005 \text{ Np/m}$ (assuming the negative sign is intrinsic to $+x$ prop).
- (b) $\beta = 2\pi/\lambda = 2\pi/3 \text{ (rad/m)}$
 $\omega = 2\pi f = 2\pi \cdot 10^8 \text{ (rad/s)}$
- (c) The wave propagates in the $+x$ direction due to negative sign in front of β . This occurs due to a phase front needing to remain constant – increasing time requires a positive increase in x to maintain neutrality with time for the phase front.
- (d) The amplitude at $t = 10^{-5} \text{ s}$ and $x = 3000\text{m}$ is given by $1.5\cos(2000\pi - 2000\pi + \pi/3)e^{-1.5}$
This value is .167 Volts which satisfies the .1V requirement for reception.

Problem 2:

- (a) $L = .1\text{m}$, $f = 1 \text{ GHz} \Rightarrow \lambda = .3\text{m}$, so $L/\lambda = 1/3 \gg .01 \Rightarrow$ do not ignore tline effects
- (b) $L = 1\text{m}$, $f = 1.8 \text{ GHz} \Rightarrow \lambda = .1667\text{m}$, so $L/\lambda = 6 \gg .01 \Rightarrow$ do not ignore tline effects
- (c) $L = .01\text{m}$, $f = .9 \text{ GHz} \Rightarrow \lambda = .333\text{m}$, so $L/\lambda = .03 > .01 \Rightarrow$ do not ignore tline effects (close)
- (d) $L = .05\text{m}$, $f = 60 \text{ GHz} \Rightarrow \lambda = .005\text{m}$, so $L/\lambda = 10 \gg .01 \Rightarrow$ do not ignore tline effects

Problem 3:

$$(a) \Gamma = \frac{30-j60-50}{30-j60+50} = .2 - .6j$$

$$(b) SWR = \frac{1+|\Gamma|}{1-|\Gamma|} = \frac{1+.6325}{1-.6325} = 4.4415$$

$$(c) Z_{in}(.35\lambda) = \frac{(30-j60)+j50 \tan(.7\pi)}{50+j(30-j60) \tan(.7\pi)} (50) = 78.4644 + j98.2431$$

(d) Under a perfect match, 10W can be delivered. This can be interpreted as the input power to the system is 10W. For the match at hand, $|\Gamma| = .6325$. Thus, the power received is given by $(1-|\Gamma|^2)P_{in} = 6W$

Problem 4:

(a) $Z_o = 50\Omega$, $L = \lambda/4$, $Z_L = 60\Omega$. Find the input impedance. For a quarter-wave length section, the input impedance is given by $Z_{in} = Z_o^2/Z_L = 2500/60 = 41.67\Omega$

(b) For an open circuit, $\Gamma = 1$. For an open circuit $Z_{in} = -jZ_o \cot(\beta l)$. So for $L = \lambda/8$, $Z_{in} = -j50\Omega$. This circuit behaves as a capacitor due to the negative complex impedance.

(c) For a short circuit, $\Gamma = -1$. For a short circuit, $Z_{in} = jZ_o \tan(\beta l)$. For $L = \lambda/6$, $Z_{in} = j86.6\Omega$. This circuit behaves as an inductor due to the positive complex impedance.

Problem 5:

(a) Because the load is a short circuit, the reflection coefficient is -1.

(b) Because the input impedance is dependent on a tangent function, it is periodic with π . Thus, every $.5\lambda$ returns to the load impedance. Thus, 2.3λ is equivalent to $.3\lambda$. So, $Z_{in} = j50 \tan(.6\pi) = -j153.88\Omega$.

(c) The input admittance is given by $1/Z_{in} = .0065j$ S (Siemens or Ω^{-1}).


Problem 6:

$$Z_o = 50 \, \Omega$$

$$Z_L = 75 - j20 \, \Omega$$

$$f_o = 6 \, \text{GHz}$$

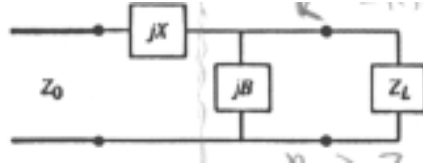- (a) Because the real component of the load is larger than Z_o , the correct circuit topology to be used is:



Using the design equations,

$$B = \frac{X_L \pm \sqrt{R_L/Z_o} \sqrt{R_L^2 + X_L^2 - Z_o R_L}}{R_L^2 + X_L^2} = .006373, -.013015$$

$$X = \frac{1}{B} + \frac{X_L Z_o}{R_L} - \frac{Z_o}{B R_L} = 38.9444, -38.9444$$

For (.006373, 38.9444)

$$L = \frac{X}{\omega} = \frac{38.9444}{2\pi \cdot 6 \cdot 10^9} = 1.033 \, \text{nH}$$

$$C = \frac{B}{\omega} = \frac{.006373}{2\pi \cdot 6 \cdot 10^9} = .16913 \, \text{pF}$$

For (-.013015, -38.9444)


$$L = \frac{1}{\omega B} = 2.0381 \, \text{nH}$$

$$C = \frac{1}{\omega X} = .68112 \, \text{nF}$$

Zin for (1.033 nH, .16913 pF)

$$Z_{in} = j\omega L + j\omega C || Z_L$$

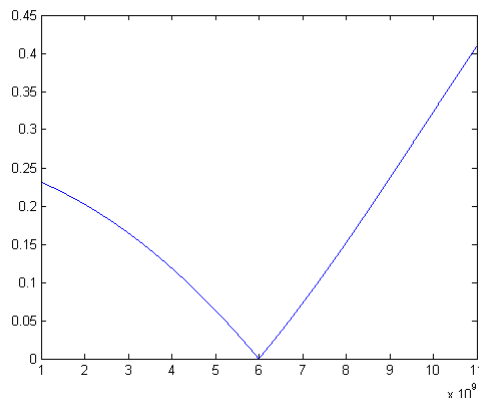This results in the following gamma plot:




Using the cursor, $\Delta f = 24.45\%$ (.05 Γ_m)

For the second set (2.0381 nH, .68112 pF)


$$Z_{in} = -\frac{j}{\omega C} + \left(\frac{-j}{\omega L}\right) || Z_L$$

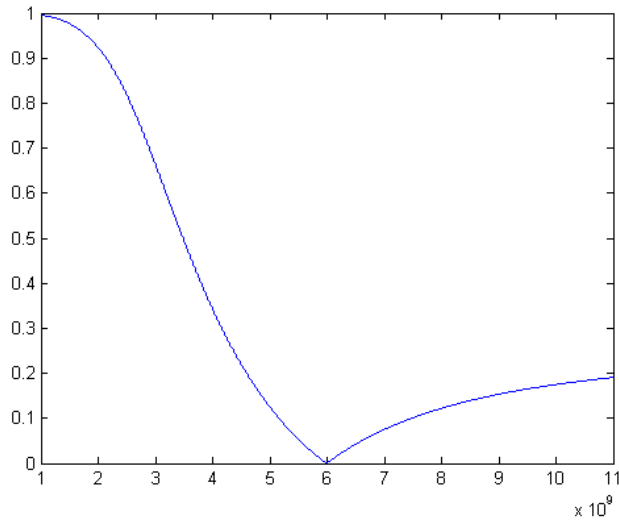This results in the following gamma plot:



Using the cursors, $\Delta f = 18.02\%$

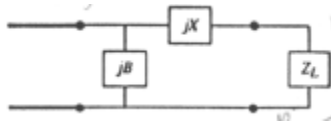(b) $Z_L = 25-j20 \Omega$. This results in the second circuit topology for matching:



Using the design equations:

$$X = \pm \sqrt{R_L(Z_L - R_L)} - X_L = 45, -5$$

$$B = \pm \frac{\sqrt{(Z_o - R_L)/R_L}}{Z_o} = \pm .02$$

This results in the first LC pair as (B, X) \Rightarrow


$$L = \frac{X}{\omega} = 1.1937 \text{ nH}$$

$$C = \frac{B}{\omega} = .53052 \text{ pF}$$

This produces a Z_{in} of

$$Z_{in} = j\omega C || (j\omega L + Z_L)$$

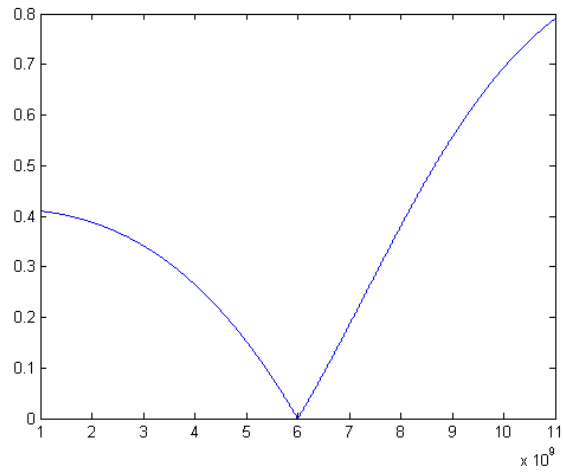This additionally yields the following gamma plot



This results in a $\Delta f = 9.7\%$

The second pair of LC (for the negative values)


$$L = \frac{1}{\omega B} = 1.3263 \text{ nH}$$

$$C = \frac{1}{\omega X} = 5.3052 \text{ pF}$$

This produces a Z_{in} of:

$$Z_{in} = \left(\frac{-j}{\omega L} \right) \parallel \left(\frac{-j}{\omega C} + Z_L \right)$$

This yields a gamma plot of:

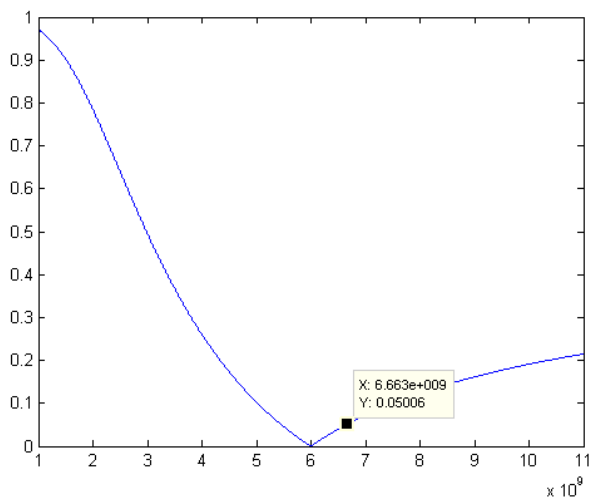

This produces a $\Delta f = 19.85\%$

Problem 7:

$$f = 100 \text{ MHz}, \quad Z_o = 300 \Omega, \quad Z_L = 73 \Omega$$

(a) Quarter-Wavelength Transformer (electrical length $\lambda/4$)

$$Z_{\lambda/4} = \sqrt{Z_o Z_L} = 147.99 \Omega$$

(b) Determine the physical length:

$$\lambda = \frac{c_o}{\sqrt{\epsilon_r} f} = \frac{3 \cdot 10^8}{1.6 \cdot 10^8} = 1.875 \text{ m} \Rightarrow \frac{\lambda}{4} = .4688 \text{ m}$$

(c) Determine the bandwidth given $\Gamma_m = .05$

$$\frac{\Delta f}{f_o} = 2 - \frac{4}{\pi} \cos^{-1} \left[\frac{\Gamma_m}{\sqrt{1 - \Gamma_m^2}} \frac{2\sqrt{Z_o Z_L}}{|Z_o - Z_L|} \right] = 2 - \frac{4}{\pi} \cos^{-1} \left[\frac{.05}{\sqrt{1 - .05^2}} \frac{2\sqrt{73 \cdot 300}}{|300 - 73|} \right] = 8.32\%$$

(d) Use a 3 Stage Binomial Transformer to Design a more bandwidth efficient match:

The recursive formula for generating the section impedances is:

$$\ln \left(\frac{Z_{n+1}}{Z_n} \right) = 2^{-N} C_n^N \ln \left(\frac{Z_L}{Z_o} \right)$$

$$\begin{aligned} Z_o &= 300 \Omega \\ Z_1 &= 251.42 \Omega \\ Z_2 &= 148 \Omega \\ Z_3 &= 87.11 \Omega \\ Z_L &= 73 \Omega \end{aligned}$$

(e) The bandwidth for this system is given by (N=3):

$$\frac{\Delta f}{f_o} = 2 - \frac{4}{\pi} \cos^{-1} \left(\frac{\frac{\Gamma_m}{2}}{\left| \frac{Z_L - Z_o}{2^N (Z_L + Z_o)} \right|} \right) = 57.3\%$$