

ECE 3050 Analog Electronics Quiz 3


September 9, 2009

Professor Leach Last Name: _____ First Name: _____

Instructions. Print your name in the spaces above. Place a box around any answer. **Honor Code Statement:**

I have neither given nor received help on this quiz. Initials _____

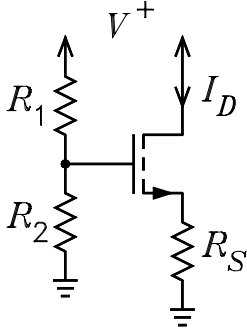- 1 of 2. For $V^+ = +24\text{ V}$, $R_1 = 1\text{ M}\Omega$, $R_2 = 1.5\text{ M}\Omega$, $K = 4 \times 10^{-4}\text{ S}$, and $V_{TO} = 1.5\text{ V}$, solve for R_S for $I_D = 2.5\text{ mA}$.
Reference equation: $i_D = K (v_{GS} - V_{TO})^2$.




$$V_p := 24 \quad R_1 := 1000000 \quad R_2 := 1500000 \quad K := 4 \cdot 10^{-4} \quad V_{TO} := 1.5 \quad I_D := 0.0025$$

$$V_{GG} := V_p \cdot \frac{R_2}{R_1 + R_2} \quad R_{GG} := R_p2(R_1, R_2) \quad V_{GG} = 14.4 \quad R_{GG} = 6 \cdot 10^5$$

$$V_{GS} := \sqrt{\frac{I_D}{K}} + V_{TO} \quad V_{GS} = 4$$

$$V_{GG} = V_{GS} + I_D \cdot R_S \quad R_S := \frac{V_{GG} - V_{GS}}{I_D} \quad R_S = 4.16 \cdot 10^3$$

- 2 of 2. The circuit on the left is the signal circuit for a CE amplifier. The two circuits on the right show the hybrid- π model for the circuit. For $R_B = 2.2\text{ k}\Omega$, $R_C = 10\text{ k}\Omega$, $I_C = 1.5\text{ mA}$, and $V_{CE} = 10\text{ V}$, solve for the voltage gain $A_v = v_c/v_s$. For the transistor, assume $\beta = 100$, $V_A = 75$, and $V_T = 25\text{ mV}$. Reference equations: $i'_c = g_m v_\pi = \beta i_b = \alpha i'_e$, $r_\pi = V_T/I_B$, $g_m = I_C/V_T$, $r_o = (V_A + V_{CE})/I_C$.

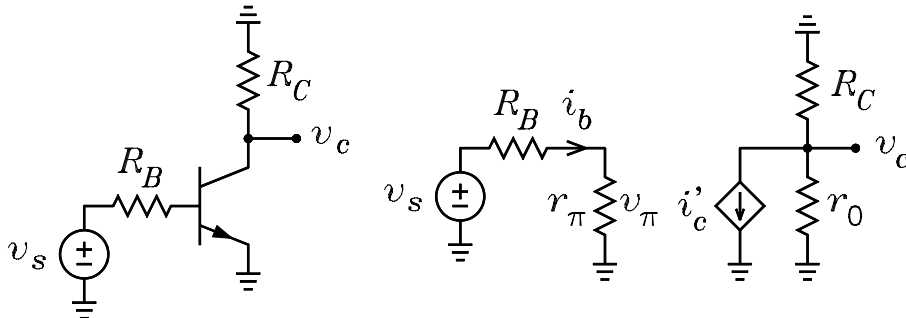

$$R_B := 2200 \quad R_C := 10000 \quad I_C := 0.0015 \quad V_{CE} := 10 \quad \beta := 100 \quad V_T := 0.025$$

$$I_B := \frac{I_C}{\beta} \quad I_B = 1.5 \cdot 10^{-5} \quad g_m := \frac{I_C}{V_T} \quad g_m = 0.06 \quad V_A := 75$$

$$r_\pi := \frac{V_T}{I_B} \quad r_\pi = 1.667 \cdot 10^3 \quad r_0 := \frac{V_A + V_{CE}}{I_C} \quad r_0 = 5.667 \cdot 10^4 \quad v_s := 1$$

$$i'_c := v_s \cdot \frac{r_\pi}{R_B + r_\pi} \cdot g_m \quad i'_c = 0.026 \quad v_{o1} := -i'_c \cdot R_{p2}(R_C, r_0) \quad v_{o1} = -219.828$$

$$i_b := \frac{i'_c}{\beta} \quad i_b = 2.586 \cdot 10^{-4} \quad v_{o2} := -\beta \cdot i_b \cdot R_{p2}(R_C, r_0) \quad v_{o2} = -219.828$$