

# ECE 3050 Analog Electronics Quiz 12

November 11, 2009

Professor Leach

Name \_\_\_\_\_


**Instructions.** Print your name in the space above. Place a box around your answers. Points will be subtracted if you do not express each numerical answer as a decimal number and if you do not put a box around answers. **Honor Code Statement:** *I have neither given nor received help on this quiz.* Initials \_\_\_\_\_

1 of 2. On the log-log scales below, sketch the Bode “straight-line” magnitude plots for the transfer functions given.

$$T_1(s) = 5000 \frac{1 + s/300}{(1 + s/30)(1 + s/5000)} \quad T_2(s) = 300 \frac{(s/30)(1 + s/300)}{(1 + s/30)(1 + s/5000)}$$

$|T_1(j\omega)|$  starts at 5000, breaks to a slope of  $-1$  at  $\omega = 30$ , shelves at a slope of 0 at  $\omega = 300$  and a gain of 500, and breaks to a slope of  $-1$  at  $\omega = 5000$

$|T_2(j\omega)|$  starts at a slope of  $+1$ , shelves at a slope of 0 at  $\omega = 30$  and a gain of 300, breaks to a slope of  $+1$  at  $\omega = 300$ , and shelves at a slope of 0 at  $\omega = 5000$  and a gain of 5000.

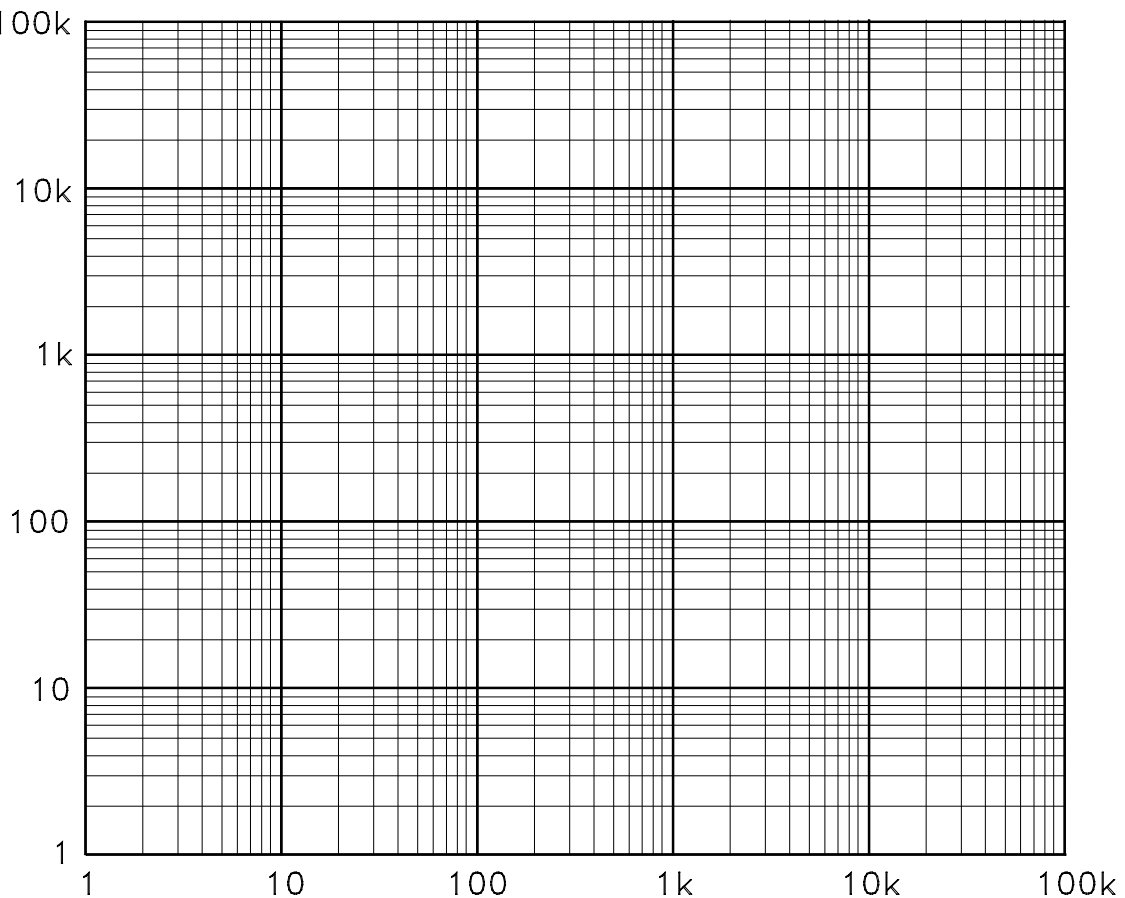

- 2 of 2. (a) What is the gain of the circuit at dc, i.e. zero frequency.  $R_3 / (R_1 + R_3)$   
 (b) What is the gain at infinite frequency?  $(R_2 \parallel R_3) / [R_1 + (R_2 \parallel R_3)]$   
 (c) Write the transfer function for  $V_o/V_i$ . It should be in standard time constant form, i.e. all pole and zero terms should be of the form  $(1 + \tau s)$ , where  $\tau$  is the time constant.

$$\frac{V_o}{V_i} = \frac{R_3}{R_1 + R_3} \frac{1 + R_2 C s}{1 + [(R_1 \parallel R_3) + R_2] C s}$$

