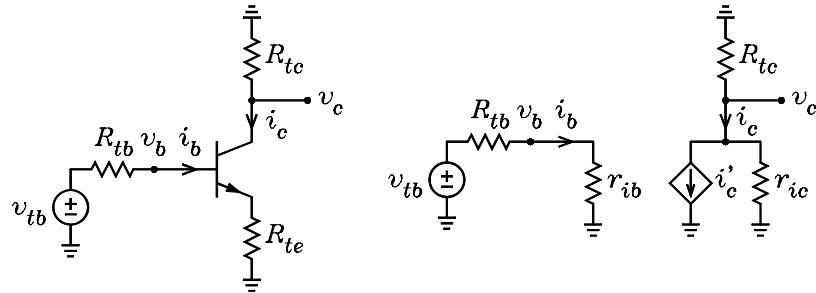


BJT Amplifier Small-Signal Equivalent Circuits


ECE 3050 – Analog Electronics

The BJT Common-Emitter Amplifier



$$\begin{aligned}
 r_e &= \frac{V_T}{I_E} & r'_e &= \frac{R_{tb} + r_x}{1 + \beta} + r_e & r_0 &= \frac{V_A + V_{CE}}{I_C} \\
 r_{ib} &= r_x + (1 + \beta) r_e + R_{te} \frac{(1 + \beta) r_0 + R_{tc}}{r_0 + R_{te} + R_{tc}} & r_{ic} &= \frac{r_0 + r'_e \| R_{te}}{1 - \frac{\alpha R_{te}}{r'_e + R_{te}}} \\
 i_b &= \frac{v_{tb}}{R_{tb} + r_{ib}} & v_b &= \frac{r_{ib}}{R_{tb} + r_{ib}} v_{tb} \\
 i'_c &= \frac{\alpha}{r'_e + R_{te} \| r_0} \frac{r_0 - R_{te}/\beta}{r_0 + R_{te}} v_{tb} & i_c &= \frac{r_{ic}}{r_{ic} + R_{tc}} i'_c & v_c &= -i'_c (r_{ic} \| R_{tc})
 \end{aligned}$$


The BJT Common-Base Amplifier

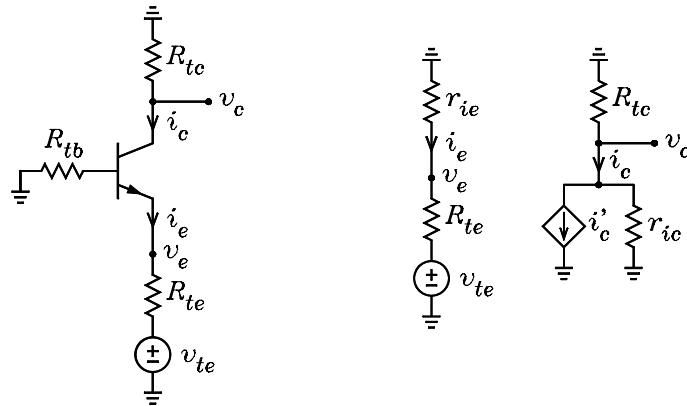

$$\begin{aligned}
 r_e &= \frac{V_T}{I_E} & r'_e &= \frac{R_{tb} + r_x}{1 + \beta} + r_e & r_0 &= \frac{V_A + V_{CE}}{I_C} \\
 r_{ie} &= \frac{r'_e \| (r_0 + R_{tc})}{1 - \frac{\alpha R_{tc}}{r'_e + r_0 + R_{tc}}} & r_{ic} &= \frac{r_0 + r'_e \| R_{te}}{1 - \frac{\alpha R_{te}}{r'_e + R_{te}}}
 \end{aligned}$$

$$\begin{aligned}
i_e &= -\frac{v_{te}}{R_{te} + r_{ie}} & v_e &= \frac{r_{ie}}{R_{te} + r_{ie}} v_{te} \\
i'_c &= -\frac{1}{R_{te} + r'_e \| r_0} \frac{\alpha r_0 + r'_e}{r_0 + r'_e} v_{te} & i_c &= \frac{r_{ic}}{r_{ic} + R_{tc}} i'_c & v_c &= -i'_c (r_{ic} \| R_{tc})
\end{aligned}$$

The BJT Common-Collector Amplifier

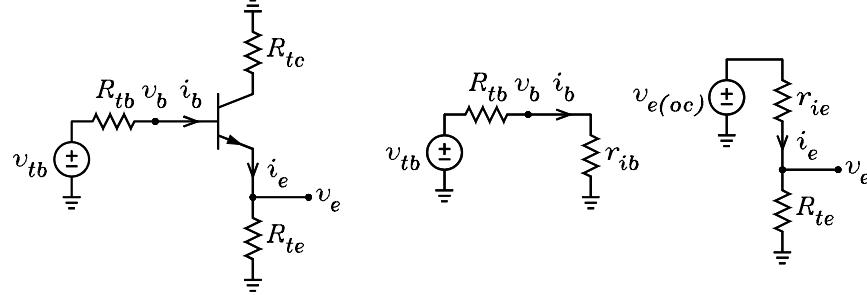

$$\begin{aligned}
r_e &= \frac{V_T}{I_E} & r'_e &= \frac{R_{tb} + r_x}{1 + \beta} + r_e & r_0 &= \frac{V_A + V_{CE}}{I_C} \\
r_{ib} &= r_x + (1 + \beta) r_e + R_{te} \frac{(1 + \beta) r_0 + R_{tc}}{r_0 + R_{te} + R_{tc}} & r_{ie} &= \frac{r'_e \| (r_0 + R_{tc})}{1 - \frac{r'_e + r_0 + R_{tc}}{r'_e + r_0 + R_{tc}}} \\
i_b &= \frac{v_{tb}}{R_{tb} + r_{ib}} & v_b &= \frac{r_{ib}}{R_{tb} + r_{ib}} v_{tb} \\
v_{e(oc)} &= \frac{v_{tb}}{1 + \frac{r'_e}{r_0 + R_{tc}/(1 + \beta)}} & i_e &= \frac{v_{e(oc)}}{r_{ie} + R_{te}} & v_e &= \frac{R_{te}}{r_{ie} + R_{te}} v_{e(oc)}
\end{aligned}$$