

The Common-Drain Amplifier

Basic Circuit

Fig. 1 shows the circuit diagram of a single stage common-drain amplifier. The object is to solve for the small-signal voltage gain, input resistance, and output resistance.

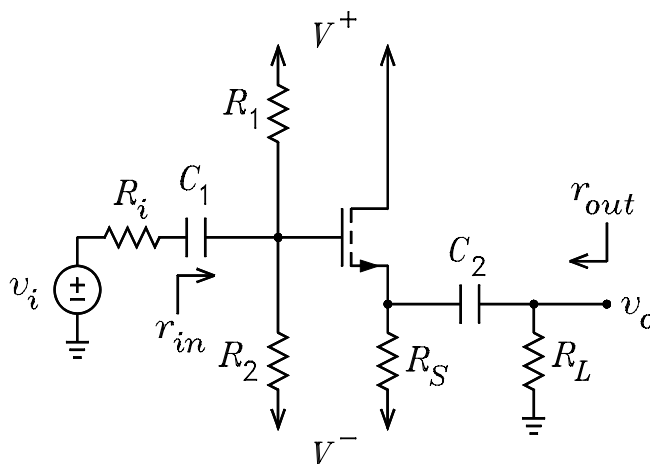


Figure 1: Common-drain amplifier.

DC Solution

(a) Replace the capacitors with open circuits. Look out of the 3 MOSFET terminals and make Thévenin equivalent circuits as shown in Fig. 2.

$$V_{GG} = \frac{V^+ R_2 + V^- R_1}{R_1 + R_2} \quad R_{GG} = R_1 \parallel R_2$$

$$V_{SS} = V^- \quad R_{SS} = R_S \quad V_{DD} = V^+ \quad R_{DD} = 0$$

(b) Write the loop equation between the V_{GG} and the V_{SS} nodes.

$$V_{GG} - V_{SS} = V_{GS} + I_S R_{SS} = V_{GS} + I_D R_{SS}$$

(c) Use the equation for the drain current to solve for V_{GS} .

$$V_{GS} = \sqrt{\frac{I_D}{K}} + V_{TO}$$

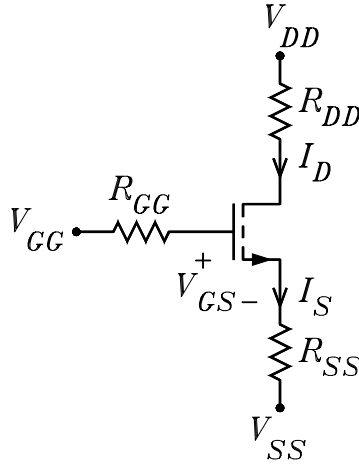


Figure 2: Bias circuit.

(d) Solve the equations simultaneously.

$$I_D R_{SS} + \sqrt{\frac{I_D}{K}} + [(V_{GG} - V_{SS}) - V_{TO}] = 0$$

(e) Let $V_1 = (V_{GG} - V_{SS}) - V_{TO}$. Solve the quadratic for I_D .

$$I_D = \left(\frac{\sqrt{1 + 4KV_1 R_{SS}} - 1}{2R_{SS}\sqrt{K}} \right)^2$$

(d) Verify that $V_{DS} > V_{GS} - V_{TO} = \sqrt{I_D/K}$ for the active mode.

$$V_{DS} = V_D - V_S = (V_{DD} - I_D R_{DD}) - V_{GG} = V_{DD} - V_{SS} - I_D R_{DD}$$

Small-Signal or AC Solutions

(a) Redraw the circuit with $V^+ = V^- = 0$ and all capacitors replaced with short circuits as shown in Fig. ??.

(b) Calculate g_m , r_s , and r_0 from the DC solution.

$$g_m = 2\sqrt{KI_D} \quad r_s = \frac{1}{g_m} \quad r_0 = \frac{V_A + V_{CE}}{I_C}$$

(c) Replace the circuits looking out of the gate with a Thévenin equivalent circuit as shown in Fig. 4.

$$v_{tg} = v_i \frac{R_1 \parallel R_2}{R_s + R_1 \parallel R_2} \quad R_{tg} = R_1 \parallel R_2$$

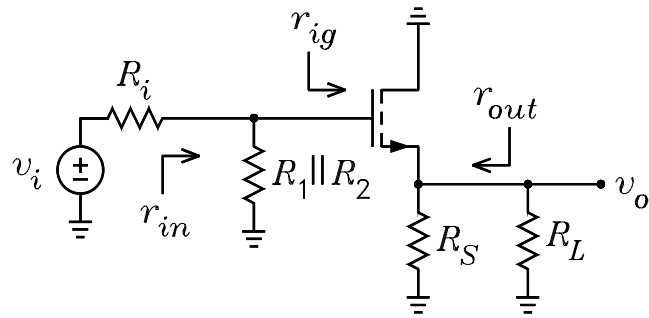


Figure 3: Signal circuit.

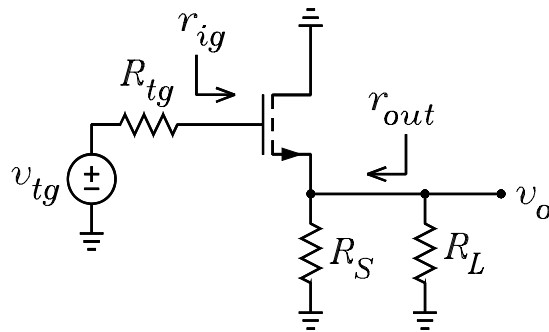


Figure 4: Signal circuit with Thévenin gate circuit.

Exact Solution

Note that the Thévenin resistance R_{td} seen looking out of the drain is zero. This exact solution is also valid for circuits where $R_{td} \neq 0$.

(a) Replace the circuit seen looking into the source with its Thévenin equivalent circuit as shown in Fig. 5. Solve for $v_{s(oc)}$.

$$v_{s(oc)} = v_{tg} \frac{r_0}{r_s + r_0} \quad r_{is} = r_s \frac{r_0 + R_{td}}{r_s + r_0} \quad R_{td} = 0$$

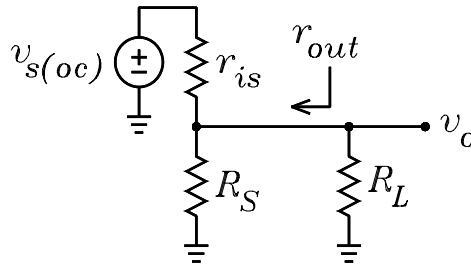


Figure 5: Thévenin source circuit.

(b) Solve for v_o .

$$v_o = v_{s(oc)} \frac{R_S \parallel R_L}{r_{is} + R_S \parallel R_L} = v_i \frac{R_1 \parallel R_2}{R_s + R_1 \parallel R_2} \frac{R_S \parallel R_L}{r_{is} + R_S \parallel R_L}$$

(c) Solve for the voltage gain.

$$A_v = \frac{v_o}{v_i} = \frac{R_1 \parallel R_2}{R_s + R_1 \parallel R_2} \frac{R_S \parallel R_L}{r_{is} + R_S \parallel R_L}$$

(d) Solve for r_{in} .

$$r_{in} = R_1 \parallel R_2$$

(e) Solve for r_{out} .

$$r_{out} = r_{is} \parallel R_S$$

(f) Special case for $r_0 = \infty$.

$$v_{s(oc)} = v_{tg} \quad r_{is} = r_s$$

Example 1 For the CS amplifier of Fig. ??, it is given that $R_i = 5 \text{ k}\Omega$, $R_1 = 5 \text{ M}\Omega$, $R_2 = 1 \text{ M}\Omega$, $R_D = 10 \text{ k}\Omega$, $R_S = 3 \text{ k}\Omega$, $R_3 = 50 \Omega$, $R_L = 20 \text{ k}\Omega$, $V^+ = 24 \text{ V}$, $V^- = -24 \text{ V}$, $K_0 = 0.001 \text{ A/V}^2$, $V_{TO} = 1.75 \text{ V}$, $\lambda = 0.016 \text{ V}^{-1}$. Solve for the gain $A_v = v_o/v_i$, the input resistance r_{in} , and the output resistance r_{out} . The capacitors can be assumed to be ac short circuits at the operating frequency.

Solution. For the dc bias solution, replace all capacitors with open circuits. The Thévenin voltage and resistance seen looking out of the gate are

$$V_{GG} = \frac{V^+ R_2 + V^- R_1}{R_1 + R_2} = -16 \text{ V} \quad R_{BB} = R_1 \parallel R_2 = 833.3 \text{ k}\Omega$$

The Thévenin voltage and resistance seen looking out of the source are $V_{SS} = V^-$ and $R_{SS} = R_S$. To calculate I_D , we neglect the Early effect by setting $K = K_0$. The bias equation for I_D is

$$I_D = \left(\frac{\sqrt{1 + 4KV_1 R_{SS}} - 1}{2\sqrt{K} R_{SS}} \right)^2 = 1.655 \text{ mA}$$

To test for the active mode, we calculate the drain-source voltage

$$V_{DS} = V_D - V_S = V^+ - (V^- + I_D R_{SS}) = 43.036 \text{ V}$$

This must be greater than $V_{GS} - V_{TO} = \sqrt{I_D/K} = 1.286 \text{ V}$. It follows that the MOSFET is biased in its active mode.

For the small-signal ac analysis, we need g_m , r_s , and r_0 . When the Early effect is accounted for, the new value of K is given by

$$K = K_0 (1 + \lambda V_{DS}) = 1.689 \times 10^{-3} \text{ A/V}^2$$

Note that this is an approximation because the Early effect was neglected in calculating V_{DS} . However, the approximation should be close to the true value. It follows that g_m , r_s , and r_0 are given by

$$g_m = 2\sqrt{KI_D} = 3.343 \times 10^{-3} \text{ A/V} \quad r_s = \frac{1}{g_m} = 299.135 \text{ }\Omega$$

$$r_0 = \frac{\lambda^{-1} + V_{DS}}{I_D} = 63.78 \text{ k}\Omega$$

For the small-signal analysis, V^+ and V^- are zeroed and the three capacitors are replaced with ac short circuits. The Thévenin voltage and resistance seen looking out of the gate are given by

$$v_{tg} = v_i \frac{R_1 \parallel R_2}{R_i + R_1 \parallel R_2} = 0.994 v_i \quad R_{tg} = R_i \parallel R_1 \parallel R_2 = 4.97 \text{ k}\Omega$$

The Thévenin voltage and resistance seen looking into the source are

$$v_{s(oc)} = v_{tg} \frac{r_0}{r_s + r_0} = 0.989 v_i \quad R_{td} = 0 \quad r_{is} = r_s \frac{r_0 + R_{td}}{r_s + r_0} = 297.738 \text{ }\Omega$$

The output voltage is given by

$$v_o = v_{s(oc)} \frac{R_S \parallel R_L}{r_{is} + R_S \parallel R_L} = 0.888 v_i$$

Thus the voltage gain is

$$A_v = \frac{v_o}{v_i} = 0.888$$

The input and output resistances are given by

$$r_{in} = R_1 \parallel R_2 = 833.3 \text{ k}\Omega \quad r_{out} = r_{is} \parallel R_S = 270.86 \text{ }\Omega$$

Alternate Solutions

Because the Thévenin resistance R_{td} seen looking out of the drain is zero, the drain-source resistance r_0 connects from source to ground. In this case, an exact solution can be obtained with r_0 in the circuit. In cases where $R_{td} > 0$, let $r_0 = \infty$ (an open circuit) to obtain approximate solutions.

Source Equivalent Circuit Solution

(a) After making the Thévenin equivalent circuits looking out of the gate, replace the MOSFET with the source equivalent circuit as shown in Fig. 6.

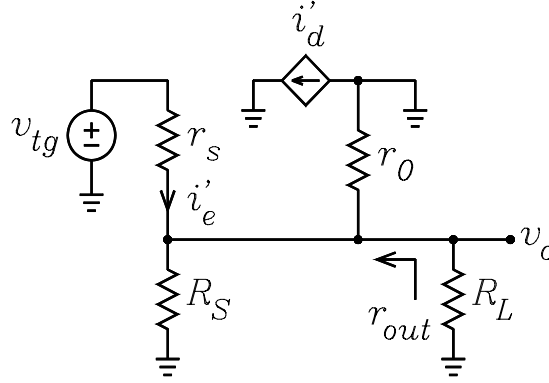


Figure 6: Source equivalent circuit.

(b) Solve for v_o .

$$v_o = v_{tg} \frac{r_0 \parallel R_S \parallel R_L}{r_s + r_0 \parallel R_S \parallel R_L} = v_i \frac{R_1 \parallel R_2}{R_s + R_1 \parallel R_2} \frac{r_0 \parallel R_S \parallel R_L}{r_s + r_0 \parallel R_S \parallel R_L}$$

(c) Solve for the voltage gain.

$$A_v = \frac{v_o}{v_i} = \frac{R_1 \parallel R_2}{R_s + R_1 \parallel R_2} \frac{r_0 \parallel R_S \parallel R_L}{r_s + r_0 \parallel R_S \parallel R_L}$$

(d) Solve for r_{in} .

$$r_{in} = R_1 \parallel R_2$$

(e) Solve for r_{out} .

$$r_{out} = r_0 \parallel r_s \parallel R_S$$

Example 2 Use the source equivalent circuit solutions to calculate the values of A_v , r_{in} , and r_{out} for Example 1.

$$A_v = 0.994 \times 0.893 = 0.888$$

$$r_{in} = R_1 \parallel R_2 = 833.3 \text{ k}\Omega \quad r_{out} = 270.86 \text{ }\Omega$$

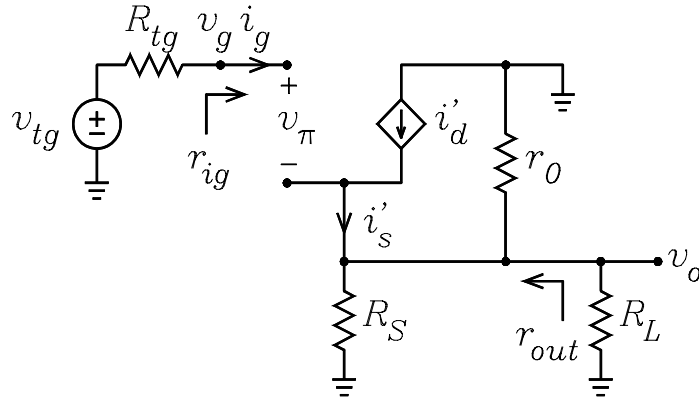


Figure 7: Hybrid- π model.

π Model Solution

(a) After making the Thévenin equivalent circuits looking out of the gate and source, replace the MOSFET with the π model as shown in Fig. 7.

(b) Solve for i'_s .

$$\begin{aligned}
 v_{tg} &= v_{\pi} + i'_s r_0 \parallel R_S \parallel R_L = \frac{i'_d}{g_m} + i'_s r_0 \parallel R_S \parallel R_L = \frac{i'_s}{g_m} + i'_s r_0 \parallel R_S \parallel R_L \\
 \implies i'_s &= \frac{v_{tg}}{\frac{1}{g_m} + r_0 \parallel R_S \parallel R_L}
 \end{aligned}$$

(c) Solve for v_o .

$$\begin{aligned}
 v_o &= i'_s r_0 \parallel R_S \parallel R_L = \frac{v_{tg}}{\frac{1}{g_m} + r_0 \parallel R_S \parallel R_L} r_0 \parallel R_S \parallel R_L \\
 &= v_i \frac{R_1 \parallel R_2}{R_s + R_1 \parallel R_2} \frac{r_0 \parallel R_S \parallel R_L}{\frac{1}{g_m} + r_0 \parallel R_S \parallel R_L}
 \end{aligned}$$

(d) Solve for the voltage gain.

$$A_v = \frac{v_o}{v_i} = \frac{R_1 \parallel R_2}{R_s + R_1 \parallel R_2} \frac{r_0 \parallel R_S \parallel R_L}{\frac{1}{g_m} + r_0 \parallel R_S \parallel R_L}$$

(e) Solve for r_{in} .

$$r_{in} = R_1 \parallel R_2$$

(f) Solve for r_{out} . First, solve for the open-circuit output voltage. This is the output voltage with $R_L = \infty$.

$$v_{o(oc)} = v_{tg} \frac{r_0 \parallel R_S}{\frac{1}{g_m} + r_0 \parallel R_S}$$

Next, solve for the short-circuit output current. This is the output current with $R_L = 0$. The output current is given by

$$i_o = \frac{v_o}{R_L} = \frac{v_{tg}}{\frac{1}{g_m} + r_0 \parallel R_S \parallel R_L} \frac{r_0 \parallel R_S \parallel R_L}{R_L} = \frac{v_{tg}}{\frac{1}{g_m} + r_0 \parallel R_S \parallel R_L} \frac{r_0 \parallel R_S}{R_L + r_0 \parallel R_S}$$

Now, let $R_L = 0$ to obtain

$$i_{o(sc)} = \frac{v_{tg}}{\frac{1}{g_m}} = g_m v_{tg}$$

The output resistance is given by

$$r_{out} = \frac{v_{o(oc)}}{i_{o(sc)}} = \frac{r_0 \parallel R_S}{\frac{1}{g_m} + r_0 \parallel R_S} \frac{1}{g_m} = \frac{1}{g_m} \parallel r_0 \parallel R_S$$

Note this is simply $r_s \parallel r_0 \parallel R_S$, an answer that is obvious using the source equivalent circuit.

Example 3 Use the π model solutions to calculate the values of A_v , r_{in} , and r_{out} for Example 1.

$$A_v = 0.994 \times 0.893 = 0.888$$

$$r_{in} = R_1 \parallel R_2 = 833.3 \text{ k}\Omega \quad r_{out} = 270.86 \text{ }\Omega$$

T Model Solution

(a) After making the Thévenin equivalent circuits looking out of the gate and source, replace the MOSFET with the T model as shown in Fig. 8.

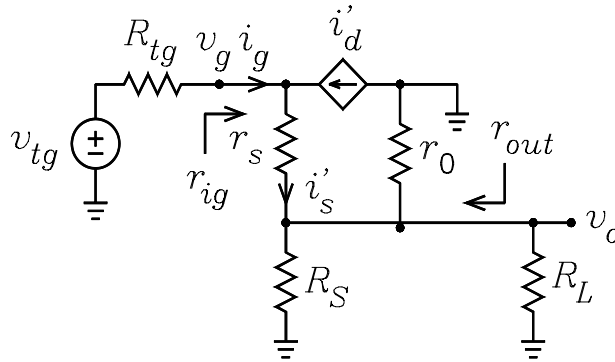


Figure 8: T model circuit.

(b) Solve for i'_s .

$$\begin{aligned} v_{tg} &= i'_s (r_s + r_0 \parallel R_S \parallel R_L) \\ \implies i'_s &= \frac{v_{tg}}{r_s + r_0 \parallel R_S \parallel R_L} \end{aligned}$$

(c) Solve for v_o .

$$\begin{aligned} v_o &= i'_s r_0 \| R_S \| R_L = \frac{v_{tg}}{r_s + r_0 \| R_S \| R_L} r_0 \| R_S \| R_L \\ &= v_i \frac{R_1 \| R_2}{R_s + R_1 \| R_2} \frac{r_0 \| R_S \| R_L}{r_s + r_0 \| R_S \| R_L} \end{aligned}$$

(d) Solve for the voltage gain.

$$A_v = \frac{v_o}{v_i} = \frac{R_1 \| R_2}{R_s + R_1 \| R_2} \frac{r_0 \| R_S \| R_L}{r_s + r_0 \| R_S \| R_L}$$

(e) Solve for r_{in} .

$$r_{in} = R_1 \| R_2$$

(f) Solve for r_{out} . First, solve for the open-circuit output voltage. This is the output voltage with $R_L = \infty$.

$$v_{o(oc)} = v_{tg} \frac{r_0 \| R_S}{r_s + r_0 \| R_S}$$

Next, solve for the short-circuit output current. This is the output current with $R_L = 0$. The output current is given by

$$i_o = \frac{v_o}{R_L} = \frac{v_{tg}}{r_s + r_0 \| R_S \| R_L} \frac{r_0 \| R_S \| R_L}{R_L} = \frac{v_{tg}}{r_s + r_0 \| R_S \| R_L} \frac{r_0 \| R_S}{R_L + r_0 \| R_S}$$

Now, let $R_L = 0$ to obtain

$$i_{o(sc)} = \frac{v_{tg}}{r_s}$$

The output resistance is given by

$$r_{out} = \frac{v_{o(oc)}}{i_{o(sc)}} = \frac{r_0 \| R_S}{r_s + r_0 \| R_S} r_s = r_s \| r_0 \| R_S$$

This is the same answer obtained from the source equivalent circuit.

Example 4 Use the *T*-model solutions to calculate the values of A_v , r_{in} , and r_{out} for Example 1.

$$A_v = 0.994 \times 0.893 = 0.888$$

$$r_{in} = R_1 \| R_2 = 833.3 \text{ k}\Omega \quad r_{out} = 270.86 \text{ }\Omega$$