

ECE 3050 Analog Electronics Quiz 11


April 1, 2009

Professor Leach

Name _____

Instructions. Print your name in the space above. **Honor Code:** *I have neither given nor received help on this quiz.* Initials _____

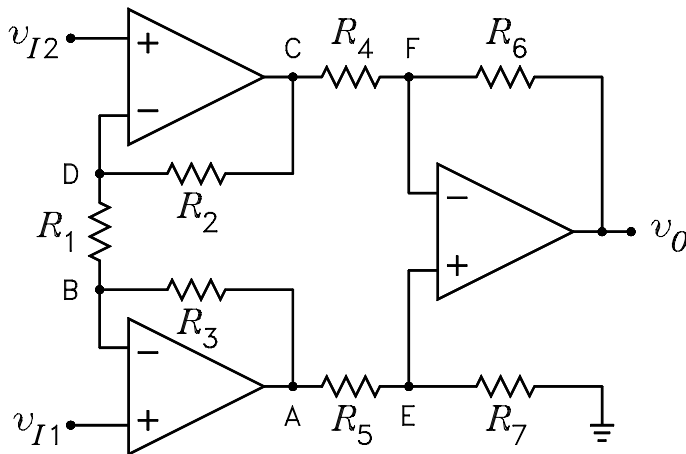- 1 of 2. The figure shows a three op amp instrumentation amplifier. It is given that $v_{I1} = 1.5\text{ V}$, $v_{I2} = -2\text{ V}$, $R_1 = 1\text{ k}\Omega$, $R_2 = 2\text{ k}\Omega$, $R_3 = 3\text{ k}\Omega$, $R_4 = 4\text{ k}\Omega$, $R_5 = 5\text{ k}\Omega$, $R_6 = 6\text{ k}\Omega$, and $R_7 = 7\text{ k}\Omega$. Solve for the node voltages v_A through v_F and the output voltage v_O .



$$v_{I1} := 1.5 \quad v_{I2} := -2 \quad R_1 := 1000 \quad R_2 := 2000 \quad R_3 := 3000 \quad R_4 := 4000$$

$$R_5 := 5000 \quad R_6 := 6000 \quad R_7 := 7000$$

$$v_A := \left(1 + \frac{R_3}{R_1}\right) \cdot v_{I1} - v_{I2} \cdot \frac{R_3}{R_1} \quad v_A = 12 \quad v_B := v_{I1} \quad v_B = 1.5$$

$$v_C := -v_{I1} \cdot \frac{R_2}{R_1} + \left(1 + \frac{R_2}{R_1}\right) \cdot v_{I2} \quad v_C = -9 \quad v_E := v_A \cdot \frac{R_7}{R_5 + R_7} \quad v_E = 7$$

$$v_F := v_E \quad v_F = 7 \quad v_O := v_E \cdot \left(1 + \frac{R_6}{R_4}\right) - v_C \cdot \frac{R_6}{R_4} \quad v_O = 31$$

- 2 of 2. (a) A circuit has the differential equation $\ddot{v}_O + 3\dot{v}_O + 4v_O = 8v_I$, where each dot indicates a time derivative. Solve for the transfer function for V_o/V_i .

$$s^2 V_o + 3s V_o + 4V_o = 8V_i \implies \frac{V_o}{V_i} = \frac{4}{s^2 + 3s + 4} = \frac{1}{(s/2)^2 + (3/2)(s/2) + 1}$$

- (b) Sketch and label the Bode magnitude and phase plots for the transfer function

$$T(s) = \frac{K}{(1 + s/\omega_0)(1 + s/r\omega_0)}$$

where r is a number such that $r\omega_0 \gg \omega_0$.

Magnitude: Starts at K at zero frequency, breaks to -1 dec/dec at $\omega = \omega_0$, and breaks to -2 dec/dec at $\omega = r\omega_0$.

Phase: Starts at 0° , approaches -90° between ω_0 and $r\omega_0$, and approaches -180° well above $r\omega_0$.