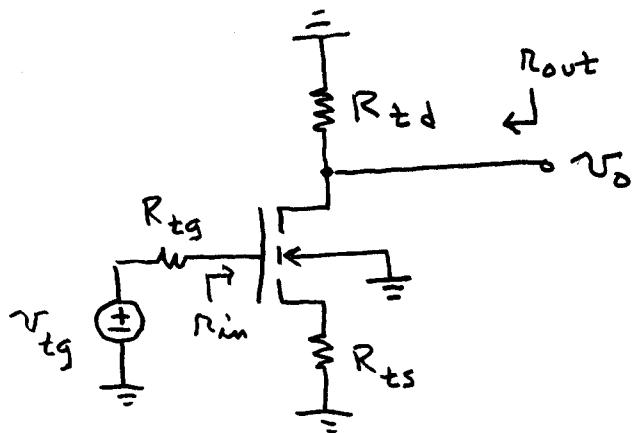


1 - 6/18/03


## The Common Source Amplifier with Body Effect

Assume a Thévenin equivalent is made of the signal source connected to the gate. The ac signal circuit is



Because no gate current flows, it follows that  $R_{in} = \infty$ .

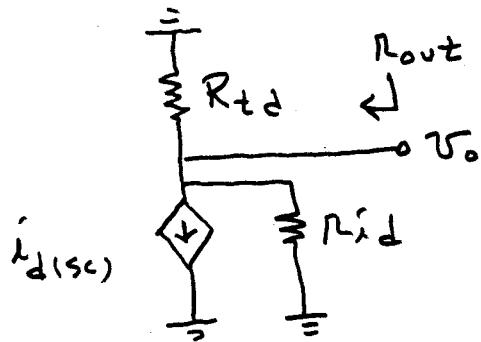To solve for  $V_o$  and  $R_{out}$ , use the Norton drain circuit.



2-6/18/03

$$\begin{aligned} V_o &= -i_{sd(\text{sc})} R_{id} \parallel R_{td} \\ &= -G_{mg} V_{tg} R_{id} \parallel R_{td} \end{aligned}$$

Thus the voltage gain is

$$\frac{V_o}{V_{tg}} = -G_{mg} R_{id} \parallel R_{td}$$

where  $G_{mg} = \frac{1}{1+\chi} \frac{1}{R_A' + R_{ts} \parallel R_o} \frac{R_o}{R_o + R_{ta}}$

$$R_A' = \frac{R_A}{1+\chi} = \frac{1}{g_m(1+\chi)}$$

$$R_{id} = R_o \left( 1 + \frac{R_{ts}}{R_A'} \right) + R_{ts}$$

The output resistance is


$$R_{out} = R_{id} \parallel R_{td}$$

If the body connects to the source lead, not to ac ground, set  $\chi = 0$  in the equations.

3 - 6 / 18 / 03
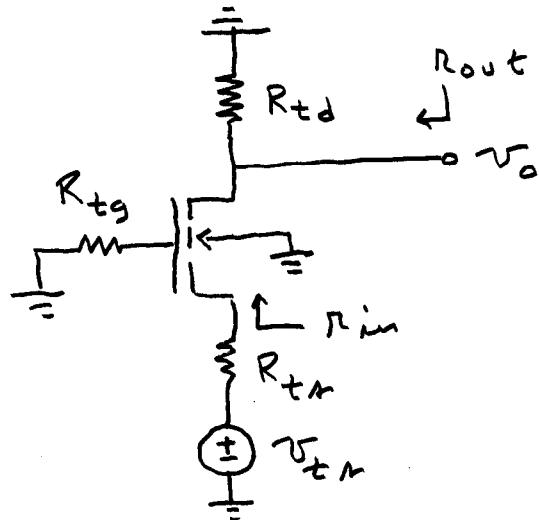
## The Common Gate Amplifier with Body Effect

Assume a Thévenin equivalent TS made of the signal source connected to the source. The ac signal circuit is




The input resistance is given by

$$R_{in} = R_{tg} = R_A' \frac{R_o + R_{td}}{R_A' + R_{td}}$$

where  $R_A' = \frac{R_A}{1+\gamma} = \frac{1}{g_m(1+\gamma)}$

4-6/18/03

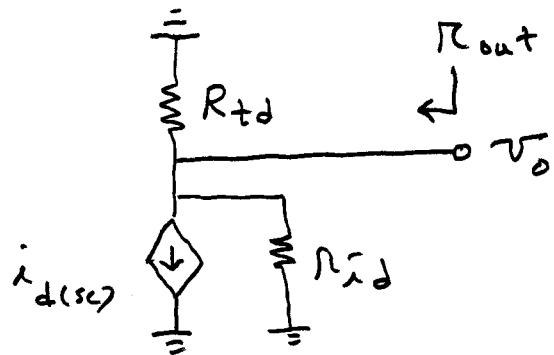To solve for  $V_o$  and  $R_{out}$ , use the Norton drain circuit.



$$\begin{aligned} V_o &= -i_d(s) R_{id} \parallel R_{td} \\ &= -(-G_m + V_{tr}) R_{id} \parallel R_{td} \end{aligned}$$

Thus the voltage gain is given by

$$\frac{V_o}{V_{tr}} = + G_m + R_{id} \parallel R_{td}$$

where

$$G_m = \frac{1}{R_{tr} + R'_A \parallel r_o}$$

$$R_{id} = r_o \left( 1 + \frac{R_{ts}}{R'_A} \right) + R_{tr}$$

The output resistance is


5- 6/18/03

$$R_{out} = R_{id} \parallel R_{td}$$

If the body lead connects to the source lead, not to ac ground, set  $\chi = 0$  in the equations.
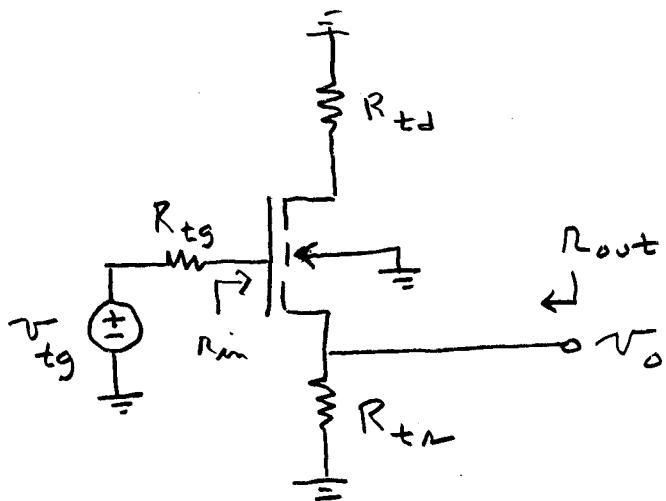
### The Common Drain Amplifier with Body Effect


Assume a Thévenin equivalent circuit is made of the signal source connected to the gate.



Because no gate current flows, it follows that  $R_{in} = \infty$ .

6 - 6/18/03

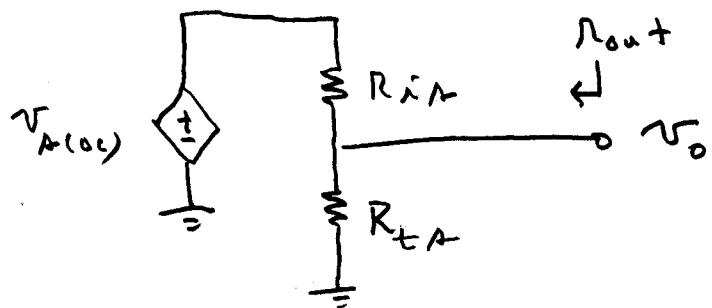To solve for  $v_o$  and  $R_{out}$ , we use the Thévenin source circuit.



where  $V_{A(oc)}$  and  $R_{in}$  are given by

$$V_{A(oc)} = \frac{V_{tg}}{1+x} \frac{R_o}{R'_A + R_o}$$

$$R_{in} = R'_A \frac{R_o + R_{tg}}{R'_A + R_o}$$

$$R'_A = \frac{R_A}{1+x} = \frac{1}{g_m(1+x)}$$

The output voltage is given by

$$\begin{aligned} v_o &= V_{A(oc)} \frac{R_{TA}}{R_{in} + R_{TA}} \\ &= \frac{V_{tg}}{1+x} \frac{R_o}{R'_A + R_o} \frac{R_{TA}}{R_{in} + R_{TA}} \end{aligned}$$

Thus the voltage gain is given by

7 - 6 / 18 / 03

$$A_v = \frac{V_o}{V_{tg}} = \frac{1}{1+k} \frac{R_o}{R'_s + R_o} \frac{R_{ts}}{R_{in} + R_{ts}}$$

The output resistance is given by

$$R_{out} = R_{in} \parallel R_{ts}$$