


ECE 3050 Analog Electronics Quiz 9

July 15, 2009

Professor Leach Last Name: \_\_\_\_\_ First Name: \_\_\_\_\_

**Instructions. Print** your name in the spaces above. Place a box around any answer. **Honor Code Statement:** *I have neither given nor received help on this quiz.* Initials \_\_\_\_\_ For credit, you must give all equations that you use to calculate your answers. Credit will not be given for any answer without full supporting work.

- 1 of 2. (a) What is the expression for the voltage gain  $V_o/V_i$  at very low frequencies?  
 (b) What is the expression for the voltage gain  $V_o/V_i$  at very high frequencies?  
 (c) What is the expression for the pole frequency in rad/s for the transfer function for  $V_o/V_i$ ?  
 (d) What is the expression for the zero frequency in rad/s for the transfer function for  $V_o/V_i$ ?  
 (e) Sketch and label the straight line Bode magnitude plot for  $|V_o/V_i|$ .

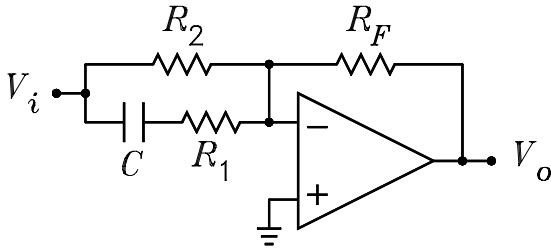


$$A_{low} = -\frac{R_F}{R_2} \quad A_{high} = -\frac{R_F}{R_1 \parallel R_2}$$

$$\omega_{pole} = \frac{1}{(R_1 + R_2)C} \quad \omega_{zero} = \frac{1}{R_1 C}$$

High-pass shelving.

- 2 of 2. (a) What is the expression for the voltage gain  $V_o/V_i$  at very low frequencies?  
 (b) What is the expression for the voltage gain  $V_o/V_i$  at very high frequencies?  
 (c) What is the expression for the pole frequency in rad/s for the transfer function for  $V_o/V_i$ ?  
 (d) What is the expression for the zero frequency in rad/s for the transfer function for  $V_o/V_i$ ?  
 (e) Sketch and label the straight line Bode magnitude plot for  $|V_o/V_i|$ .

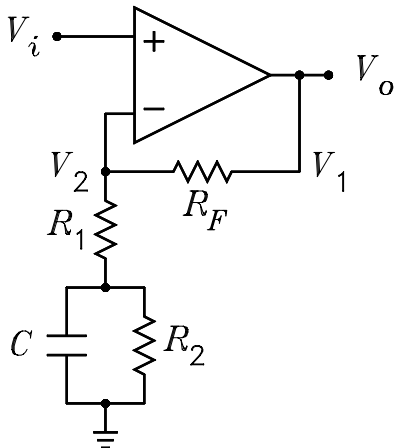

$$A_{low} = 1 + \frac{R_F}{R_1 + R_2} \quad A_{high} = 1 + \frac{R_F}{R_1}$$

$$\omega_{zero} = \frac{1}{(R_1 + R_F) \parallel R_2 C} \quad \omega_{pole} = \frac{1}{R_1 \parallel R_2 C}$$

High-pass shelving.