

**Homework Assignment No. 1 – Solutions****Problem 1**

(a.) The first thing to do is to find Thevenin's equivalent circuit seen from the diode.

The Thevenin voltage is,

$$V_{TH} = V_{IN} \left( \frac{2}{3} - \frac{1}{3} \right) = \frac{V_{IN}}{3}$$

The Thevenin resistance is,

$$R_{TH} = 1\text{k}\Omega \parallel 2\text{k}\Omega + 1\text{k}\Omega \parallel 2\text{k}\Omega = \frac{4}{3} \text{ k}\Omega$$



The equivalent circuit now becomes,

Now, with  $V_{IN} = 10\text{V}$ , we know the diode is forward biased. Therefore, replacing it with a short-circuit gives,

$$V_D = \underline{0\text{V}} \quad \text{and} \quad I_D = \frac{10}{3} \times \frac{3}{4\text{k}\Omega} = \underline{2.5 \text{ mA}}$$

(b.) With  $V_{IN} = -10\text{V}$ , we know the diode is reverse biased. Therefore replacing it with an open-circuit gives,

$$V_D = \underline{-3.33\text{V}} \quad \text{and} \quad I_D = \underline{0 \text{ mA}}$$

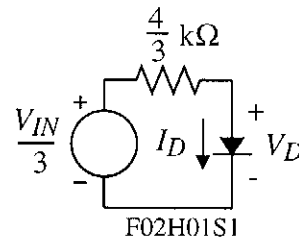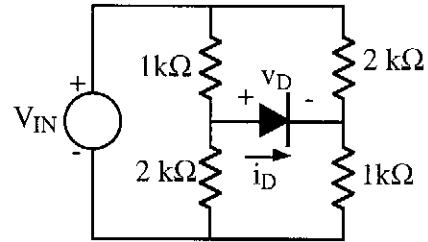**Problem 2****4.52**

$$V_{GG} = \frac{100\text{k}\Omega}{100\text{k}\Omega + 220\text{k}\Omega} 12\text{V} = 3.75\text{V}$$

$$3.75 = V_{GS} + 24 \times 10^3 I_{DS} = V_{GS} + 24 \times 10^3 \frac{5}{1} \frac{25 \times 10^{-6}}{2} (V_{GS} - 1)^2$$


$$1.5V_{GS}^2 - 2V_{GS} - 2.25 = 0 \rightarrow V_{GS} = 2.061\text{V} \quad \text{and} \quad I_{DS} = 70.36\mu\text{A}$$

$$V_{DS} = 12 - 36 \times 10^3 I_{DS} = 9.467\text{V}$$

$$\text{Q - point: } (70.4\mu\text{A}, 9.47\text{V})$$

Problem 3

A pnp BJT circuit is shown. (a.) Find the dc values of  $I_E$ ,  $I_C$ ,  $I_B$ ,  $V_E$ ,  $V_C$  and  $V_B$  if  $\beta = 50$  and  $V_{EB(on)} = 0.65V$ . (b.) For what value of  $R_C$  does the BJT become saturated? (Recall that saturation of a BJT corresponds to the  $BE$  and  $BC$  junctions forward biased.)

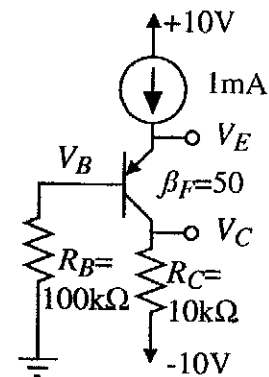Solution

(a.) Note that  $I_E = 1\text{mA}$   $\alpha_F = \frac{\beta_F}{1 + \beta_F} = \frac{50}{51} = 0.98$

$\therefore I_C = \alpha_F I_E = 0.98 \cdot 1\text{mA} = 0.98\text{mA} \Rightarrow I_C = 0.98\text{mA}$

$I_B = \frac{I_C}{\beta_F} = \frac{0.98\text{mA}}{50} = 19.6\mu\text{A} \Rightarrow I_B = 19.6\mu\text{A}$

Now,  $V_B = I_B \cdot 100\text{k}\Omega = 1.96\text{V} \Rightarrow V_B = 1.96\text{V}$

$V_E = V_B + V_{EB(on)} = 1.96\text{V} + 0.65\text{V} = 2.61\text{V} \Rightarrow V_E = 2.61\text{V}$

Finally,  $V_C = -10\text{V} + I_C \cdot 10\text{k}\Omega = -10\text{V} + 0.98\text{mA} \cdot 10\text{k}\Omega = -0.2\text{V} \Rightarrow V_C = -0.2\text{V} \approx 0\text{V}$

(b.) Saturation occurs when  $V_{BC} = 0$  or  $V_B = V_C$ . Therefore,  $V_C = 1.96\text{V}$ . The current through  $R_C$  is still  $0.98\text{mA}$ , so solving for  $R_C$  gives,

$R_C = \frac{V_C + 10\text{V}}{I_C} = \frac{11.96\text{V}}{0.98\text{mA}} = 12.20\text{k}\Omega \Rightarrow R_C = 12.2\text{k}\Omega$

Problem 45.47

$V_{BB} = 15 \frac{120}{120 + 240} = 5.00\text{V}$  and  $R_{BB} = 120\text{k}\Omega \parallel 240\text{k}\Omega = 80\text{k}\Omega$

$I_C = 100 \frac{5.00 - 0.700}{80000 + 101(100000)} = 42.2\mu\text{A}$

$V_{CE} = 15 - 42.2 \times 10^{-6} (10^5) - \frac{101}{100} 42.2 \times 10^{-6} (1.5 \times 10^5) = 4.39\text{V}$

Q - point: (42.2  $\mu\text{A}$ , 4.39 V)