

Homework Assignment No. 2

Due on Wednesday, September 4, 2002

- 1.) Problem 11.16 of the text.
- 2.) Problem 11.34 of the text.
- 3.) Problem 11.37 of the text.
- 4.) Problem 11.43 of the text.
- 5.) Problem 11.55 of the text
- 6.) (a.) Find $V_{out}(s)/V_{in}(s)$ and identify the numerical value of the midband gain and all poles and zeros if g_m is 1mA/V.
(b.) If the transfer function above is

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{100 s}{s+100}$$

sketch an asymptotic magnitude on the curve below.

