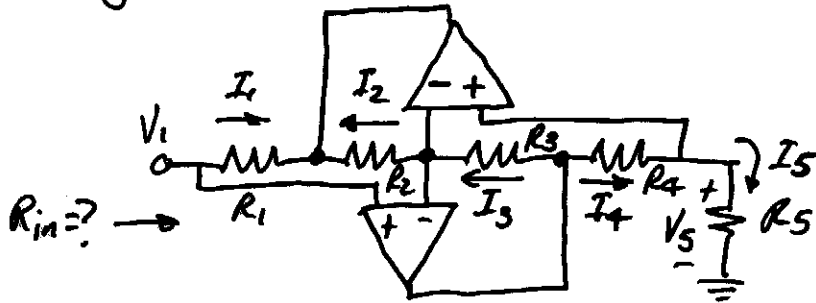


Challenge from last lecture -



Because  $N_{id} = 0$  and no current flows into the op amp inputs, we can write -


- (1)  $I_1 + I_2 = 0$
- (2)  $I_1 R_1 = I_2 R_2$
- (3)  $I_3 + I_4 = 0$
- (4)  $I_3 R_3 = I_4 R_4$
- (5)  $I_4 = I_5$
- (6)  $V_5 = I_5 R_5$
- (7)  $V_1 = V_5$
- (8)  $I_2 = I_3$

Now,  $V_1 = V_5 = I_5 R_5 = I_4 R_5 = \left(\frac{I_3 R_3}{R_4}\right) R_5 = I_2 \left(\frac{R_3 R_5}{R_4}\right)$

$$V_1 = \left(\frac{I_1 R_1}{R_2}\right) \left(\frac{R_3 R_5}{R_4}\right) = \frac{R_1 R_3 R_5}{R_2 R_4} I_1 \rightarrow \boxed{\frac{V_1}{I_1} = \frac{R_1 R_3 R_5}{R_2 R_4}}$$

Frequency Response of Op Amp -

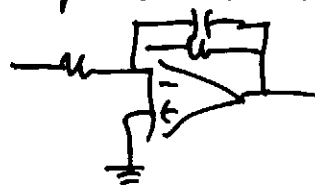
1.) Op amp ideal  $A \rightarrow \infty$   $GB (U_{GB}) \rightarrow \infty$



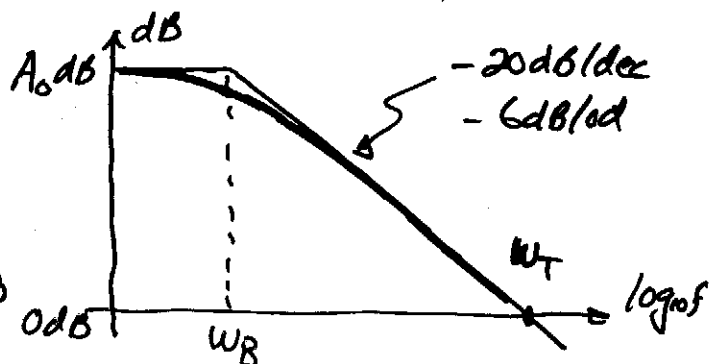
2.) Op amp has a finite  $GB (\neq \infty)$



$$A(s) = \frac{A_0 \omega_B}{s + \omega_B} = \frac{\omega_T}{s + \omega_B}$$



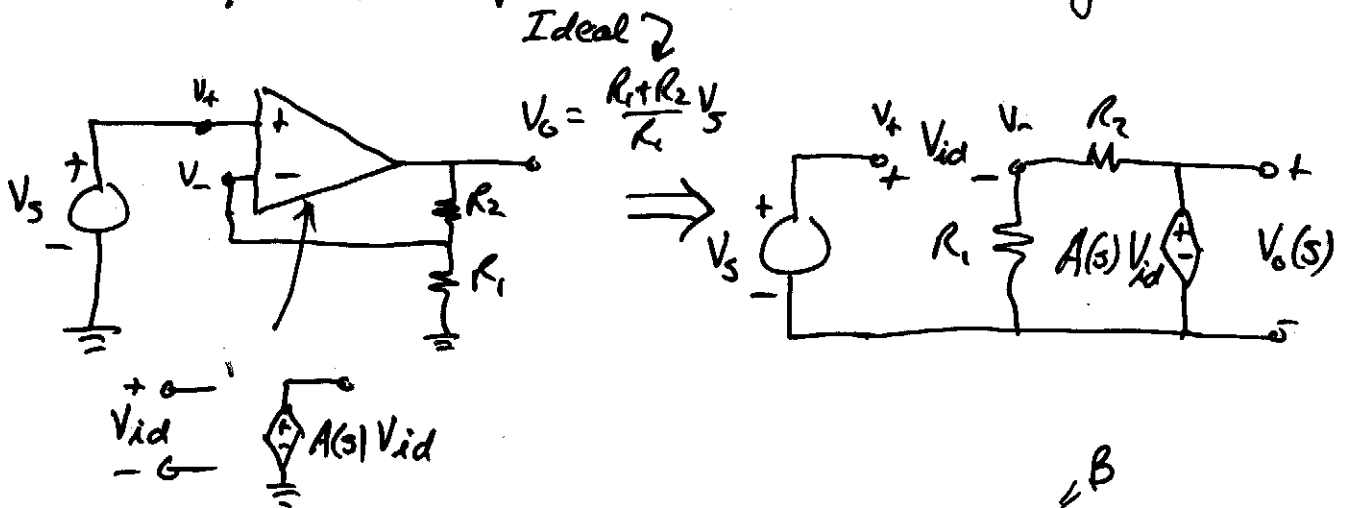2.) Frequency response of the noninverting amplifier.



$$V_o = A(s)V_{id} = A(s)[V_+ - V_-] = A(s)V_s - A(s)\frac{R_1}{R_1 + R_2}V_o$$

$$V_o = A(s)V_s - A(s)\beta V_o \quad \text{where } \beta = \frac{R_1}{R_1 + R_2}$$

$$V_o[1 + A(s)\beta] = A(s)V_s \rightarrow \frac{V_o}{V_s} = A_v(s) = \frac{A(s)}{1 + \beta A(s)}$$


Note:  $\lim_{A(s) \rightarrow \infty} \frac{V_o}{V_s} = \frac{1}{\beta} = \frac{R_1 + R_2}{R_1}$

$$A_v(s) = \frac{1}{\frac{1}{A(s)} + \beta} = \frac{1}{\frac{s + \omega_B}{A_0 \omega_B} + \beta} = \frac{A_0 \omega_B}{s + \omega_B + \beta A_0 \omega_B}$$

$$= \frac{A_0 \omega_B}{s + \omega_B (1 + A_0 \beta)} = \frac{A_0 \omega_B}{\omega_B (1 + A_0 \beta)} \left( \frac{1}{\frac{s}{\omega_B (1 + A_0 \beta)} + 1} \right)$$

$$= \frac{A_v(0)}{\frac{s}{\omega_H} + 1} \quad \text{where } A_v(0) = \frac{A_0}{1 + A_0 \beta} \quad \omega_H = \omega_B (1 + A_0 \beta) \approx \omega_B A_0 \beta$$

Noninverting Conf. - Cont'd

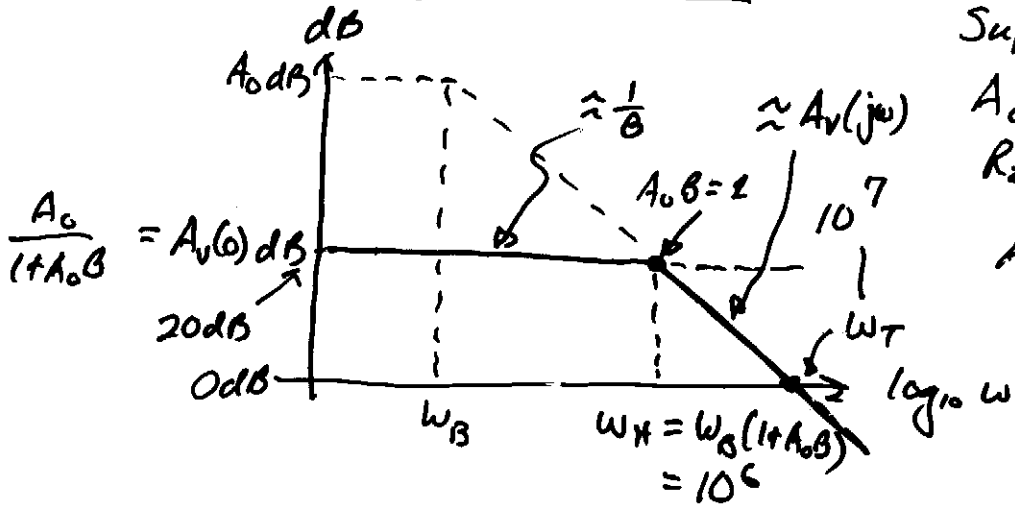

Suppose:

$A_0 = 10,000$  &  $w_B = 10^3$

$R_2 = 9R_1 \Rightarrow \beta = \frac{1}{10}$


$A_v(0) = \frac{10^4}{1+10^3} \approx 10$

$w_H = 10^3(1+10^3)$

$w_H \approx 10^6$

$w_T = A_0 w_B$

3.) Inverting Amplifier-

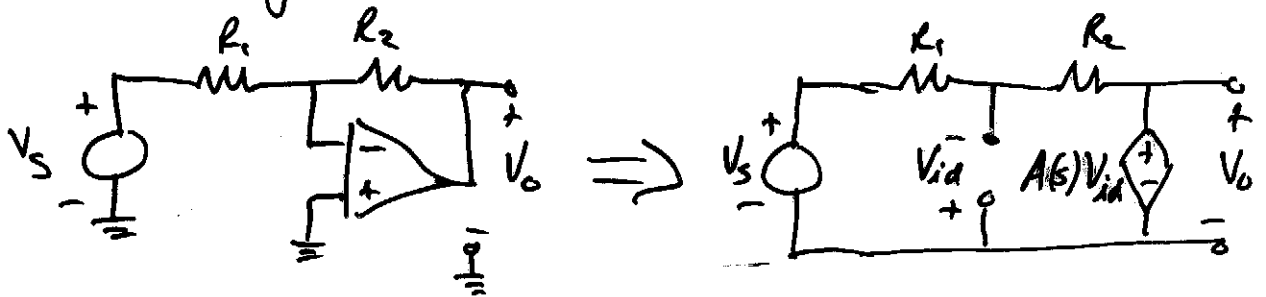


**Homework Assignment No. 2 – Solutions****11.16**

$$g_{11} = \frac{i_1}{v_1} \Big|_{i_2=0} : v_1 = 10^4 i_1 + 101 i_1 (240k\Omega) \rightarrow g_{11} = 4.124 \times 10^{-8} S = 4.12 \times 10^{-8} S$$

$$g_{12} = \frac{i_1}{i_2} \Big|_{v_1=0} : i_1 = -\frac{240k\Omega}{240k\Omega + 10k\Omega} (i_2 + 100i_1) \rightarrow g_{12} = -9.90 \times 10^{-3}$$

$$g_{21} = \frac{v_2}{v_1} \Big|_{i_2=0} : v_2 = 101 i_1 (240k\Omega) \mid i_1 = g_{11} v_1 \rightarrow g_{21} = 1.00$$

$$g_{22} = \frac{v_2}{i_2} \Big|_{v_1=0} : i_2 = \frac{v_2}{240k\Omega} + \frac{v_2}{10k\Omega} + 100 \frac{v_2}{10k\Omega} \rightarrow g_{22} = 99.0 \Omega$$

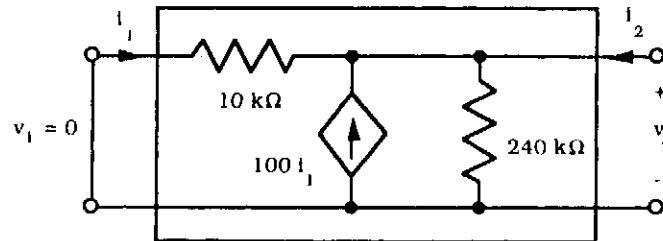**11.34**

$$V_O = V_S \frac{R_{IN}}{R_{IN} + R_S} A \frac{R_{IN}}{R_{IN} + R_{OUT}} A \frac{R_L}{R_L + R_{OUT}}$$

$$A_V = \frac{5000}{5000 + 1000} (-1000) \frac{5000}{5000 + 250} (-1000) \frac{100}{100 + 250} = +2.27 \times 10^5$$

$$A_I = \frac{I_O}{I_S} = \frac{2.27 \times 10^5 V_S}{100} \frac{1}{\frac{V_S}{6000}} = +1.36 \times 10^7$$

$$A_P = \frac{2.27 \times 10^5 V_S (+1.36 \times 10^7 I_S)}{V_S I_S} = +3.09 \times 10^{12}$$

**11.37**


$$A_V = \frac{2\pi \times 10^7 s}{(s + 20\pi)(s + 2\pi \times 10^4)} = \frac{1000s}{(s + 20\pi) \left(1 + \frac{s}{2\pi \times 10^4}\right)} \mid A_{mid} = +1000 = 60 \text{ dB}$$

$$f_L = \frac{20\pi}{2\pi} = 10 \text{ Hz} \mid f_H = \frac{2\pi \times 10^4}{2\pi} = 10 \text{ kHz} \mid \text{BW} = 10\text{kHz} - 10\text{Hz} = 9.99 \text{ kHz}$$

Bandpass Amplifier

**11.43**

Using MATLAB: `n=[2e7*pi 0]; d=[1 (20*pi+2e4*pi) 40e4*pi^2]; bode(n,d)`

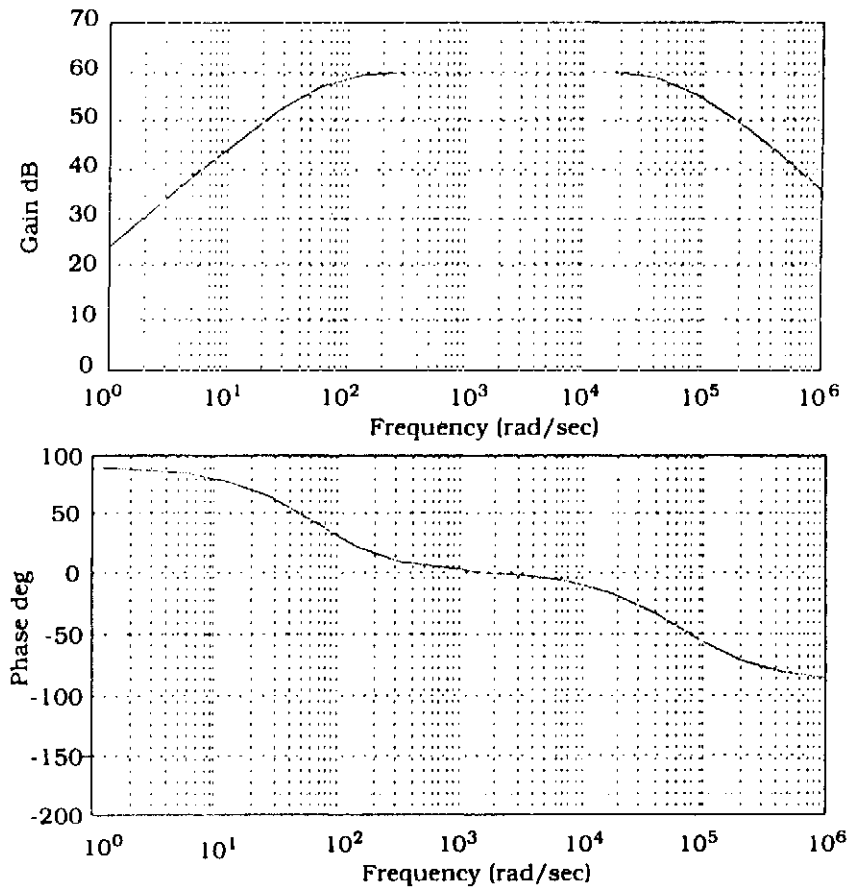**11.55**

$$(a) A_{\text{mid}} = +10^{\frac{20}{20}} = +10 \quad | \quad A_V = \frac{10}{1 + \frac{s}{2\pi \times (5 \times 10^6)}} = \frac{10}{1 + \frac{s}{10^7 \pi}} = \frac{10^8 \pi}{s + 10^7 \pi}$$

$$(b) A_{\text{mid}} = -10^{\frac{20}{20}} = -10 \quad | \quad A_V = -\frac{10^8 \pi}{s + 10^7 \pi}$$

Problem 6

(a.) Find  $V_{out}(s)/V_{in}(s)$  and identify the numerical value of the midband gain and all poles and zeros if  $g_m$  is 1mA/V.

$$\frac{V_{out}}{V_{in}} = \left( \frac{V_{out}}{V_1} \right) \left( \frac{V_1}{V_{in}} \right) = \left( \frac{g_m R_2 R_3}{R_2 + R_3 + \frac{1}{sC_1}} \right) \left( \frac{V_1}{V_{in}} \right)$$


$$V_1 = V_{in} - V_{R2} \rightarrow V_1 = V_{in} - \frac{g_m V_1 R_2 \left( R_3 + \frac{1}{sC_1} \right)}{R_2 + R_3 + \frac{1}{sC_1}} \rightarrow \frac{V_1}{V_{in}} = \frac{1}{1 + \frac{g_m R_2 \left( R_3 + \frac{1}{sC_1} \right)}{R_2 + R_3 + \frac{1}{sC_1}}}$$

$$\begin{aligned} \therefore \frac{V_{out}}{V_{in}} &= \left( \frac{g_m R_2 R_3}{R_2 + R_3 + \frac{1}{sC_1}} \right) \left( \frac{R_2 + R_3 + \frac{1}{sC_1}}{R_2 + R_3 + \frac{1}{sC_1} + g_m R_2 \left( R_3 + \frac{1}{sC_1} \right)} \right) \\ &= \frac{(g_m R_2 R_3) s}{s(R_2 + R_3 + g_m R_2 R_3) + \frac{1 + g_m R_2}{C_1}} = \left( \frac{\frac{g_m R_2 R_3}{R_2 + R_3}}{1 + \frac{g_m R_2 R_3}{R_2 + R_3}} \right) \left( \frac{s}{s + \frac{1 + g_m R_2}{C_1 (R_2 + R_3 + g_m R_2 R_3)}} \right) \end{aligned}$$

$$\therefore \text{MBG} = \frac{\frac{g_m R_2 R_3}{R_2 + R_3}}{1 + \frac{g_m R_2 R_3}{R_2 + R_3}} = \frac{5}{6}$$

$$\begin{aligned} &\text{Zero at } s = 0 \\ &\text{Pole at } s = \frac{-(1 + g_m R_2)}{C_1 (R_2 + R_3 + g_m R_2 R_3)} = -91.67 \text{ rads/sec.} \end{aligned}$$

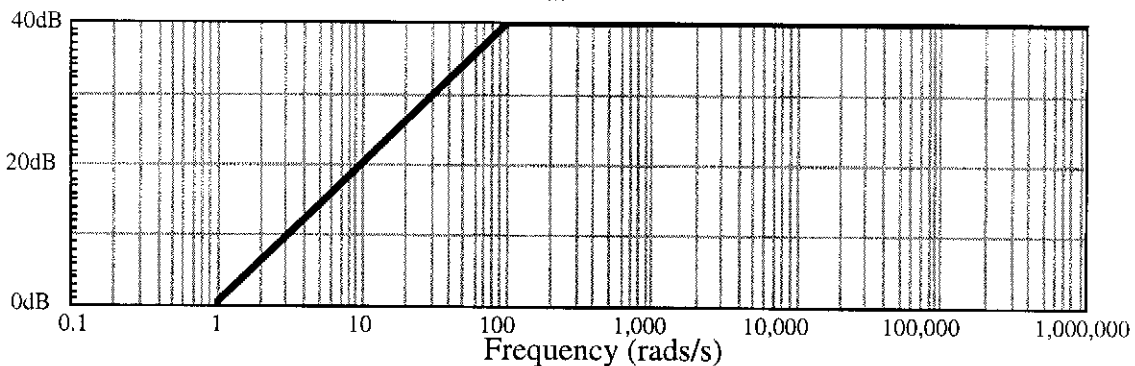(b.) The asymptotic magnitude plot for  $\frac{V_{out}(s)}{V_{in}(s)} = \frac{100s}{s+100}$  is shown below.




**Homework Assignment No. 3**


Due on Monday, September 9, 2002

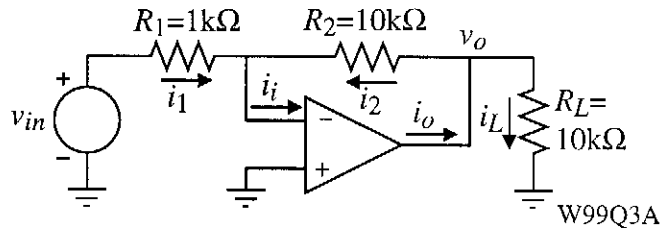1.) The op amps in this problem are ideal.


a.) If  $v_{in} = +1V$ , find the value the currents  $i_1$ ,  $i_i$ ,  $i_2$ ,  $i_o$ , and  $i_L$  including the sign.



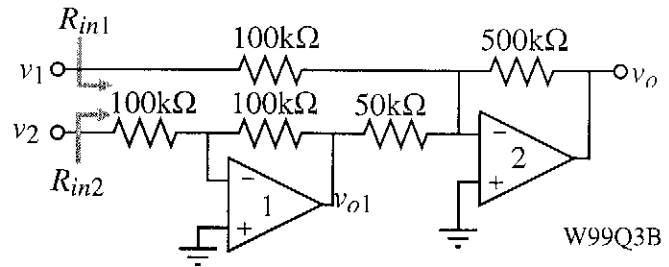b.) Express  $v_o$  as a function of  $v_1$  and  $v_2$  and find  $R_{in1}$  and  $R_{in2}$ .



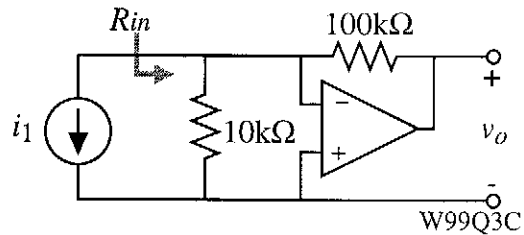c.) Find  $R_{in}$  and  $v_o$  if  $i_1 = 0.1mA$ .



2.) Problem 12.24 of the text [Ans.  $v_{o2} = -\frac{R_2}{R_1} v_s$ , and  $v_{o1} = -\left(\frac{R_2}{R_1} + \frac{R_3}{R_1}\right) v_s$ ]

3.) Problem 12.29 of the text.

4.) Problem 12.74 of the text.