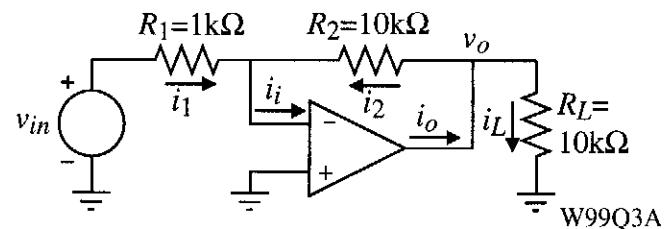


Homework Assignment No. 3 - Solution

1.) The op amps in this problem are ideal.

- a.) If $v_{in} = +1V$, find the value the currents i_1 , i_i , i_2 , i_o , and i_L including the sign.

$$i_1 = \frac{1V}{1k\Omega} = 1mA$$



$$i_i = 0$$

$$i_2 = \frac{-10V}{10k\Omega} = -1mA$$

$$i_L = \frac{-10V}{1k\Omega} = -1mA$$


$$i_o = i_2 + i_L = -2mA$$

- b.) Express v_o as a function of v_1 and v_2 .

Note: $v_{o1} = -v_2$

And

$$v_o = -5v_1 - 10v_{o1}$$

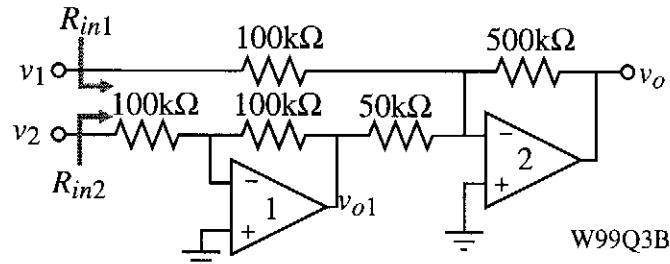

$$\therefore v_o = -5v_1 - 10(-v_2) = -5v_1 + 10v_2$$

$$v_o = -5v_1 + 10v_2$$

$$R_{in1} = R_{in2} = 100k\Omega$$


- c.) Find R_{in} and v_o if $i_1 = 0.1mA$.

$$R_{in} = 0$$

and

$$v_o = 100k\Omega \cdot i_1 = 100k\Omega \cdot 0.1mA = 10V$$

R_{in} and v_o if $i_1 = 0.1mA$.

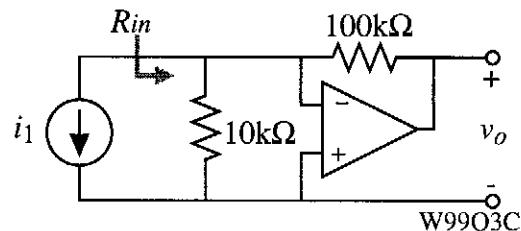

12.24 Applying op-amp assumption 1 to the circuit on the next page, the voltage at the top of R_2 is v_{O2} , and applying op-amp assumption 2,


$$\frac{v_s}{R_1} = -\frac{v_{O2}}{R_2} \quad \text{or} \quad v_{O2} = -v_s \frac{R_2}{R_1}$$

Since the op-amp input currents are zero, and

$$I = \frac{v_s}{R_1}, \quad v_{O1} = -IR_2 - IR_3 = -\left(\frac{R_2}{R_1} + \frac{R_3}{R_1}\right)v_s$$

Alternatively, the voltage at the bottom of R_2 is zero, so
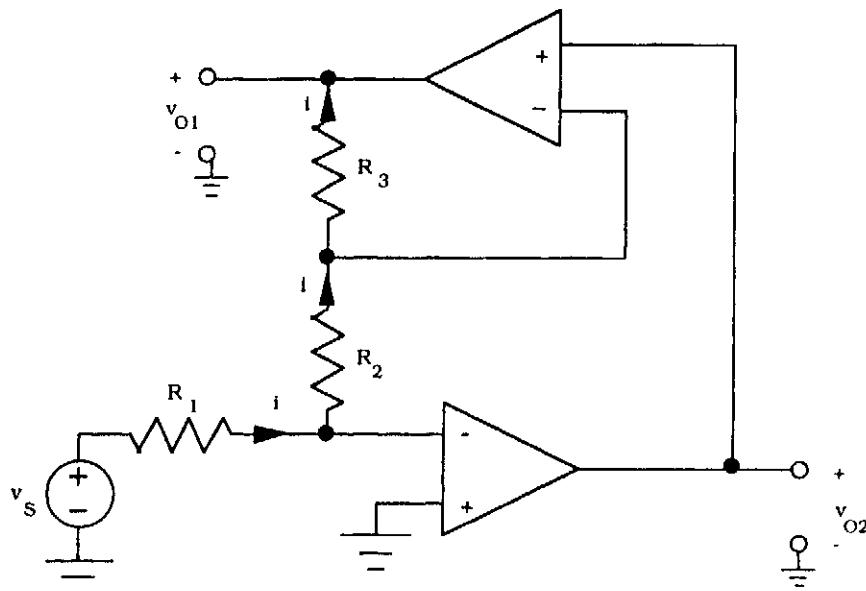
$$v_{O1} = \left(1 + \frac{R_3}{R_2}\right)v_{O2} = \left(1 + \frac{R_3}{R_2}\right)\left(-\frac{R_2}{R_1}\right)v_s = -\left(\frac{R_2}{R_1} + \frac{R_3}{R_1}\right)v_s$$



12.29 Taking successive Thévenin equivalent circuits at each ladder node yields:

$$-\frac{V_{REF}}{16} = -0.3V \quad | \quad -\frac{V_{REF}}{8} = -0.6V \quad | \quad -\frac{V_{REF}}{4} = -1.2V \quad | \quad -\frac{V_{REF}}{2} = -2.4V$$

12.74

$$\beta = \frac{2k\Omega}{2k\Omega + 40k\Omega} = \frac{1}{21} \quad | \quad A\beta = \frac{10^5}{21} = 4760 \gg 1$$

$$(a) A_V = -\frac{R_2}{R_1} = -\frac{40k\Omega}{2k\Omega} = -20 \quad | \quad f_H = \beta f_T = \frac{3 \times 10^6 \text{ Hz}}{21} = 143 \text{ kHz}$$

$$(b) A_V = (-20)^3 = -8000 \text{ (78dB)} \quad | \quad f_{H3} = 0.51f_H = 72.9 \text{ kHz}$$