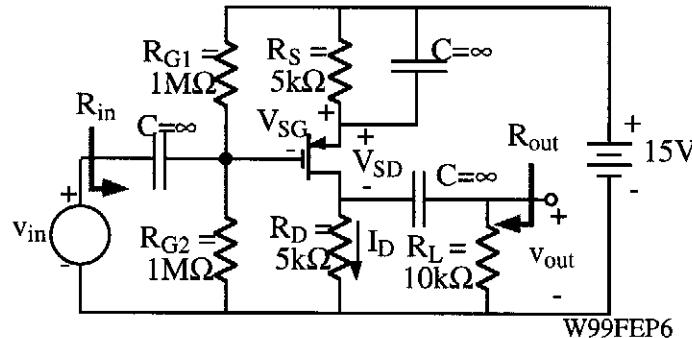


**Homework Assignment No. 5 - Solutions**

- 1.) Find the dc operating point, the small signal voltage gain,  $v_{out}/v_{in}$ , the small signal input resistance,  $R_{in}$ , and the small signal output resistance,  $R_{out}$ , if  $K = 0.1\text{mA/V}^2$ ,  $V_t = -1\text{V}$ , and  $\lambda = 0.01\text{V}^{-1}$ .

**Solution**

Finding the dc Thevenin equivalent circuit looking out the gate gives  $V_{GG} = 7.5\text{V}$  and  $R_G = 0.5\text{M}\Omega$ . Assuming saturation gives  $I_D = K(V_{GS} - V_t)^2$ . Combining with

$$V_{GG} = 7.5\text{V} = V_{GS} + I_D R_S$$

$$\text{gives } 7.5 = V_{GS} + 5\text{k}\Omega \cdot 0.1\text{mA/V}^2 (V_{GS} - 1)^2 = V_{GS} + 0.5V_{GS}^2 - V_{GS} + 0.5$$

$$\text{which reduces to } V_{GS}^2 = 14 \rightarrow V_{GS} = \sqrt{14} = 3.74\text{V}$$


This gives  $I_D = 0.1\text{mA}(3.75-1)^2 = 0.752\text{mA}$ . Finally,  $V_{DS} = 15 - I_D(R_D + R_S) = 7.48\text{V}$

$$\therefore \boxed{V_{SG} = 3.74\text{V}, I_D = 0.752\text{mA} \text{ and } V_{SD} = 7.48\text{V}}$$

Note that the MOSFET is indeed saturated.

The small signal model parameters are  $g_m = 2\sqrt{KI_D} = 2\sqrt{0.1 \cdot 0.752} = 0.548\text{mA/V}$  and  $r_{ds} = (\lambda I_D)^{-1} = 100/0.752 = 133\text{k}\Omega$ .

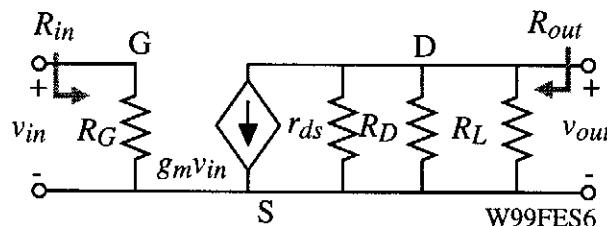The small-signal model for this problem is,



$$\frac{v_{out}}{v_{in}} = -g_m(r_{ds} \| R_D \| R_L) = -0.548(133 \| 5 \| 10) = -1.782\text{V/V}, \quad R_{in} = 500\text{k}\Omega$$

$$\text{and } R_{out} = r_{ds} \| R_D \| R_L = 3.25\text{k}\Omega.$$

$$\therefore \boxed{R_{in} = 500\text{k}\Omega, R_{out} = 3.25\text{k}\Omega \text{ and } \frac{v_{out}}{v_{in}} = -1.782 \text{ V/V}}$$

**13.91**

$$g_m = \sqrt{2 \left( 500 \frac{\mu A}{V^2} \right) (100\mu A) (1 + 0.02(5))} = 332\mu S \quad | \quad r_o = \frac{50 + 5V}{100\mu A} = 550k\Omega$$

$$A_v = - \left( \frac{6.8M\Omega}{6.8M\Omega + 0.1M\Omega} \right) (332\mu S) (550k\Omega \| 50k\Omega \| 120k\Omega) = -10.9$$

**13.100**

$$g_m = \frac{2}{3} \sqrt{ImA(1mA)[1 + 0.015(9)]} = 710\mu S \quad | \quad r_o = \frac{\frac{1}{0.015} + 9V}{1mA} = 75.7k\Omega$$

$$A_v = - \left( \frac{1M\Omega}{1M\Omega + 10k\Omega} \right) (710\mu S) (75.7k\Omega \| 7.5k\Omega \| 160k\Omega) = -4.60$$

**13.108**

$$R_{IN} = R_G = 6.8M\Omega \quad | \quad R_{OUT} = 50k\Omega \| r_o$$

$$r_o = \frac{(50 + 5)V}{0.1mA} = 550k\Omega \quad | \quad R_{OUT} = 50k\Omega \| 550k\Omega = 45.8k\Omega$$

**13.119**

$$I_B = \frac{(5 - 0.7)V}{10000\Omega + 66(1600)\Omega} = 37.2 \mu A \quad | \quad I_C = 65I_B = 2.42 mA \quad | \quad I_E = 66I_B = 2.46 mA$$

$$V_{CE} = 10 - 1000I_C - 1600I_E - (-5) = 8.64 V$$

$$g_m = 40(0.00242) = 0.0968S \quad | \quad r_\pi = \frac{65}{0.0968S} = 672\Omega \quad | \quad r_o = \frac{50 + 8.64}{0.00242} = 24.2k\Omega$$

$$R_{IN} = R_B \| r_\pi = 10k\Omega \| 672\Omega = 630\Omega \quad | \quad R_{OUT} = 1k\Omega \| 24.2k\Omega = 960 \Omega$$

$$A_v = - \left( \frac{630}{330 + 630} \right) (0.0968)(1k\Omega \| 24.2k\Omega \| 220k\Omega) = -60.7$$

Note that the gain has been reduced by 25% by the lower value of  $R_{IN}$ . Also note that  $R_{IN}$  and  $R_{OUT}$  have changed directly with the current.