
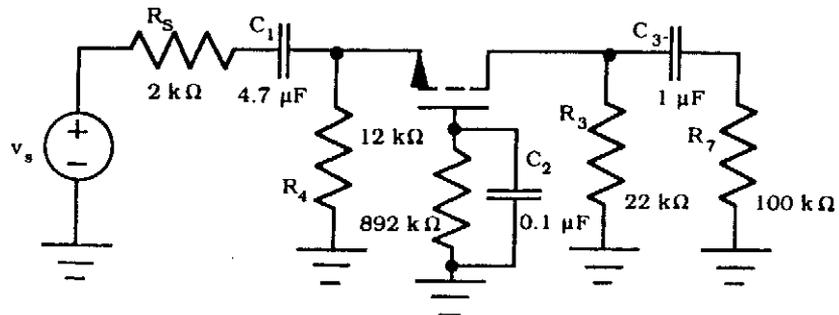


**Homework Assignment No. 10 - Solutions****17.14**

Low Frequency:

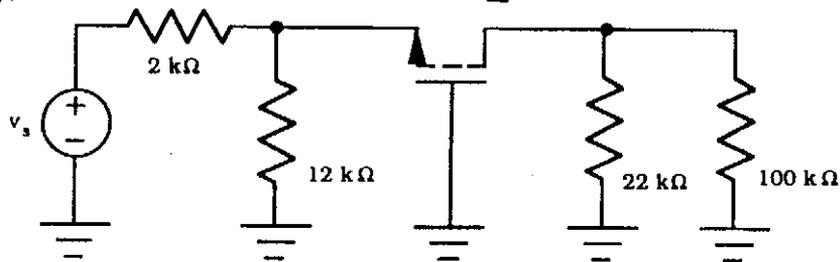

Mid-band:

$$g_m = \frac{2(0.1\text{mA})}{1\text{V}} = 0.200\text{mS} \quad \left| \quad \frac{1}{g_m} = 5000\Omega \quad \left| \quad v_{th} = \frac{12\text{k}\Omega}{12\text{k}\Omega + 2\text{k}\Omega} v_s = 0.857 v_s \right.$$

$$R_{th} = 12\text{k}\Omega \parallel 2\text{k}\Omega = 1.71\text{k}\Omega \quad \left| \quad R_L = 22\text{k}\Omega \parallel 100\text{k}\Omega = 18.0\text{k}\Omega$$

$$A_{mid} = 0.857 \frac{R_L}{R_{th} + \frac{1}{g_m}} = 0.857 \frac{18.0\text{k}\Omega}{1.71\text{k}\Omega + 5\text{k}\Omega} = 2.30 \quad (7.24\text{dB})$$

$$\omega_1 = \frac{1}{4.7 \times 10^{-6} (2\text{k}\Omega + 12\text{k}\Omega \parallel 5\text{k}\Omega)} = 38.5 \frac{\text{rad}}{\text{s}} \quad \left| \quad \omega_2 = \text{doesn't matter since } i_g = 0 \right.$$

$$\omega_3 = \frac{1}{10^{-7} (100\text{k}\Omega + 22\text{k}\Omega)} = 82.0 \frac{\text{rad}}{\text{s}} \quad \left| \quad f_L = \frac{1}{2\pi} (38.5 + 82.0) = 19.2\text{Hz}$$

**17.17**

$$\text{SCTC requires: } \omega_L \cong \sum_{i=1}^3 \frac{1}{R_{is} C_i} = 2\pi(500) = 3140 \frac{\text{rad}}{\text{s}}$$

$$\omega_1 = \frac{1}{(10^{-7}\text{F})(2.43\text{M}\Omega + 1\text{k}\Omega)} = 4.11 \frac{\text{rad}}{\text{s}} \quad \left| \quad \omega_2 = \frac{1}{(10^{-7}\text{F})(43\text{k}\Omega + 1\text{M}\Omega)} = 9.59 \frac{\text{rad}}{\text{s}}$$

$$\omega_1 + \omega_2 \ll \omega_L \quad \left| \quad \omega_3 \text{ will be dominant} \rightarrow \omega_3 \cong \omega_L$$


$$\omega_3 = \frac{1}{C_3 \left( R_4 \parallel \frac{1}{g_m} \right)} \quad \left| \quad g_m = \frac{2I_{DS}}{V_{GS} - V_{TN}} = \frac{2(0.2\text{mA})}{1\text{V}} = 0.400\text{mS} \quad \left| \quad \frac{1}{g_m} = 2.50\text{k}\Omega$$

$$C_3 = \frac{1}{3140(13\text{k}\Omega \parallel 2.5\text{k}\Omega)} = 0.152 \mu\text{F} \rightarrow 0.15 \mu\text{F} \text{ from Appendix C}$$

**17.25**

$$C_{\pi} = g_m \tau_F \quad | \quad C_{\pi} = \frac{g_m}{\omega_T} - C_{\mu} \quad | \quad V_{CB} = 5 - 0.7 = 4.3 \text{ V} \quad | \quad C_{\mu} = \frac{C_{\mu 0}}{\sqrt{1 + \frac{V_{CB}}{\phi_{jc}}}} = \frac{2 \text{ pF}}{\sqrt{1 + \frac{4.3 \text{ V}}{0.9 \text{ V}}}} = 0.832 \text{ pF}$$

$$C_{\pi} = \frac{40(2 \times 10^{-3})}{2\pi(5 \times 10^8)} - 0.832 \text{ pF} = 24.6 \text{ pF} \quad | \quad \tau_F = \frac{C_{\pi}}{g_m} = \frac{24.6 \times 10^{-12}}{40(2 \times 10^{-3})} = 0.308 \text{ ns} = 308 \text{ ps}$$

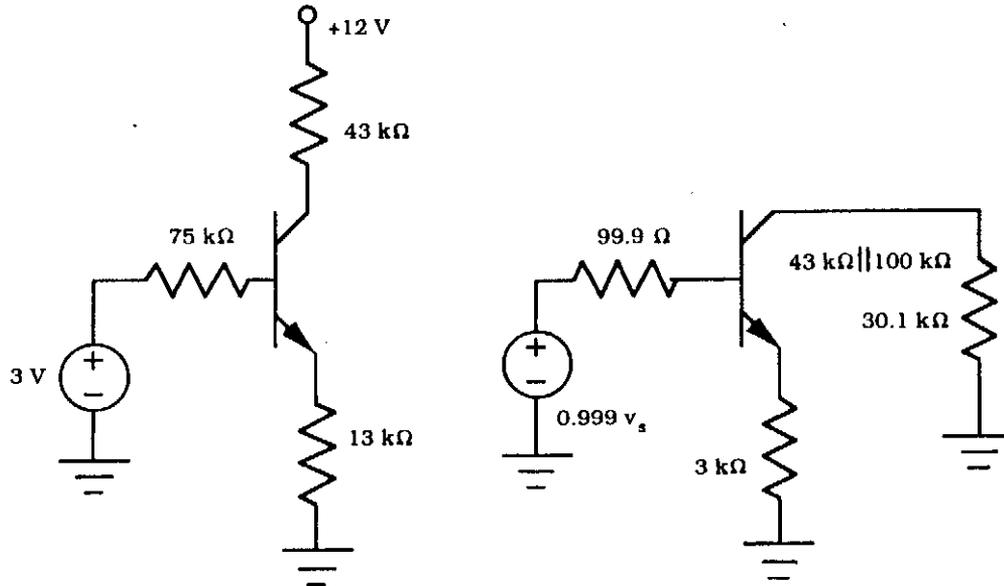**17.41**

$$I_B = \frac{3 - 0.7}{75 \text{ k}\Omega + 101(13 \text{ k}\Omega)} = 1.657 \mu\text{A} \quad | \quad I_C = 166 \mu\text{A} \quad | \quad V_{CE} = 12 - 43 \text{ k}\Omega(I_C) - 13 \text{ k}\Omega \left( \frac{I_C}{\alpha_F} \right) = 2.70 \text{ V}$$

$$2.70 \text{ V} \geq 0.7 \text{ V} \quad \text{Forward - active region is correct.} \quad | \quad r_{\pi} = \frac{100(0.025)}{0.166 \text{ mA}} = 15.1 \text{ k}\Omega$$

$$g_m = 40(0.166 \text{ mA}) = 6.63 \text{ mS} \quad | \quad C_{\pi} = \frac{6.63 \text{ mS}}{2\pi(3 \times 10^8)} - 0.5 = 3.02 \text{ pF} \quad | \quad r_x = 300 \Omega \quad | \quad C_{\mu} = 0.5 \text{ pF}$$

$$v_{th} = \frac{75 \text{ k}\Omega}{75 \text{ k}\Omega + 100 \Omega} v_s = 0.999 v_s \quad | \quad R_{th} = 75 \text{ k}\Omega \parallel 100 \Omega = 99.9 \Omega \quad | \quad R_L = 43 \text{ k}\Omega \parallel 100 \text{ k}\Omega = 30.1 \text{ k}\Omega$$

$$A_{mid} = 0.999 \frac{-100(30.1 \text{ k}\Omega)}{99.9 \Omega + 300 \Omega + 15.1 \text{ k}\Omega + 101(3 \text{ k}\Omega)} = -9.44$$

**Short-Circuit Time Constants**

$$R_{1S} = 100 \Omega + 75 \text{ k}\Omega \parallel \left[ 300 \Omega + 15.1 \text{ k}\Omega + 101(3 \text{ k}\Omega) \right] = 60.8 \text{ k}\Omega$$

$$R_{2S} = 43 \text{ k}\Omega + 100 \text{ k}\Omega = 143 \text{ k}\Omega$$

$$R_{3S} = 10 \text{ k}\Omega \parallel \left( 3 \text{ k}\Omega + \frac{15.1 \text{ k}\Omega + 99.9 \Omega}{101} \right) = 2.40 \text{ k}\Omega$$

$$f_L \approx \frac{1}{2\pi} \left[ \frac{1}{(60.8 \text{ k}\Omega)(1 \mu\text{F})} + \frac{1}{(143 \text{ k}\Omega)(0.1 \mu\text{F})} + \frac{1}{(2.40 \text{ k}\Omega)(2.2 \mu\text{F})} \right] = 43.9 \text{ Hz}$$

Prob. 7.41- Continued


## Open-Circuit Time Constants

Using the result in Table 17.2 on page 944:  $R_{th} + r_x = 99.9\Omega + 300\Omega = 400\Omega$

$$C_{TB} = \frac{3.02\text{pF}}{1 + (6.63\text{mS})(3\text{k}\Omega)} \left(1 + \frac{3\text{k}\Omega}{400\Omega}\right) + 0.5\text{pF} \left[1 + \frac{(6.63\text{mS})(30.1\text{k}\Omega)}{1 + (6.63\text{mS})(3\text{k}\Omega)} + \frac{30.1\text{k}\Omega}{400\Omega}\right]$$

$$C_{TB} = 44.1\text{pF} \quad f_H = \frac{1}{2\pi(400\Omega)(44.1\text{pF})} = 9.02\text{ MHz}$$

17.48

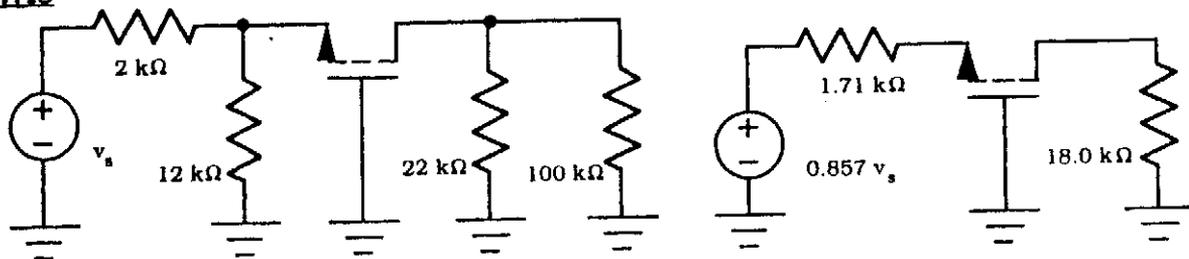

$$v_{th} = \frac{12\text{k}\Omega}{12\text{k}\Omega + 2\text{k}\Omega} v_s = 0.857 v_s \quad | \quad R_{th} = 12\text{k}\Omega \parallel 2\text{k}\Omega = 1.71\text{k}\Omega \quad | \quad R_L = 22\text{k}\Omega \parallel 100\text{k}\Omega = 18.0\text{k}\Omega$$

$$g_m = \frac{2(0.1\text{mA})}{1\text{V}} = 0.2\text{mS} \quad | \quad C_{GS} = 3.0\text{pF} \quad | \quad C_{GD} = 0.6\text{pF}$$

$$A_{mid} = 0.857 \frac{R_L}{R_{th} + \frac{1}{g_m}} = 0.857 \frac{18.0\text{k}\Omega}{1.71\text{k}\Omega + \frac{1}{0.2\text{mS}}} = +2.30$$

$$f_H = \frac{1}{2\pi} \left( \frac{1}{\frac{C_{GS}}{G_{th} + g_m} + C_{GD}R_L} \right) = \frac{1}{2\pi} \left( \frac{1}{\frac{3.0\text{pF}}{(0.5848 + 0.2)\text{mS}} + 0.6\text{pF}(18.0\text{k}\Omega)} \right) = 10.9\text{ MHz}$$