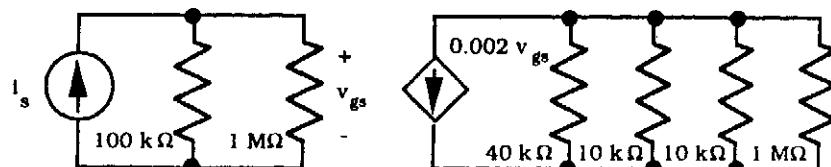


Homework Assignment No. 13 - Solutions**18.22**

$$y_{11}^F = \left. \frac{i_1}{v_1} \right|_{v_2=0} = 10^{-6} S \quad | \quad y_{22}^F = \left. \frac{i_2}{v_2} \right|_{v_1=0} = 10^{-6} S \quad | \quad y_{12}^F = \left. \frac{i_1}{v_2} \right|_{v_1=0} = -10^{-6} S$$

$$v_{gs} = i_s(100k\Omega \parallel 1M\Omega) = (90.9k\Omega)i_s \quad | \quad v_o = -(2 \times 10^{-3})v_{gs}(40k\Omega \parallel 10k\Omega \parallel 10k\Omega \parallel 1M\Omega)$$

$$A = \frac{v_o}{i_s} = -(2mS)(4.44k\Omega)(90.9k\Omega) = -8.08 \times 10^5$$

$$A_{TR} = \frac{A}{1 + A\beta} = \frac{-8.08 \times 10^5}{1 + (-8.08 \times 10^5)(-10^{-6})} = \frac{-8.08 \times 10^5}{1.81} = -446 k\Omega$$

$$R_{IN} = \frac{(100k\Omega \parallel 1M\Omega)}{(1 + A\beta)} = \frac{90.9k\Omega}{1.81} = 50.2 k\Omega$$


$$R_{OUT} = \frac{(40k\Omega \parallel 10k\Omega \parallel 10k\Omega \parallel 1M\Omega)}{(1 + A\beta)} = \frac{4.44k\Omega}{1.81} = 2.45k\Omega$$

**18.23**

$$g_{11}^F = \left. \frac{i_1}{v_1} \right|_{i_2=0} = \frac{1}{11k\Omega} \quad | \quad g_{22}^F = \left. \frac{v_2}{i_2} \right|_{v_1=0} = 1k\Omega \parallel 10k\Omega = 909\Omega \quad | \quad g_{12}^F = \left. \frac{i_1}{i_2} \right|_{v_1=0} = -\frac{1k\Omega}{10k\Omega + 1k\Omega} = -\frac{1}{11}$$

$$A = \frac{i_2}{i_s} = -(100k\Omega \parallel 11k\Omega \parallel 15k\Omega) \frac{5k\Omega}{(5+1+0.909)k\Omega} = -4.32 \times 10^3$$
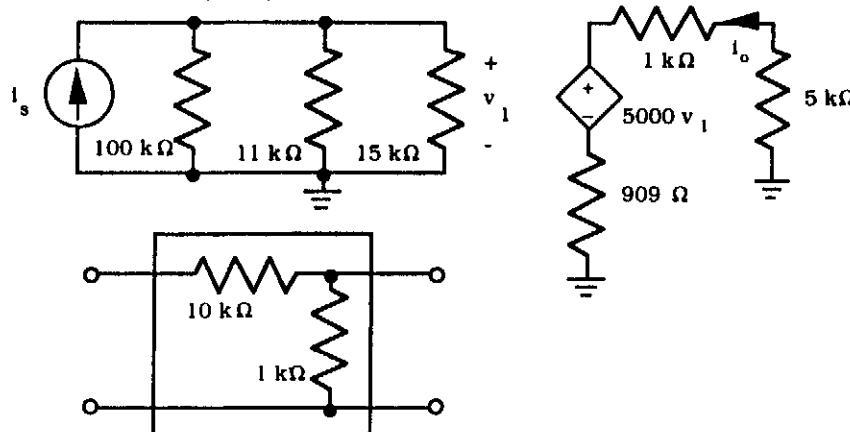
$$A_I = \frac{A}{1 + A\beta} = \frac{-4.32 \times 10^3}{1 + (-4.32 \times 10^3)\left(-\frac{1}{11}\right)} = -11.0$$



$$R_{IN} = \frac{(100k\Omega \parallel 11k\Omega \parallel 15k\Omega)}{(1 + A\beta)} = \frac{5.97k\Omega}{394} = 15.2 \Omega$$

$$R_{OUT} = (5k\Omega + 1k\Omega + 0.909k\Omega)(1 + A\beta) = (6.91k\Omega)(394) = 2.72M\Omega$$

**18.24** See Problem 18.16 for the Q-point calculation.

$$g_{11}^F = \left. \frac{i_1}{v_1} \right|_{i_2=0} = \frac{1}{37 \text{ k}\Omega} \quad | \quad g_{22}^F = \left. \frac{v_2}{i_2} \right|_{v_1=0} = 36\text{k}\Omega \parallel 1\text{k}\Omega = 973 \text{ }\Omega \quad | \quad g_{12}^F = \left. \frac{i_1}{i_2} \right|_{v_1=0} = -\frac{1\text{k}\Omega}{1\text{k}\Omega + 36\text{k}\Omega} = -\frac{1}{37}$$

$$1\text{k}\Omega \parallel 37\text{k}\Omega = 974 \text{ }\Omega \quad | \quad r_{\pi 1} = \frac{100(0.025)}{491\mu\text{A}} = 5.09 \text{ k}\Omega \quad | \quad r_{\pi 2} = \frac{100(0.025)}{873\mu\text{A}} = 2.86 \text{ k}\Omega$$



$$A = \frac{i_o}{i_s} = -\frac{974\Omega}{974\Omega + 5090\Omega} (-100)(101) \left( \frac{4700\Omega}{973\Omega + 4700\Omega} \right) = -1340$$

$$A_t = \frac{A}{1 + A\beta} = \frac{-1340}{1 + (-1340)\left(-\frac{1}{37}\right)} = \frac{-1340}{37.2} = -36.0 \quad | \quad 1 + A\beta = 37.2$$

$$A_v = \frac{v_o}{v_s} = \frac{973i_o}{1000i_s} = 0.973 \frac{i_o}{i_s} = -35.0$$

$$R_{IN} = \frac{(1\text{k}\Omega \parallel 37\text{k}\Omega \parallel r_{\pi 1})}{1 + A\beta} = \frac{(1\text{k}\Omega \parallel 37\text{k}\Omega \parallel 5.09\text{k}\Omega)}{37.2} = 22.0 \text{ }\Omega \quad | \quad r_{o1} = \frac{50 + 1.6}{493 \times 10^{-6}} = 105 \text{ k}\Omega$$
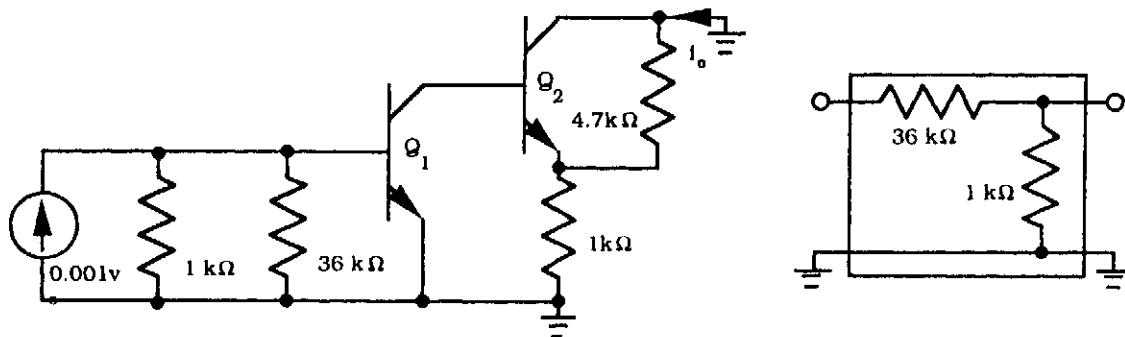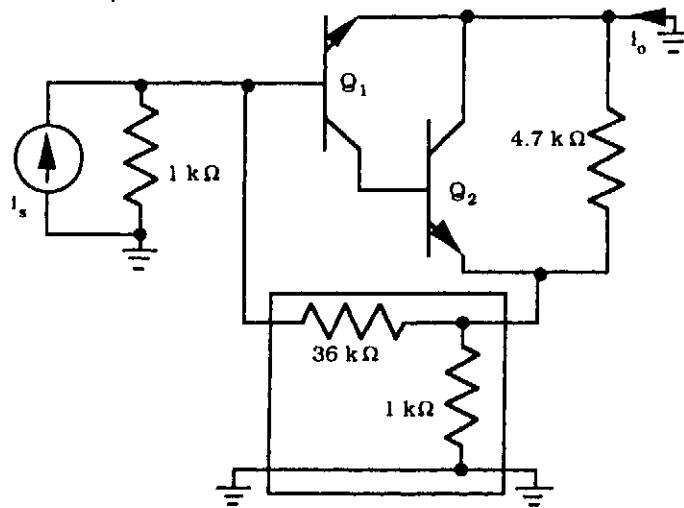
$$R_{OUT} = \frac{\left( 1\text{k}\Omega \parallel 36\text{k}\Omega \parallel 4.7\text{k}\Omega \parallel \frac{r_{\pi 2} + r_{o1}}{101} \right)}{1 + A\beta} = \frac{\left( 1\text{k}\Omega \parallel 36\text{k}\Omega \parallel 4.7\text{k}\Omega \parallel \frac{5.09\text{k}\Omega + 105\text{k}\Omega}{101} \right)}{37.2} = 12.5 \text{ }\Omega$$




4.) Use the method of feedback analysis to find  $v_2/v_1$ ,  $R_{in} = v_1/i_1$ , and  $R_{out} = v_2/i_2$ .

Assume that all transistors are matched and that  $g_{m1} = g_{m2} = 1\text{mS}$ . Neglect  $r_{ds}$ .

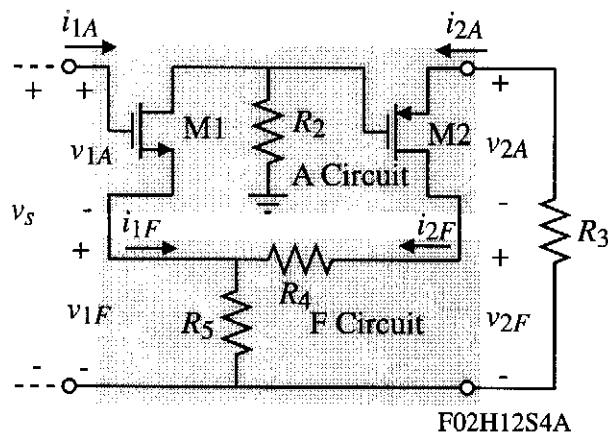
### Solution

The topology is series-series.

The circuit is redrawn below in order to help identify the various terms for the analysis:



Calculation of the A circuit:

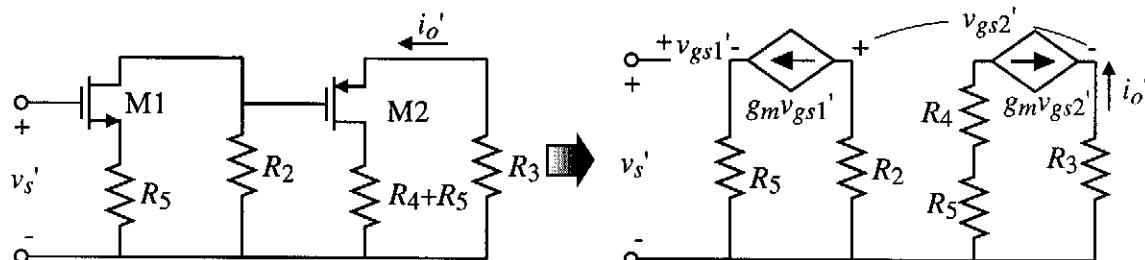

$$A = \frac{i_o'}{v_s'} = \left( \frac{i_o'}{v_{gs2'}} \right) \left( \frac{v_{gs2'}}{v_{gs1'}} \right) \left( \frac{v_{gs1'}}{v_s'} \right) = (-g_m) \left( \frac{-g_m R_2}{1 + g_m R_3} \right) \left( \frac{1}{1 + g_m R_5} \right) = (10^{-3})(-5)(-0.5) = 2.5 \text{ mS}$$

$$\therefore \frac{i_o}{v_s} = \frac{A}{1+A\beta} = \frac{2.5 \text{ mS}}{1+2.5} = 0.714 \text{ mS}$$


Since,  $z_{11A} = \infty$ , then  $R_{in} = 50\text{k}\Omega \parallel \infty = 50\text{k}\Omega$

$$\frac{v_2}{v_1} = \frac{-i_o R_3}{v_s} = \frac{-i_o}{v_s} R_3 = -0.714 \text{ mS} (1\text{k}\Omega) = \underline{\underline{-0.714 \text{ V/V}}}$$

$$R_o = (z_{22T} + R_3)(1 + A\beta) = \left( \frac{1}{g_m} + R_3 \right) (1 + A\beta) = 2\text{k}\Omega (3.5) = 7\text{k}\Omega$$

However, the output resistance specified by the problem,  $R_{out}$ , is found as
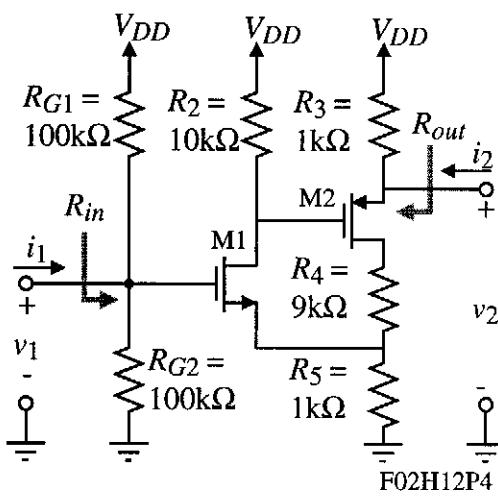
$$R_{out} = (R_o - R_3) \parallel R_3 = 6\text{k}\Omega \parallel 1\text{k}\Omega = \underline{\underline{857\Omega}}$$



$$z_{11F} = \frac{v_{1F}}{i_{1F}} \mid i_{2F}=0 = R_5 = 1\text{k}\Omega$$

$$z_{22F} = \frac{v_{2F}}{i_{2F}} \mid i_{1F}=0 = R_4 + R_5 = 10\text{k}\Omega$$

$$z_{12F} = \beta = \frac{v_{1F}}{i_{2F}} \mid i_{1F}=0 = R_5 = 1\text{k}\Omega$$

**18.32**

$$(a) A(s) = \frac{\frac{2 \times 10^{14} \pi^2}{(2\pi \times 10^3)(2\pi \times 10^5)}}{\left(1 + \frac{s}{2\pi \times 10^3}\right)\left(1 + \frac{s}{2\pi \times 10^5}\right)} = \frac{5 \times 10^5}{\left(1 + \frac{s}{2\pi \times 10^3}\right)\left(1 + \frac{s}{2\pi \times 10^5}\right)}$$

$A(s)$  represents a low - pass amplifier with two widely - spaced poles

Open - loop:  $A_o = 5 \times 10^5 = 114 \text{ dB}$  |  $f_L = 0$  |  $f_H \approx f_t = 1000 \text{ Hz}$

(b) A common mistake would be the following:

$$\text{Closed - loop: } f_H = 1000 \text{ Hz} [1 + 5 \times 10^5 (0.01)] = 5 \text{ MHz}$$

Oops! - This exceeds  $f_2 = 100 \text{ kHz}$ ! This is a two - pole amplifier.

$$A_V(s) = \frac{\frac{2 \times 10^{14} \pi^2}{(s + 2\pi \times 10^3)(s + 2\pi \times 10^5)}}{1 + \frac{\frac{2 \times 10^{14} \pi^2}{(s + 2\pi \times 10^3)(s + 2\pi \times 10^5)}}{(0.01)}} = \frac{2 \times 10^{14} \pi^2}{s^2 + 1.01(2\pi \times 10^5)s + 2 \times 10^{12} \pi^2}$$

Using dominant - root factorization:  $f_1 = 101 \text{ kHz}$ ,  $f_2 = 4.95 \text{ MHz}$

So the closed - loop values are  $f_H = 101 \text{ kHz}$  and  $f_L = 0$ .

---