
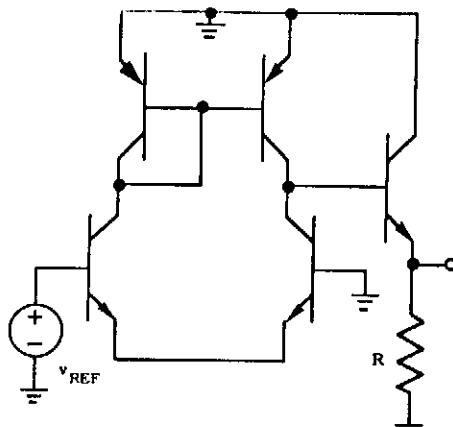


Homework Assignment No. 12 - Solutions

1.) Problem 18.11 of the text.

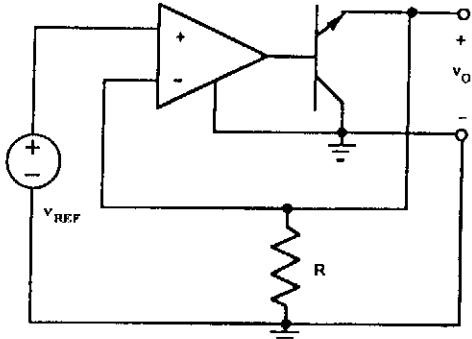

A-Circuit

$$h_{11}^F = \left. \frac{v_1}{i_1} \right|_{v_2=0} = 0 \quad | \quad h_{22}^F = \left. \frac{i_2}{v_2} \right|_{i_1=0} = \frac{1}{R} \quad | \quad h_{12}^F = \left. \frac{v_1}{v_2} \right|_{i_1=0} = 1$$

$$A = g_m r_{o1} \parallel r_{o4} \parallel [r_{\pi 5} + (\beta_o + 1)R] \frac{(\beta_o + 1)R}{r_{\pi 5} + (\beta_o + 1)R} = g_m \frac{r_{o1} \parallel r_{o4}}{(r_{o1} \parallel r_{o4}) + r_{\pi 5} + (\beta_o + 1)R} (\beta_o + 1)R$$

$$r_{o1} = \frac{50 + 1.4}{10^{-4}} = 514 \text{ k}\Omega \quad | \quad r_{o4} = \frac{50 + 11.3}{10^{-4}} = 613 \text{ k}\Omega \quad | \quad r_{o1} \parallel r_{o4} = 280 \text{ k}\Omega$$

$$I_{C5} = \frac{12}{10^4} = 1.2 \text{ mA} \quad | \quad r_{\pi 5} = \frac{100(0.025)}{1.2 \text{ mA}} = 2.08 \text{ k}\Omega$$

$$A = 40(10^{-4})(280 \text{ k}\Omega) \frac{(101)10 \text{ k}\Omega}{280 \text{ k}\Omega + 2.08 \text{ k}\Omega + (101)10 \text{ k}\Omega} = 876$$



$$A_V = \frac{A}{1+T} = \frac{876}{1+876(1)} = \frac{109}{110} = 0.999$$

$$R_{IN} = R_{ID}(1+T) = 2r_{\pi 1}(1+T) = 2 \frac{100(0.025)}{10^{-4}} (877) = 43.9 \text{ M}\Omega$$

$$R_{OUT} = \frac{R \left| \frac{r_{\pi 5} + r_{o2} \parallel r_{o4}}{\beta_o + 1} \right|}{1+T} = \frac{10 \text{ k}\Omega \left| \frac{2.08 \text{ k}\Omega + 280 \text{ k}\Omega}{101} \right|}{877} = 2.49 \text{ }\Omega$$

$$I_o = \alpha_o I_s = \alpha_o \frac{v_o}{R} \quad | \quad \frac{I_o}{v_{ref}} = \frac{\alpha_o}{R} \frac{v_o}{v_{ref}} = \frac{100}{101} \left( \frac{1}{10^4} \right) (0.999) = 98.9 \mu\text{s}$$

## Prob. 18.16

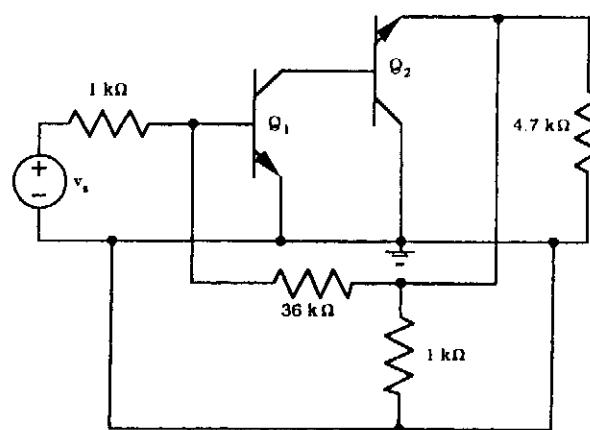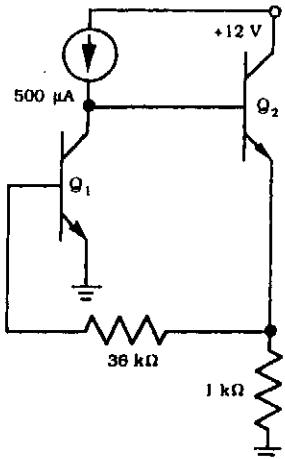


2.) Problem 18.16 of the text - *continued*

$$I_{C1} = 500\mu A - I_{B2} \quad I_{E2} = I_{B1} + \frac{36000I_{B1} + 0.7}{1000} = 37I_{B1} + 700\mu A \quad I_{B2} = \frac{I_{E2}}{101}$$

$$I_{C1} = 500\mu A - \frac{37I_{B1} + 700\mu A}{101} = 493\mu A - 0.366I_{B1} \rightarrow I_{C1} = 491.2\mu A$$
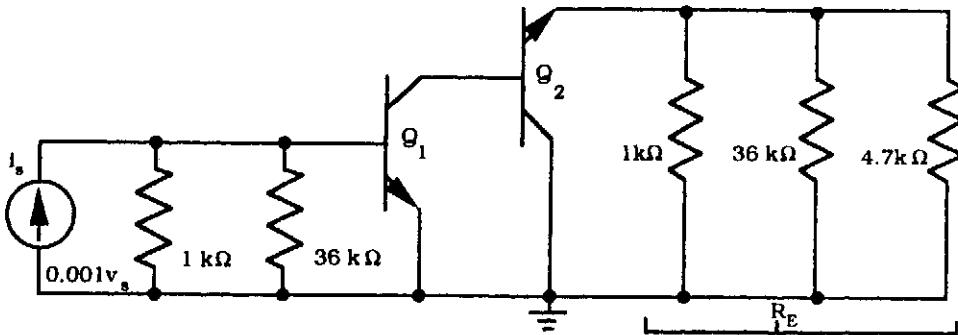
$$I_{E2} = 37 \frac{I_{C1}}{100} + 700\mu A = 881.7\mu A \quad I_{C2} = \frac{100}{101} I_{E2} = 873\mu A$$



$$y_{11}^F = \left. \frac{i_1}{v_1} \right|_{v_2=0} = \frac{1}{36k\Omega} \quad | \quad y_{22}^F = \left. \frac{i_2}{v_2} \right|_{v_1=0} = \frac{1}{36k\Omega || 1k\Omega} \quad | \quad y_{12}^F = \left. \frac{i_1}{v_2} \right|_{v_1=0} = -\frac{1}{36k\Omega}$$

$$r_{\pi 1} = \frac{100(0.025)}{491\mu A} = 5.09k\Omega \quad | \quad r_{\pi 2} = \frac{100(0.025)}{873\mu A} = 2.86k\Omega \quad | \quad r_{o1} = \frac{50 + 1.6}{493 \times 10^{-6}} = 105k\Omega$$

$$R_E = (1k\Omega || 36k\Omega || 4.7k\Omega) = 807\Omega$$

$$A = \frac{v_o}{i_s} = (1k\Omega || 36k\Omega || r_{\pi 1}) g_m [r_{o1} || (r_{\pi 2} + (\beta_o + 1)R_E)] \frac{r_{\pi 2} + (\beta_o + 1)R_E}{r_{o1} + r_{\pi 2} + (\beta_o + 1)R_E}$$

$$(1k\Omega || 36k\Omega || r_{\pi 1}) = (1k\Omega || 36k\Omega || 5.09k\Omega) = 817\Omega \quad | \quad g_m = 40(491\mu A) = 19.6mS$$

$$[r_{o1} || (r_{\pi 2} + (\beta_o + 1)R_E)] = [105k\Omega || (2.86k\Omega + (101)806\Omega)] = 46.8k\Omega$$

$$\frac{r_{\pi 2} + (\beta_o + 1)R_E}{r_{o1} + r_{\pi 2} + (\beta_o + 1)R_E} = \frac{2.86k\Omega + (101)806\Omega}{105k\Omega + 2.86k\Omega + (101)806\Omega} = 0.430$$

$$A = -(817\Omega)(19.6mS)(46.8k\Omega)(0.430) = -322 \text{ k}\Omega$$

$$A_{TR} = \frac{A}{1 + A\beta} = \frac{-322k\Omega}{1 + (-322k\Omega)\left(-\frac{1}{36k\Omega}\right)} = -\frac{322k\Omega}{9.94} = -32.4 \text{ k}\Omega$$




$$R_{IN} = \frac{(1k\Omega || 36k\Omega || 5.09k\Omega)}{1 + A\beta} = \frac{817\Omega}{9.94} = 82.2 \Omega$$

$$R_{OUT} = \frac{\left(1k\Omega || 36k\Omega || 4.7k\Omega \parallel \frac{r_{\pi 2} + r_{o1}}{101}\right)}{1 + A\beta} = \frac{\left(806\Omega \parallel \frac{2.86k\Omega + 105k\Omega}{101}\right)}{9.94} = 46.2 \Omega$$

$$i_s = 10^{-3}v_s \rightarrow A_v = \frac{v_o}{v_s} = \frac{v_o}{1000i_s} = -32.4$$

Note that this amplifier can be analyzed as a shunt-shunt feedback amplifier. This is good for student practice - See Problem 18.25.

3.) For each of the MOSFET amplifiers shown below, show how to connect a single resistor from the output to the input that achieves a series-shunt, series-series, shunt-shunt and shunt-series negative feedback amplifier. For each of the four configurations, identify on the schematic the correct variables (voltage or current) for  $x_s$ ,  $x_f$ ,  $x_i$ , and  $x_o$ . The outputs should be at the drain or source of M3.

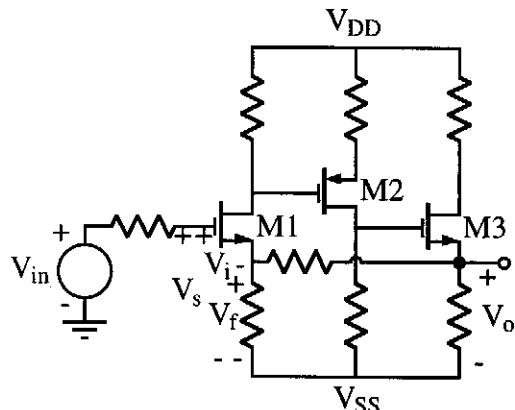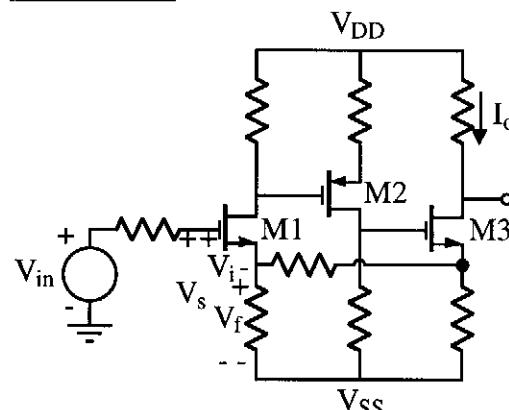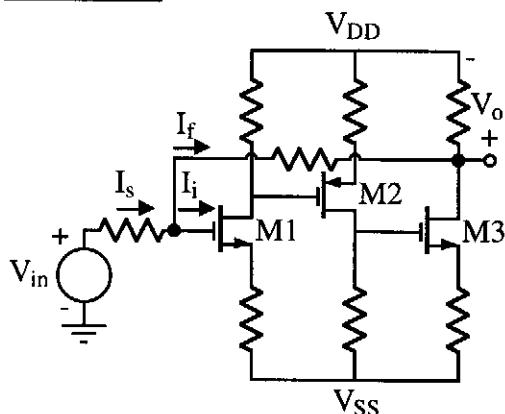Series-ShuntSeries-SeriesShunt-ShuntShunt-Series