
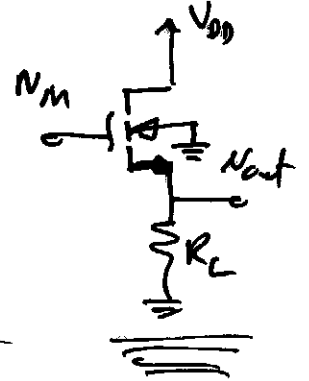
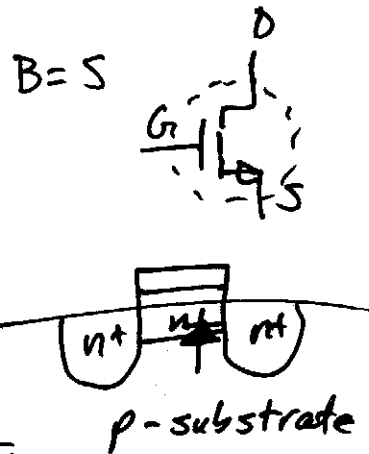


New office hours

MW - 10-10:55am, 2-2:55pm - Dr. Phil Allen, Room E292-B
 TTh - 1-2:55pm - Richard Tarbell (ECE3050 TA), Room E292

Question -
 p 4.52


$\gamma = 0$

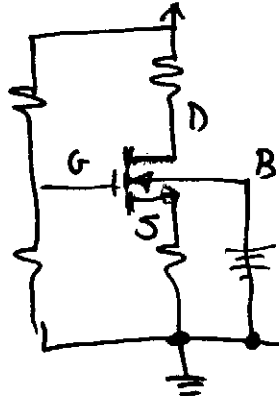

$V_{TN} = V_{T0} + \gamma \sqrt{2\phi_F - V_{BS}} - \gamma \sqrt{2\phi_F}$

Chapter 11 - Amplifiers and Frequency Response

1.) Linearity

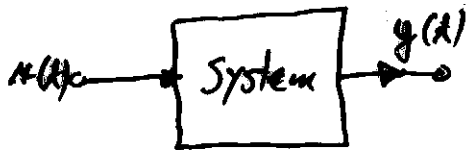

A system is linear iff


$x_1(t) \rightarrow y_1(t)$

$x_2(t) \rightarrow y_2(t)$

$x_1(t) + x_2(t) \rightarrow y_1(t) + y_2(t)$

A system is linear if the relationship between $y(t)$ and $x(t)$ is constant for all values of $x(t)$.

2.) Linear amplifier

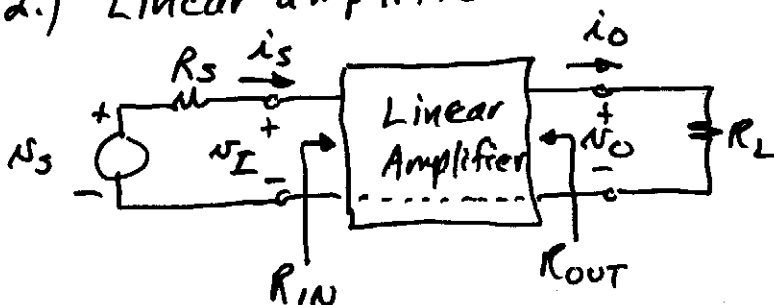

a.) Voltage gain:

$A_V = \frac{v_o}{v_i}$ or $A_V = \frac{v_o}{v_s}$

$v_i = \frac{R_{IN}}{R_s + R_{IN}} v_s$

$A_V = \frac{R_{IN}}{R_s + R_{IN}} A_V$

2.) Cont'd

b.) Current gain $A_I = \frac{i_o}{i_s} = \frac{N_o/R_L}{N_s/(R_{in}+R_s)} = \frac{R_{in}+R_s}{R_L} \frac{N_o}{N_s}$

$A_I = \frac{R_{in}+R_s}{R_L} A_V$

c.) Power gain

$A_p = \frac{N_o i_o}{N_s i_s} = A_V A_I$

$R_s = 0 \ \& \ \downarrow$
 If $R_{in} = R_L$,
 then
 $A_I = A_V$

3.) Decibels


$A_p \text{ dB} \equiv 10 \log_{10}(A_p)$


Assume that $A_V^2 \propto A_p \rightarrow A_V \text{ dB} = 10 \log_{10}(A_V^2)$

$A_V \text{ dB} = 20 \log_{10}(A_V)$

Ratio of same units

4.) Amplifier Power Supplies

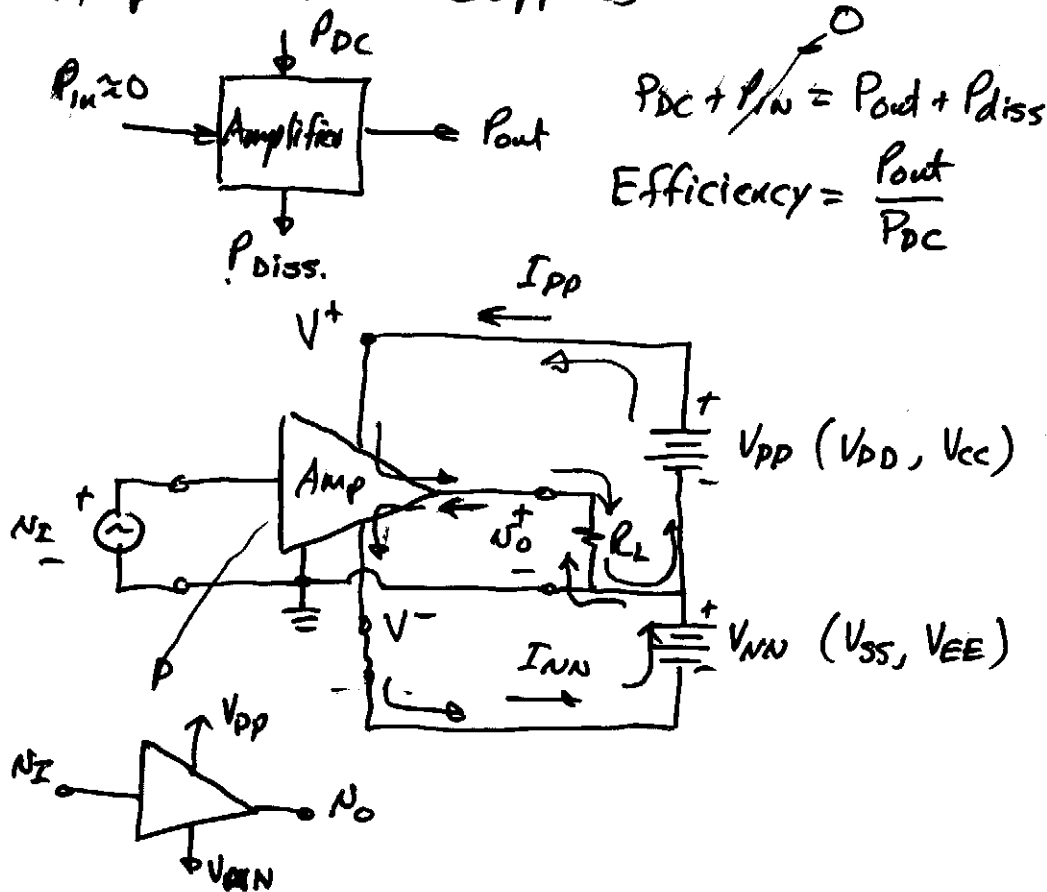

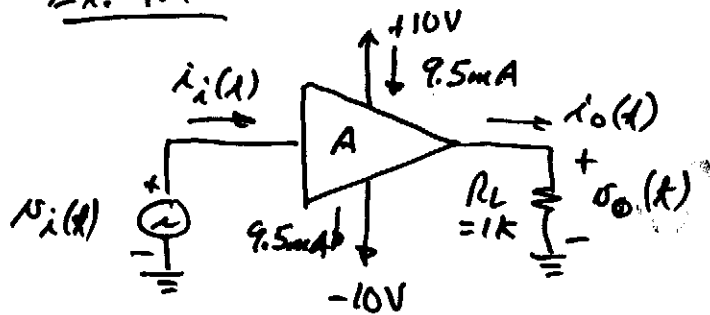Ex. 4.1

If $v_i(t) = 1 \sin \omega t$,
 then $v_o(t) = 9 \sin \omega t$
 and $i_i(t) = 0.0001 \sin \omega t$.
 Find the efficiency.

$$A_N = \frac{9V}{1V} = 9 V/V \rightarrow A_N (dB) = 20 \log_{10} 9 = 19.1 dB$$

$$i_o(\text{peak}) = \frac{v_o(\text{peak})}{R_L} = 9 mA \rightarrow i_o(t) = 9 mA \sin \omega t$$

$$A_i = \frac{9 mA}{0.1 mA} = 90 A/A \rightarrow A_i (dB) = 20 \log_{10} (90) = 39.1 dB$$

$$P_L = (9V/\sqrt{2}) \left(\frac{9mA}{\sqrt{2}} \right) = \frac{81 mW}{\sqrt{2}\sqrt{2}} = 40.5 mW$$

$$P_I = \left(\frac{1V}{\sqrt{2}} \right) \left(\frac{0.1 mA}{\sqrt{2}} \right) = \frac{0.1 mW}{2} = 0.05 mW$$

$$A_p = \frac{40.5}{0.05} = 810 W/W$$

$$A_p (dB) = 10 \log_{10} (810) = 29.1 dB$$

$$P_{DC} = 10V(9.5mA) + 10V(9.5mA) = 190 mW$$

$$P_{diss} = P_{DC} + P_I - P_L = 190 + 0.05 - 40.5 = 149.65 mW$$

$$M = \frac{P_L}{P_{DC}} = \frac{40.5 mW}{190 mW} \times 100\% = \underline{\underline{21.3\%}}$$