
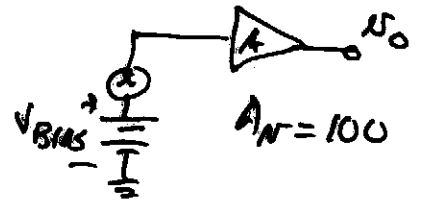


Quiz No.1 - Friday 8/30 Open book for this quiz.


Amplifiers

1.) Voltage transfer characteristic

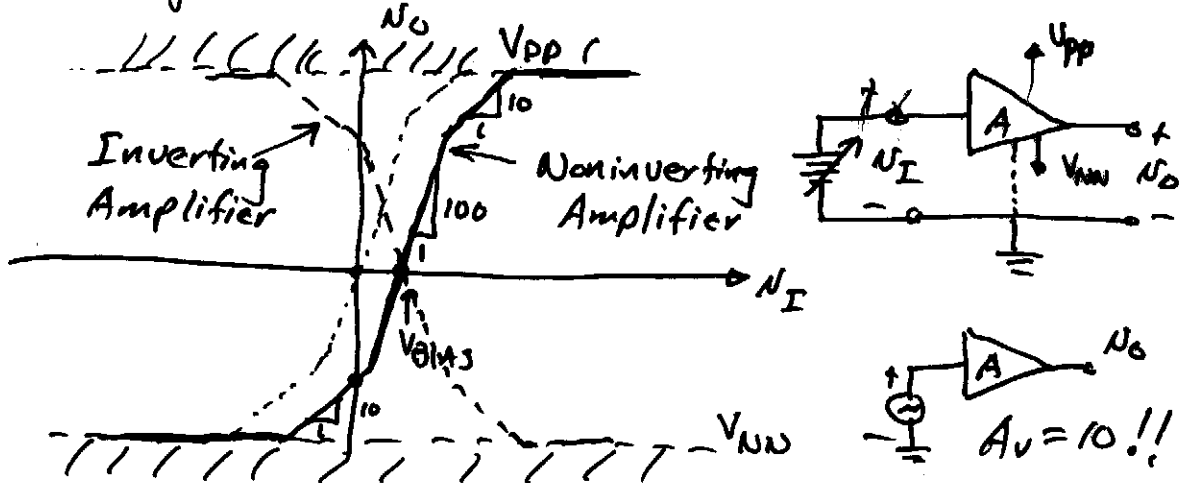

2.) Two-Port Models for Linear Amplifier

a.) g-parameters

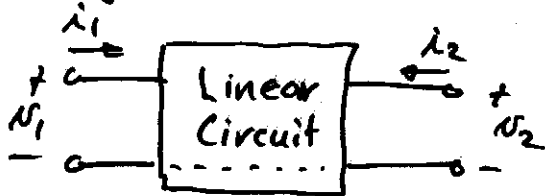

$$i_1 = g_{11} N_1 + g_{12} i_2$$


$$N_2 = g_{21} N_1 + g_{22} i_2$$

$$g_{11} = \left. \frac{i_1}{N_1} \right|_{i_2=0}$$

$$g_{12} = \left. \frac{i_1}{i_2} \right|_{N_1=0}$$

$$g_{21} = \left. \frac{N_2}{N_1} \right|_{i_2=0}$$

$$g_{22} = \left. \frac{N_2}{i_2} \right|_{N_1=0}$$

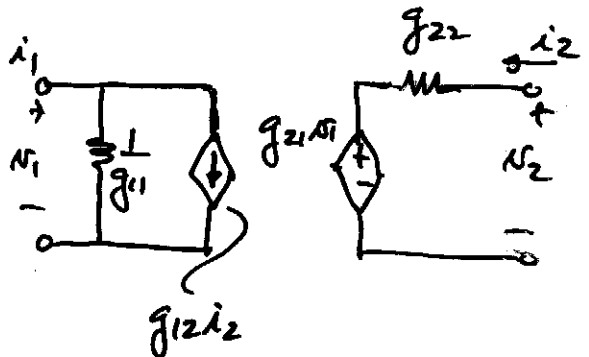

b.) h-parameters


c.) y-parameters

d.) z-parameters

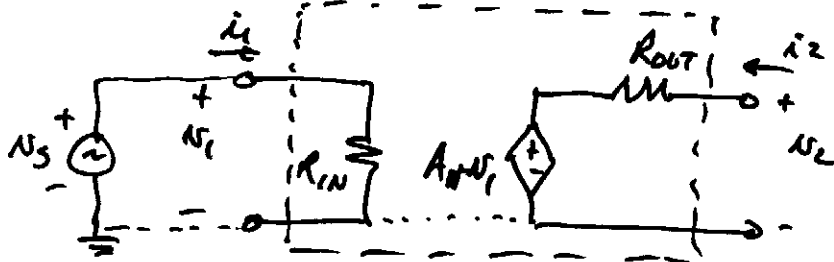3.) Two-port representation of amplifiers


Basically, an amplifier is a two-port network when the  $i_2$  parameter  $\approx 0$ .

a.) An unloaded voltage amplifier - ( $R_S=0, R_L=\infty$ )



$$i_1 = g_{11} N_1 + g_{12} i_2$$

$$N_2 = g_{21} N_1 + g_{22} i_2$$

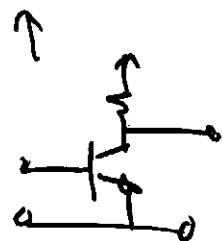


$$g_{11} = \left. \frac{i_1}{N_1} \right|_{i_2=0} = \frac{1}{R_{IN}}$$

$$g_{21} = \left. \frac{N_2}{N_1} \right|_{i_2=0} = A_V$$

$$g_{22} = \left. \frac{N_2}{i_2} \right|_{N_1=0} = R_{OUT}$$

b.) Loaded Voltage Amplifier

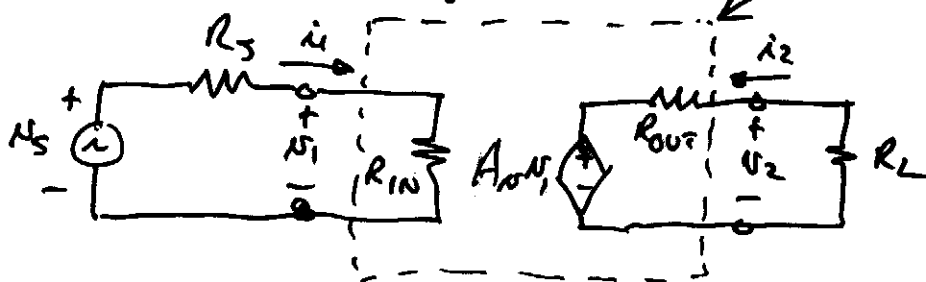


$$A_V = \frac{N_2}{N_S} = \left( \frac{N_2}{N_1} \right) \left( \frac{N_1}{N_S} \right) = \left( \frac{A_V R_L}{R_L + R_{OUT}} \right) \left( \frac{R_{IN}}{R_{IN} + R_S} \right)$$

$$A_V = \frac{A_V R_{IN} R_L}{(R_{IN} + R_S)(R_L + R_{OUT})}$$

$A_V \rightarrow A_V$  if  $R_{IN} \gg R_S$  and  $R_L \gg R_{OUT}$

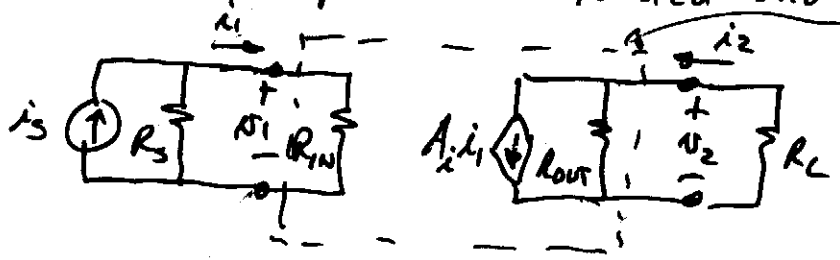4.) Current amplifiers - loaded and unloaded



n-parameter


$$R_L \ll R_{OUT}$$

$$R_{IN} \ll R_S$$

5) Amplifier transfer functions



Time domain -

Convolution

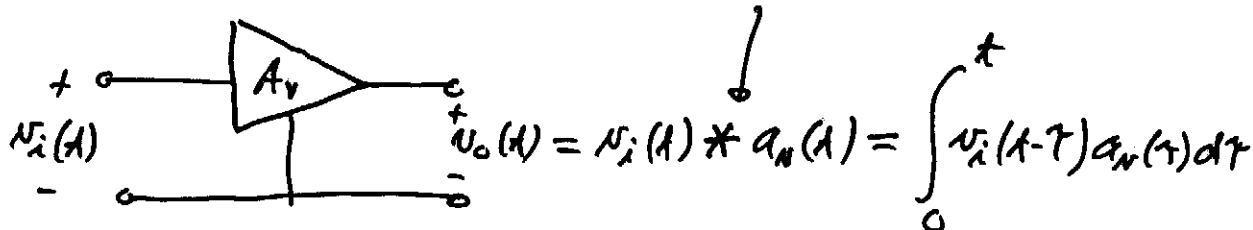

$a_N(t)$  = impulse response of the voltage amplifier

Frequency domain -

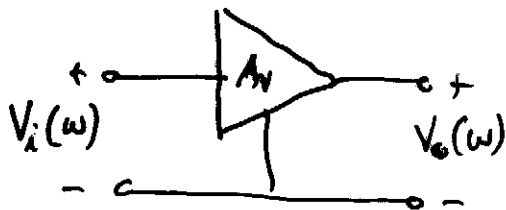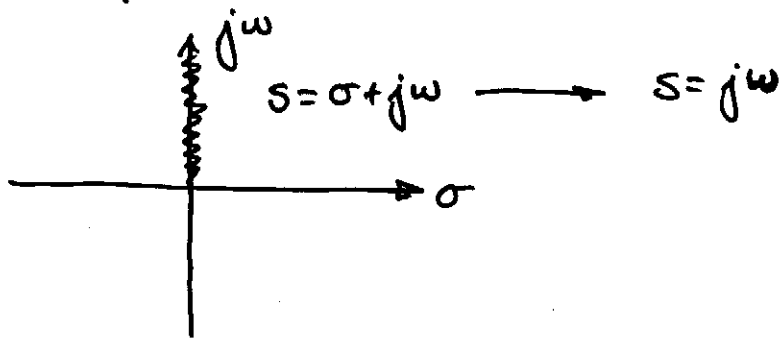

$$A_v(\omega) = A_v(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{V_o(\omega)}{V_i(\omega)}$$

$$V_o(j\omega) = A_v(j\omega) V_i(j\omega)$$

6) General frequency domain transfer function

$$A_v(s) = \frac{N(s)}{D(s)} = \frac{a_m s^m + \dots + a_1 s + a_0}{b_n s^n + \dots + b_1 s + b_0} \quad m \leq n$$

$$= K \frac{(s+z_1)(s+z_2)\dots(s+z_m)}{(s+p_1)(s+p_2)\dots(s+p_n)}$$

Zeros = Values of  $s$  where  $A_v(s) = 0 \rightarrow -z_1, -z_2, \dots -z_m$

Poles = " " " "  $A_v(s) = \infty \rightarrow -p_1, -p_2, \dots -p_n$

## Example 1


$$\text{Suppose } A_V(s) = \frac{100(s^2 + s)}{s^2 + 110s + 1000} = \frac{100s(s+1)}{(s+10)(s+100)}$$

$$z_1 = 0, z_2 = -1 \text{ rads/sec}$$

$$p_1 = -10, p_2 = -100$$

An Example not done in class.

Prob. 11.17 of text.

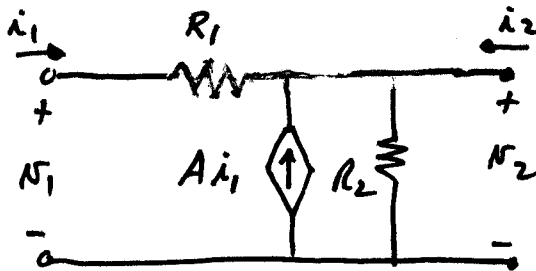


Find the  $h$ -parameters

$$N_1 = h_{11}i_1 + h_{12}N_2$$

$$i_2 = h_{21}i_1 + h_{22}N_2$$

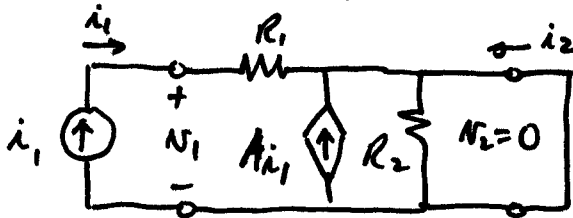$h_{11}$  and  $h_{21}$  (output short-circuited):




$$N_1 = R_1 i_1 + 0 \rightarrow h_{11} = \frac{N_1}{i_1} = R_1$$

$$\text{or } \underline{\underline{h_{11} = 10 \text{ k}\Omega}}$$

$$i_2 = -(i_1 + A i_1) = -i_1(1+A) \rightarrow h_{21} = -(1+A) = \underline{\underline{-101 \text{ A/A}}}$$

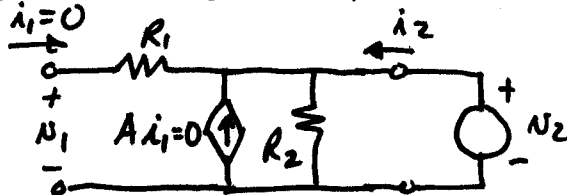$h_{12}$  and  $h_{22}$  (input open-circuited):



$$N_1 = N_2 \rightarrow \underline{\underline{h_{12} = 1 \text{ V/V}}}$$

$$\frac{i_2}{N_2} = \frac{1}{R_2} \rightarrow \underline{\underline{h_{22} = \frac{1}{240 \text{ k}\Omega}}}$$