

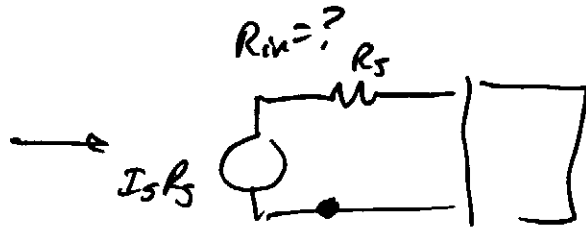
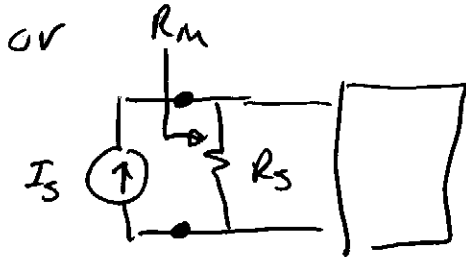
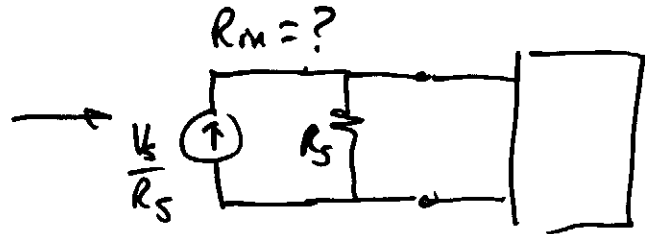


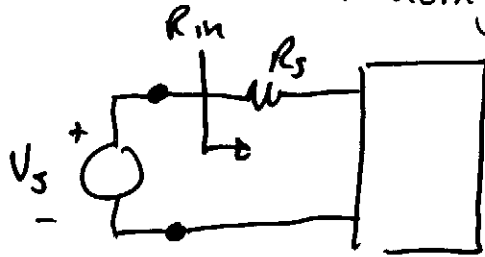Watch out when using Thevenin-Norton transformation-



1.) BJT small signal model

a.) Large Signal Viewpoint

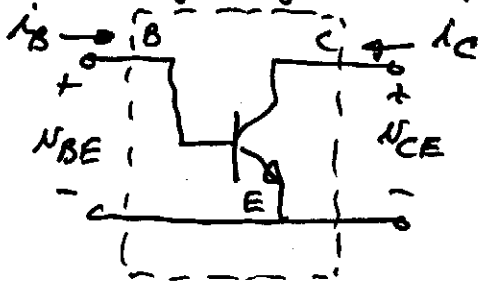


Mathematical Model

Forward active region:

$$i_c = I_s \left[\exp\left(\frac{V_{BE}}{V_T}\right) \left(1 + \frac{V_{CE}}{V_A}\right) \right]$$

$$i_b = \frac{i_c}{\beta_F} = \frac{I_s}{\beta_F} \exp\left(\frac{V_{BE}}{V_T}\right)$$

b.) Small-signal model (linear)

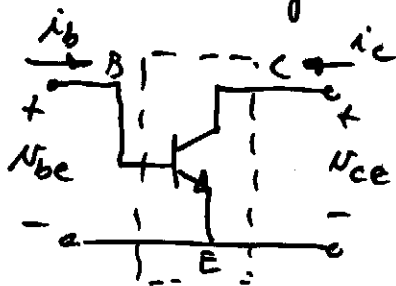

Mathematical Model

$$i_c = k_1 v_{be} + k_2 v_{ce}$$

$$i_b = k_3 v_{be}$$

$$k_1 = \left. \frac{i_c}{v_{be}} \right|_{v_{ce}=0} = \left. \frac{\Delta i_c}{\Delta V_{BE}} \right|_Q = \left. \frac{\partial i_c}{\partial V_{BE}} \right|_Q = \frac{I_s}{V_T} \exp\left(\frac{V_{BE}}{V_T}\right) \left(1 + \frac{V_{CE}}{V_A}\right)$$

$$k_1 = \boxed{\frac{I_c}{V_T} = g_m}$$

$$k_2 = \left. \frac{i_c}{v_{ce}} \right|_{v_{be}=0} = \left. \frac{\partial i_c}{\partial V_{CE}} \right|_Q = \frac{\left(\frac{I_s}{V_T} \exp\left(\frac{V_{BE}}{V_T}\right)\right) \left(\frac{1}{V_A}\right)}{k_F} = \frac{I_c}{V_A + V_{CE}} \approx \frac{I_c}{V_A}$$

$$k_F = \boxed{g_o = \frac{1}{r_o} = \frac{I_c}{V_A}}$$

NOTE: This V_T should not be here.

Cont'd

$$h_{33} = \frac{i_b}{N_{be}} = \left. \frac{\partial i_B}{\partial N_{BE}} \right|_Q = \frac{I_C}{\beta_F V_T} = \frac{g_m}{\beta_F} = \frac{1}{r_{\pi}}$$


Note that $\beta_F = g_m r_{\pi}$

$$r_{\pi} = \frac{1}{g_m} = \frac{\beta_F}{g_m} = \frac{\beta_F V_T}{I_C}$$

o
oc

$$i_c = g_m N_{be} + g_o N_{ce}$$


$$i_b = \frac{1}{r_{\pi}} N_{be}$$

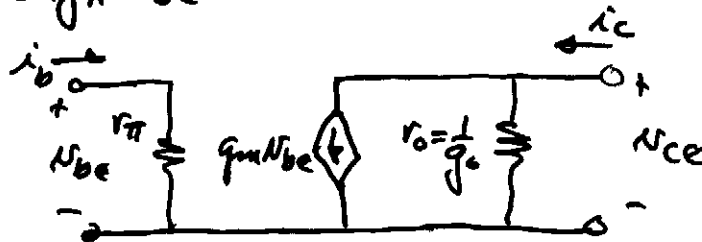

NPN
or
PNP

$$g_m = \frac{I_C}{V_T}, \quad r_{\pi} = \frac{\beta_F}{g_m}, \quad \text{and } r_o \hat{=} \frac{V_A}{I_C}$$



Example

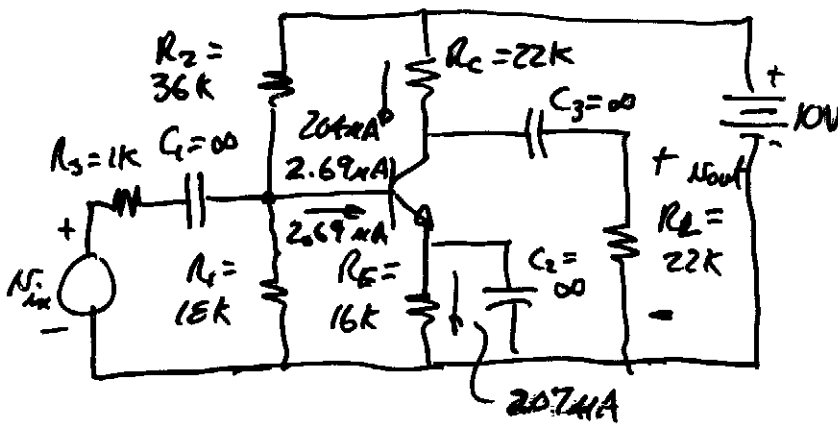

$$\beta_F = \beta_o = 100 \quad \& \quad V_T = 25mV$$

Find $\frac{N_{out}}{N_{in}}, R_{in}, \& R_{out}$

$$V_A = \infty$$

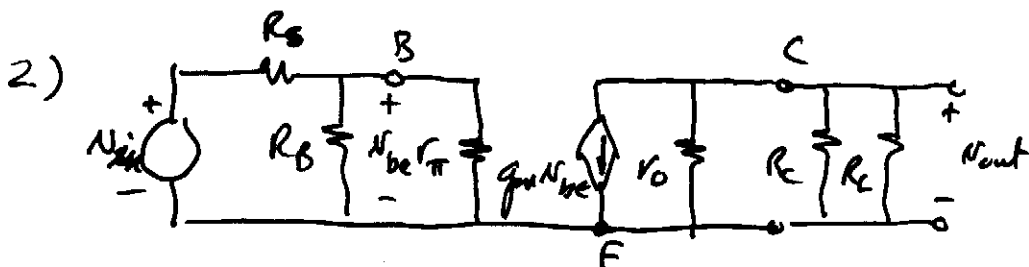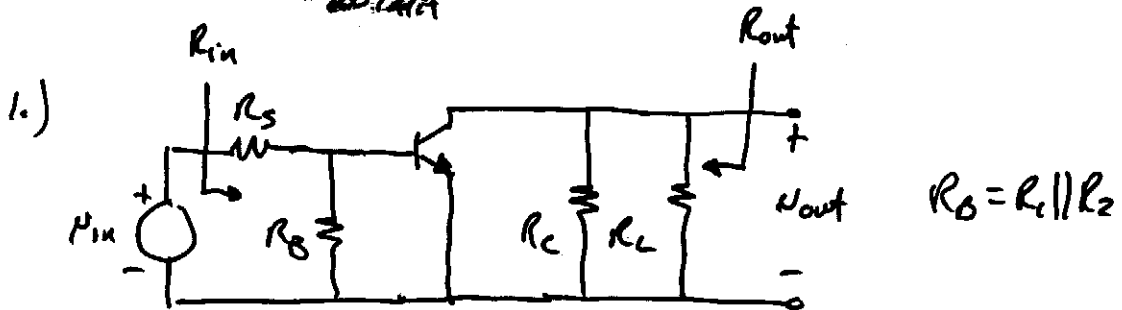

$$g_m = \frac{I_C}{V_T} = \frac{204 \mu A}{25 mV} = 8.16 mS \quad r_{\pi} = \frac{\beta_0}{g_m} = 9.19 k\Omega$$

$$r_o \approx \frac{V_A}{I_C} = \infty$$

3) Analysis

$$R_{in} = R_S + R_B \parallel r_{\pi} = \underline{6.205 k\Omega}$$

$$R_{out} = R_C \parallel R_L = \underline{11 k\Omega}$$

$$\frac{N_{out}}{N_{in}} = \frac{N_{out}}{N_{be}} \times \frac{N_{be}}{N_{in}} = (-g_m R_{out}) \left(\frac{R_M}{R_S + R_{in}} \right) = \underline{-75.3 V/V}$$

Wrong

More detail (not included in class lecture)

$$\frac{N_{out}}{N_{be}} = -g_m (R_L \parallel R_C) = -g_m R_{out}$$

$$\frac{N_{be}}{N_{in}} = \frac{R_B \parallel r_{\pi}}{R_S + R_B \parallel r_{\pi}} = \frac{R_B \parallel r_{\pi}}{R_M}$$

$$\therefore \frac{N_{out}}{N_{in}} = (-g_m R_{out}) \left(\frac{R_B \parallel r_{\pi}}{R_M} \right) = (-8.16 \cdot 11) \left(\frac{5.205}{6.205} \right)$$

$$\frac{N_{out}}{N_{in}} = -75.3 V/V$$