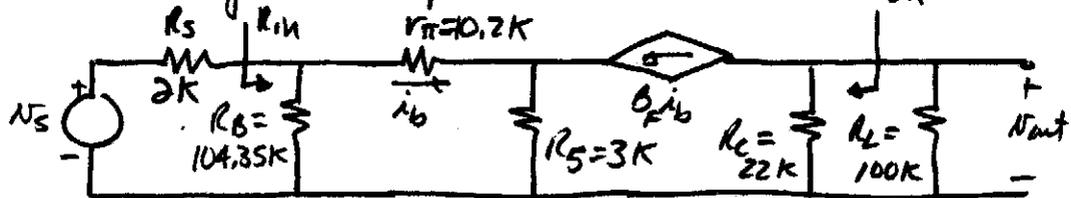


LECTURE 16

1.) Inverting CE Amplifier - Continued



$$R_{in} = R_B \parallel [r_{\pi} + (1 + \beta_F) R_E] = 104.35k \parallel 313.2k = \underline{\underline{78.3k\Omega}}$$


$$R_{out} \approx R_C = \underline{\underline{22k\Omega}}$$

$$\frac{N_{out}}{N_s} = \left(\frac{N_{out}}{i_b} \right) \left(\frac{i_b}{N_s} \right) \quad \frac{N_{out}}{i_b} = -g_m (R_C \parallel R_L)$$

$$i_b = \frac{N_s}{R_s + R_{in}} \times \frac{R_B}{R_B + r_{\pi} + (1 + \beta_F) R_E}$$

$$\begin{aligned} \therefore \frac{N_{out}}{N_s} &= \frac{-\beta_F (R_C \parallel R_L) R_B}{(R_s + R_{in}) [R_B + r_{\pi} + (1 + \beta_F) R_E]} \\ &= \frac{-100 (18.03k) (104.35k)}{(80.3k) [104.35k + 313.2k]} = \underline{\underline{-5.61 V/V}} \end{aligned}$$

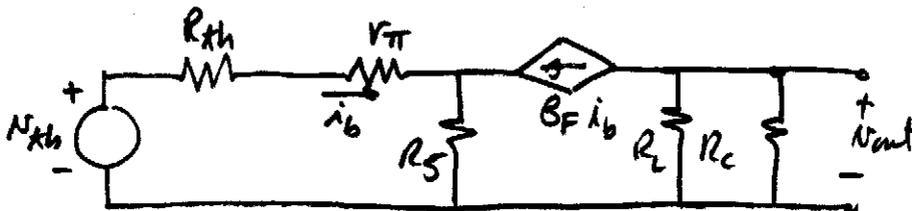Text: calculates $\frac{N_{out}}{N_{Th}}$ What is the difference?




$$R_{Th} = R_s \parallel R_B = 1.96k\Omega \approx R_s$$

$$N_{Th} = \frac{R_B}{R_s + R_B} N_s = \frac{104.35}{106.35} N_s \approx N_s$$

$$\frac{N_{out}}{N_{Th}} = \frac{-\beta (R_C \parallel R_L)}{R_{Th} + r_{\pi} + (1 + \beta_F) R_E} = \frac{-1803k}{(1.96 + 10.2 + 303)k} = -5.72 V/V$$

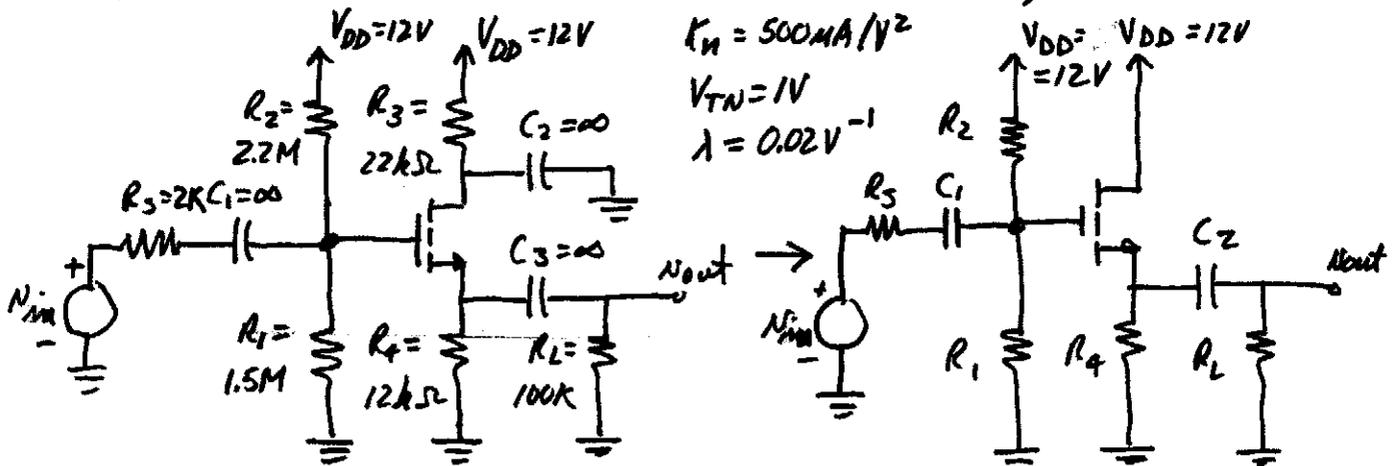
2.) Common Drain Amplifier (Source Follower)




R_3 accomplishes nothing so remove it.

Q point: $I_{DS} = 241\mu A$, $V_{DS} = 3.81V$

Small signal model -

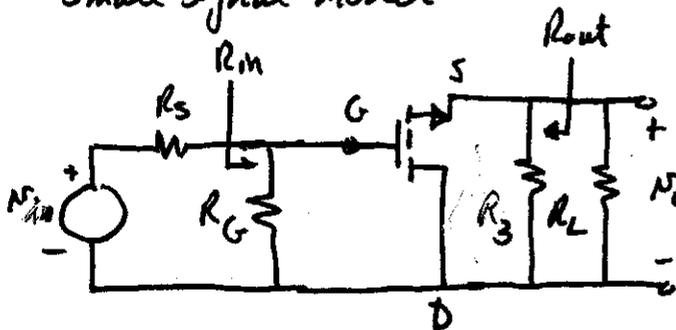

$R_G = R_1 || R_2 = 892k\Omega$

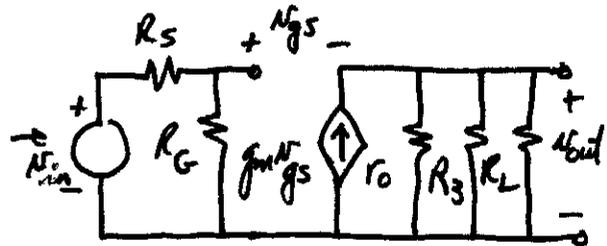


$g_m = \sqrt{2K_n I_{DS} (1 + \lambda V_{DS})} = 509\mu S$

$r_o = \frac{1/\lambda + V_{DS}}{I_{DS}} = 223k\Omega$

$\therefore R_{in} = R_G = \underline{892k\Omega}$

$R_{out} = ?$ Be careful, consider

the following

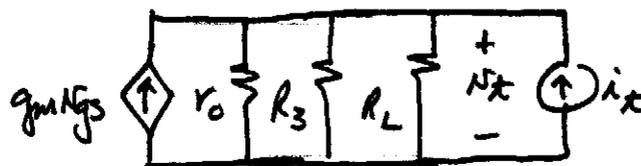


$R_{out} = \left. \frac{V_x}{I_x} \right|_{N_{in}=0}$

$\sum i = 0 \rightarrow -g_m V_{gs} + g_o V_x + G_3 V_x + G_L V_x = I_x$

But $V_{gs} = V_g - V_s = 0 - V_s$ (because the input, $N_{in} = 0$)

$\therefore \frac{V_x}{I_x} = \frac{1}{g_m + g_o + G_3 + G_L} \approx \frac{1}{g_m} = \underline{1.96k\Omega}$ (1.76kΩ otherwise)

2.) CD Amplifier - Cont'd

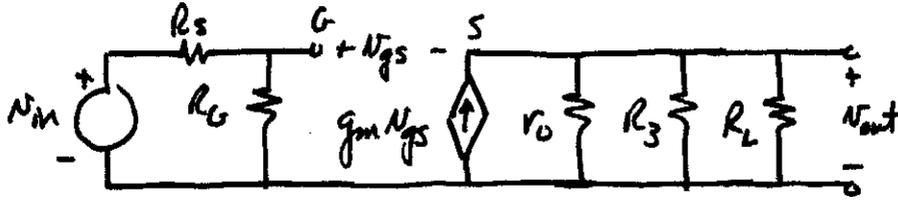Find $\frac{N_{out}}{N_{in}}$ -

$$\frac{N_{out}}{N_{in}} = \left(\frac{N_{out}}{N_{gs}}\right) \left(\frac{N_{gs}}{N_{in}}\right) = [g_m(r_o \parallel R_S \parallel R_L)] [?]$$

$$N_{gs} = N_g - N_s = \left(\frac{R_G}{R_S + R_G}\right) N_{in} - g_m N_{gs} (r_o \parallel R_S \parallel R_L)$$

$$N_{gs} [1 + g_m (r_o \parallel R_S \parallel R_L)] = \left(\frac{R_G}{R_S + R_G}\right) N_{in}$$

$$\therefore \frac{N_{gs}}{N_{in}} = \frac{\frac{R_G}{R_S + R_G}}{1 + g_m (r_o \parallel R_S \parallel R_L)}$$

$$\frac{N_{out}}{N_{in}} = \left(\frac{R_G}{R_S + R_G}\right) \frac{g_m (r_o \parallel R_S \parallel R_L)}{1 + g_m (r_o \parallel R_S \parallel R_L)} = \left(\frac{892}{894}\right) \left(\frac{30.5}{1 + 30.5}\right) = \underline{\underline{0.966 V/V}}$$