
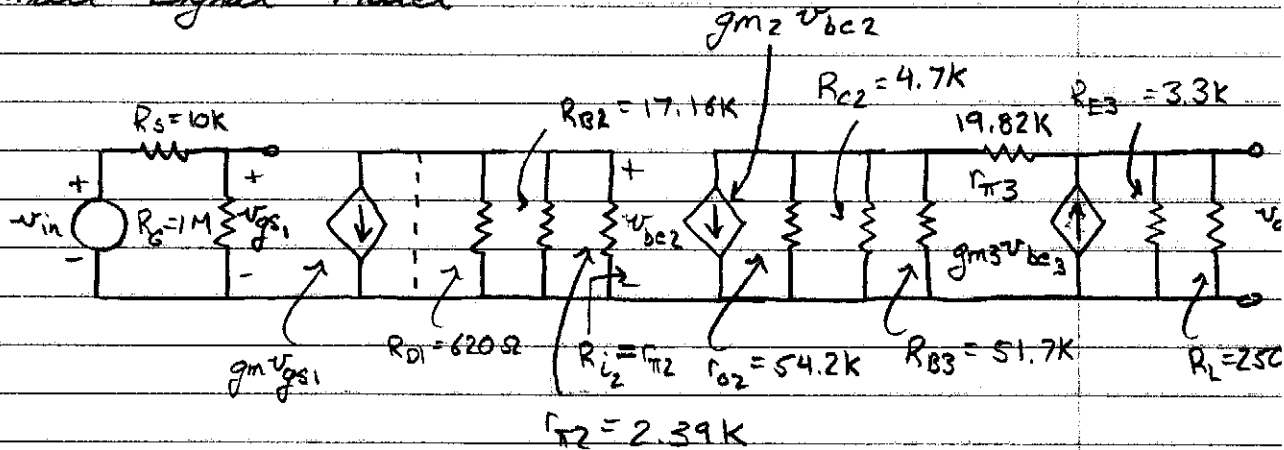


Voltage Amplifier - continued ...

Small Signal Model -

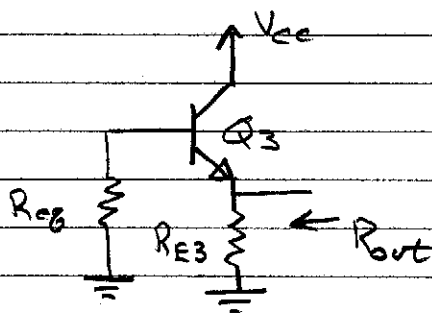

- $\beta_2 = 150$
- $\beta_3 = 80$
- $g_{m1} = 10 \text{ mS}$
- $g_{m2} = 62.8 \text{ mS}$
- $g_{m3} = 79.6 \text{ mS}$



$$R_{out} = 3.3 \text{ k} \parallel \left[\frac{r_{\pi 3} + r_{o2} \parallel R_{C2} \parallel R_{B3}}{1 + \beta_3} \right]$$

$$= 3.3 \text{ k} \parallel \left[\frac{1 \text{ k} + (54.2 \text{ k} \parallel 51.75 \text{ k} \parallel 4.7 \text{ k})}{81} \right]$$

$$= 3.3 \text{ k} \parallel 11.6 \text{ } \Omega$$

$$= 60.4 \text{ } \Omega$$

$$\frac{v_{out}}{v_{in}} = \left(\frac{v_{out}}{v_{be3}} \right) \left(\frac{v_{be3}}{v_{be2}} \right) \left(\frac{v_{be2}}{v_{gs1}} \right) \left(\frac{v_{gs1}}{v_{in}} \right)$$

$$\frac{v_{out}}{v_{be3}} = + \left(g_{m3} + \frac{1}{r_{\pi3}} \right) (R_{E3} \parallel R_L) = \frac{1 + \beta_3}{r_{\pi3}} (R_{E3} \parallel R_L)$$

$$= 81 \left(\frac{2.32}{1000} \right)$$

$$= 18.82$$

$$\frac{v_{be3}}{v_{be2}} = -g_{m2} \left[\frac{r_{o2} \parallel R_{c2} \parallel R_{B2}}{R_{i3} + r_{o2} \parallel R_{c2} \parallel R_{B2}} \right] r_{\pi3}$$

$$= \left(\frac{v_{be3}}{v_{b3}} \right) \left(\frac{v_{b3}}{v_{be2}} \right) = \left(\frac{r_{\pi3}}{R_{i3}} \right) (-g_{m2} R_{eq})$$

$$R_{eq} = r_{o2} \parallel R_{c2} \parallel R_{B2} \parallel R_{i3}$$

$$\frac{v_{be3}}{v_{be2}} = \left(\frac{v_{be3}}{v_{b3}} \right) \left(\frac{v_{b3}}{v_{be2}} \right) = \left(\frac{1}{19.82} \right) (-62.8 \times 3.322)$$

$$= -\frac{208.6}{19.2} \text{ V/V}$$

$$\frac{v_{be2}}{v_{gs1}} = -g_{m1} (R_{D1} \parallel R_{B2} \parallel r_{\pi2})$$

$$= (-10)(0.478)$$

$$= -4.786 \text{ V/V}$$

$$\frac{v_{gs1}}{v_{in}} = \frac{R_g}{R_s + R_g} = \frac{1}{1.01}$$

All together:

$$\frac{v_{out}}{v_{in}} = \left[(18.82) \left(\frac{1}{19.82} \right) \right] (-208.6) (-4.786) \left(\frac{1}{1.01} \right) = 938.6 \text{ V/V}$$

$$\frac{i_{out}}{i_{in}} = \frac{v_{out}/R_L}{\frac{v_{in}}{R_s + R_e}} = \frac{v_{out}}{v_{in}} \times \frac{R_s + R_e}{R_L} = 3.79 \times 10^6 \text{ A/A}$$

Max input for small-signal operation:



$$v_{be} < 5 \text{ mV}$$

$$v_{gs} < \frac{V_{gs} - V_{TN}}{5}$$


Therefore, max input for SS. operation is

$$100 \mu\text{V} \text{ or } 0.1 \text{ mV}$$

DC Coupled Amplifier

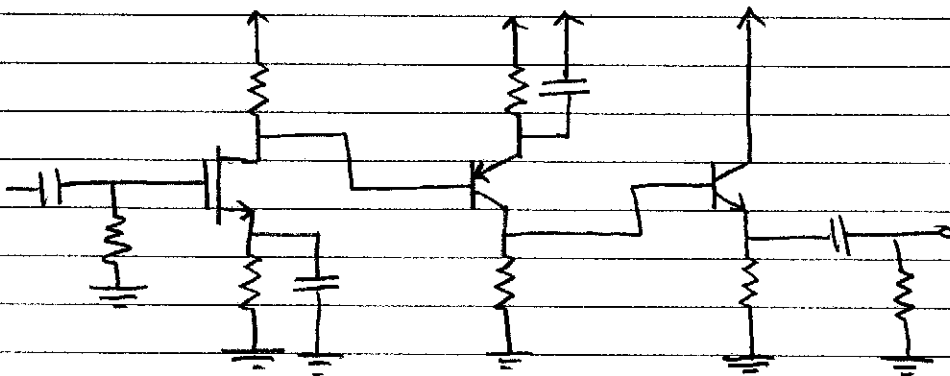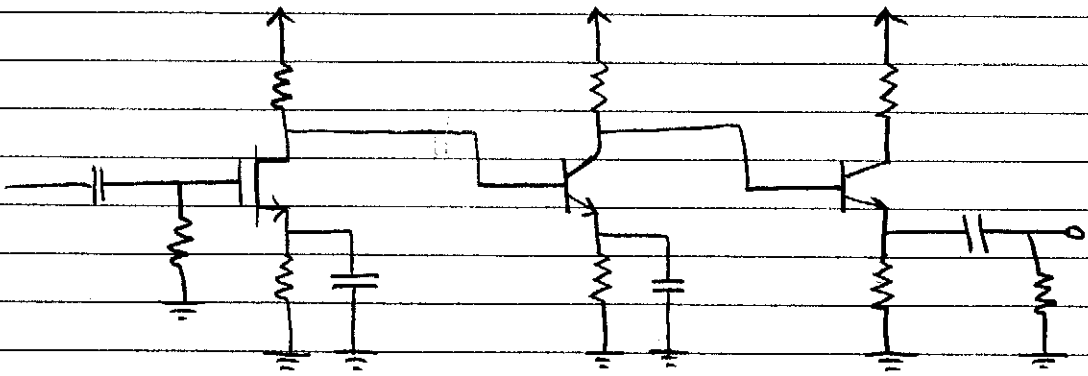

Differential Amplifier

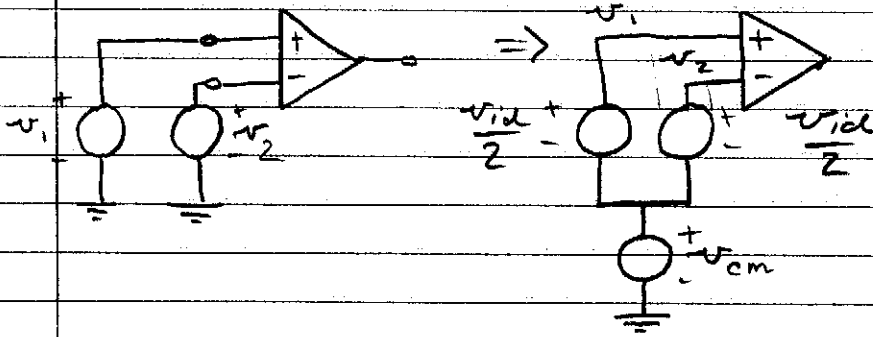


$$v_{id} = v_1 - v_2$$

$$v_{cm} = \frac{v_1 + v_2}{2}$$

$$v_1 = \frac{v_{id}}{2} + v_{cm}$$

$$v_2 = -\frac{v_{id}}{2} + v_{cm}$$

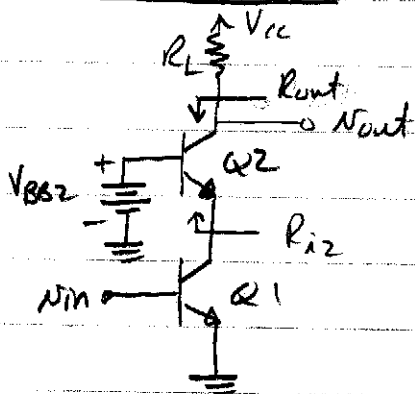
Cascode Amplifier (Not covered in class)

$$\frac{v_{out}}{v_{in}} \approx -g_{m1} R_L$$

$$R_{in} = r_{\pi 1}$$

$$R_{out} \approx \beta_{o2} r_{o2}$$
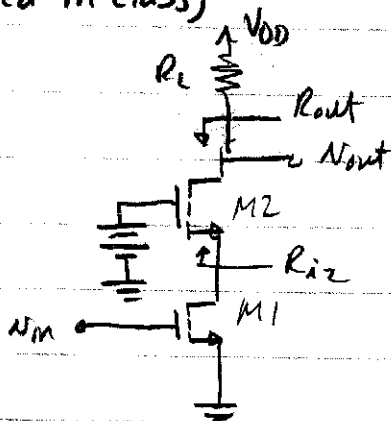
$$R_{i2} \approx \frac{1}{g_{m2}} \text{ (depends on } R_L \text{)}$$



$$\frac{v_{out}}{v_{in}} \approx -g_{m1} R_L$$

$$R_{in} = \infty$$

$$R_{out} \approx g_{m2} v_{o2} r_{o1}$$

$$R_{i2} \approx \frac{1}{g_{m2}} \text{ (depends on } R_L \text{)}$$