
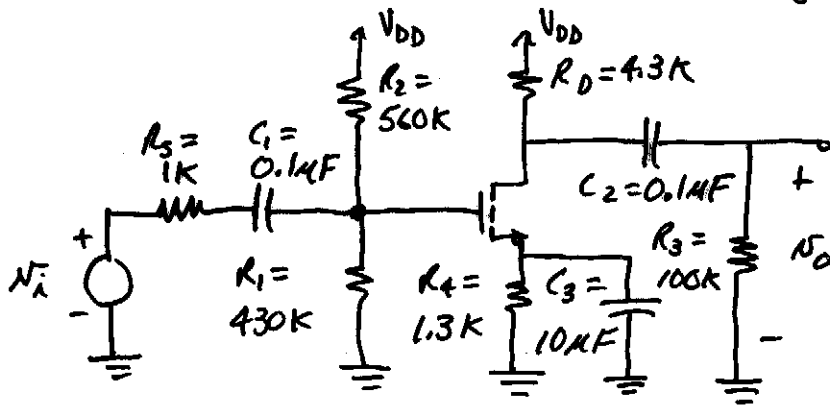


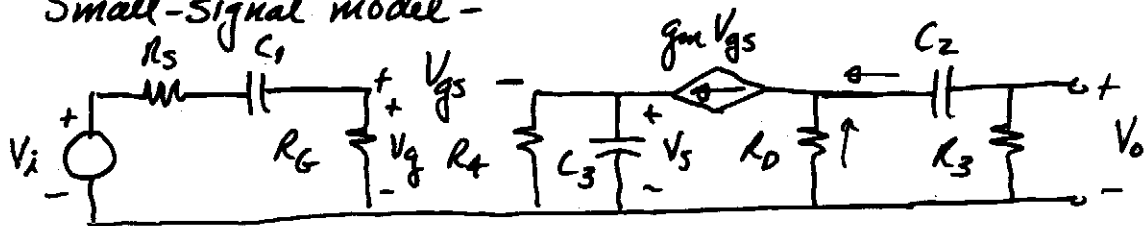Example of Frequency Analysis using a MOSFET



$g_m = 1.23 \text{ mS}$
 $r_o \approx \infty$

Small-signal model -



$$R_G = R_1 || R_2 = 243 \text{ K}$$

1.) Direct analysis of low frequency poles and zeros.

$$\frac{V_o(s)}{V_i(s)} = \left(\frac{V_o}{V_{gs}} \right) \left(\frac{V_{gs}}{V_g} \right) \left(\frac{V_g}{V_i} \right)$$

$$V_o = -g_m V_{gs} \left(\frac{R_D}{R_D + R_3 + \frac{1}{sC_2}} \right) R_3 \rightarrow \frac{V_o}{V_{gs}} = \left(\frac{-g_m R_D R_3}{R_D + R_3} \right) \left(\frac{s}{s + \frac{1}{C_2(R_3 + R_D)}} \right)$$

$$V_{gs} = V_g - V_s = V_g - g_m V_{gs} \left(\frac{R_4 + \frac{1}{sC_3}}{R_4 + \frac{1}{sC_3}} \right) = V_g - g_m R_4 V_{gs} \left(\frac{\frac{1}{R_4 C_3}}{s + \frac{1}{R_4 C_3}} \right)$$

$$V_{gs} \left[1 + g_m R_4 \left(\frac{\frac{1}{R_4 C_3}}{s + \frac{1}{R_4 C_3}} \right) \right] = V_g$$

$$\frac{V_{gs}}{V_g} = \frac{s + \frac{1}{R_4 C_3}}{s + \frac{1}{R_4 C_3} + g_m R_4 \frac{1}{R_4 C_3}} = \frac{s + \frac{1}{R_4 C_3}}{s + \frac{(1 + g_m R_4)}{R_4 C_3}}$$


$$\frac{V_g}{V_i} = \frac{R_G}{R_s + R_G + \frac{1}{sC_i}} = \left(\frac{R_G}{R_s + R_G} \right) \left(\frac{s}{s + \frac{1}{C_i(R_s + R_G)}} \right)$$

$$\omega_{p1} = -\frac{1}{C_1(R_{S1}R_0)} = \frac{-1}{(0.1\mu F)(244k)} = -41 \text{ rad/s}$$

$$\omega_{p2} = -\frac{1}{C_2(R_{S2}R_0)} = \frac{-1}{(0.1\mu F)(104.3k)} = -96 \text{ rad/s}$$

$$\omega_{p3} = -76.9 [1 + 1.23(13)] \quad z = \frac{-1}{R_4 C_3} = \frac{-1}{(4.3k)(10\mu F)}$$
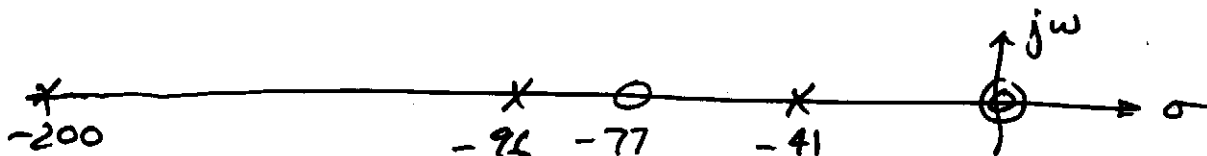
$$= -200 \text{ rad/s} \quad = -76.7 \text{ rad/s}$$





$$f_L = ?$$


1.) Dominant root $\rightarrow \omega_L = 200 \text{ rad/s} \rightarrow f_L = \frac{200}{6.28} \approx \underline{\underline{30 \text{ Hz}}}$

2.) $f_L = \frac{1}{2\pi} \sqrt{200^2 + 41^2 + 96^2 - 2(76.7^2)} = \underline{\underline{31.5 \text{ Hz}}}$

3.) Bode plot

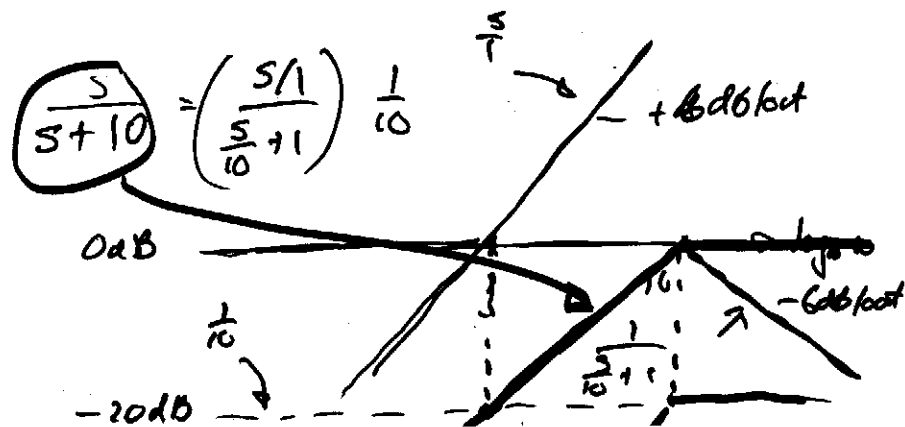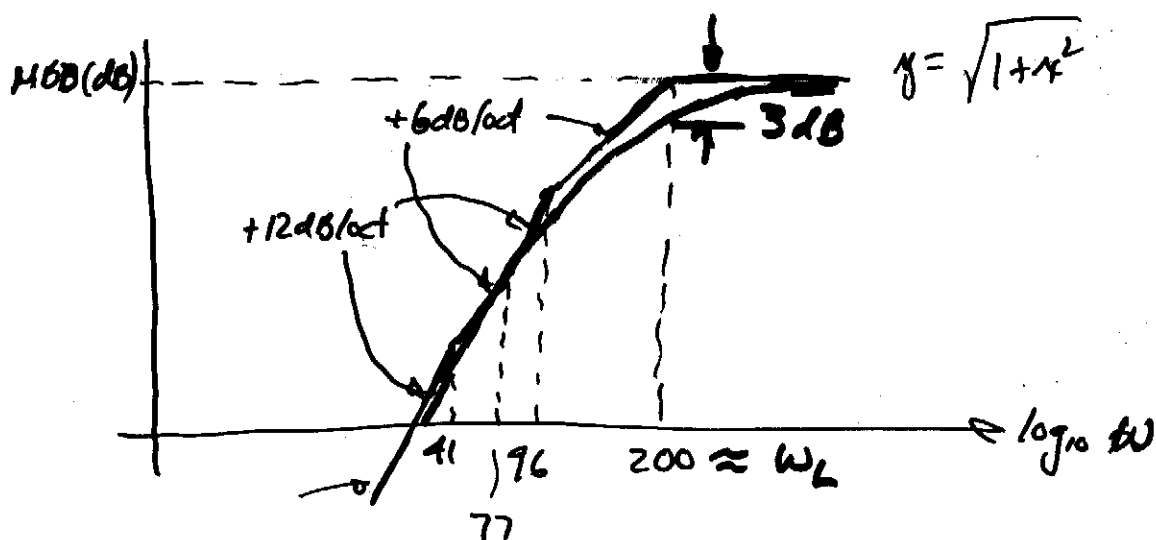

Find ω_L by s.c. time constants -

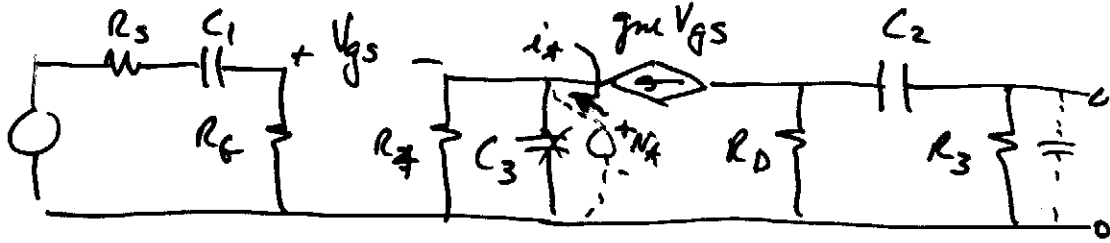


$$\omega_L \approx \sum \frac{1}{R_{i5} C_i} \quad R_{15} = R_s + R_G = 243K \quad R_{25} = R_D + R_3 = 104.3K$$

$$R_{35} = \frac{1}{g_m} \parallel R_4 = \frac{V_x}{i_x} = \frac{V_x}{2x} = 0.5K$$

$$\omega_L = \frac{1}{(243K)(0.1\mu F)} + \frac{1}{(104.3K)(0.1\mu F)} + \frac{1}{0.5K(10\mu F)} = (0.04 + 0.096 + 0.2)x$$

$$= 337 \text{ rad/s} \rightarrow f_L \approx \underline{\underline{53.6 \text{ Hz}}} \quad (\text{ignores zeros})$$


BJT

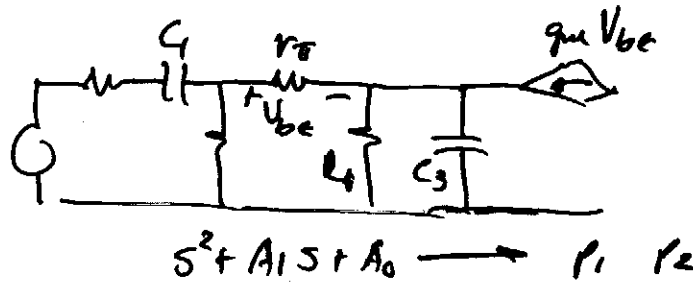

$$s^2 + A_1 s + A_0 \rightarrow p_1 \quad p_2$$

High Frequency Response

Small-signal model -

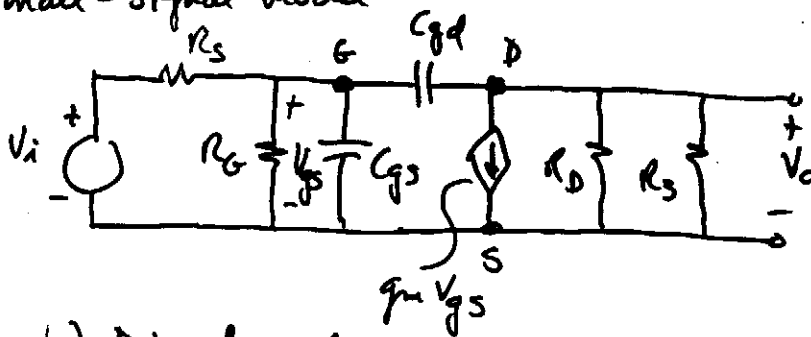

$$C_{gd} = 2 \text{ pF}$$

$$C_{gs} = 10 \text{ pF}$$


1.) Direct analysis

Two sheets later -

$$\frac{V_o}{V_i} = \frac{-10^{-3} [1.23 \times 10^{-3} - 2 \times 10^{-12}]}{20 \times 10^{24} [s^2 + 3.628 \times 10^8 s + 1.165 \times 10^{16}]}$$

$$p_1 = -0.385 \times 10^8 \text{ rads/sec} \quad p_2 = -3.272 \times 10^8 \text{ rad/s}$$
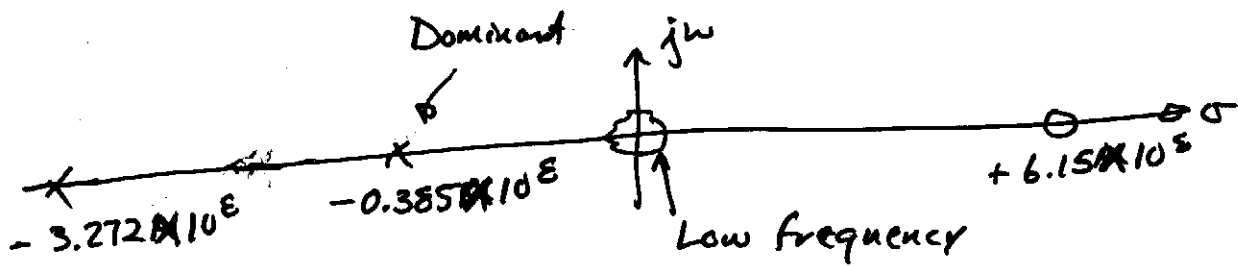
$$z_1 = +6.15 \times 10^8 \text{ rad/sec}$$




$$\omega_H \approx 385 \text{ M rad/s} \rightarrow \underline{\underline{5.67 \text{ MHz}}}$$

Miller multiplication -

Assume that $\frac{1}{\omega C_{gd}} \gg R_D \parallel R_3$

$$C_m = C_{gd}(1-k) \quad k = \frac{V_o}{V_{gs}} \hat{=} -g_m R_D \parallel R_3 = -5.07 \frac{V}{V}$$
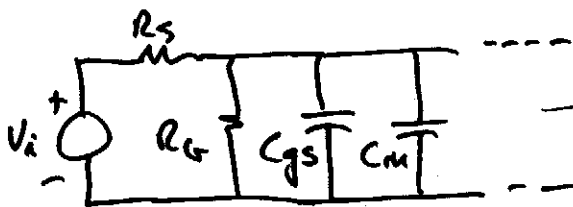
$$C_m = 2 \text{ pF}(6.07) = 12 \text{ pF}$$



$$\omega_H = \frac{1}{(R_s \parallel R_g)(C_{gs} + C_m)} = 45.3 \times 10^6 \frac{\text{rad}}{\text{s}}$$

$$f_H = \underline{\underline{7.22 \text{ MHz}}}$$

O.C. Time Constant

$$R_{Cgs} = R_s \parallel R_g = 0.996 \text{ k}$$

$$R_{Cgs} = (R_s \parallel R_g) [1 + g_m (R_D \parallel R_3)] + R_D \parallel R_3 = 10.168 \text{ k}$$

$$\omega_H = \frac{1}{(0.996 \text{ k})10 \text{ pF} + 10.168 \text{ k}(2 \text{ pF})} = 33.33 \times 10^6 \text{ rad/s}$$

$$f_H \approx \underline{\underline{5.3 \text{ MHz}}}$$

$$\omega_T = \frac{g_m}{C_{gs} + C_{gd}}$$