


$$\frac{dA_f}{dA} = ?$$

$$A_f = \frac{A}{1 + AB}$$

$$A_{ideal} = 200 = \frac{1}{B}$$

Voltage Amplifiers - Series-Shunt Feedback

Topology

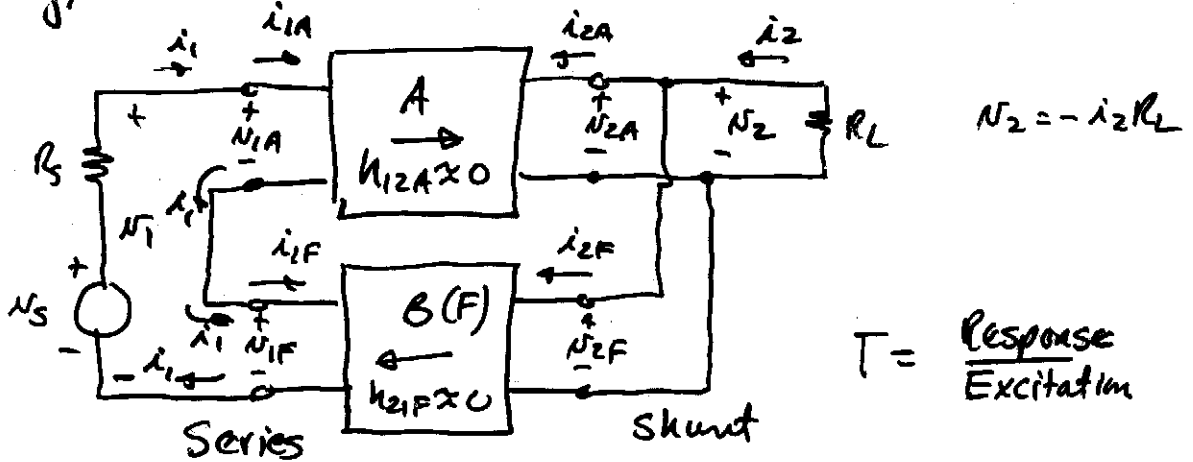

Choose h-parameters

$$\begin{bmatrix} N_{1A} = h_{11A} i_{1A} + h_{12A} N_{2A} \\ i_{2A} = h_{21A} i_1 + h_{22A} N_2 \end{bmatrix} + \begin{bmatrix} N_{1F} = h_{11F} i_1 + h_{12F} N_2 \\ i_{2F} = h_{21F} i_1 + h_{22F} N_2 \end{bmatrix} =$$

$$\begin{bmatrix} N_1 = h_{11T} i_1 + h_{12T} N_2 \\ i_2 = h_{21T} i_1 + h_{22T} N_2 \end{bmatrix} \quad \begin{matrix} h_{11T} = h_{11A} + h_{11F} \\ \vdots \end{matrix}$$

$$h_{11T} = \left. \frac{N_1}{i_1} \right|_{N_2=0} \quad h_{12T} = \left. \frac{N_1}{N_2} \right|_{i_1=0} \quad h_{21T} = \left. \frac{i_2}{i_1} \right|_{N_2=0}$$

$$h_{22} = \left. \frac{i_2}{N_2} \right|_{i_1=0}$$

Include  $R_L$  and  $R_S$

$$N_S = i_1 R_S + N_1 \quad N_S = i_1 (R_S + h_{11T}) + h_{12F} N_2$$



$$-\frac{N_2}{R_L} = i_2 = h_{21A} i_1 + h_{22T} N_2 \rightarrow 0 = h_{21A} i_1 + (G_L + h_{22T}) N_2$$

∴ Solving for  $\frac{N_2}{N_3}$ , gives

$$\frac{N_2}{N_3} = \frac{-h_{21A}}{(R_s + h_{11T})(G_L + h_{22T}) + h_{12F}h_{21A}} = \frac{-h_{21A}}{(R_s + h_{11T})(G_L + h_{22T})} \left( 1 + \frac{-h_{21A}}{(R_s + h_{11T})(G_L + h_{22T})} (h_{12F}) \right)$$

$$\therefore A = \frac{-h_{21A}}{(R_s + h_{11T})(G_L + h_{22T})} \quad \left\{ \quad B = \frac{h_{12F}}{1} \right.$$

To illustrate -

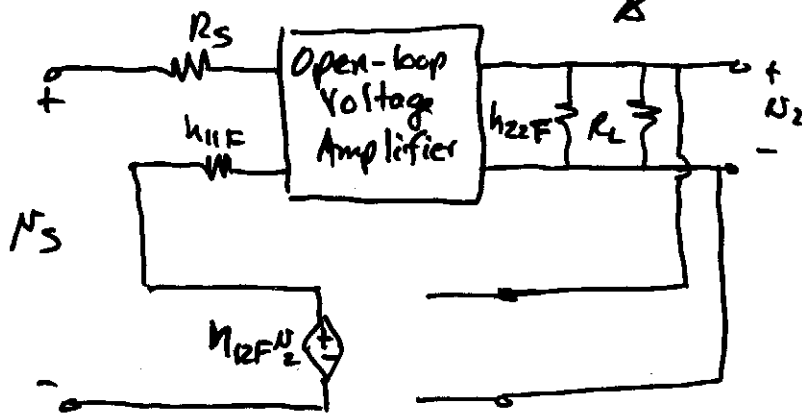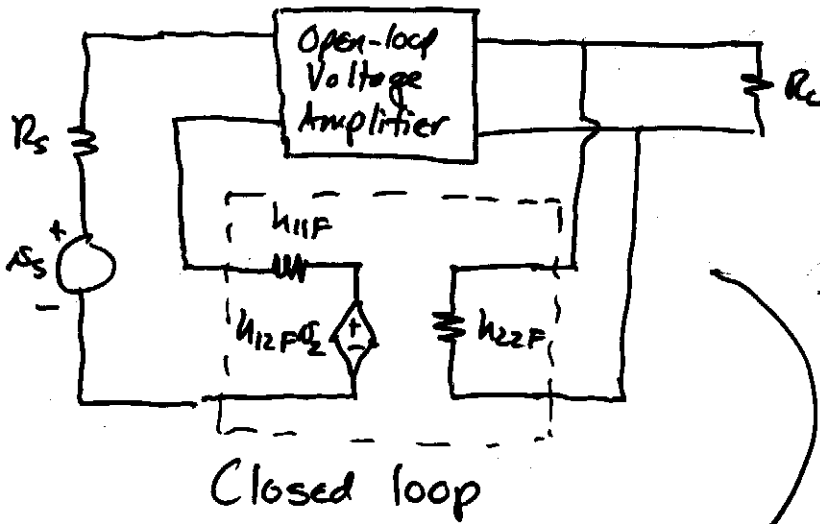


If  $N_2 = 0 \rightarrow$  Loop is open

$$h_{11F} = \left. \frac{N_1 F}{I_1} \right|_{N_2=0}$$

$$h_{22F} = \left. \frac{I_2 F}{N_2 F} \right|_{I_1=0}$$

$$h_{12F} = \left. \frac{N_1 F}{N_2} \right|_{I_1=0}$$

Example of Series-Shunt Feedback

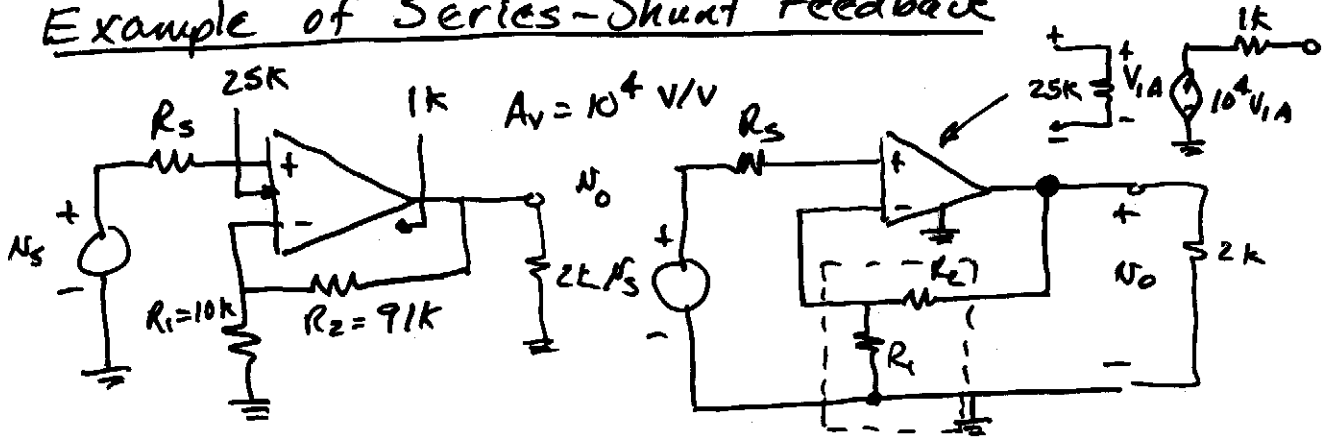

Find  $\frac{N_o}{N_s}$  using fb. concepts

How do we approach this problem?


1.) Find  $h_{11F}$ ,  $h_{22F}$  and  $h_{12F} = \beta$

2.) Go for A

3.)  $\frac{N_o}{N_s} = \frac{A}{1 + AB}$

$h_{11F} = \left. \frac{N_{1F}}{i_{1F}} \right|_{N_2=0} = R_1 || R_2 = 9.01K$        $h_{22F} = \left. \frac{i_{2F}}{N_{2F}} \right|_{i_1=0} = \frac{1}{R_1 + R_2} = \frac{1}{101K}$

$h_{12F} = \beta = \left. \frac{N_{1F}}{N_2} \right|_{i_1=0} = \frac{R_1}{R_1 + R_2} = \frac{10}{101} = 0.099$  (Ans.  $\approx \frac{10}{10} = 10$ )

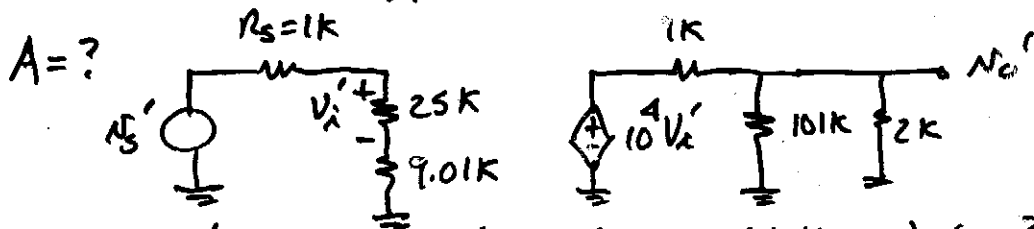

$A = \frac{N_o'}{N_s'} = \left( \frac{N_o'}{N_1'} \right) \left( \frac{N_1'}{N_s'} \right) = \left( 10^4 \frac{2K || 101K}{1K + 2K || 101K} \right) \left( \frac{25K}{1K + 25K + 9.01K} \right)$   
 $= 4730 \frac{V}{V}$

$A_f = \frac{A}{1 + AB} = \frac{4730}{1 + 4730 \left( \frac{1}{101} \right)} = \underline{\underline{10.05 V/V}}$