

Generalization of Feedback Circuit Analysis

Let  $\alpha = h, g, \gamma$  or  $z$  (parameters)

- 1.) Find  $\alpha_{11F}$
- 2.) Find  $\alpha_{22F}$
- 3.) Find  $\alpha_{12F} = B$
- 4.) Find  $A$  which has the input-output variables of  $(\alpha_{12})^{-1}$  incorporating the loading of  $\alpha_{11F}$  and  $\alpha_{22F}$ .
- 5.)  $A_F = \frac{A}{1+AB}$
- 6.)  $R_{inF} = \begin{cases} (R_s + \alpha_{11T})(1+AB) & \text{if the input is series} \\ \frac{1}{(G_s + \alpha_{11T})(1+AB)} & \text{if the input is shunt} \end{cases}$
- 7.)  $R_{outF} = \begin{cases} \frac{1}{(G_L + \alpha_{22T})(1+AB)} & \text{if the output is shunt} \\ (R_L + \alpha_{22T})(1+AB) & \text{if the output is series} \end{cases}$

Type of Amplifier	Series-shunt	Shunt-shunt	Shunt-series	Series-series
Voltage	Transresistance	Current	Transconductance	
Two-Port Parameters	$i_1 = h_{11}i_1 + h_{12}v_2$	$i_1 = \gamma_{11}v_1 + \gamma_{12}v_2$	$i_1 = g_{11}v_1 + g_{12}i_2$	$v_1 = z_{11}i_1 + z_{12}i_2$
	$i_2 = h_{21}i_1 + h_{22}v_2$	$i_2 = \gamma_{21}v_1 + \gamma_{22}v_2$	$N_2 = g_{21}v_1 + g_{22}i_2$	$N_2 = z_{21}i_1 + z_{22}i_2$
Units of A	$\frac{V_2}{V_1}$	$\frac{V_2}{I_1}$	$\frac{I_2}{I_1}$	$\frac{I_2}{V_1}$

## Shunt-Shunt Neg. Feedback Example


$\gamma$ -parameters are the appropriate parameters

$$y_{HF} = \frac{c_F}{x_F} \Big|_{\sum c_F = 0}$$

$$\gamma_{22F} = \frac{\lambda_{2F}}{N_{2F}} |_{N_{1F}=0}$$


$$y_{12F=0} = \frac{\lambda_{1F}}{N_{2F}} \Big|_{\lambda_{1F}=0}$$

A ( $\frac{Y}{A}$ )

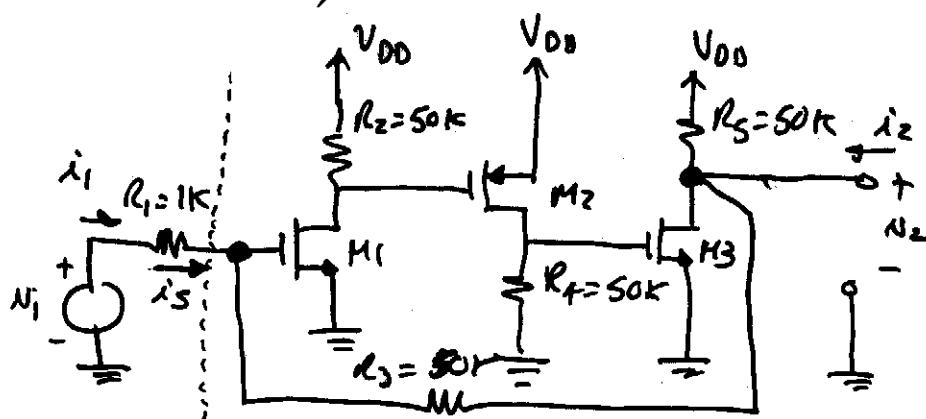

Find  $\frac{N_2}{N_1}$ ,  $\frac{N_1}{N_2}$ , and  $\frac{N_2}{N_3}$

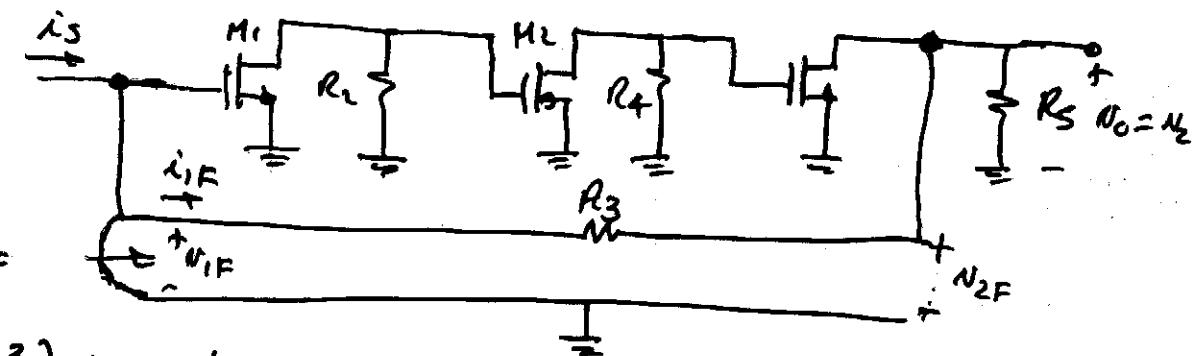if  $g_{m1} = g_{m2} = g_{m3} = 0$ ,  $Z_{m1N} \neq r_{as} = \infty$




$$1.), 2.) \left\{ 3.) \quad f_{HF} = \frac{1}{R_3}$$

$$Y_{12F} = \frac{j_{1F}}{N_{2F}} \Big|_{N_{1F}=0} = -\frac{1}{R_3}$$

$$\gamma_{22F} = \frac{1}{k_3}$$

4)

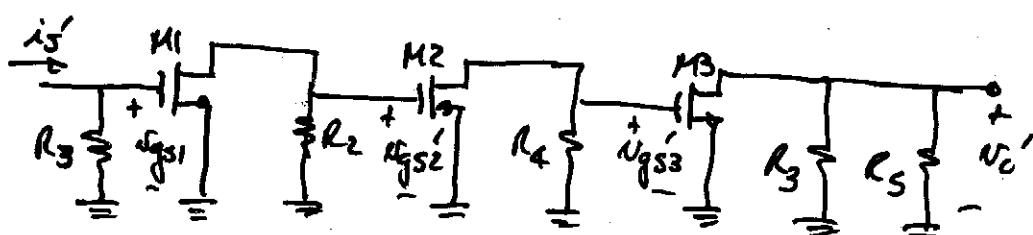

$$\frac{N_0'}{I_3'} = \left( \frac{N_0'}{N_{g53'}} \right) \left( \frac{U_{g53}'}{I_{g52}'} \right) \left( \frac{U_{g52}'}{I_{g51}'} \right) \left( \frac{N_{g51}'}{I_{g51}'} \right)$$

$$= \left( -q_{m3} R_3 / R_5 \right) \left( -q_{m2} R_4 \right) \left( -q_{m1} R_2 \right) \left( \frac{1}{R_3} \right)$$

Example - Cont'd

5.)  $A = \frac{N_0'}{i_3} = (-0.2 \times 25)(-0.2 \times 50)(-0.2 \times 50) \left(\frac{1}{50k}\right) = -25M\Omega$


$$A_F = \frac{N_2}{i_2} = \frac{A}{1+AB} = \frac{-25M\Omega}{1+(-25M\Omega)\left(\frac{1}{50k}\right)} = \frac{-25M\Omega}{1+500} = -49.9k\Omega$$

6.)  $R_{inF} = \frac{1}{(G_S + g_{mT})(1+AB)} = \frac{1}{\left(0 + \frac{1}{50k}\right)(501)} = 99.8\Omega$

$$\frac{N_1}{i_1} = R_{in} = R_i + R_{inF} = 1k + 0.0998k = \underline{1.0998k\Omega} \approx 1099\Omega$$

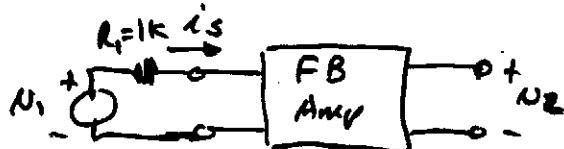7.)  $R_{outF} = \frac{1}{(G_L + g_{zTF})(1+AB)} = \frac{1}{\left(\frac{1}{R_S} + \frac{1}{R_3}\right)(1+AB)} = \frac{R_3/R_S}{1+AB} = \frac{25k}{501} = \underline{\underline{49.9\Omega}}$

$$\frac{N_2}{i_2} = R_{outF} = \underline{\underline{49.9\Omega}}$$




$$\frac{N_2}{N_1} = \left(\frac{N_2}{i_2}\right) \left(\frac{i_2}{N_1}\right) = A \frac{1}{R_{in}} = -\frac{49.9k}{1099\Omega} = -\underline{\underline{45.4V/V}}$$

Shunt-Series Fb. Example - Current Amplifier



$g$ -parameters

$$g_{11F} = \frac{i_{1F}}{N_{1F}} \Big|_{i_{2F}=0}, \quad g_{22F} = \frac{N_{2F}}{i_{2F}} \Big|_{N_{1F}=0}, \quad g_{12F} = \frac{i_{1F}}{i_{2F}} \Big|_{N_{1F}=0} \quad \left(A = \frac{A}{A}\right)$$

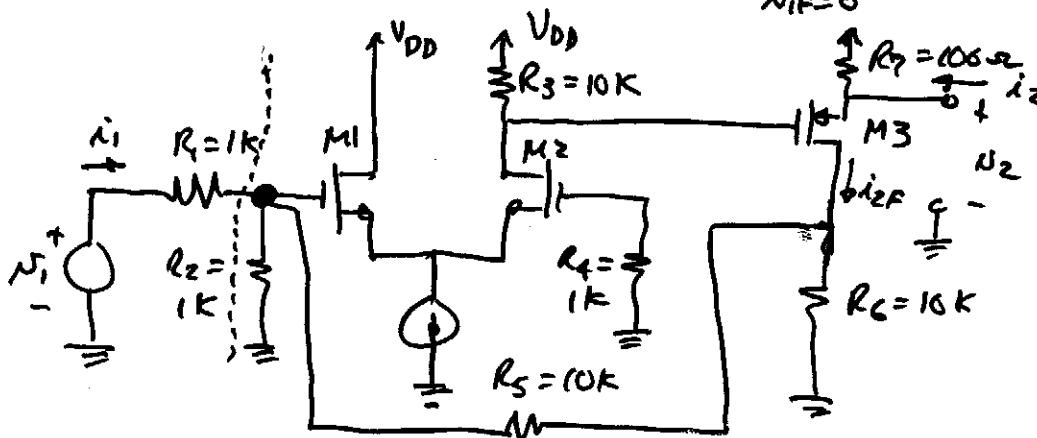

Find  $\frac{N_2}{N_1}$ ,  $\frac{N_1}{i_1}$ ,  
and  $\frac{N_2}{i_2}$  if  
 $g_{m1} = g_{m2} = g_{m3} = 1mS$   
and  $r_{ds} = \infty$ .

$$1.) \quad g_{12F} = \left| \frac{i_{IF}}{i_{2F}} \right| = \left| \frac{-R_6}{R_5 + R_6} \right| = -\frac{1}{2}$$

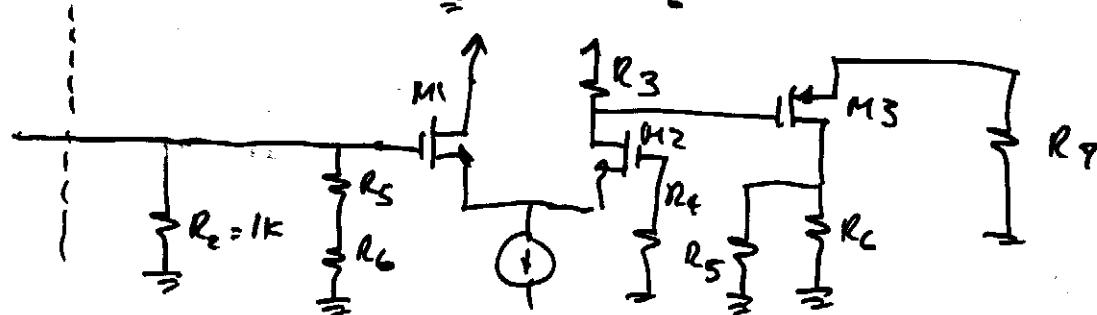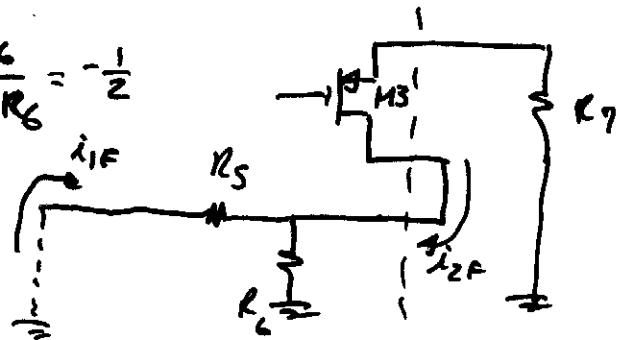

To be continued