
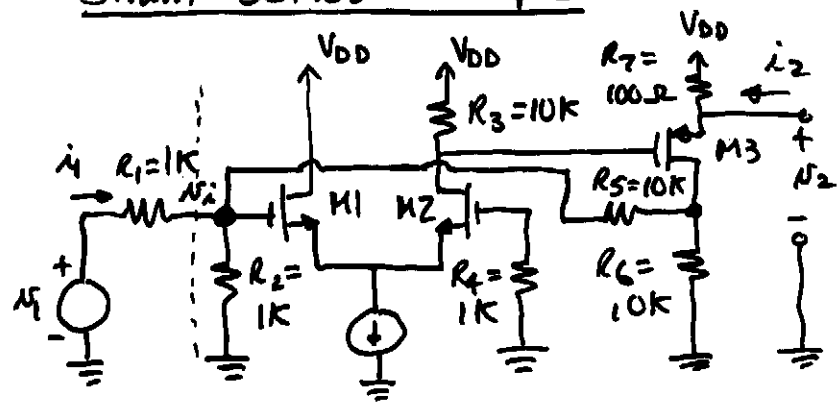


Shunt-Series Example

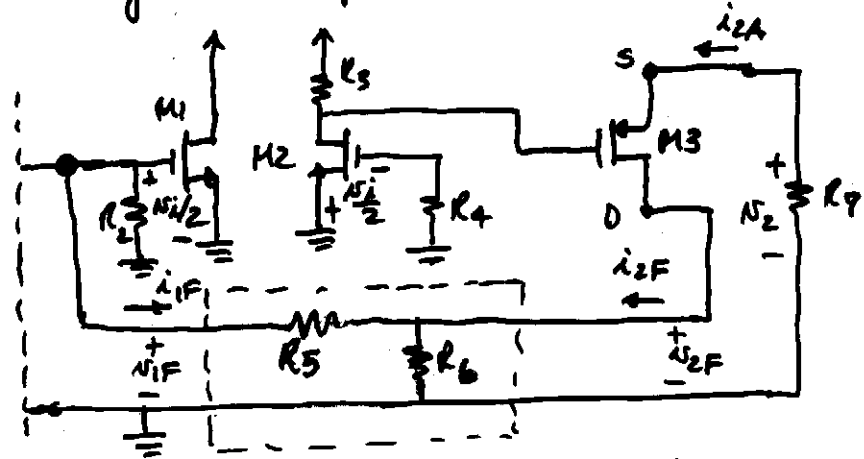

If  $g_{m1} = g_{m2} = g_{m3} = 1 \text{ mS}$   
 and  $r_{ds} = \infty$ , find  
 $\frac{N_2}{N_1}$ ,  $\frac{N_1}{N_i}$ , and  $\frac{N_2}{i_2}$   
 using feedback analysis  
 methods.


Rewriting in two-port form - (Closed loop)



$$\beta = g_{12F} = \frac{i_{1F}}{i_{2F}} \Big|_{N_{1F}=0}$$

$$\beta = -\frac{R_6}{R_5 + R_6} = -\frac{1}{2}$$

Small-signal model - (Open loop)

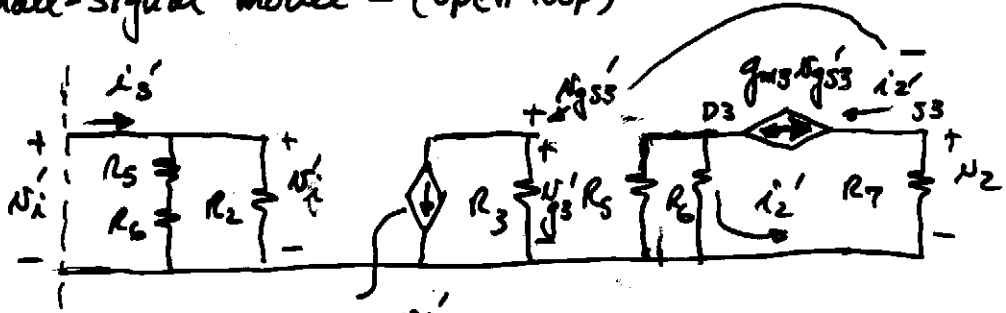

$$v_{gs3}' = v_{gs}' - v_{ss}'$$

$$v_{gs3}' = v_{gs}' - g_{m3} v_{gs3}' R_7$$

$$v_{gs3}' = \frac{v_{gs}'}{1 + g_{m3} R_7}$$

$$i_{2'}' = \left( \frac{i_{2'}'}{v_{gs3}'} \right) \left( \frac{v_{gs3}'}{v_{gs}'} \right) \left( \frac{v_{gs}'}{v_{i2}'} \right) \left( \frac{v_{i2}'}{i_{s'}'} \right)$$

$$= (-g_{m3}) \left( \frac{1}{1 + g_{m3} R_7} \right) \left( \frac{g_{m2} R_3}{2} \right) \left[ R_2 \parallel (R_5 + R_6) \right] \frac{v_{gs3}'}{v_{gs}'} = \frac{1}{1 + g_{m3} R_7}$$

$$\infty A = \frac{i_{2'}'}{i_{s'}'} = (-1 \text{ mS}) \left( \frac{1}{1 + 0.1} \right) \left( \frac{10}{2} \right) (1 \text{K} \parallel 20 \text{K}) = -4.33 \text{ A/A}$$

$$A_F = \frac{i_2}{i_s} = \frac{A}{1 + A\beta} = \frac{-4.33}{1 + (\frac{1}{2})(4.33)} = -1.365 \text{ A/A} \approx \frac{1}{8} = -2$$

$$R_{INF} = \frac{1}{(g_{mT} + G_S)(1 + A_B)} = \frac{R_2 \parallel (R_5 + R_6)}{1 + A_B} = \frac{1}{\frac{1}{R_2} + \frac{1}{R_5 + R_6}}$$


$$= \frac{952 \Omega}{3.164} = 301 \Omega$$

∴  $\frac{N_1}{\lambda_1} = R_i + R_{INF} = \underline{\underline{1.301 k\Omega}} = R_{in}$

$$\frac{N_2}{N_1} = \frac{-i_o R_T}{\lambda_1 R_{in}} \quad \left( i_o = i_2 \text{ of } A = \frac{\lambda_2'}{\lambda_5'} = \frac{\lambda_2'}{\lambda_5'} \right)$$

$$= A_F \frac{R_T}{R_{in}} = (-1.368 \frac{A}{V}) \frac{100 \Omega}{1301 \Omega} =$$
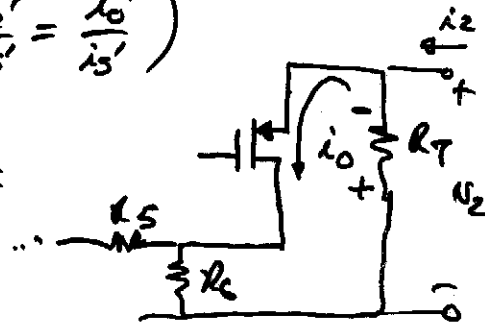
$$\frac{N_2}{N_1} = \underline{\underline{0.105 V/V}}$$





$$R_{out} = \frac{N_2}{i_2} = ?$$

$$R_{OUTF} = (g_{m3} + R_T)(1 + A_B)$$

$$R_{OUTF} = \left( \frac{1}{g_{m3}} + R_T \right) (1 + A_B)$$


$$= (1k + 0.1k)(3.164) = 3.48k\Omega$$

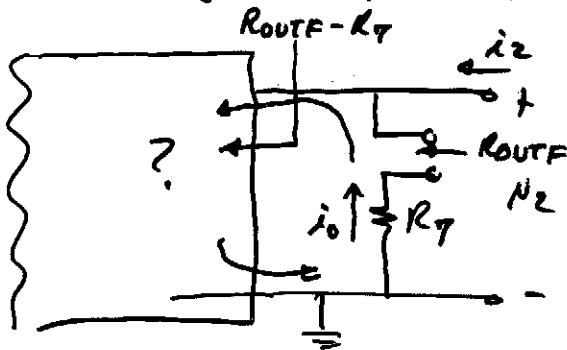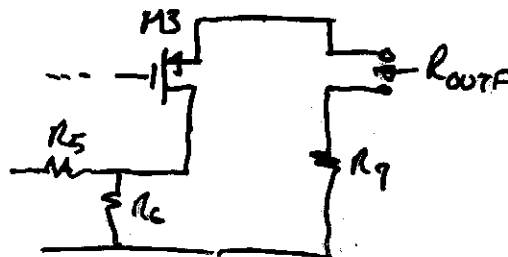

$$R_{out} = \frac{N_2}{i_2} = \left[ (R_{OUTF} - R_T) \parallel R_T \right]$$

$$R_{out} = \frac{N_2}{i_2} = \left[ (3.48k - 100) \parallel 100 \right] = \underline{\underline{97.12 \Omega}}$$

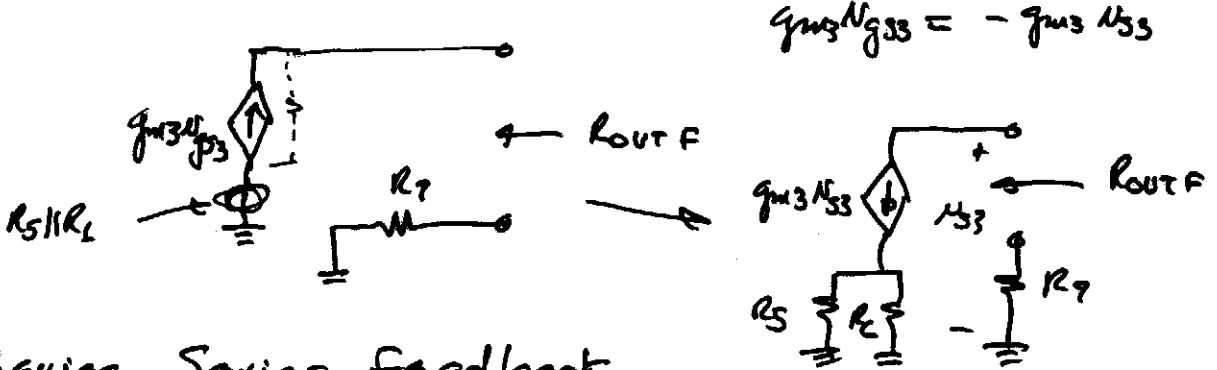Question? Why not include  $R_5$  &  $R_6$  in  $z_{22T}$ ?




$$g_{m3} v_{gs3} = -g_{m3} v_{gs}$$

Series-Series feedback

Z parameters  $Z_{12F} = \frac{V_{1F}}{I_{2F}} \Big|_{I_{1F}=0} = \beta$

Example -

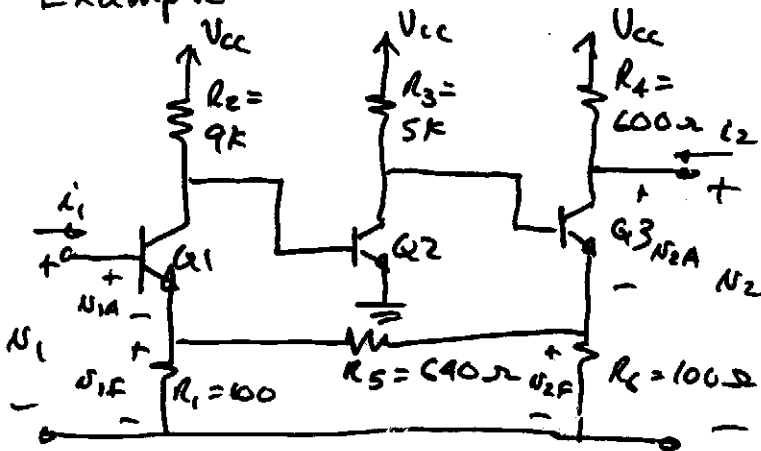

$$F_{mid} \frac{N_2}{N_1}, \frac{N_1}{N_2}, \frac{1}{\beta} \frac{N_2}{N_1}$$

When  $h_{fe1} = h_{fe2} = h_{fe3} =$

$$= 100$$

$$I_{C1} = 0.6 \text{ mA}$$

$$I_{C2} = 1 \text{ mA}$$

$$I_{C3} = 4 \text{ mA}$$

$$V_A = \infty$$

