
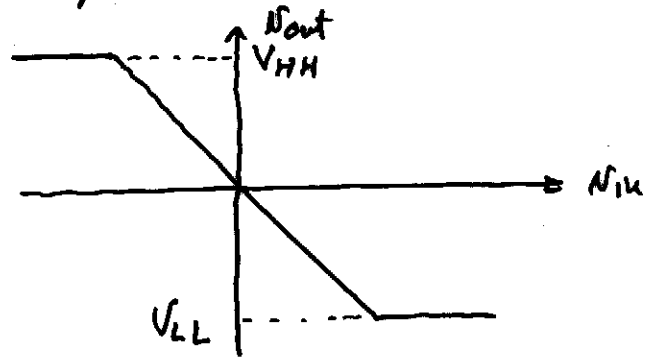


LIMITING AMPLIFIERS

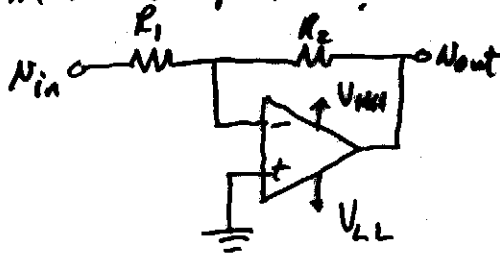
How do you introduce an output saturation/limit in an amplifier?




Problem:

- 1.) Limits not well controlled
- 2.) Saturation too "hard".

Solution -

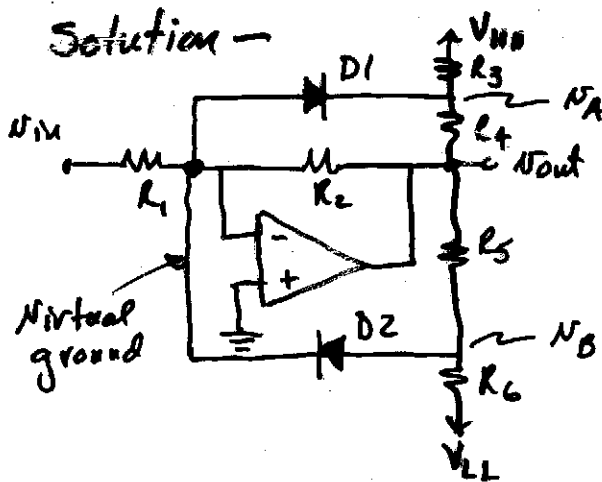

Assume Ideal diodes

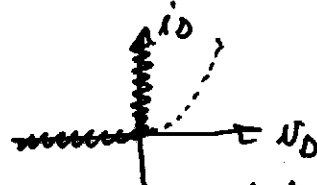

Three possible states

- 1.) Both diodes off.
- 2.) D1 ON, D2 OFF
- 3.) D1 OFF, D2 ON

1.) D1 and D2 off

$$N_{out} = -\frac{R_2}{R_1} N_{in}$$

2.) $N_A \leq 0 \rightarrow$ D1 ON and D2 off


To find where D1 turns on, assume D1 is off and solve for N_A .

$$N_A = \frac{R_4}{R_3 + R_4} V_{HH} + \frac{R_3}{R_3 + R_4} N_{out} = 0$$

Setting $N_A = 0 \rightarrow$ N_{out} where D1 turns on

$$N_{out} = -\frac{R_4}{R_3} V_{HH}$$

Amplitude Limiter - Cont'd

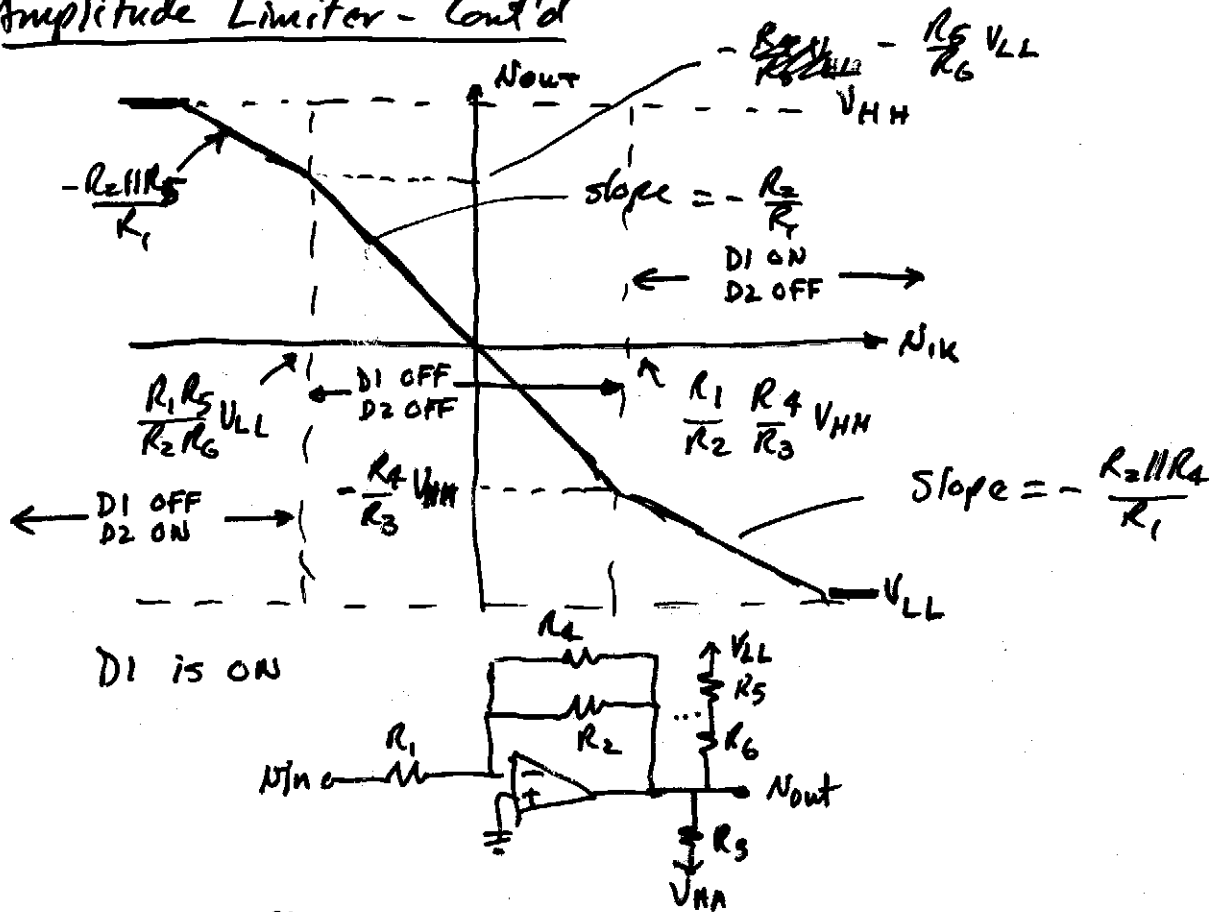

Added after class -

3.) $N_B \geq 0 \rightarrow D2 ON and D1 OFF$

To find where D2 turns ON, assume D2 is off and find N_B .

$$N_B = \frac{R_5}{R_5 + R_6} V_{LL} + \frac{R_6}{R_5 + R_6} N_{out} = 0 \rightarrow N_{out} = -\frac{R_5}{R_6} V_{LL}$$

Corresponding input voltage is $N_{in} = \frac{R_1 R_5}{R_2 R_6} V_{LL}$

$\therefore D2 is ON$

