

QUIZ NO. 7

NAME _____ Score _____ /10

If $k_n = 1\text{mA/V}^2$, $V_{TN} = 1\text{V}$, $I_{DS} = 0.5\text{mA}$ and $\lambda = 0\text{V}^{-1}$,
 find the numerical values of the following small signal
 functions: v_{o2}/v_{in} , v_{o1}/v_{in} , R_{o1} and R_{o2} .

