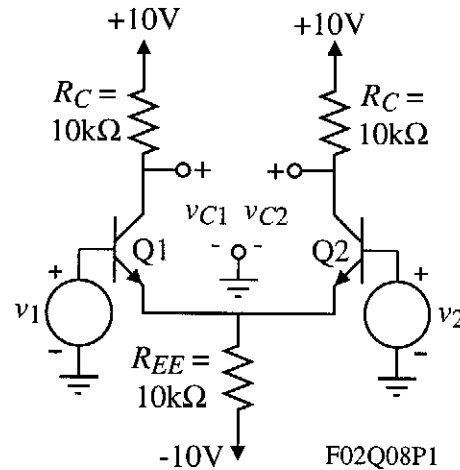


QUIZ NO. 8 - SOLUTION

(Average score = 7.7/10 for only those students taking the quiz)

Assume that Q1 and Q2 and the resistors R_C of the differential amplifier shown are matched. If $\beta_F = 100$, $V_t = 25\text{mV}$, $V_{BE} = 0.7\text{V}$ and $V_A = \infty$, find (a.) the numerical value of I_{C1} and I_{C2} if $v_1 = v_2 = 0$. (b.) Assume that $I_{C1} = I_{C2} = 0.5\text{mA}$ and find the numerical value of v_{C1}/v_{id} where $v_{id} = v_1 - v_2$. (c.) Continuing to assume that $I_{C1} = I_{C2} = 0.5\text{mA}$, find the numerical value of v_{C1}/v_{ic} where $v_{ic} = v_1 = v_2$.


Solution

$$(a.) I_{C1} = I_{C2} = \frac{\alpha(V_{EE} - V_{BE})}{2R_{EE}} = \frac{10 - 0.7}{2 \cdot 10} \text{ mA} = \underline{0.465\text{mA}}$$

$$(b.) \text{ If } I_{C1} = I_{C2} = 0.5\text{mA}, \text{ then } g_m = \frac{I_{C1}}{V_t} = \frac{0.5}{25} \text{ S} = 20\text{mS} \text{ and } r_\pi = \frac{\beta_F}{g_m} = 5\text{k}\Omega$$

Small-signal model:
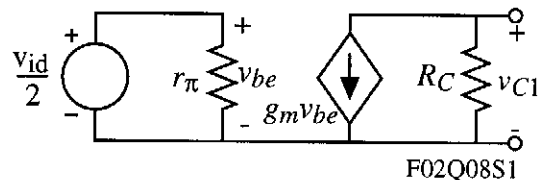
$$v_{C1}/v_{id} = \frac{-g_m R_C}{2} = \frac{-20 \cdot 10}{2} = \underline{-100\text{V/V}}$$



(c.) The small-signal model for this part is shown.

$$\frac{v_{C1}}{v_{id}} = \left(\frac{v_{C1}}{v_{be}} \right) \left(\frac{v_{be}}{v_{ic}} \right) = -g_m R_C \left(\frac{v_{be}}{v_{ic}} \right)$$

$$v_{be} = v_{ic} - 2R_{EE} \left(\frac{1}{r_\pi} + g_m \right) v_{be} = v_{ic} - \frac{2R_{EE}}{r_\pi} (1 + \beta_F) v_{be}$$

$$\therefore \frac{v_{be}}{v_{ic}} = \frac{1}{1 + \frac{2R_{EE}}{r_\pi} (1 + \beta_F)}$$

$$\frac{v_{C1}}{v_{id}} = \left(\frac{v_{C1}}{v_{be}} \right) \left(\frac{v_{be}}{v_{ic}} \right) = \frac{-g_m R_C}{1 + \frac{2R_{EE}}{r_\pi} (1 + \beta_F)} = \frac{-200}{1 + 404} = \underline{-0.494\text{V/V}}$$

