



QUIZ NO. 12 - SOLUTION

(Average score = 6.2/10 of those taking the quiz)

A shunt-shunt feedback amplifier is shown. Use the methods of feedback analysis to find the numerical values of v_2/v_1 , v_1/i_1 , and v_2/i_2 . For Q1, assume that $h_{fe} = 100$, $g_m = 50\text{mS}$ and $r_o = \infty$. For M2, assume that $g_m = 1\text{mS}$ and $r_{ds} = \infty$.

Solution


Quasi-ac model of this circuit.

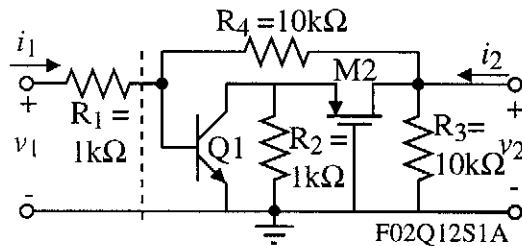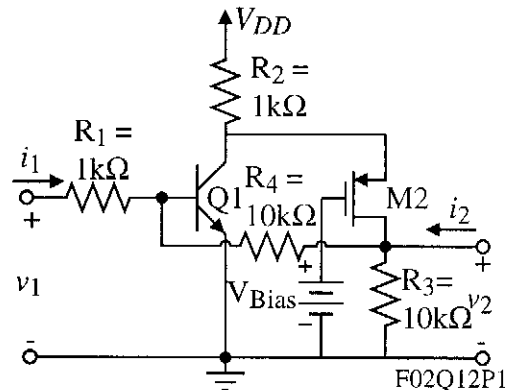

The feedback β is given as

$$\beta = g_{12F} = \frac{i_{1F}}{v_{2F}} \Big|_{v_{2F}=0} = \frac{-1}{R_4} = \frac{-1}{10\text{K}}$$

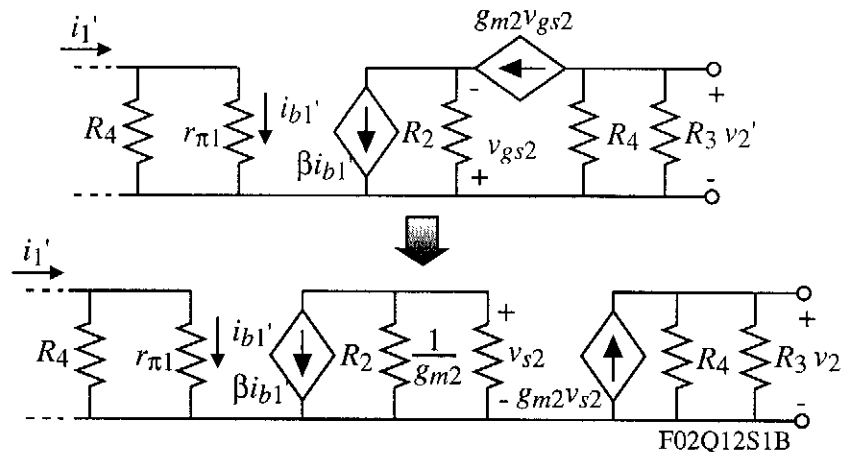The open-loop circuit to calculate A is given as,



$$A = \frac{v_2'}{i_1'} = \left(\frac{v_2'}{v_{s2'}} \right) \left(\frac{v_{s2'}}{i_{b1}'} \right) \left(\frac{i_{b1}'}{i_1'} \right) = (g_{m2} \cdot R_3 \parallel R_4) [-\beta_1 \cdot R_2 \parallel (1/g_{m2})] \left(\frac{R_4}{R_4 + r_{\pi 1}} \right)$$

$$= (5)(-50\text{K})(10/12) = -208.33\text{k}\Omega \quad (r_{\pi 1} = \frac{100}{50\text{mS}} = 2\text{k}\Omega)$$

$$A_F = \frac{v_2}{i_1} = \frac{A}{1+A\beta} = \frac{-208.33\text{K}}{1+(-208.33\text{K}/-10\text{K})} = \frac{-208.33\text{K}}{1+20.833} = \frac{-208.33\text{K}}{21.833} = -9.542\text{k}\Omega$$

$$R_{in} = R_4 \parallel r_{\pi 1} = 2\text{k} \parallel 10\text{K} = 1.67\text{K} \quad \rightarrow R_{inF} = \frac{1.67\text{k}}{21.833} = 76.34\Omega$$

$$\therefore \frac{v_1}{i_1} = 1\text{k}\Omega + 76.34\Omega = \underline{1.076\text{k}\Omega} \quad \frac{v_2}{v_1} = \left(\frac{v_2}{i_1} \right) \left(\frac{i_1}{v_1} \right) = \frac{-9.542\text{k}\Omega}{1.076\text{k}\Omega} = \underline{-8.652 \text{ V/V}}$$

$$R_{out} = R_3 \parallel R_4 = 5\text{k}\Omega \quad \rightarrow \frac{v_2}{i_2} = \frac{5\text{k}\Omega}{21.833} = \underline{229\Omega}$$