

ECE 3041 Spring 2012
Homework Problem Set 10
Homework Problem 10 for Experiment No. 12

Due Week of April 16

1. Use SPICE to plot the dc transfer characteristic V_O versus V_i for the circuit shown below as V_i varies from -20 to 20 V. Use the following parameters for the SPICE simulations for the 1N4148 signal diode: reverse saturation current, 3 nA; emission coefficient, 1.8 ; and breakdown voltage, 100 V. The values of the circuit components are: $E_1 = E_2 = 3$ V, $R_1 = 2$ k Ω and $R_2 = 1$ k Ω .
2. Use SPICE to plot the output voltage as a function of time for the circuit shown below if the input is a sine wave with a peak to peak value of 30 V, a dc level of 0 V and a frequency of 1 kHz. Plot the output voltage for two cycles of the input.

