

## The BJT Differential Amplifier

### ECE 3050 Analog Electronics

The differential amplifier or diff amp is used in applications where it is desired to have an output voltage that is proportional to the difference between two input voltages. Fig. 1(a) shows the basic circuit diagram. The tail supply is modeled as a current source  $I'_Q$  having an output resistance  $R_Q$ . In the case of an ideal current source,  $R_Q$  is an open circuit. Often a diff amp is designed with a resistive tail supply. In this case,  $I'_Q = 0$ . There are two outputs shown. Either or both can be used. Often the difference voltage between the two outputs is used.

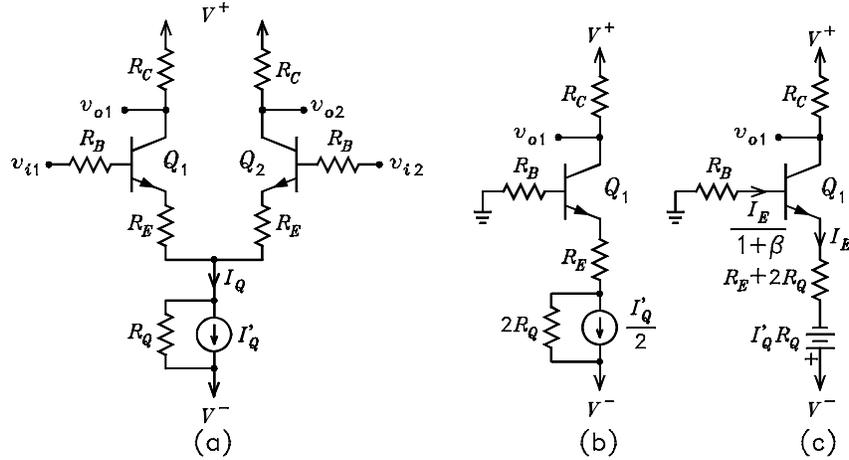


Figure 1: (a) Circuit diagram of the differential amplifier. (b) First equivalent bias circuit for  $Q_1$ . (c) Second equivalent bias circuit for  $Q_1$ .

The dc bias circuit is obtained by setting  $v_{i1} = v_{i2} = 0$ . The tail supply can be divided into two parallel current sources of value  $I'_Q/2$ , each having an output resistance  $2R_Q$ . By symmetry, no dc current flows between the two sides of the circuit so that the two sides can be separated. The circuit obtained for  $Q_1$  is shown in Fig. 1(b). The circuit for  $Q_2$  is identical. The circuit shown in Fig. 1(c) is obtained by making a Thévenin equivalent of the tail supply in Fig. 1(b). The bias equation for  $I_E$  is

$$0 - (V^- - I'_Q R_Q) = \frac{I_E}{1 + \beta} R_B + V_{BE} + I_E (R_E + 2R_Q)$$

This can be solved  $I_E$  to obtain

$$I_E = \frac{-V^- + I'_Q R_Q - V_{BE}}{R_B / (1 + \beta) + R_E + 2R_Q}$$

The dc collector-to-base voltage is given by

$$V_{CB} = V_C - V_B = (V^+ - \alpha I_E R_C) - \left( -\frac{I_E}{1 + \beta} R_B \right) = V^+ - \alpha I_E R_C + \frac{I_E}{1 + \beta} R_B$$

This must be greater than zero for the two BJTs to be biased in the active mode. The collector to emitter voltage is given by

$$V_{CE} = V_C - V_E = V_C - (V_B - V_{BE}) = V_{CB} + V_{BE}$$

It follows that  $r_e$ ,  $r'_e$ , and  $r_0$  for each transistor are given by

$$r_e = \frac{V_T}{I_E} \quad r'_e = \frac{R_B + r_x}{1 + \beta} + r_e \quad r_0 = \frac{V_A + V_{CE}}{\alpha I_E}$$

To solve for the small-signal value of  $v_{o1}$ , we zero  $V^+$ ,  $V^-$ , and  $I'_Q$  to form the ac signal circuit. Then the circuit seen looking out of the emitter of  $Q_1$  is replaced by a Thévenin equivalent circuit. To obtain this, we first replace the circuit seen looking into the emitter of  $Q_2$  with a Thévenin equivalent circuit. This circuit is shown in Fig. 2(a), where

$$v_{e2(oc)} = v_{i2} \frac{r_0 + R_C / (1 + \beta)}{r'_e + r_0 + R_C / (1 + \beta)} \quad r_{ie2} = r'_e \frac{r_0 + R_C}{r'_e + r_0 + R_C / (1 + \beta)}$$

The Thévenin voltage and resistance seen looking out of the emitter of  $Q_1$  are given by

$$v_{te1} = v_{e2(oc)} \frac{R_Q}{R_Q + R_E + r_{ie2}} \quad R_{te} = R_E + R_Q \parallel (R_E + r_{ie2})$$

The new circuit is shown in Fig. 2(b).

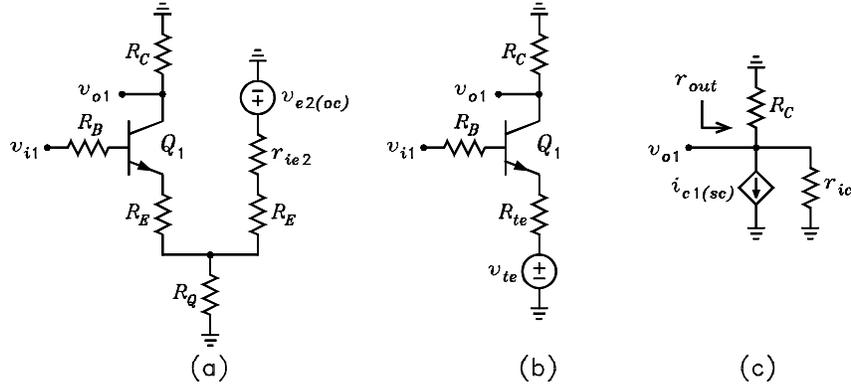


Figure 2: (a) Ac signal circuit for  $Q_1$ . (b) Circuit for calculating  $v_{o1}$  and  $r_{out}$ .

The circuit for calculating  $v_{o1}$  and  $r_{out}$  is shown in Fig. 2(c). We can write

$$v_{o1} = -i_{c1(sc)} \times r_{ic} \parallel R_C = (G_{mb}v_{i1} - G_{me}v_{te1}) \times r_{ic} \parallel R_C \quad r_{out} = r_{ic} \parallel R_C$$

where

$$G_{mb} = \frac{\alpha}{r'_e + R_{te} \parallel r_0} \frac{r_0 - R_{te} / \beta}{r_0 + R_{te}} \quad G_{me} = \frac{1}{R_{te} + r'_e \parallel r_0} \frac{\alpha r_0 + r'_e}{r_0 + r'_e} \quad r_{ic} = \frac{r_0 + r'_e \parallel R_{te}}{1 - \alpha R_{te} / (r'_e + R_{te})}$$

When the above results are combined, we obtain

$$v_{o1} = -A_{v1}v_{i1} + A_{v2}v_{i2} = -A_{v1} \left( v_{i1} - \frac{A_{v2}}{A_{v1}} v_{i2} \right)$$

where  $A_{v1}$  and  $A_{v2}$  are the voltage gains given by

$$A_{v1} = G_{mb} \times r_{ic} \parallel R_C \quad A_{v2} = G_{me} \times r_{ic} \parallel R_C \times \frac{R_Q}{R_Q + R_E + r_{ie2}} \frac{r_0 + R_C / (1 + \beta)}{r'_e + r_0 + R_C / (1 + \beta)}$$

By symmetry,  $v_{o2}$  is given by

$$v_{o2} = -v_{o1} = -A_{v1} \left( v_{i2} - \frac{A_{v2}}{A_{v1}} v_{i1} \right)$$

We see that the gains for  $v_{i1}$  and  $v_{i2}$  differ by the ratio  $A_{v2}/A_{v1}$ . This is given by

$$\frac{A_{v2}}{A_{v1}} = \frac{G_{me}}{G_{mb}} \frac{R_Q}{R_Q + R_E + r_{ie2}} \frac{r_0 + R_C / (1 + \beta)}{r'_e + r_0 + R_C / (1 + \beta)}$$

If this ratio is unity,  $v_{o1}$  and  $v_{o2}$  are proportional to the difference between the two input voltages. It can be seen that the ratio is exactly unity only if  $R_Q \rightarrow \infty$  and  $r_0 \rightarrow \infty$ .

Let  $v_o$  be the differential output voltage. This is given by

$$v_o = v_{o1} - v_{o2} = -(A_{v1} + A_{v2})(v_{i1} - v_{i2}) = -A_{v1} \left( 1 + \frac{A_{v2}}{A_{v1}} \right) (v_{i1} - v_{i2})$$

This is proportional to the difference between the two input voltages even if  $R_Q < \infty$  and  $r_0 < \infty$ .

The  $r_0$  approximations to the gains are obtained by letting  $r_0 \rightarrow \infty$  except in the expression for  $r_{ic}$ . We obtain

$$A_{v1} \simeq G_m \times r_{ic} \parallel R_C \quad A_{v2} = G_m \times r_{ic} \parallel R_C \times \frac{R_Q}{R_Q + R_E + r'_e}$$

where

$$G_m = \frac{\alpha}{r'_e + R_{te}} \quad R_{te} = R_E + R_Q \parallel (R_E + r'_e)$$

The expression for  $r_{out}$  is the same except  $r_{ic}$  is calculated with  $R_{te} = R_E + R_Q \parallel (R_E + r'_e)$ .

The equivalent circuit seen looking into the base of  $Q_1$  consists of the resistor  $r_{ib}$  in series with the voltage  $v_{b1(oc)}$ . These are given by

$$r_{ib} = r_x + (1 + \beta) r_e + R_{te} \frac{(1 + \beta) r_0 + R_C}{r_0 + R_{te} + R_C}$$

$$v_{b1(oc)} = v_{te1} \frac{r_0 + R_C}{R_{te} + r_0 + R_C} = v_{i2} \frac{r_0 + R_C / (1 + \beta)}{r'_e + r_0 + R_C / (1 + \beta)} \frac{r_0 + R_C}{R_{te} + r_0 + R_C}$$

The equivalent circuit is shown in Fig. 3(a). The circuit for  $Q_2$  is shown in Fig. 3(b), where  $v_{b2(oc)}$  is given by

$$v_{b2(oc)} = v_{te2} \frac{r_0 + R_C}{R_{te} + r_0 + R_C} = v_{i1} \frac{r_0 + R_C / (1 + \beta)}{r'_e + r_0 + R_C / (1 + \beta)} \frac{r_0 + R_C}{R_{te} + r_0 + R_C}$$

The two base equivalent circuits can be used to calculate the base currents  $i_{b1}$  and  $i_{b2}$ .

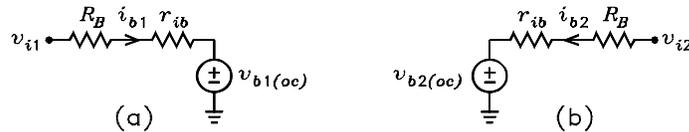


Figure 3: (a) Equivalent circuit for  $i_{b1}$ . (b) Equivalent circuit for  $i_{b2}$ .

**Example 1** It is given that  $I'_Q = 2\text{ mA}$ ,  $R_Q = 50\text{ k}\Omega$ ,  $R_B = 1\text{ k}\Omega$ ,  $R_E = 100\ \Omega$ ,  $R_C = 10\text{ k}\Omega$ ,  $V^+ = 20\text{ V}$ ,  $V^- = -20\text{ V}$ ,  $V_T = 0.025\text{ V}$ ,  $r_x = 20\ \Omega$ ,  $\beta = 99$ ,  $V_{BE} = 0.65\text{ V}$ , and  $V_A = 50\text{ V}$ . Calculate the small-signal values for  $v_{o1}$  and  $v_{o2}$ , the output resistance  $r_{out}$ , and the equivalent input circuit seen by each source.

*Solution.* First, we solve for the dc emitter current in each transistor. It is

$$I_E = \frac{-V^- + I'_Q R_Q - V_{BE}}{R_B / (1 + \beta) + R_E + 2R_Q} = 1.192\text{ mA}$$

To verify that the transistors are in the active mode, we calculate the collector-to-base voltage

$$V_{CB} = V^+ - \alpha I_E R_C + \frac{I_E}{1 + \beta} R_B = 8.209\text{ V}$$

Because this is greater than zero, both BJTs are in the active mode. The collector-to-emitter voltage is  $V_{CE} = V_{CB} + V_{BE} = 8.859\text{ V}$ . Thus the resistances  $r_e$ ,  $r'_e$ , and  $r_0$  are

$$r_e = \frac{V_T}{I_E} = 20.97\ \Omega \quad r'_e = \frac{R_B + r_x}{1 + \beta} + r_e = 31.17\ \Omega \quad r_0 = \frac{V_A + V_{CE}}{\alpha I_E} = 49.87\text{ k}\Omega$$

The resistances  $r_{ie}$  and  $R_{te}$  are

$$r_{ie} = r'_e \frac{r_0 + R_C}{r'_e + r_0 + R_C / (1 + \beta)} = 37.32\ \Omega \quad R_{te} = R_E + R_Q \parallel (R_E + r_{ie}) = 236.9\ \Omega$$

The transconductances  $G_{mb}$  and  $G_{me}$  and the resistance  $r_{ic}$  are

$$G_{mb} = \frac{\alpha}{r'_e + R_{te} \parallel r_0} \frac{r_0 - R_{te} / \beta}{r_0 + R_{te}} = \frac{1}{271}\text{ S} \quad G_{me} = \frac{1}{R_{te} + r'_e \parallel r_0} \frac{\alpha r_0 + r'_e}{r_0 + r'_e} = \frac{1}{270.8}\text{ S}$$

$$r_{ic} = \frac{r_0 + r'_e \parallel R_{te}}{1 - \alpha R_{te} / (r'_e + R_{te})} = 398.9\ \Omega$$

It follows that the gains  $A_{v1}$  and  $A_{v2}$  are

$$A_{v1} = G_{mb} \times r_{ic} \parallel R_C = 36$$

$$A_{v2} = G_{me} \times r_{ic} \parallel R_C \times \frac{R_Q}{R_Q + R_E + r_{ie2}} \frac{r_0 + R_C / (1 + \beta)}{r'_e + r_0 + R_C / (1 + \beta)} = 35.91$$

Thus  $v_{o1}$  and  $v_{o2}$  are

$$v_{o1} = -36v_{i1} + 35.91v_{i2} \quad v_{o2} = -36v_{i2} + 35.91v_{i1}$$

The differential output voltage is

$$v_o = v_{o1} - v_{o2} = 71.91(v_{i1} - v_{i2})$$

The output resistance is

$$r_{out} = r_{ic} \parallel R_C = 9.755\text{ k}\Omega$$

In the equivalent input circuits,  $r_{ib}$ ,  $v_{b1(oc)}$ , and  $v_{b2(oc)}$  are

$$r_{ib} = r_x + (1 + \beta)r_e + R_{te} \frac{(1 + \beta)r_0 + R_C}{r_0 + R_{te} + R_C} = 19.82\text{ k}\Omega$$

$$v_{b1(oc)} = v_{i2} \frac{r_0 + R_C / (1 + \beta)}{r'_e + r_0 + R_C / (1 + \beta)} \frac{r_0 + R_C}{R_{te} + r_0 + R_C} = 0.9953v_{i2}$$

$$v_{b2(oc)} = v_{i1} \frac{r_0 + R_C / (1 + \beta)}{r'_e + r_0 + R_C / (1 + \beta)} \frac{r_0 + R_C}{R_{te} + r_0 + R_C} = 0.9953v_{i1}$$