

Hybrid- π Model with Body Effect

Let the drain current and each voltage be written as the sum of a dc component and a small-signal ac component as follows:

$$i_D = I_D + i_d \quad (1)$$

$$v_{GS} = V_{GS} + v_{gs} \quad (2)$$

$$v_{BS} = V_{BS} + v_{bs} \quad (3)$$

$$v_{DS} = V_{DS} + v_{ds} \quad (4)$$

If the ac components are sufficiently small, we can write

$$i_d = \frac{\partial I_D}{\partial V_{GS}} v_{gs} + \frac{\partial I_D}{\partial V_{BS}} v_{bs} + \frac{\partial I_D}{\partial V_{DS}} v_{ds} \quad (5)$$

where the derivatives are evaluated at the dc bias values. Let us define

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = K (V_{GS} - V_{TH}) = 2\sqrt{KI_D} \quad (6)$$

$$g_{mb} = \frac{\partial I_D}{\partial V_{BS}} = \frac{\gamma\sqrt{KI_D}}{\sqrt{\phi - V_{BS}}} = \chi g_m \quad (7)$$

$$\chi = \frac{\gamma}{2\sqrt{\phi - V_{BS}}} \quad (8)$$

$$r_0 = \left[\frac{\partial I_D}{\partial V_{DS}} \right]^{-1} = \left[\frac{k'}{2} \frac{W}{L} \lambda (V_{GS} - V_{TH})^2 \right]^{-1} = \frac{V_{DS} + 1/\lambda}{I_D} \quad (9)$$

The small-signal drain current can thus be written

$$i_d = i_{dg} + i_{db} + \frac{v_{ds}}{r_0} \quad (10)$$

where

$$i_{dg} = g_m v_{gs} \quad (11)$$

$$i_{db} = g_{mb} v_{bs} \quad (12)$$

The small-signal circuit which models these equations is given in Fig. 1. This is called the hybrid- π model.

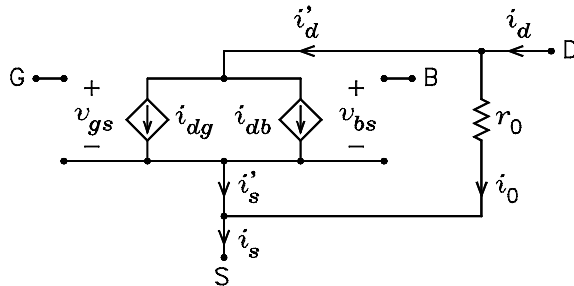


Figure 1: Hybrid- π model of the MOSFET.