
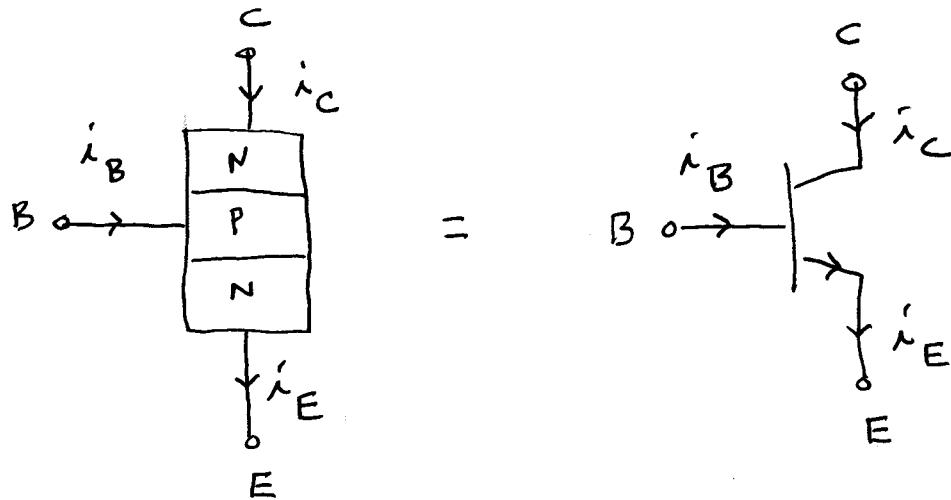


## The BJT - NPN Device

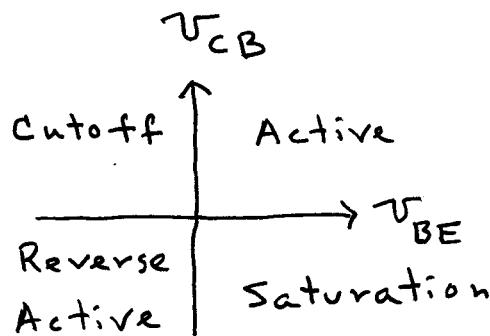

## Modes of Operation




In the active mode, the B-E junction is forward biased. The C-B junction is reverse biased. The labeled current directions are for the active mode. For the PNP device, the current directions are reversed.

2-05/16/03

In the NPN device, the p type impurity doping in the base is very small compared to the n type impurity doping in the collector and emitter. For this reason, electrons are the majority current carriers. In the PNP device, holes are the majority current carriers.

### NPN BJT in the Active Mode

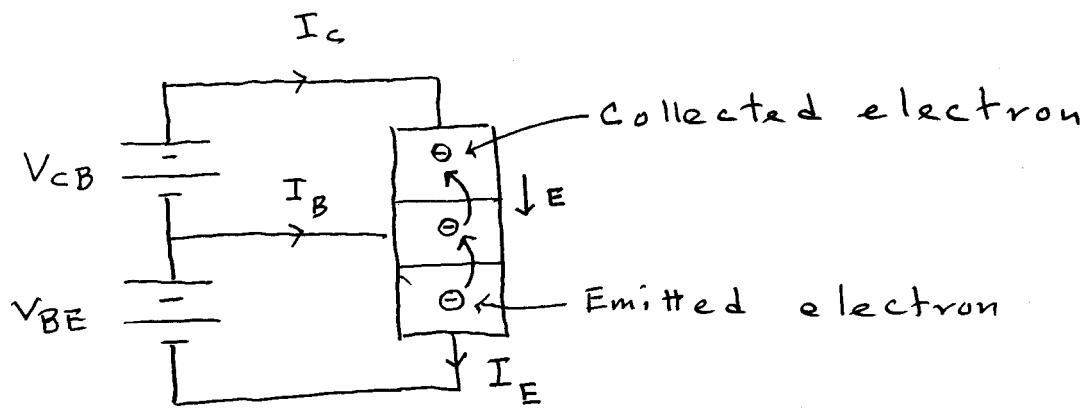

Electrons are emitted from the emitter region across the forward biased B-E junction into the base region. The E field across

3 - 05/16/03

the reversed biased CB junction attracts these electrons and they are collected by the collector. The fraction of collected electrons is denoted by  $\alpha$ . Thus we have

$$I_C = \alpha I_E$$

$$I_B = I_E - I_C = (1-\alpha) I_E$$

$$\Rightarrow I_E = \frac{1}{1-\alpha} I_B$$

$$\Rightarrow I_C = \frac{\alpha}{1-\alpha} I_B$$

The current gain  $\beta$  is defined by

$$\beta = \frac{\alpha}{1-\alpha}$$

$$\Rightarrow I_C = \beta I_B = \alpha I_E$$

1-05/19/03

In general, we can write


$$i_C = \beta i_B = \alpha i_E$$

## The Transfer Characteristics

These are plots of  $i_C$  versus  $v_{BE}$  for  $v_{CE} = \text{constant}$

$$i_C = I_s e^{\frac{v_{BE}}{V_T}}$$

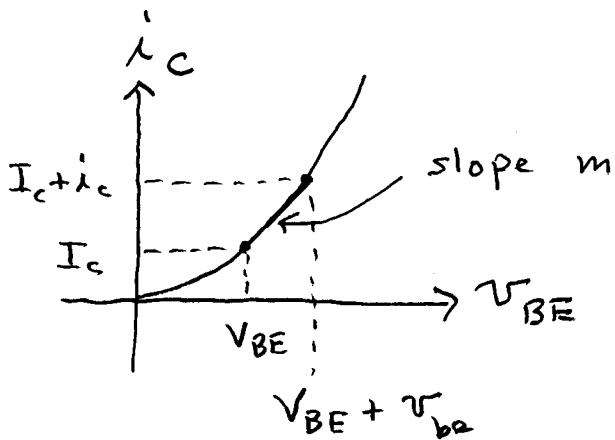where  $I_s = I_{s0} \left(1 + \frac{v_{CE}}{V_T}\right) = \text{constant}$



Draw a tangent line at the point  $(v_{BE}, i_C)$ . The slope of the line can be used to relate changes in  $i_C$  to changes in  $v_{BE}$ .

2-05/19/03

$$m = \frac{\partial I_C}{\partial V_{BE}} = I_S e^{\frac{V_{BE}}{V_T}} \times \frac{1}{V_T}$$


$$= \frac{I_C}{V_T}$$

$$\Rightarrow i_c = \frac{I_c}{V_T} V_{be}$$
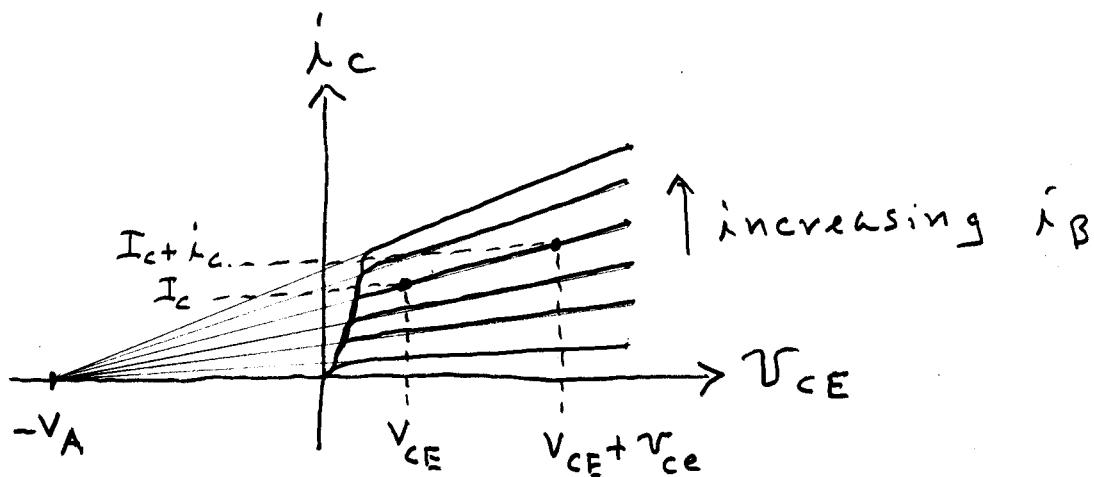
## The output characteristics

These are plots of  $i_c$  versus  $V_{CE}$  for  $i_B = \text{constant}$ .

$$i_c = \beta i_B = \beta_0 \left( 1 + \frac{V_{CE}}{V_A} \right) i_B$$



3-05/19/03

Draw a tangent line at the point  $(V_{CE}, I_c)$ . The slope of the line can be used to relate changes in  $I_c$  to changes in  $V_{CE}$ .

$$\begin{aligned}
 m &= \frac{\partial I_c}{\partial V_{CE}} = \beta_0 \frac{1}{V_A} I_B \\
 &= \beta_0 \frac{1}{V_A} \frac{I_c}{\beta} \\
 &= \frac{\beta_0}{V_A} \frac{I_c}{\beta_0 \left(1 + \frac{V_{CE}}{V_A}\right)} \\
 &= \frac{I_c}{V_A + V_{CE}}
 \end{aligned}$$

$$\Rightarrow I_c = \frac{I_c}{V_A + V_{CE}} V_{CE}$$

Thus, in general, we have

$$I_c = \frac{I_c}{V_T} V_{be} + \frac{I_c}{V_A + V_{CE}} V_{CE}$$

4-05/19/03

Let us define


$$g_m = \frac{I_c}{V_T} \quad R_o = \frac{V_A + V_{CE}}{I_c}$$

$$\Rightarrow i_c = g_m v_{be} + \frac{V_{ce}}{R_o}$$

Next, we relate the change in  $i_B$  to a change in  $V_{BE}$ .

$$i_B = \frac{i_c}{\beta} = \frac{I_{so} \left(1 + \frac{V_{ce}}{V_A}\right) e^{V_{BE}/V_T}}{\beta_0 \left(1 + \frac{V_{ce}}{V_A}\right)}$$
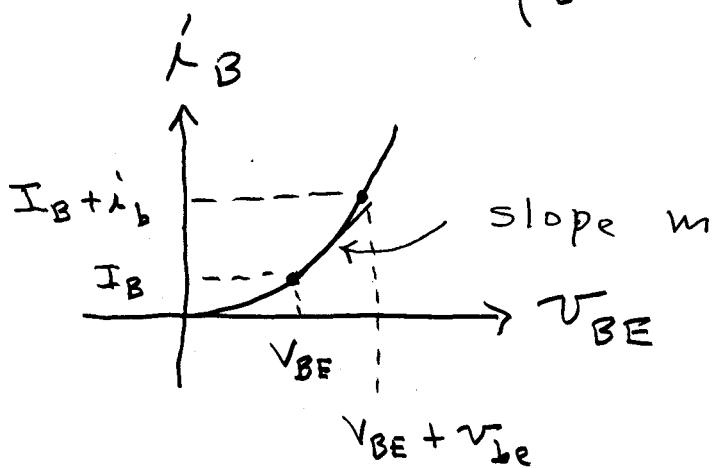
$$= \frac{I_{so}}{\beta_0} e^{V_{BE}/V_T}$$



Draw a tangent line at the point  $(V_{BE}, I_B)$ . The slope of the line

5 - 05/19/03

can be used to relate changes in  $i_B$  to changes in  $V_{BE}$ .

$$m = \frac{dI_B}{dV_{BE}} = I_{so} e^{\frac{V_{BE}}{V_T}} \times \frac{1}{V_T}$$
$$= \frac{I_B}{V_T}$$

$$\Rightarrow i_b = \frac{I_B}{V_T} V_{be}$$

Let us define  $R_\pi = \frac{V_T}{I_B}$

$$\Rightarrow i_b = \frac{V_{be}}{R_\pi}$$

### The Hybrid- $\pi$ Model


The basic equations are

$$i_c = g_m V_{be} + \frac{V_{ce}}{R_o}$$

$$i_b = \frac{V_{be}}{R_\pi}$$

We can draw the model as follows:

6 - 05/19/03

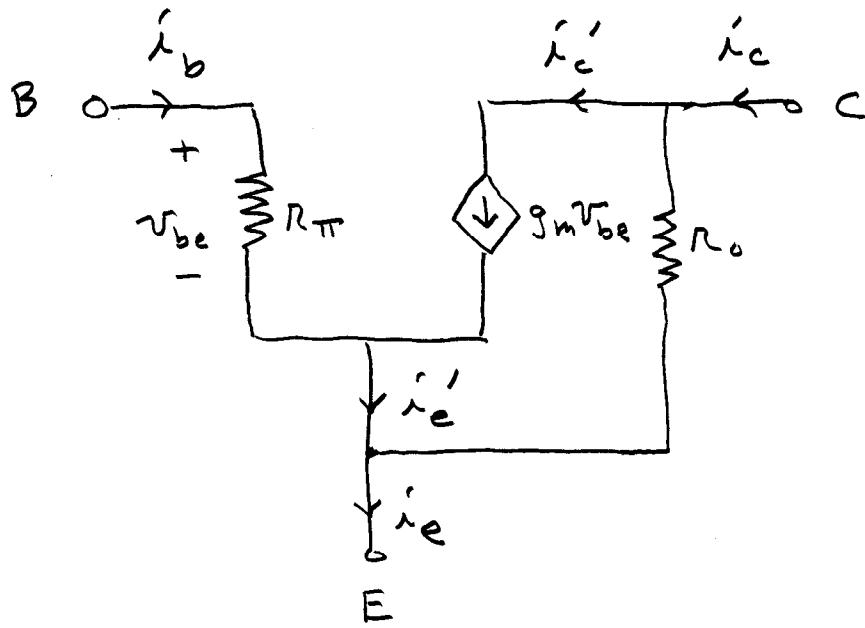

We seek the relationships between  $i'_c$ ,  $i'_b$ , and  $i'_e$ .

$$i'_c = g_m v_{be} = g_m (i_b R_\pi)$$

$$= g_m R_\pi i_b = \frac{I_c}{V_T} \frac{V_T}{I_B} i_b$$

$$= \frac{I_c}{I_B} i_b = \beta i_b$$

$$i'_e = i'_c + i_b = i'_c + \frac{1}{\beta} i'_c$$

$$= i'_c (1 + \frac{1}{\beta}) = i'_c \frac{1 + \beta}{\beta}$$

$$= \frac{i'_c}{\alpha}$$


7-05/19/03

Thus we have

$$i'_c = g_m v_{be} = \beta i'_b = \alpha i'_e$$


If  $R_o = \infty$  (open circuit), the primes can be dropped.

### The Base Spreading Resistance

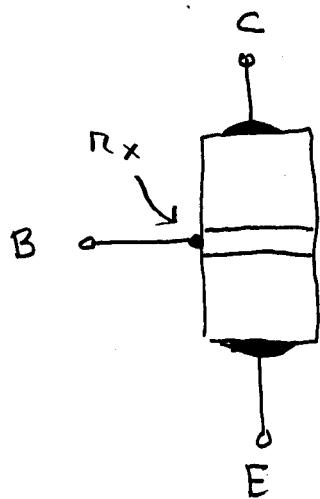

The base region is narrow and its ohmic contact is small. Its resistance is denoted by  $R_x$ .

### Completed Hybrid- $\pi$ Model

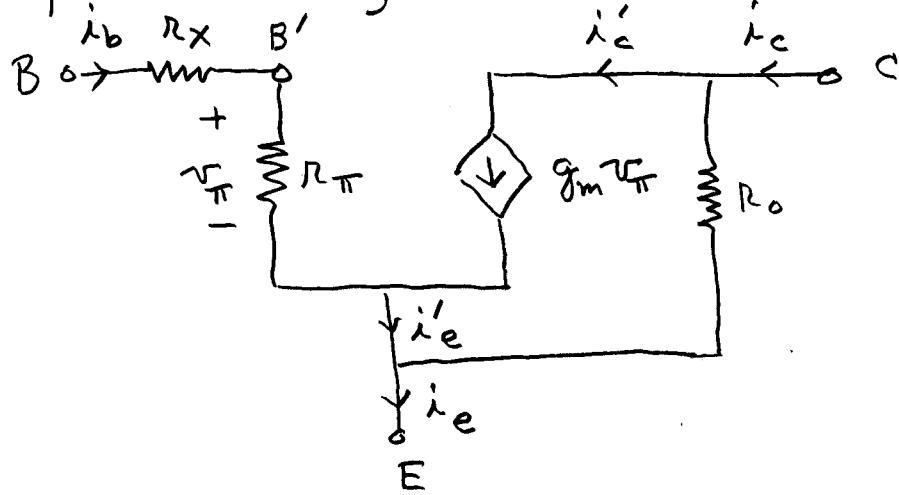


8 - 05/19/03

In this case, we write

$$i'_c = g_m v_{\pi} = \beta i'_b = \alpha i'_e$$

DC Current Relations

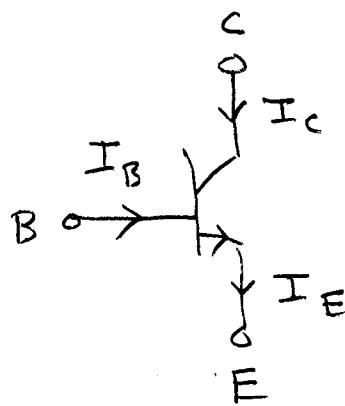

$$I_B = \frac{I_C}{\beta}$$

$$I_E = I_B + I_C$$

$$= I_C \left( \frac{1}{\beta} + 1 \right)$$

$$= I_C \frac{1 + \beta}{\beta}$$

$$= \frac{I_C}{\alpha}$$

$$\Rightarrow I_C = \beta I_B = \alpha I_E$$

$$I_B = I_E - I_C = I_E - \alpha I_E$$

$$= I_E (1 - \alpha) = I_E \left( 1 - \frac{\beta}{1 + \beta} \right)$$

$$= \frac{I_E}{1 + \beta}$$

9 - 05/19/03

## Summary

$$I_C = \beta I_B = \alpha I_E$$

$$I_E = \frac{I_C}{\alpha} = (1 + \beta) I_B$$

$$I_B = \frac{I_C}{\beta} = \frac{I_E}{1 + \beta}$$

$$\alpha = \frac{\beta}{1 + \beta} \quad \beta = \frac{\alpha}{1 - \alpha}$$

## The BJT T Model

The T model replaces  $R_\pi$  through which  $i_b$  flows with  $R_e$  through which  $i'_e$  flows. The voltage  $v_\pi$  must be the same for the two.

$$v_\pi = i_b R_\pi = \frac{i_c''}{\beta} R_\pi = \frac{\alpha i'_e}{\beta} R_\pi$$

$$= i'_e \frac{\alpha}{\beta} R_\pi = i'_e \frac{\alpha}{\beta} \frac{V_T}{I_B} = i'_e \frac{\alpha V_T}{I_C}$$

$$= i'_e \frac{V_T}{I_E}$$


10 - 05/19/03

$$\text{Let } R_E = \frac{V_T}{I_E}$$

$$\Rightarrow V_{\pi} = i'_e R_E$$

The resistor  $R_E$  is called the intrinsic emitter resistance.

The T model is

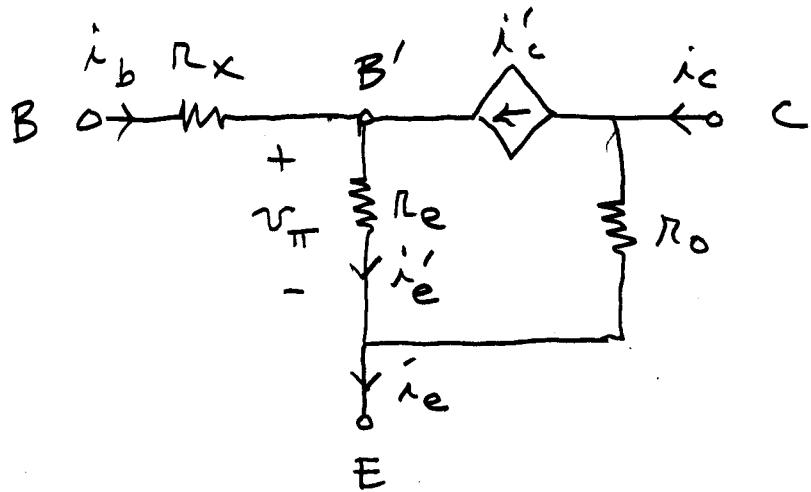

$$i'_c = g_m V_{\pi} = \beta i_b = \alpha i'_e$$

Both the T model and the hybrid- $\pi$  models give identical answers when numbers are substituted into the equations.