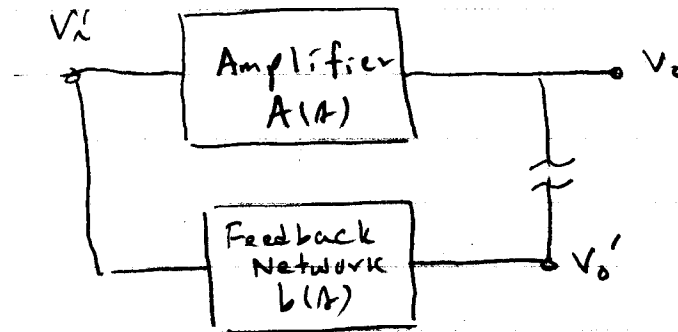


Oscillators



The loop gain is

$$\frac{V_o}{V_o'} = b(s)A(s)$$

For $A = j\omega$, if there is an ω for which


$$b(j\omega)A(j\omega) = 1 \angle 0^\circ$$

the circuit will oscillate at that frequency if the loop is closed.

11/29/99

(2)

The Wein Bridge Oscillator

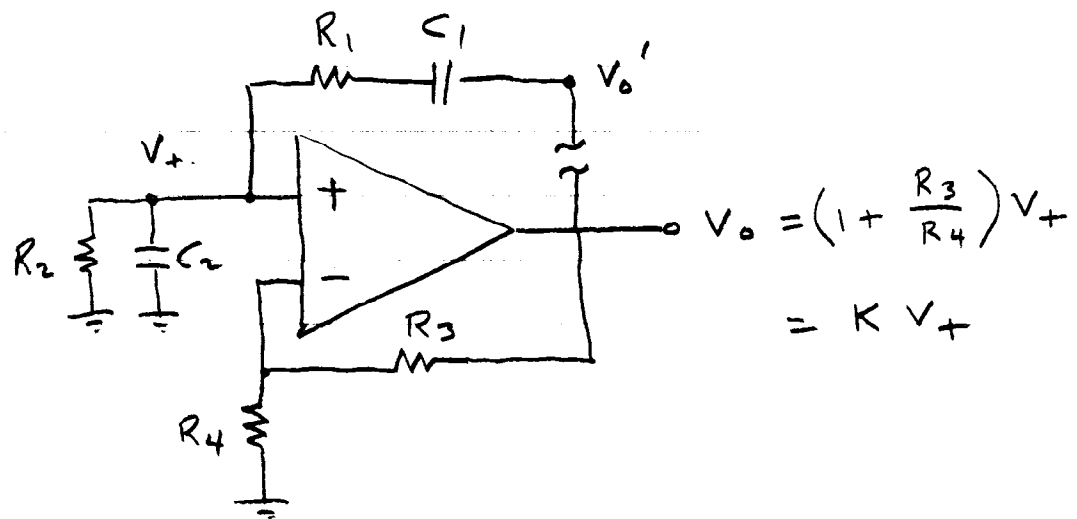

$$\begin{aligned}
 V_+ &= V_0' \frac{R_2 \parallel \frac{1}{C_2 s}}{R_1 + \frac{1}{C_1 s} + R_2 \parallel \frac{1}{C_2 s}} \\
 &= V_0' \frac{\frac{R_2 \times \frac{1}{C_2 s}}{R_2 + \frac{1}{C_2 s}}}{R_1 + \frac{1}{C_1 s} + \frac{R_2 \times \frac{1}{C_2 s}}{R_2 + \frac{1}{C_2 s}}} \\
 &= V_0' \frac{\frac{R_2}{1 + R_2 C_2 s}}{\frac{1 + R_1 C_1 s}{C_1 s} + \frac{R_2}{1 + R_2 C_2 s}} \\
 &= V_0' \frac{R_2 C_1 s}{(1 + R_1 C_1 s)(1 + R_2 C_2 s) + R_2 C_1 s}
 \end{aligned}$$

11/29/99

(3)

$$\Rightarrow V^+ = V_o' \frac{R_2 C_1 A}{R_1 R_2 C_1 C_2 A^2 + (R_1 C_1 + R_2 C_1 + R_2 C_2) A + 1}$$

$$\Rightarrow \frac{V_o}{V_o'} = K \frac{R_2 C_1 A}{R_1 R_2 C_1 C_2 A^2 + (R_1 C_1 + R_2 C_1 + R_2 C_2) A + 1}$$

Let $A = j\omega$

$$\Rightarrow \frac{V_o}{V_o'} = K \frac{j\omega R_2 C_1}{1 - \omega^2 R_1 R_2 C_1 C_2 + j\omega (R_1 C_1 + R_2 C_1 + R_2 C_2)}$$

For $\omega = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$

$$\frac{V_o}{V_o'} = K \frac{R_2 C_1}{R_1 C_1 + R_2 C_1 + R_2 C_2} \angle 0^\circ$$

Adjust R_3 & R_4 such that

$$K = 1 + \frac{R_3}{R_4} = \frac{R_1 C_1 + R_2 C_1 + R_2 C_2}{R_2 C_1}$$

$$= 1 + \frac{R_1}{R_2} + \frac{C_2}{C_1}$$

$$\Rightarrow \frac{R_3}{R_4} = \frac{R_1}{R_2} + \frac{C_2}{C_1}$$

11/29/99


(4)

In this case

$$\frac{V_o}{V_o'} = 1 \angle 0^\circ$$


and the circuit will oscillate at the freq
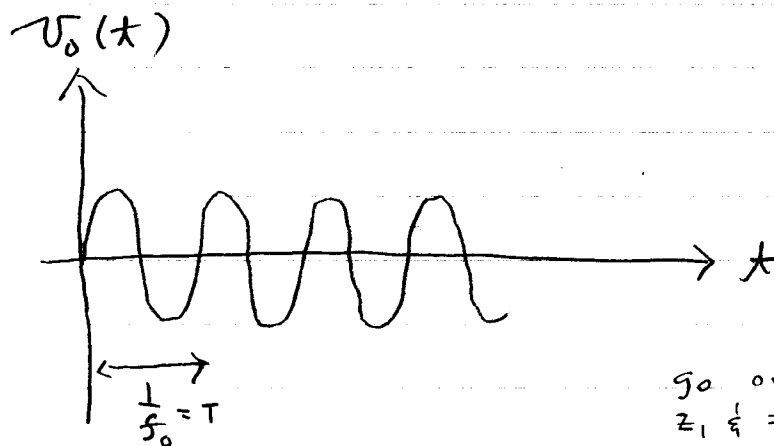
$$f_0 = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$



go over ckt with Z_1 & Z_2 reversed.

Phase Shift Oscillator

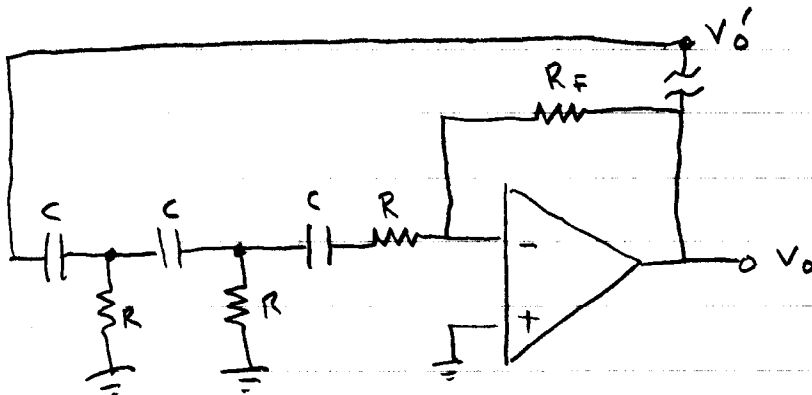

11/29/99

(5)

It can be shown that

$$\frac{V_o}{V_o'} = - \frac{R_F}{R} \frac{(RC\omega)^3}{(RC\omega)^3 + 6(RC\omega)^2 + 5(RC\omega) + 1}$$

Let $A = j\omega$

$$\frac{V_o}{V_o'} = - \frac{R_F}{R} \frac{-j(\omega RC)^3}{1 - 6(\omega RC)^2 + j(5\omega RC - (\omega RC)^3)}$$

Let $\omega = \omega_0 = \frac{1}{RC\sqrt{6}}$

$$\begin{aligned} \frac{V_o}{V_o'} &= + \frac{R_F}{R} \frac{(\omega_0 RC)^3}{5\omega_0 RC - (\omega_0 RC)^3} \\ &= + \frac{R_F}{R} \frac{1}{\frac{5}{(\omega_0 RC)^2} - 1} \end{aligned}$$

The circuit will oscillate at ω_0 if

$$\frac{R_F}{R} \frac{1}{\frac{5}{(\omega_0 RC)^2} - 1} = 1$$

11/29/99

④

$$\Rightarrow \frac{R_F}{R} = \frac{5}{(\omega_0 RC)^2} - 1$$

$$= 30 - 1$$

$$= 29$$


$$\Rightarrow R_F = 29R$$

12/2/99

①

Non-Linear Circuits

The Log Converter

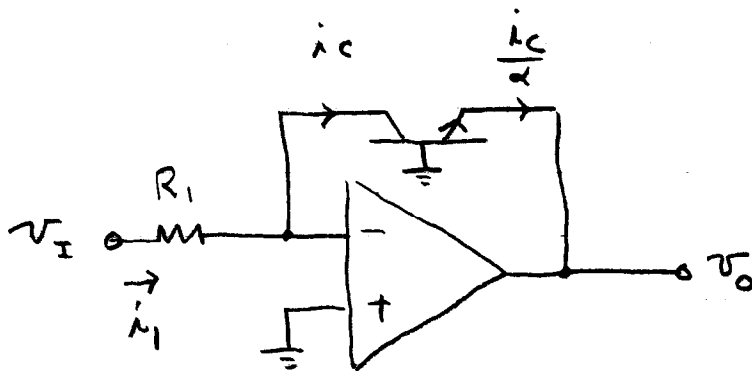

$$i_c = i_1 = \frac{v_I}{R_1}$$

$$\text{But } i_c = I_s e^{v_{BE}/V_T} = I_s e^{-v_O/V_T}$$

$$\Rightarrow \frac{v_I}{R_1} = I_s e^{-v_O/V_T}$$


$$\Rightarrow v_O = -V_T \ln\left(\frac{v_I}{I_s R_1}\right)$$

12/2/99


②

The Precision Rectifier

First, let us look at a diode rectifier

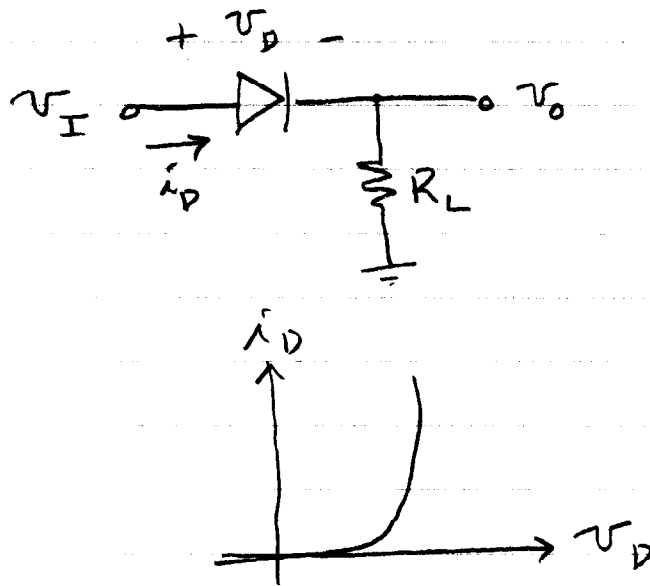


Let v_I be a triangle wave

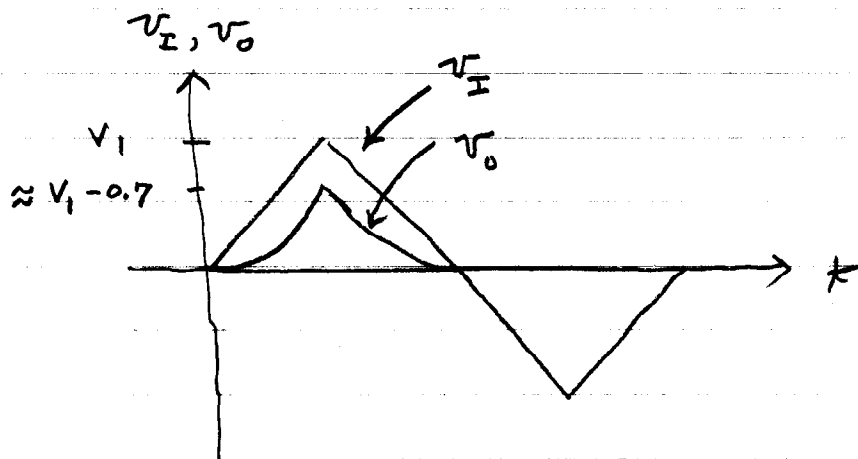

12/2/99

③

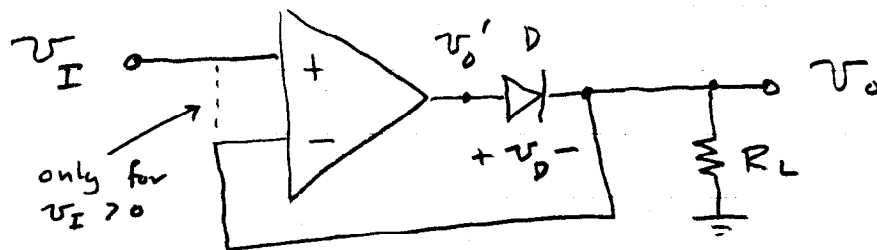For a better rectifier, we can use an op amp circuit as follows



$$v_I > 0 \Rightarrow v_o' > 0 \Rightarrow D \text{ on}$$

$\Rightarrow v_o = v_I$ because the op amp has feedback

$$v_o' = v_o + v_D$$

$$v_I < 0 \Rightarrow v_o' < 0 \Rightarrow D \text{ off}$$

the op-amp loses feedback and v_o' drops to




$$v_o' = -V_{SAT} \text{ (the neg. sat. volt.)}$$

$$v_o = 0 \text{ because } D \text{ is off}$$


12/2/99

④

Let v_I be a triangle wave

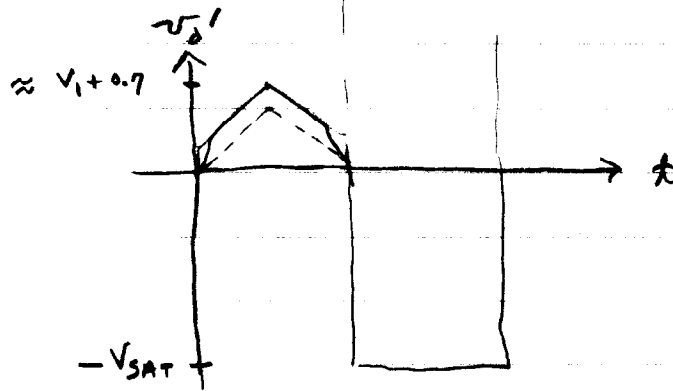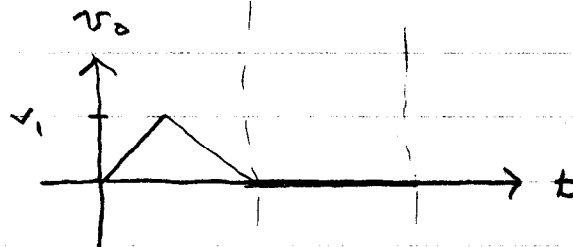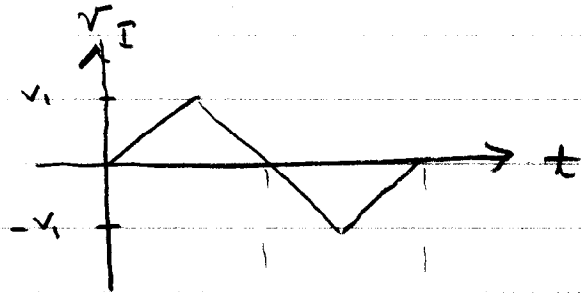

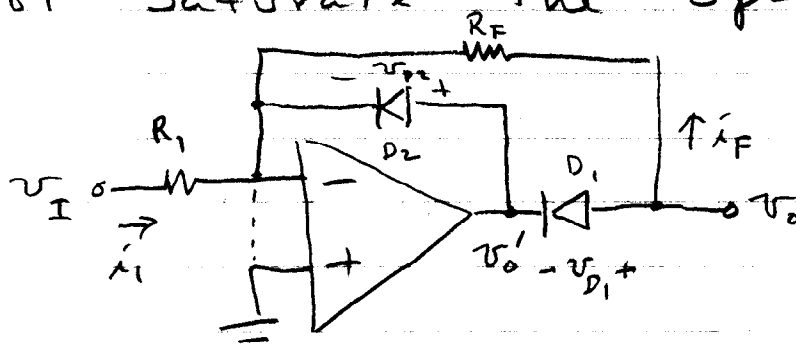An inverting rectifier which does not saturate the op-amp



12/2/99

⑤

$$v_I > 0 \Rightarrow v_o' < 0 \Rightarrow D_1 \text{ on } D_2 \text{ off}$$

$$\hat{i}_1 = \frac{v_I}{R_1} \quad \hat{i}_F = \frac{v_o}{R_F}$$


$$\hat{i}_1 + \hat{i}_F = 0 \Rightarrow \frac{v_I}{R_1} + \frac{v_o}{R_F} = 0 \Rightarrow v_o = -\frac{R_F}{R_1} v_I$$

$$v_o' = v_o - v_{D1} < v_o$$

$$v_I < 0 \Rightarrow v_o' > 0 \Rightarrow D_1 \text{ off } D_2 \text{ on}$$


$$\Rightarrow v_o = 0$$

$$v_o' = +v_{D2} > 0$$

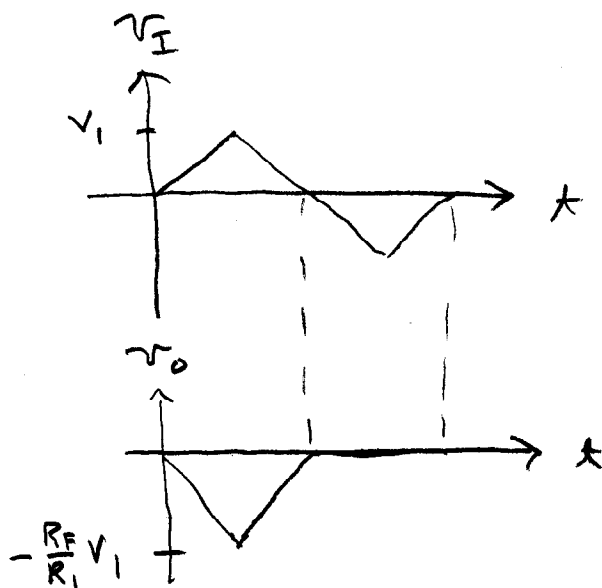


12/2/99

(6)

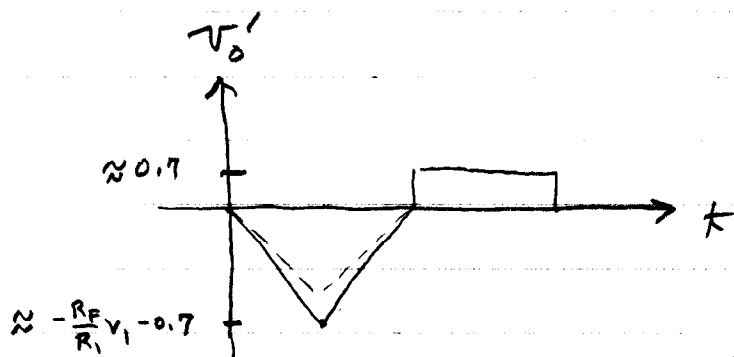


A Full Wave Rectifier

Basic Scheme

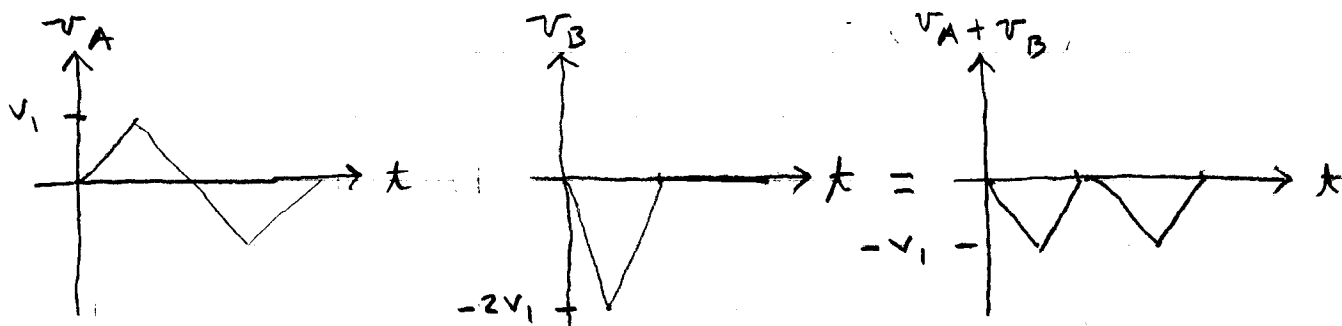

$-(v_A + v_B)$

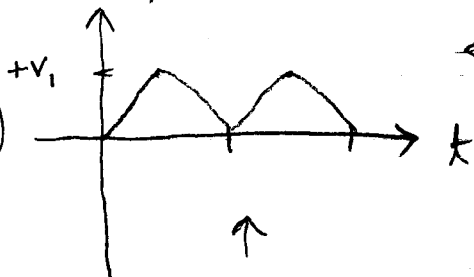


↑
requires
inv.
Summer

2 operations can be done with an inverting summer

12/2/99

⑦

Inverting Summer

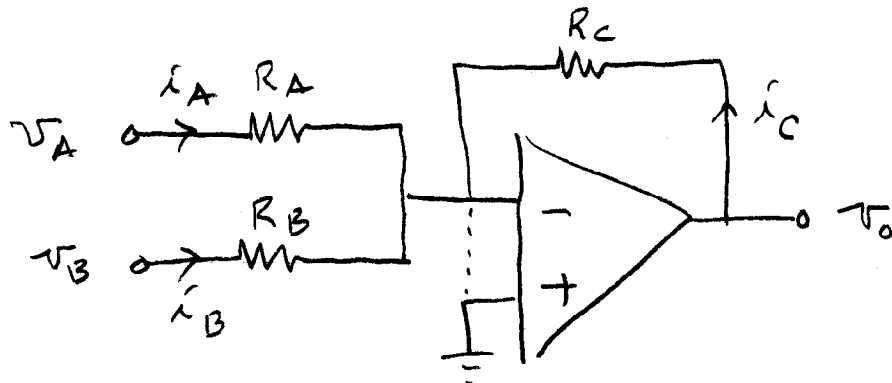


$$\hat{I}_A + \hat{I}_B + \hat{I}_C = 0$$

$$\Rightarrow \frac{V_A}{R_A} + \frac{V_B}{R_B} + \frac{V_O}{R_C} = 0$$

$$\Rightarrow V_O = -\frac{R_C}{R_A} V_A - \frac{R_C}{R_B} V_B$$

Let $R_A = R_B = R_C = R_2$

Half Wave Rectifier



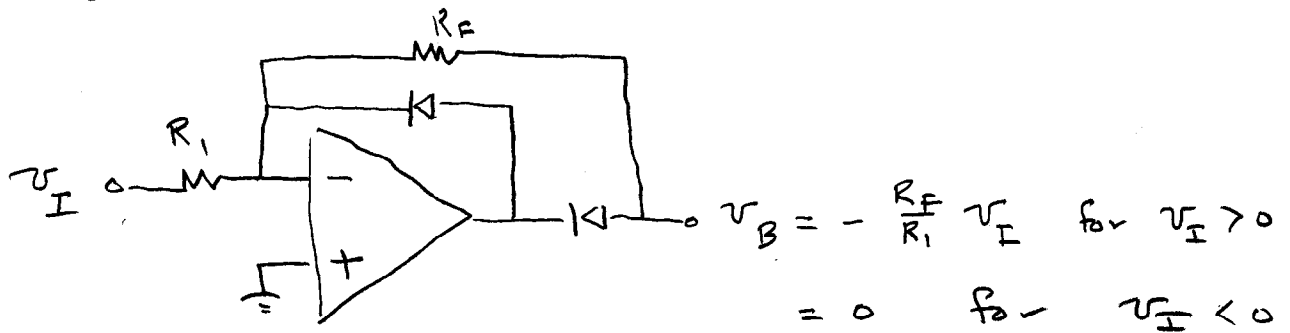


$$\begin{aligned} \text{Let } R_F &= 2R_1 \\ \Rightarrow V_B &= -2V_I \text{ for } V_I > 0 \\ &= 0 \text{ for } V_I < 0 \end{aligned}$$

12/2/99


⑧

Final Circuit

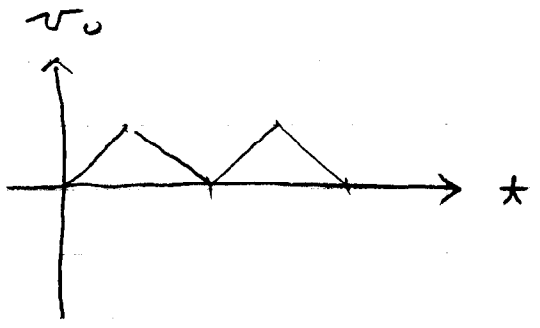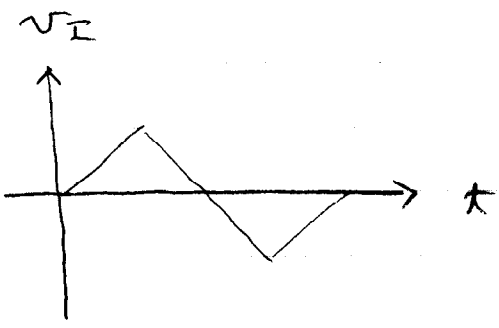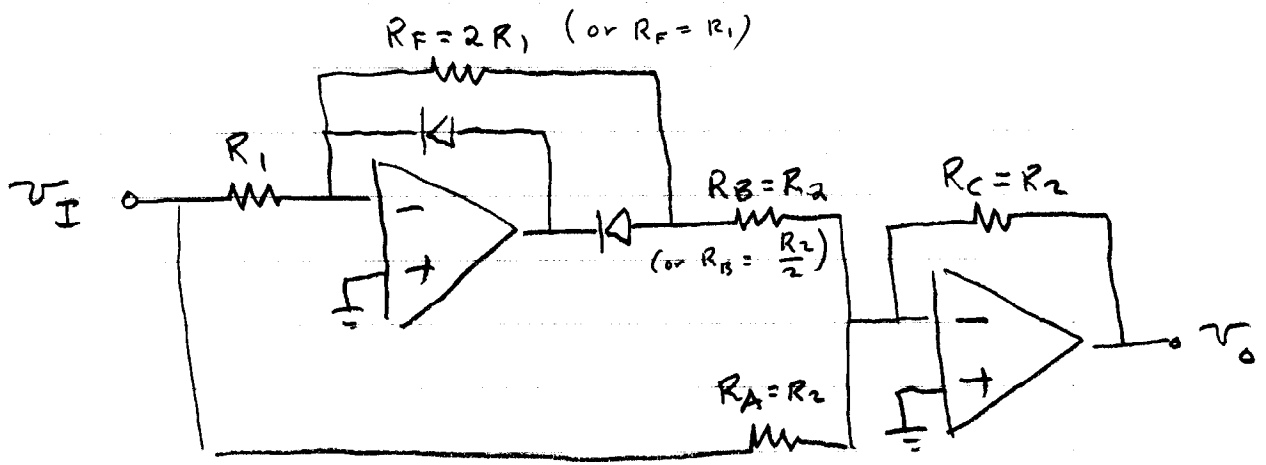

could also make $R_F = R_1$ & $R_B = \frac{R_2}{2}$ for same output - is preferable to minimize clipping

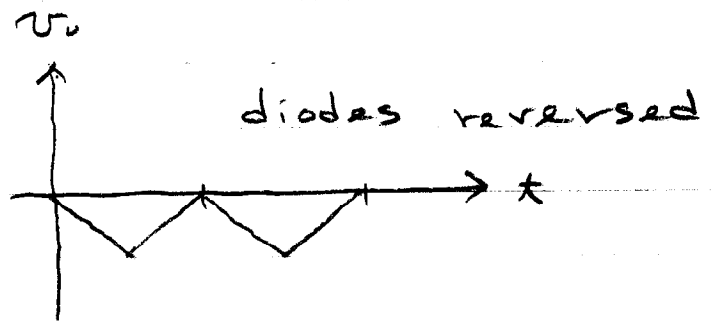
If the diodes are reversed, V_0 is inverted



12/5/99


①

Peak Detector

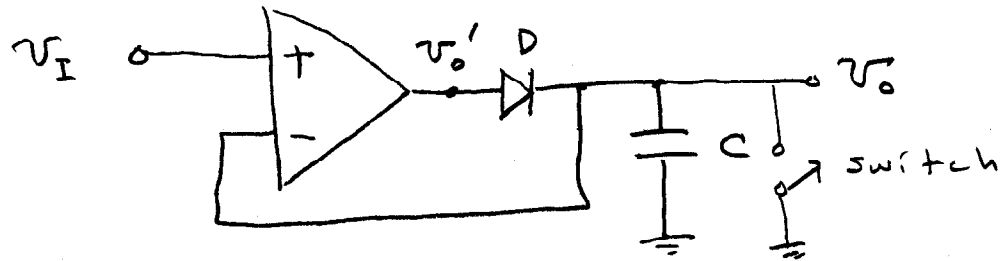

$v_I < v_o \Rightarrow D$ OFF, the op amp loses feedback $\Rightarrow v_o' = -V_{SAT}$.
 v_o cannot change because the capacitor current is zero.

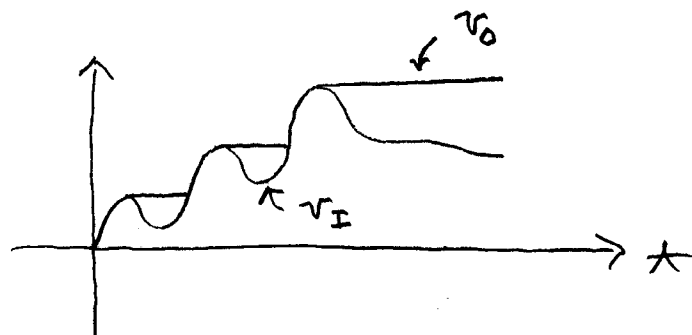$v_I > v_o \Rightarrow D$ ON, the op amp has feedback. The capacitor charges until $v_o = v_I$.





The switch can be closed to reset the circuit. Often, the switch is a FET.


12/5/99

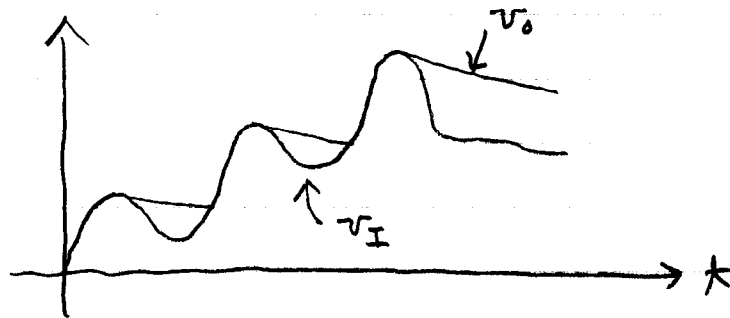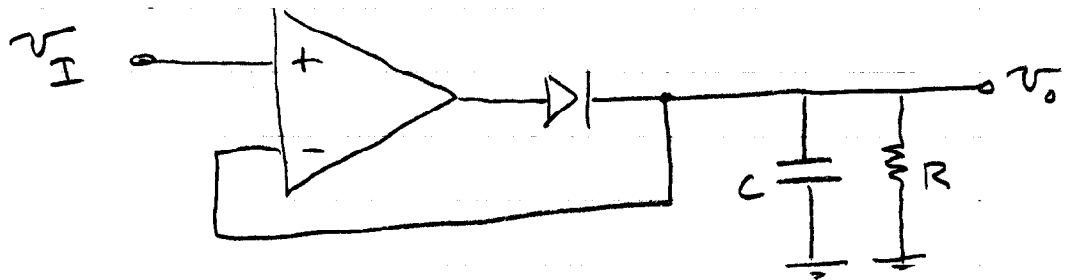(2)

In some applications, the switch is replaced with a resistor, e.g. in a VU meter.



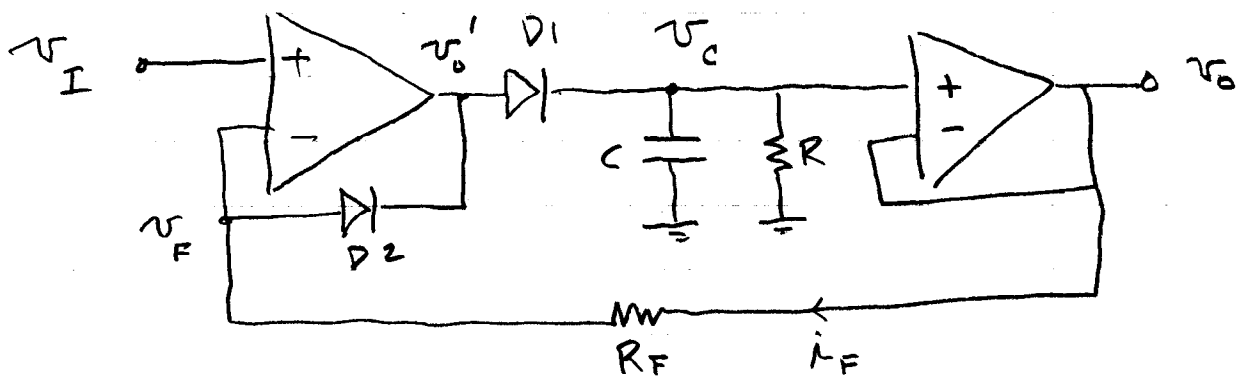The following circuit is better because the op amp does not saturate



12/5/99

③

$v_I > v_O \Rightarrow v_O'$ goes positive
 $\Rightarrow D_1$ ON, D_2 OFF
 $\Rightarrow i_F = 0 \Rightarrow$ drop across R_F is zero
 $\Rightarrow v_F = v_O$


the op amp has feedback
 $\Rightarrow v_F = v_I \Rightarrow v_O = v_I$

But $v_O = v_C \Rightarrow$ the capacitor
 charges up to v_I

$v_I < 0 \Rightarrow v_O'$ goes negative
 $\Rightarrow D_1$ OFF, D_2 ON
 $\Rightarrow v_O' = v_F - v_{D2}$

The op amp has feedback

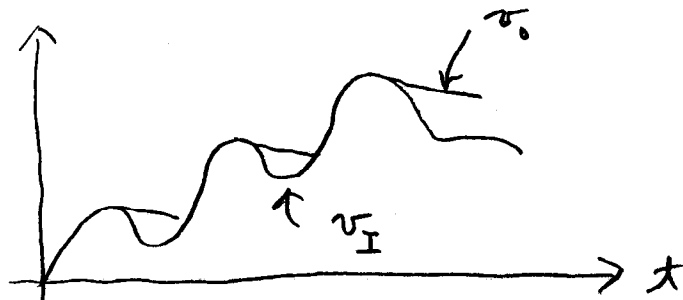
$\Rightarrow v_F = v_I \Rightarrow v_O' = v_I - v_{D2}$
 $i_F = \frac{v_O - v_I}{R_F}$ (Note R_F cannot be 0)



12/5/99

(4)

A Guitar "Fuzzy Box" Clipper

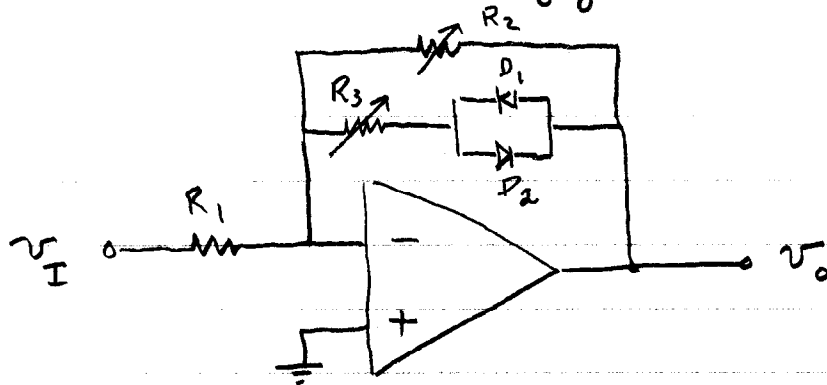

If $R_3 = \infty$, the circuit is an inverting amplifier with gain

$$\frac{v_O}{v_I} = -\frac{R_2}{R_1}$$

If $R_3 = 0$, the output is limited to the value $\pm v_D \approx \pm 0.7$ V.

