

EE4086 Quiz 2


MARCH 3, 1997

Professor Leach

Name _____

Instructions. Print your name in the space above and on all quiz work sheets. Place a box around all answers. Write the word “over” if you continue your work on another page.

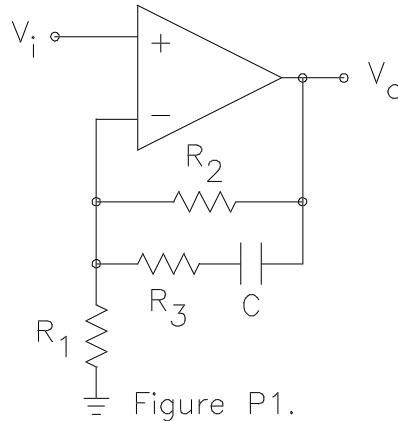1. The op-amp in Fig. P1 is ideal. It is given that $R_1 = 1 \text{ k}\Omega$, $R_2 = 49 \text{ k}\Omega$, $R_3 = 4.36 \text{ k}\Omega$, and $C = 5.97 \text{ nF}$.




- (a) Solve for the transfer function for V_o/V_i . Put it into the form

$$\frac{V_o}{V_i} = K \frac{1 + \tau_2 s}{1 + \tau_1 s}$$

where you must specify K , τ_1 , and τ_2 .

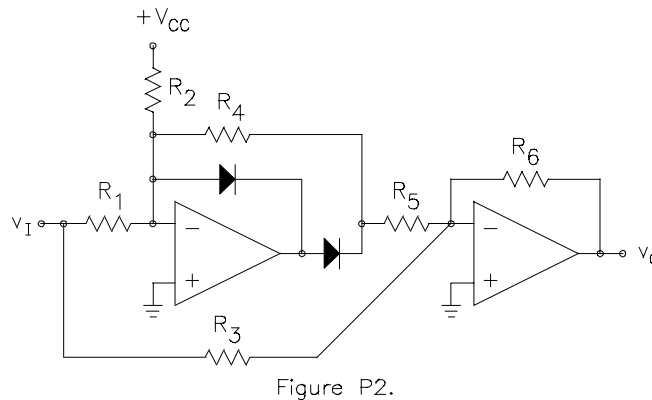- (b) Sketch the Bode magnitude plot for V_o/V_i . Label the asymptotic gains and the break frequencies in both rad/s and in Hz.
2. The op-amp in Fig. P2 is ideal. It is given that $R_1 = 10 \text{ k}\Omega$, $R_2 = 300 \text{ k}\Omega$, $R_3 = 10 \text{ k}\Omega$, $R_4 = 20 \text{ k}\Omega$, $R_5 = 10 \text{ k}\Omega$, $R_6 = 20 \text{ k}\Omega$, and $V_{CC} = 15 \text{ V}$.



- (a) Solve for v_o/v_I for $v_I/R_1 + V_{CC}/R_2 > 0$.

- (b) Solve for v_O/v_I for $v_I/R_1 + V_{CC}/R_2 < 0$.
- (c) Sketch the plot of v_O versus v_I .
- (d) For $v_I = 4\sin\omega t$, sketch and label the waveform for $v_O(t)$.
3. The transfer function for V_o in the circuit of Fig. P3 is given by

$$V_o = \frac{A_o}{1 + s/\omega_o} (V_+ - V_-)$$

where $A_o = 10^5$ and $\omega_o = 20\pi$. It is given that $R_1 = 1\text{ k}\Omega$, $R_2 = 10\text{ k}\Omega$, and $R_F = 20\text{ k}\Omega$.

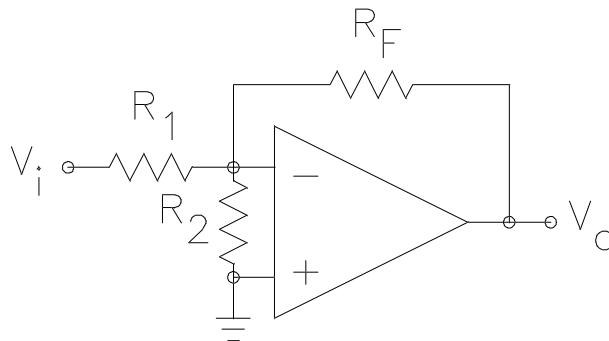


Figure P3.

- (a) Use superposition of V_i and V_o to write the equation for V_- . Use this equation and the above equation for V_o to solve for the transfer function for V_o/V_i .
- (b) Sketch the Bode magnitude plot for V_o/V_i . Label the asymptotic gain and the break frequency in rad/s and in Hz.
- (c) What is the gain-bandwidth product of the amplifier?