

ECE 6416 Quiz 1
September 28, 2005

Professor Leach

Name _____


Instructions. Print your name in the space above and at the top of all other pages in your quiz. Place a box around each answer. Express each numerical answer as a decimal number. Staple your formula sheet to the back of the quiz. Numerical values are $4kT_0 = 1.6 \times 10^{-20}$ J and $q = 1.6 \times 10^{-19}$ C. **Honor Code:** *I have neither given nor received help on this quiz.*
Initials _____

Formulas:

$$v_n^2 = 4kT \operatorname{Re}(Z) \Delta f \quad i_n^2 = 4kT \operatorname{Re}(Y) \Delta f \quad \omega = 2\pi f \quad j = \sqrt{-1}$$

$$Z_C = \frac{1}{j\omega C} \quad Z_L = j\omega L \quad \overline{V_n V_n^*} = v_n^2 \quad \overline{I_n I_n^*} = i_n^2 \quad \overline{V_n I_n^*} = \gamma v_n i_n$$

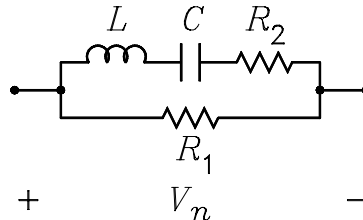1. (a) Use the Thévenin noise model for each resistor to solve for the phasor noise voltage V_n across the circuit shown. Express V_n as a function of V_{t1} and V_{t2} .




$$V_n = V_{t1} \frac{R_2 + j\omega L + 1/j\omega C}{R_1 + R_2 + j\omega L + 1/j\omega C} + V_{t2} \frac{R_1}{R_1 + R_2 + j\omega L + 1/j\omega C}$$

- (b) Use the expression for V_n to obtain the mean-square noise voltage v_n^2 in the band Δf .

$$v_n^2 = 4kT \Delta f \frac{R_1 [R_2^2 + (\omega L - 1/\omega C)^2] + R_1^2 R_2}{(R_1 + R_2)^2 + (\omega L - 1/\omega C)^2}$$

- (c) For this problem, do you think it is simpler to use the Thévenin noise model of each resistor or the generalized Nyquist formula to solve for v_n^2 ? Explain your logic. It is more difficult to determine $\operatorname{Re}(Z)$ than $|Z|^2$ for this problem.

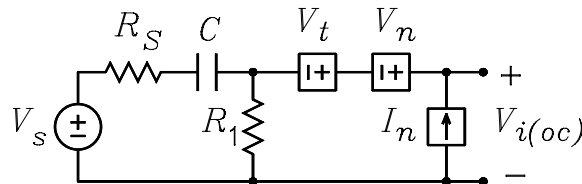2. The figure shows the circuit for calculating the open-circuit input voltage to a particular amplifier. The sources V_n and I_n , respectively, are the amplifier input noise voltage and noise current. The complex correlation coefficient between these is γ . The source V_t represents the thermal noise generated by the circuit to the left of V_t .



(a) Solve for $V_{i(oc)}$ as a function of V_s , V_t , V_n , and I_n .

$$V_{i(oc)} = V_s \frac{R_1}{R_S + R_1 + 1/j\omega C} + V_t + V_n + I_n R_1 \parallel \left(R_S + \frac{1}{j\omega C} \right)$$

(b) Write the equation for $V_{i(oc)}$ in the form $V_{i(oc)} = A_v (V_s + V_{ni})$ and obtain the phasor equation for the noise equivalent input voltage V_{ni} in series with V_s that generates the same noise as all noise sources in the circuit.

$$V_{i(oc)} = A_v \left[V_s + (V_t + V_n) \left(1 + \frac{R_S}{R_1} + \frac{1}{j\omega R_1 C} \right) + I_n \left(R_S + \frac{1}{j\omega C} \right) \right]$$

$$V_{ni} = (V_t + V_n) \left(1 + \frac{R_S}{R_1} + \frac{1}{j\omega R_1 C} \right) + I_n \left(R_S + \frac{1}{j\omega C} \right)$$

(c) Solve for the expression for the mean-square value of V_t .

$$Z_{eq} = R_1 \parallel \left(R_S + \frac{1}{j\omega C} \right) = R_1 \frac{1 + j\omega R_S C}{1 + j\omega (R_S + R_1) C}$$

$$v_t^2 = 4kT \operatorname{Re}(Z_{eq}) \Delta f = 4kT R_1 \frac{1 + \omega^2 R_S (R_S + R_1) C^2}{1 + [\omega (R_S + R_1) C]^2} \Delta f$$

(d) Solve for the expression for the mean-square value of V_{ni} .

$$\begin{aligned} v_{ni}^2 &= (v_t^2 + v_n^2) \left[\left(1 + \frac{R_S}{R_1} \right)^2 + \frac{1}{(\omega R_1 C)^2} \right] + i_n^2 \left(R_S^2 + \frac{1}{(\omega C)^2} \right) \\ &\quad + 2v_n i_n \operatorname{Re} \left[\gamma \left(1 + \frac{R_S}{R_1} + \frac{1}{j\omega R_1 C} \right) \left(R_S - \frac{1}{j\omega C} \right) \right] \end{aligned}$$