

## ECE 6416 Quiz 2


November 9, 2005

Professor Leach

Name \_\_\_\_\_

**Instructions.** Print your name in the space above and at the top of all other pages in your quiz. Place a box around each answer. Express each numerical answer as a decimal number. Staple your formula sheet to the back of the quiz. Do not place the staple over any of your work or over a problem number. Numerical values are  $4kT_0 = 1.6 \times 10^{-20}$  J and  $q = 1.6 \times 10^{-19}$  C. **Honor Code:** *I have neither given nor received help on this quiz.* Initials \_\_\_\_\_

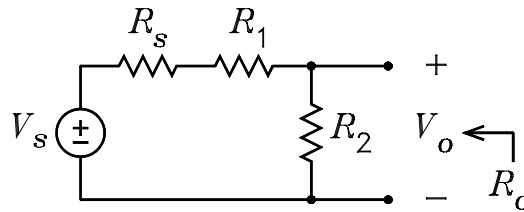1. (a) The figure shows a source ( $V_s$  and  $R_s$ ) connected to an attenuator ( $R_1$  and  $R_2$ ). It is desired to have  $V_o = kV_s$  and  $R_o = R_s$ . What are the equations for  $R_1$  and  $R_2$  as functions of  $R_s$  and  $k$ ?  
 (b) When the source is connected to an amplifier having the noise parameters  $v_n^2$ ,  $i_n^2$ , and  $\gamma$ , the noise factor is  $F_1$ . With the attenuator between the source and the amplifier, show that the noise factor is  $F_2 = k^2 F_1$ .



$$\frac{R_2}{R_s + R_1 + R_2} = k \quad R_2 \parallel (R_s + R_1) = R_s \implies k(R_s + R_1) = R_s \implies R_1 = \frac{1-k}{k} R_s$$

$$R_2 = k \left( R_s + \frac{1-k}{k} R_s + R_2 \right) \implies R_2 = (1-k) R_s$$

$$V_{o(oc)} = kV_s + V_{ni} = k \left( V_s + \frac{V_{ni}}{k} \right) \implies v_{ni}^2 = k^2 v_n^2 \implies F_2 = k^2 F_1$$

2. (a) The figure shows the T model of a BJT common-emitter amplifier with the collector and emitter connected to signal ground. Assuming that the flicker noise can be neglected, redraw the figure with all noise sources added.  
 (b) Solve for the Thévenin equivalent circuit seen looking out of the base.  
 Treating  $r_x$  as an external resistor, we can write

$$V_{tb} = V_s + V_{ts} + V_{tx} + I_{shb} (R_s + r_x) \quad R_{tb} = R_s + r_x$$

- (c) Use the equivalent circuit found in part (b) to solve for  $I'_e$  as a function of all appropriate sources.

$$I'_e = \frac{V_{tb}}{R_{tb} + r_e} + \alpha I'_e \frac{R_{tb}}{R_{tb} + r_e} \implies I'_e = \frac{V_{tb}}{(1-\alpha) R_{tb} + r_e}$$

(d) Making use of the equation for  $I'_e$ , solve for  $I_{c(sc)}$ .

$$I_{c(sc)} = \alpha I'_e + I_{shc} = \alpha \frac{V_s + V_{ts} + V_{tx} + I_{shb}(R_s + r_x)}{(1 - \alpha)R_{tb} + r_e} + I_{shc}$$

(e) From the equation for  $I_{c(sc)}$ , solve for the equation for  $V_{ni}$  in series with  $V_s$ . You do not have to solve for the mean-square value of  $V_{ni}$ .

$$I_{c(sc)} = \frac{\alpha}{(1 - \alpha)R_{tb} + r_e} \left[ V_s + V_{ts} + V_{tx} + I_{shb}(R_s + r_x) + I_{shc} \frac{(1 - \alpha)R_{tb} + r_e}{\alpha} \right]$$

$$\implies V_{ni} = V_{ts} + V_{tx} + I_{shb}(R_s + r_x) + I_{shc} \frac{(1 - \alpha)R_{tb} + r_e}{\alpha}$$

