

ECE 6416 Quiz 1

October 6, 2008


Professor Leach

Name _____

Instructions. Print your name in the space above and at the top of all other pages in your quiz. Place a box around each answer. Express each numerical answer as a decimal number. Numerical values are $4kT_0 = 1.6 \times 10^{-20}$ J and $q = 1.6 \times 10^{-19}$ C. **Honor Code:** *I have neither given nor received help on this quiz.* Initials _____

1. The circuit shows a series resistor R and ideal inductor L . You are given that

$$\int_0^\infty dx / (1 + x^2) = \pi/2$$

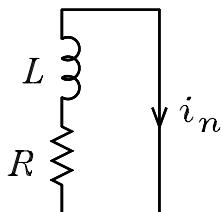

- (a) Using the Thévenin form for the thermal noise generated by R , solve for the mean-square value of the short-circuit noise current i_n^2 over the frequency band from $f = 0$ to $f = \infty$.

$$\begin{aligned} i_n^2 &= \int_0^\infty \frac{v_t^2}{|R + j2\pi fL|^2} = \int_0^\infty \frac{4kTRdf}{R^2 + (2\pi fL)^2} = \frac{4kT}{R} \int_0^\infty \frac{df}{1 + \left(\frac{2\pi fL}{R}\right)^2} \\ &= \frac{2kT}{\pi L} \int_0^\infty \frac{dx}{1 + x^2} = \frac{kT}{L} \end{aligned}$$


- (b) Repeat part (a) using the generalized admittance Nyquist theorem. Show that the same result is obtained.

$$\begin{aligned} i_n^2 &= \int_0^\infty 4kT \operatorname{Re} \left(\frac{1}{R + j2\pi fL} \right) df = 4kT \int_0^\infty \frac{R}{R^2 + (2\pi fL)^2} df \\ &= \frac{4kT}{R} \int_0^\infty \frac{df}{1 + \left(\frac{2\pi L}{R} f\right)^2} = \frac{kT}{L} \end{aligned}$$

2. The op amp shown is ideal. It is given that $\Delta f = 10$ kHz, $R_S = 2$ k Ω , $R_1 = 1$ k Ω , $R_2 = 5.1$ k Ω , $R_F = 47$ k Ω , $v_n = 2$ nV/ $\sqrt{\text{Hz}}$, and $i_{n1} = i_{n2} = 1.5$ pA/ $\sqrt{\text{Hz}}$. The op-amp noise sources are shown. The thermal noise sources of the resistors must be added. Assume that all noise sources are uncorrelated.

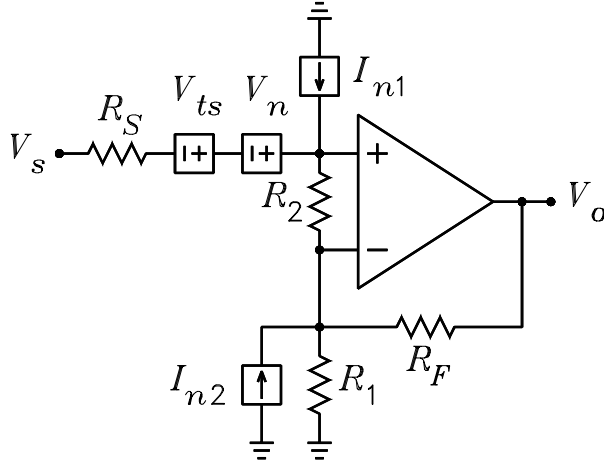- (a) Using the Norton noise model for R_2 , add the thermal noise sources and solve for the equation for V_o as a function of V_s and all noise sources. Note that R_2 does not affect the gain.

$$\begin{aligned} V_s + V_{ts} + V_n + (I_{n1} + I_{t2}) R_S &= \frac{R_1}{R_F + R_1} V_o + V_{teq} + (I_{n2} - I_{t2}) R_1 \parallel R_F \\ V_o &= \left(1 + \frac{R_F}{R_1} \right) [V_o + V_{ts} + V_n + I_{n1} R_S - I_{n2} R_1 \parallel R_F - V_{teq} + I_{t2} (R_S + R_1 \parallel R_F)] \end{aligned}$$



(b) Put the equation obtained in part (a) into the form $V_o = K (V_s + V_{ni})$ and give the symbolic equations for K and V_{ni} .

$$K = 1 + \frac{R_F}{R_1} \quad V_{ni} = V_{ts} + V_n + I_{n1}R_S - I_{n2}R_1 \parallel R_F - V_{teq} + I_{t2}(R_S + R_1 \parallel R_F)$$

(c) Over the band $\Delta f = 10$ kHz, solve for the numerical values of v_{ni} , F , and NF .

$$v_{ni} = \sqrt{\left[4kTR_S + v_n^2 + i_{n1}^2 R_S^2 + i_{n2}^2 (R_1 \parallel R_F)^2 + 4kTR_1 \parallel R_F + \frac{4kT}{R_2} (R_S + R_1 \parallel R_F)^2 \right] \Delta f}$$

$$= 9.522 \times 10^{-7} \text{ V}$$

$$F = \frac{v_{ni}^2}{4kTR_S \Delta f} = 2.833 \quad NF = 10 \log(F) = 4.523 \text{ dB}$$

(d) If V_{ni} is written $V_{ni} = V_{ts} + V'_n + I'_n R_S$, solve for the symbolic equations for V'_n , I'_n , and $\gamma' = \frac{V'_n I'_n}{v'_n i'_n}$.

$$V'_n = V_n - I_{n2}R_1 \parallel R_F - V_{teq} + I_{t2}R_1 \parallel R_F$$

$$I'_n = I_{n1} + I_{t2} \quad \gamma = \frac{1}{v'_n i'_n} i_{t2}^2 R_1 \parallel R_F$$

(e) Over the band $\Delta f = 10$ kHz, solve for the numerical values of v'_n , i'_n , and γ' .

$$v'_n = \sqrt{\left[v_n^2 + 4kT (R_1 \parallel R_F) + \left(\frac{4kT}{R_2} + i_{n2}^2 \right) (R_1 \parallel R_F)^2 \right] \Delta f} = 4.983 \times 10^{-7} \text{ V}$$

$$i'_n = \sqrt{\left(i_{n1}^2 + \frac{4kT}{R_2} \right) \Delta f} = 2.2321 \times 10^{-10} \text{ A} \quad \gamma = \frac{1}{v'_n i'_n} \frac{4kT \Delta f}{R_2} (R_1 \parallel R_F) = 0.266$$