

Frequency Response of Hysteretic Comparators in Switching Converters

Dongwon Kwon and Gabriel A. Rincón-Mora
Georgia Tech Analog, Power, and Energy IC Research

March 18, 2010

Abstract

Hysteretic switching dc-dc converters are popular because they are (i) relatively simple (i.e., self-oscillating and self-compensating), (ii) fast (i.e., able to respond within one switching cycle: $f_{\text{odB}} = f_{\text{SW}}$), and (iii) robust (i.e., reliably stable). Although the time-domain operation of a hysteretic comparator can at times be intuitive, its ac transfer response in a switching converter (i.e., gain and phase) is not because linearizing what is already an inherently nonlinear circuit is difficult. This presentation illustrates how to derive a *describing* (rather than *transfer*) *function* that conveys more ac insight and shows how the oscillator circuit ensures there is just enough phase shift across the feedback loop to sustain oscillations (i.e., reach 180° of phase shift at $f_{\text{odB}} = f_{\text{SW}}$).

Summary

- Hysteretic switching converter \equiv **Oscillator** (i.e., $f_{SW} = f_{0dB} = f_{180\circ}$);
- AC **Response** \equiv **Large Signal** (i.e., loop processes f_{SW} signal);
- **LC eliminates higher-than- f_{SW} frequencies**
 - \therefore **Only comparator's f_{SW} component is relevant.**

$$\text{Gain} \equiv \frac{\Delta v_{OUT}(f_{SW})}{\Delta v_{IN}(f_{SW})} = \frac{\left(\frac{4}{\pi}\right)V_{DD}}{\Delta v_{IN(PP)}} \leq \frac{\left(\frac{4}{\pi}\right)V_{DD}}{V_{HYST}}$$

Square Wave's Fundamental Component
Input Ripple's Amplitude

- If comparator's $T_{DLY} \ll T_{SW} \therefore$ **No in-band comparator pole**;
- **Comparator waits for v_{IN} to reach trip point**
 - \therefore **90° if $\Delta v_{IN} = V_{HYST}$** AND **$< 90^\circ$ if $\Delta v_{IN} > V_{HYST}$** ;
- **-FB adjusts Δv_{IN} (gain and phase) until oscillations are sustained.**

Introduction: Problem Statement

“Hysteretic buck converters are always stable.”

[1] K. -C. Lee et al., ISSCC 2010.

[2] C. -H. Tso et al., IEEE Power Electronics Letters, Sept. 2003.


[3] J. H. Park et al., IEEE COMPEL Workshop, 2006.

• Hysteretic DC-DC Converters:

- Simple system and intuitive operation, but **always stable?**
- **Output voltage ripple often exceeds hysteretic window, why?**
- Output can **ring rail-to-rail when** the output impedance lacks resistive components (e.g., R_{ESR} is low in C_O), **why?**


➔ How can we explain the stability and dynamics of hysteretic comparators in switching dc-dc converters?

PWM Switching Converters

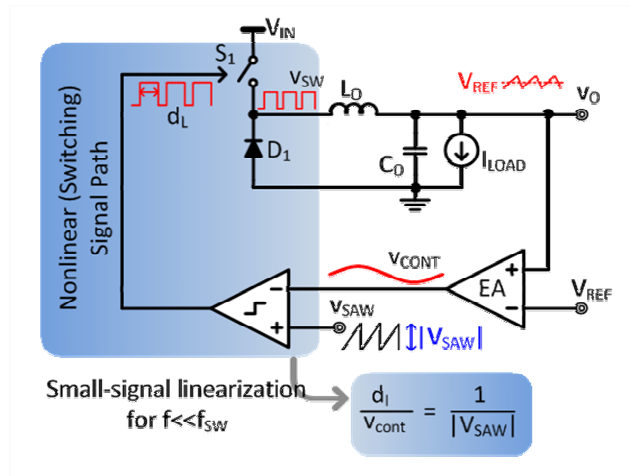


→ A PWM switching converter **can be averaged and linearized across a switching cycle.**

Hysteretic Switching Converters

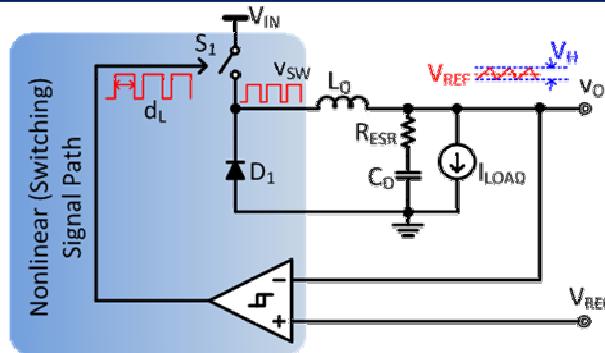

- No error amp, Digital output, Circuit processes frequencies near f_{sw} :
 - Hysteretic comparator is **difficult to linearize** (i.e., extract ac transfer function).
- It is well known that the circuit **sustains oscillations at f_{sw} , but how?**

Linearizing a Hysteretic Comparator

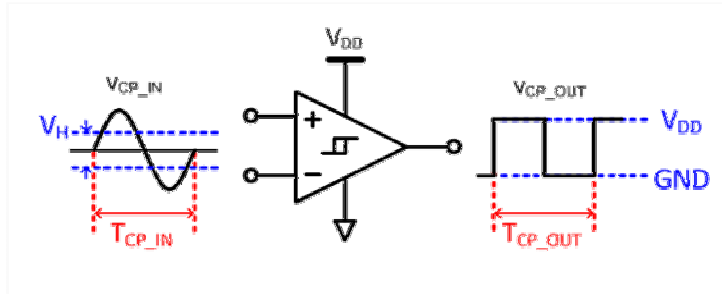


Observations:

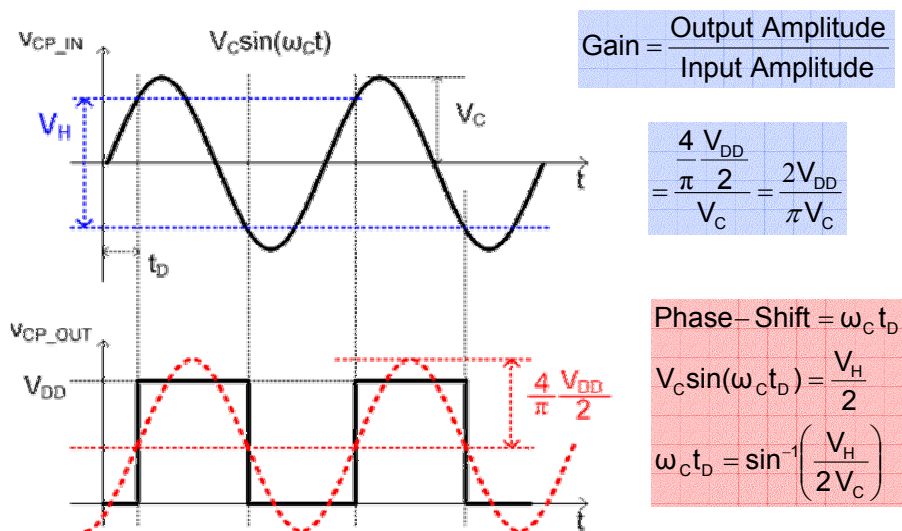
- 1) Nonlinear block
- 2) $T_{CP_IN} = T_{CP_OUT} \rightarrow f_{CP_IN(fund)} = f_{CP_OUT(fund)}$
- 3) Gain and phase-shift relationships can be defined.

* Reference: Chestnut and Mayer, "Servomechanisms and Regulating System Design," New York: John Wiley & Sons, 1955.


Describing Function: Gain and Phase Shift



Frequency Response

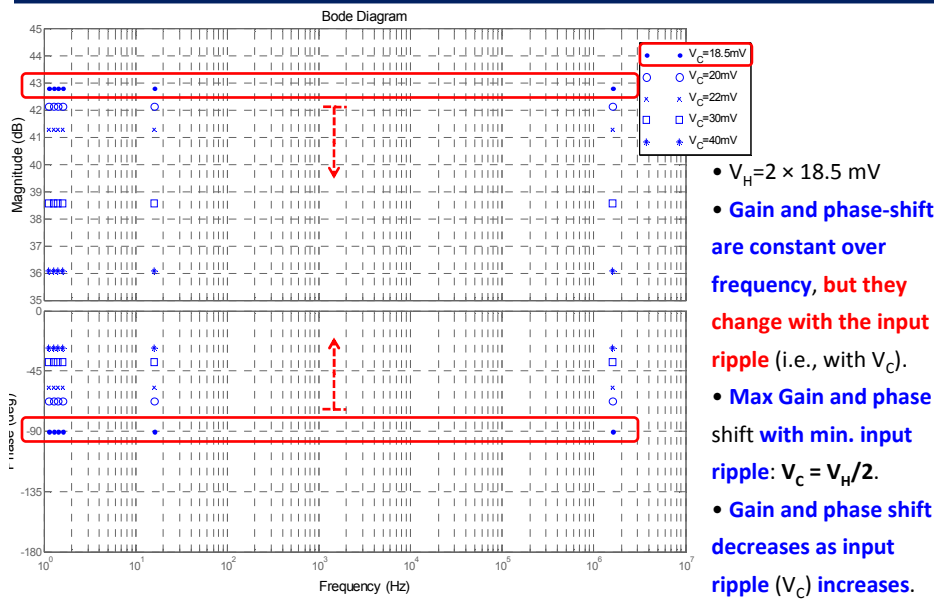


Loop-Gain Transfer Function

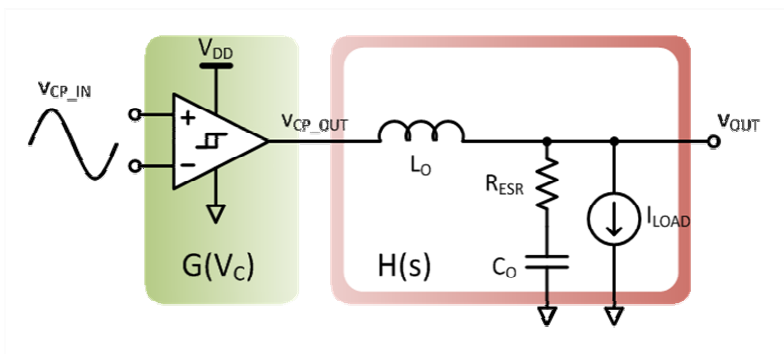


$$G(V_C) = \frac{2V_{DD}}{\pi V_C} \angle \sin^{-1}\left(\frac{V_H}{2V_C}\right) \quad H(s) = \frac{1 + sR_{ESR}C_O}{1 + sR_{ESR}C_O + s^2L_OC_O}$$

→ Loop-Gain = $G(V_C) \times H(s)$


Frequency Response of the Loop-Gain

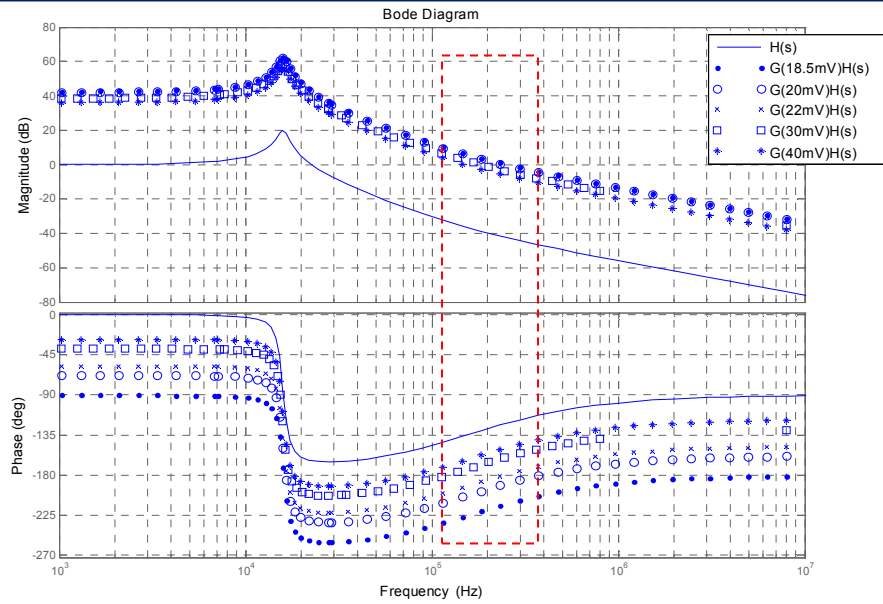

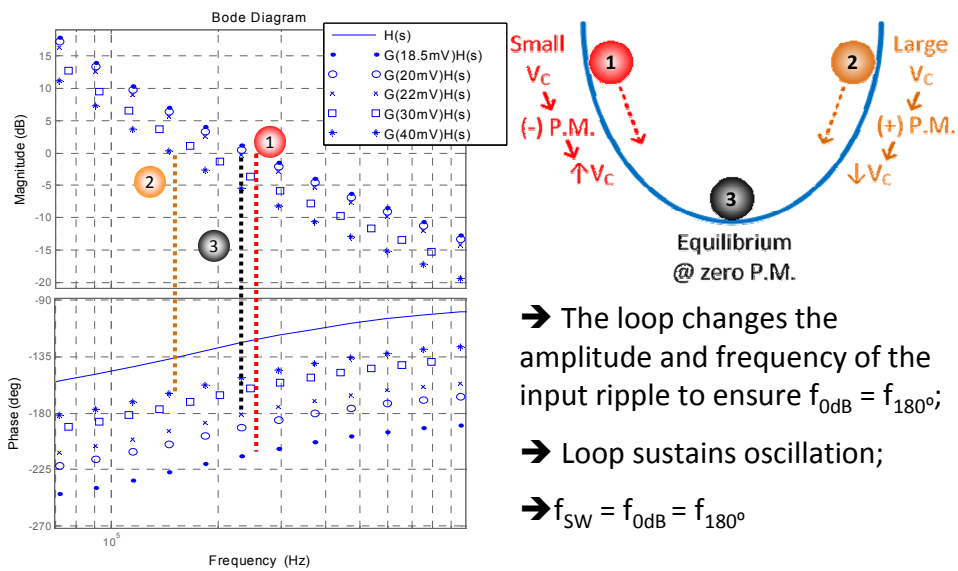Frequency Response of the Loop-Gain (zoom in)



Theory vs. Simulation

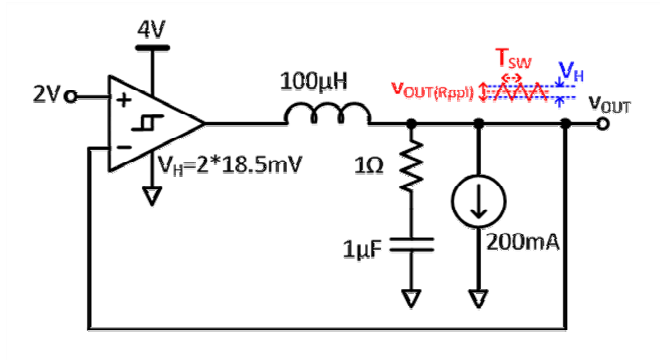

Parameters	Theoretical Estimation	Simulated Result
f_{SW}	230 KHz	262 KHz
$V_{OUT(Rpp)}$	22 mV	20 mV

* **Source of Error:** v_{OUT} is not a sinusoidal waveform.

Conclusions

Hysteretic DC-DC Switching Converters:

- **Sustained oscillation** of v_{OUT} about $V_{REF} \rightarrow f_{odB} = f_{180^\circ}$;
- **Respond within 1 switching cycle** $\rightarrow f_{odB} = f_{SW}$;
 \therefore Faster than PWM counterparts.
- Hysteretic comparator is **nonlinear**.

Describing Function of Hysteretic Comparators:

- Linearize by **analyzing fundamental frequency**;
- Supply V_{DD} fixes Δv_{OUT} 's amplitude to a constant;
- **Hysteresis delays** (phase-shifts) response;
 \rightarrow **Gain and phase change with input ripple's amplitude.**