

Homework 5

- 1) Purpose: Understanding the common-emitter amplifier.

In the circuit below, assume the npn BJT is operating in forward-active mode. Let $\beta = 130$, $V_A = 60$ V, and $V_{BE} = 0.7$ V. Assume the capacitors have negligible impedance at the frequency of the ac signal.

- a. What are the purposes of capacitors C_1 , C_2 , and C_3 in this circuit?

Capacitors C_1 and C_3 are coupling capacitors. Their purpose is to allow ac signals to enter/exit the circuit at particular nodes while leaving DC signals unchanged. Capacitor C_2 is a bypass capacitor. Its purpose is to rout ac signals around the emitter resistor, effectively allowing the emitter to act as an ac ground.

- b. Determine all DC terminal voltages and currents as well as the small-signal voltage gain A_v of the amplifier circuit if $R_E = 12$ k Ω .

Step 1: Obtain the DC equivalent circuit by treating capacitors as open circuits and Thevenizing the base input.

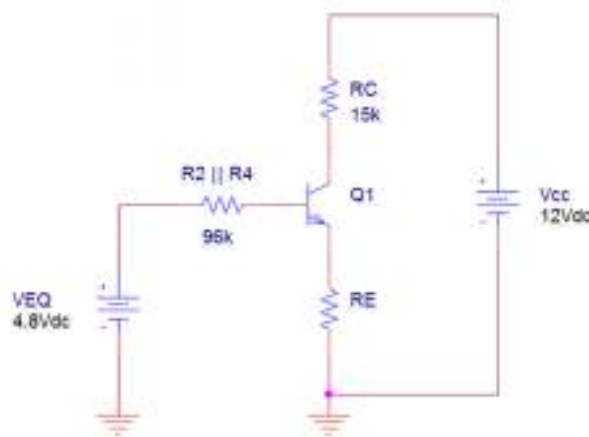


Figure 1S: The DC equivalent circuit.

Step 2: Use KVL and the assumption that the transistor is biased in forward-active mode to determine the Q-point currents and voltages.

Relevant transistor equations:

$$I_C = \beta I_B$$
$$I_E = (\beta + 1)I_B$$

Following the left side of the circuit:

$$V_{EQ} - (R_2 || R_4)I_B - V_{BE} - R_E I_E = 0$$

$$V_{EQ} - (R_2 || R_4)I_B - V_{BE} - R_E(\beta + 1)I_B = 0$$

$$I_B = \frac{V_{EQ} - V_{BE}}{(R_2 || R_4) + R_E(\beta + 1)}$$

$$= \frac{4.8V - 0.7V}{96 \text{ k}\Omega + (12 \text{ k}\Omega)131}$$

$$I_B = 2.46 \mu\text{A}$$

$$I_C = \beta I_B = 130(2.46 \mu\text{A}) = 0.320 \text{ mA}$$

$$I_E = (\beta + 1)I_B = 131(2.46 \mu\text{A}) = 0.322 \text{ mA}$$

Knowing the DC terminal currents, we can find the DC terminal voltages by again using KVL.

$$V_B = V_{EQ} - (R_2 || R_4)I_B = 4.8 \text{ V} - (96 \text{ k}\Omega)(2.46 \mu\text{A})$$

$$V_B = 4.56 \text{ V}$$

$$V_C = V_{CC} - R_C I_C = 12 \text{ V} - (15 \text{ k}\Omega)(0.320 \text{ mA})$$

$$V_C = 7.20 \text{ V}$$

$$V_E = V_B - V_{BE} = 4.56 \text{ V} - 0.7 \text{ V}$$

$$V_E = 3.86 \text{ V}$$

Step 3: Obtain the ac equivalent circuit by treating all capacitors as short circuits and all DC sources as short circuits.

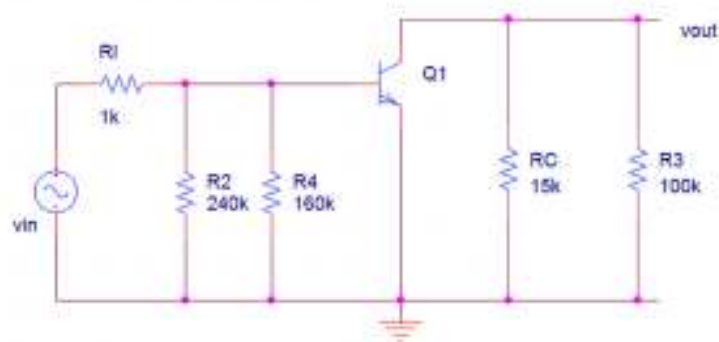


Figure 2S: The ac equivalent circuit.

Step 4: Obtain the Hybrid-Pi circuit by replacing the transistor with the Hybrid-Pi model. From analyzing this circuit, obtain the small-signal voltage gain.

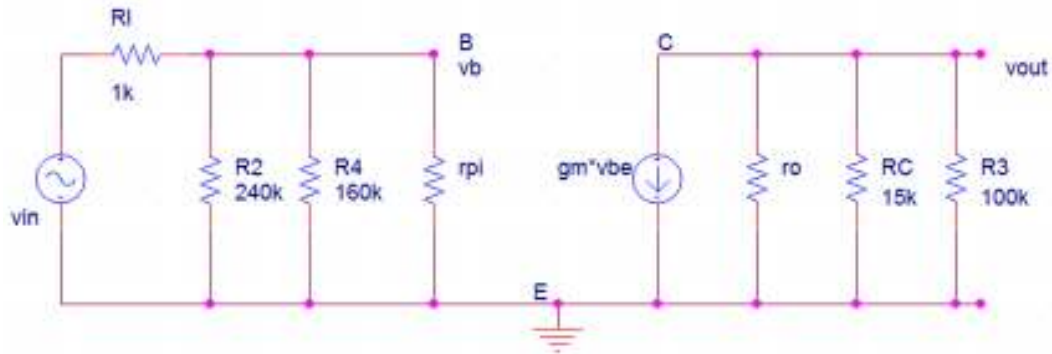


Figure 3S: The Hybrid-Pi equivalent circuit.

The small-signal parameters, as determined from the Q-point found in Step 2, are as follows.

$$g_m = \frac{I_C}{V_T} = \frac{0.320 \text{ mA}}{0.0259 \text{ V}} = 12.4 \text{ mS}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{130}{12.4 \text{ mS}} = 10.5 \text{ k}\Omega$$

$$r_o = \frac{V_A + V_{CE}}{I_C} = \frac{60 \text{ V} + 7.20 \text{ V} - 3.86 \text{ V}}{0.320 \text{ mA}} = 198 \text{ k}\Omega$$

To determine $A_v = v_{out}/v_{in}$, we first relate v_{in} to v_{be} and then relate v_{be} to v_{out} .

$$v_{be} = \frac{R_2 || R_4 || r_\pi}{R_1 + R_2 || R_4 || r_\pi} v_{in}$$

$$v_{out} = -g_m v_{be} (r_o || R_C || R_3) = -g_m (r_o || R_C || R_3) \frac{R_2 || R_4 || r_\pi}{R_1 + R_2 || R_4 || r_\pi} v_{in}$$

$$A_v = \frac{v_{out}}{v_{in}} = -g_m (r_o || R_C || R_3) \frac{R_2 || R_4 || r_\pi}{R_1 + R_2 || R_4 || r_\pi}$$

$$= -(12.4 \text{ mS})(12.92 \text{ k}\Omega) \left(\frac{9.46 \text{ k}\Omega}{1 \text{ k}\Omega + 9.46 \text{ k}\Omega} \right)$$

$$A_v = -137.3 \text{ V/V}$$

Note that the voltage gain is negative. This is because the current passing through r_o is moving upwards, while v_{out} is defined as the voltage drop across r_o in the opposite direction. Physically, this means that the output signal is 180° out of phase with the input signal.

- c. Repeat part (b) with $R_E = 80 \text{ k}\Omega$.

Following the exact same procedures as part (b), the following results are obtained:

$$I_B = 0.388 \mu\text{A}$$

$$I_C = 50.4 \mu\text{A}$$

$$I_E = 50.8 \mu\text{A}$$

$$V_B = 4.76 \text{ V}$$

$$V_C = 11.24 \text{ V}$$

$$V_E = 4.06 \text{ V}$$

$$g_m = 1.95 \text{ mS}$$

$$r_\pi = 66.8 \text{ k}\Omega$$

$$r_o = 1.33 \text{ M}\Omega$$

$$A_v = -24.6 \text{ V/V}$$

- d. If the goal is to maximize the voltage gain, what general design rule for common-emitter amplifiers can you infer from the results of parts (b) and (c)?

In general, we want the emitter resistor to be as low as possible.

2) Purpose: Coupling diodes and BJTs.

In the circuit below, find the Q-point of both the Zener diode and BJT. Assume the BJT is biased in the forward-active regime, that $V_Z = 5\text{ V}$, $R_Z = 0\ \Omega$, $\beta = 100$, and $V_{BE} = 0.7\text{ V}$.

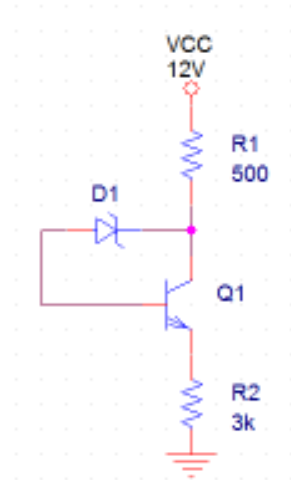


Figure 2: Zener diode with BJT.

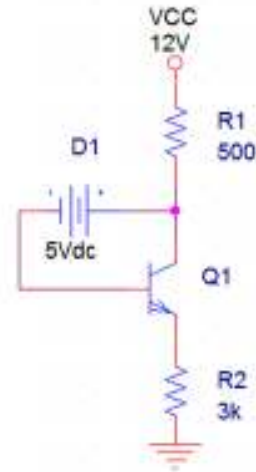


Figure 2S: Zener diode in breakdown regime, represented as a DC voltage source.

From inspection of the circuit, and if we are assuming the BJT is biased in the forward-active regime, it is safe to assume the Zener diode is operating in the breakdown regime. Therefore, we can replace it with a 5 V DC source, as seen in Figure 2S.

Starting KVL from the power supply,

$$12\text{ V} - (I_C + I_B)R_C - V_Z - V_{BE} - I_E R_E = 0$$

$$12\text{ V} - (\beta + 1)I_B R_C - V_Z - V_{BE} - (\beta + 1)I_B R_E = 0$$

$$I_B = \frac{12\text{ V} - V_Z - V_{BE}}{(\beta + 1)(R_C + R_E)} = \frac{6.3\text{ V}}{(101)(3500\ \Omega)}$$

$$I_B = 17.8\ \mu\text{A}$$

$$I_C = \beta I_B = 1.78\text{ mA}$$

$$I_E = (\beta + 1)I_B = 1.80\text{ mA}$$

$$V_C = 12\text{ V} - I_E R_C = 12\text{ V} - (1.80\text{ mA})(500\ \Omega)$$

$$V_C = 11.1\text{ V}$$

$$V_B = V_C - V_Z = 11.1\text{ V} - 5\text{ V}$$

$$V_B = 6.1\text{ V}$$

$$V_E = V_B - V_{BE} = 6.1\text{ V} - 0.7\text{ V}$$

$$V_E = 5.4\text{ V}$$

Obviously, from inspection, the current through the Zener diode is the current that goes directly into the base of the BJT. Therefore,

$$I_Z = I_B = 17.8 \mu\text{A}$$

And, of course, given from the problem statement, $V_Z = 5 \text{ V}$

3. Purpose: BJT application in circuit designing
Assume forward active mode bias and identical BJTs Q_1 and Q_2 in the following “current mirror” circuit.

Given, $R_2 = 10\text{k}\Omega$, $R_3 = 1\text{k}\Omega$, $R_7 = 100\Omega$, $R_8 = 100\Omega$, $\beta = 416.4$, and $I_S = 6.73\text{ fA}$.

(a) Find the current flowing in R_3 and compare it to the current flowing in R_2 .
Note: it may be helpful to use Ebers Moll model only for determining collector currents in the two transistors, but otherwise use Beta/CVD model.

(b) What happens to the currents if R_3 is replaced with a $5\text{k}\Omega$ resistor?

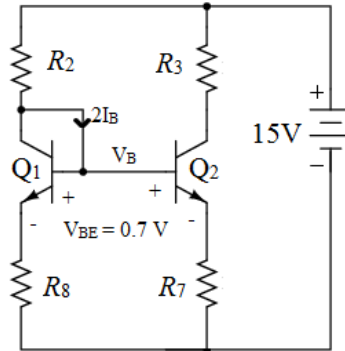


Figure 3. Current mirror circuit.

(a)
 V_B is same for both Q_1 and Q_2 transistors, so is V_E . Also, $V_{C1} = V_{B1}$.
Since, $V_{E1} = V_{E2}$ and $R_8 = R_7$, we can calculate, $I_{E1} = I_{E2}$.
We know,

$$I_E = \left(\frac{\beta + 1}{\beta} \right) I_C$$

$$I_B = \frac{I_C}{\beta}$$

Now,

$$15\text{ V} = I_{E1}R_8 + 0.7 + R_2(I_{C1} + 2I_B)$$

$$\Rightarrow I_{C1} = \frac{15 - 0.7}{R_2 \left(\frac{2}{\beta} \right) + R_2 + \left(\frac{\beta + 1}{\beta} \right) R_8} = 1.409\text{ mA}$$

So,

$$I_{E1} = \left(\frac{\beta + 1}{\beta} \right) I_{C1} = 1.412\text{ mA}$$

Since, $V_{BE1} = V_{BE2}$ and $I_C = I_S e^{V_{BE}/V_T}$,

$$I_{C1} = I_{C2} = 1.409\text{ mA}$$

(b)

Nothing changes if $R_3=5k\Omega$, since the current through collector (I_{C2}) is set by Q_1 . The circuit acts as a dc current source as long as Q_1 and Q_2 remain forward active. For this to happen, I_C must not be too high. I_C are set by R_2 (primarily) and R_8+R_7 . Also, for $I_{C1} = I_{C2}$, the choice of $R_8=R_7$ was important.

Note, multiple current sources can be made from this configuration. For this configuration, common power supply is not required, only common ground is necessary.

