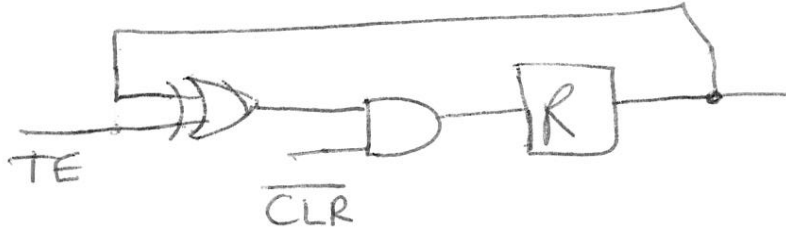



# ECE 2030 Spring 2006 Test 3 sol, Dr. Heck

Problem 1 (25 Points):

- a) Draw the schematic of a toggle cell using gates and registers.



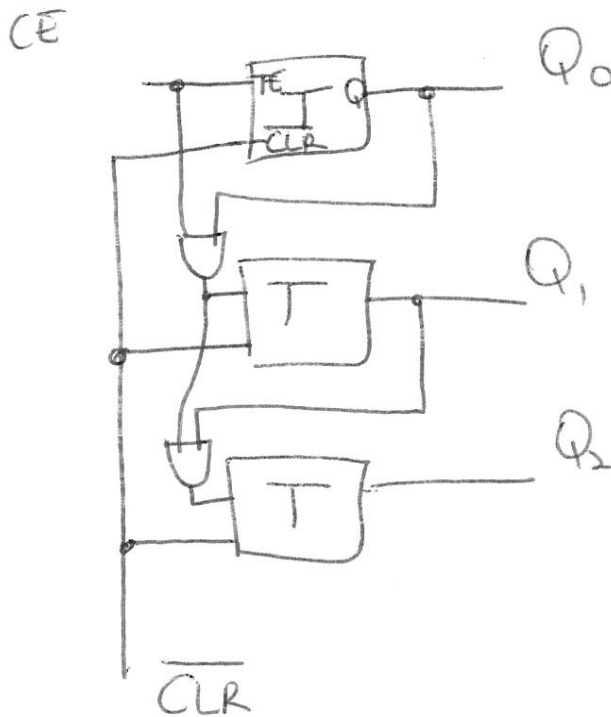- b) Draw the schematic of a 3-bit counter using toggle cells and gates.





Problem 2 (25 Points): Different size memory systems are to be built from 64M x 8 memory chips. Answer the following questions.

How many memory cells are in the memory chip? 2<sup>29</sup>

$2^{26} \cdot 2^3$


How many address lines are used for the memory chip? 26

Case 1: A 64M x 32 memory system.

How many banks are in the memory system? 1

How many address lines are used for the memory system? 26

Show the schematic of the memory system using the memory chips shown below. Identify all buses (using the notation  $A_n:A_m$  and  $D_n:D_m$ , where  $n$  and  $m$  represent the starting and the ending line numbers), the sizes of all buses, and add any extra components needed to complete the schematic.

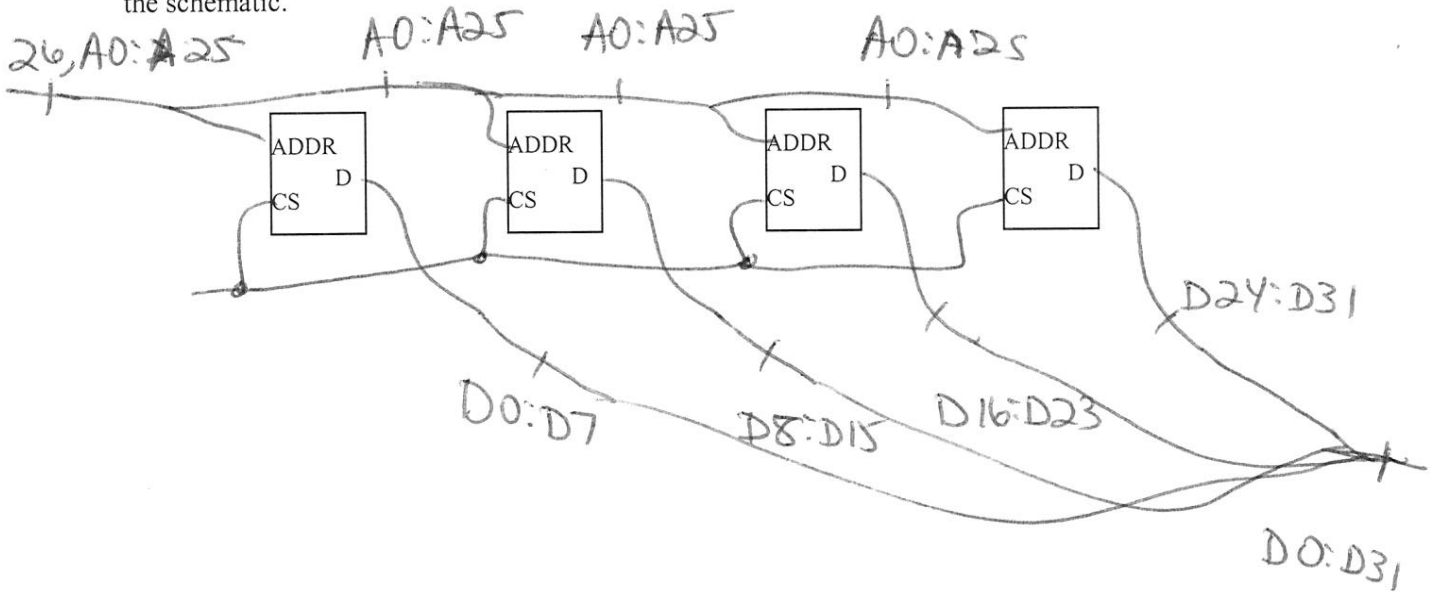


Case 2: A 128M x 16 memory system.

How many banks are in the memory system? 2

How many address lines are used for the memory system? 27

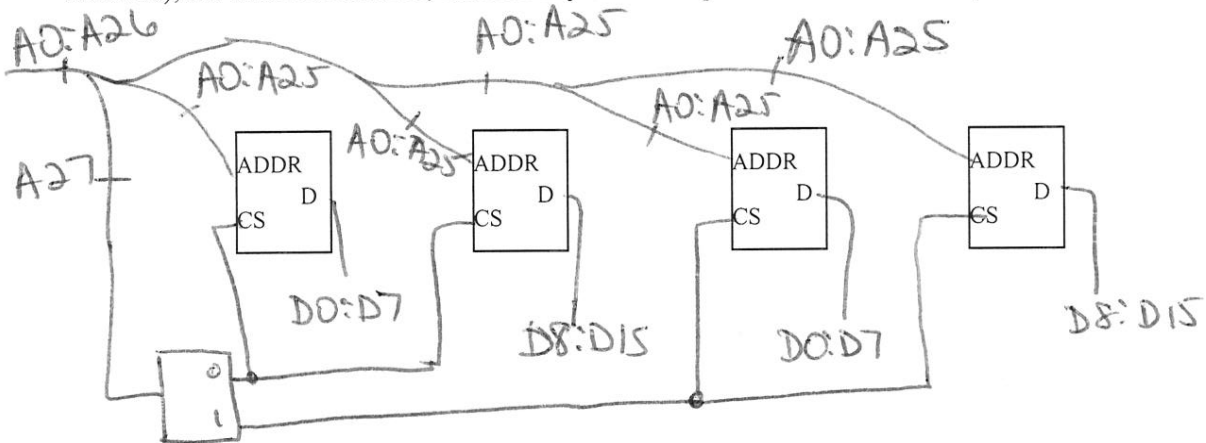
Show the schematic of the memory system using the memory chips shown below. Identify all buses (using the notation  $A_n:A_m$  and  $D_n:D_m$ , where  $n$  and  $m$  represent the starting and the ending line numbers), the sizes of all buses, and add any extra components needed to complete the schematic.




1 to 2 decoder

Problem 3 (20 Points):

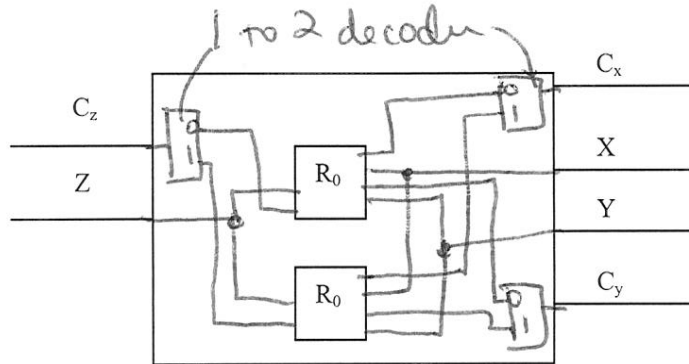
- a) Complete the schematic of a register file that contains 2 registers. Identify all lines and components used. (You do not need to show the register write enable in this schematic.)



Expanded view of the register icon.

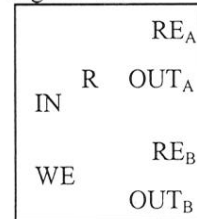

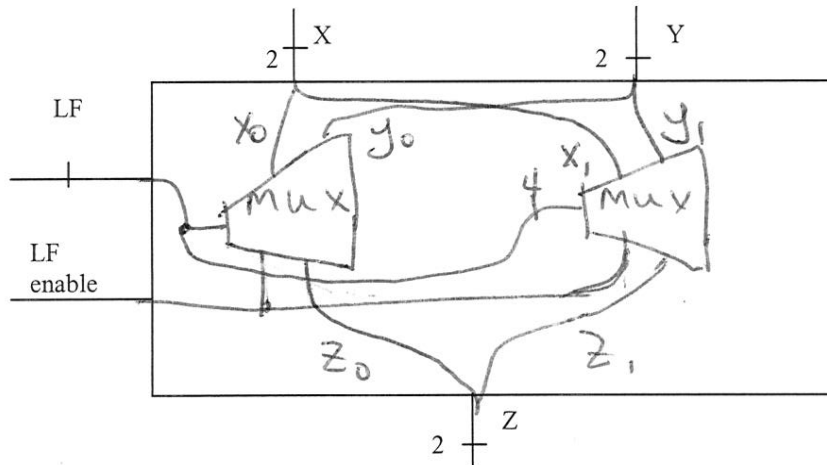- b) Complete the schematic of a 2 bit logic unit.



Problem 4 (30 Points):

Write the microcode to complete the following operations

- 1  $R_2 = R_1 \text{ AND } R_5$
- 2  $R_3 = R_4 / 8$
- 3  $R_4 = R_5 \times 4$
- 4  $R_{10} = R_1 - R_3$
- 5  $M[R_2] = R_3$
- 6  $R_4 = M[R_1]$

*unmarked spots are don't cares*

Step	cX	cY	cZ	RWE	imm. en.	imm val.	au en	$\bar{a}/s$	lu. en.	l.f.	st. en.	s.t.	store en.	load en.	r/ $\bar{w}$	mem. sel.
1	1	5	2	1	0		0		1	1000	0		0	0		0
2	4		3	1	1	3	0		0		1	1	0	0		0
3	5		4	1	1	-2	0		0		1	1	0	0		0
4	1	3	10	1	0		1	1	0		0		0	0		0
5	2	3		0	0		0		0		0		1	0	0	1
6	1		4	1	0		0		0		0		0	1	1	1

Consider the following assembly code. Write the corresponding microcode for these instructions.

1. ADD \$1,\$2,\$3
2. ADDI \$1,\$1,1
3. OR \$4,\$3,\$2

Step	cX	cY	cZ	RWE	imm. en.	imm val.	au en	$\bar{a}/s$	lu. en.	l.f.	st. en.	s.t.	store en.	load en.	r/ $\bar{w}$	mem. sel.
1	2	3	1	1	0		1	0	0		0		0	0		0
2	1		1	1	1	1	1	0	0		0		0	0		0
3	3	2	4	1	0		0		1	1110	0		0	0		0