

ECE2030 Homework 1  
Due 1/15/04

1. Build switch circuits to implement the following Boolean algebra expressions. In each case, determine the number of transistors used for the design.

a)  $F = A\overline{B}\overline{C}(D+E)$

b)  $F = AB\overline{(C+D)}$

b)  $F = (A+B)\overline{(C+D)}$

2. Use DeMorgan's Law to simplify the following expressions to remove long bars (bars over multiple signals).

a)  $F = A\overline{(B + \overline{CD})}$

b)  $F = \overline{(A + \overline{B})(C + \overline{D})}$

c)  $F = \overline{AB + CD}$