

CHAPTER VI



COMBINATIONAL LOGIC BUILDING BLOCKS

- Combinational logic
 - Output at any time is determined completely by the current input.
 - We will later consider circuits where the output is determined by the input and the current state (memory) of the system.
 - In this chapter we will consider some useful building blocks that can be pieced together and used in larger designs. This will include:
 - Multiplexers (selectors) and demultiplexers (distributors)
 - Encoders, priority encoders, decoders
 - Adders (full and half)
 - Parity generators and parity checkers
 - Shifters and rotators
 - Comparators

DECODERS

BASIC DECODER

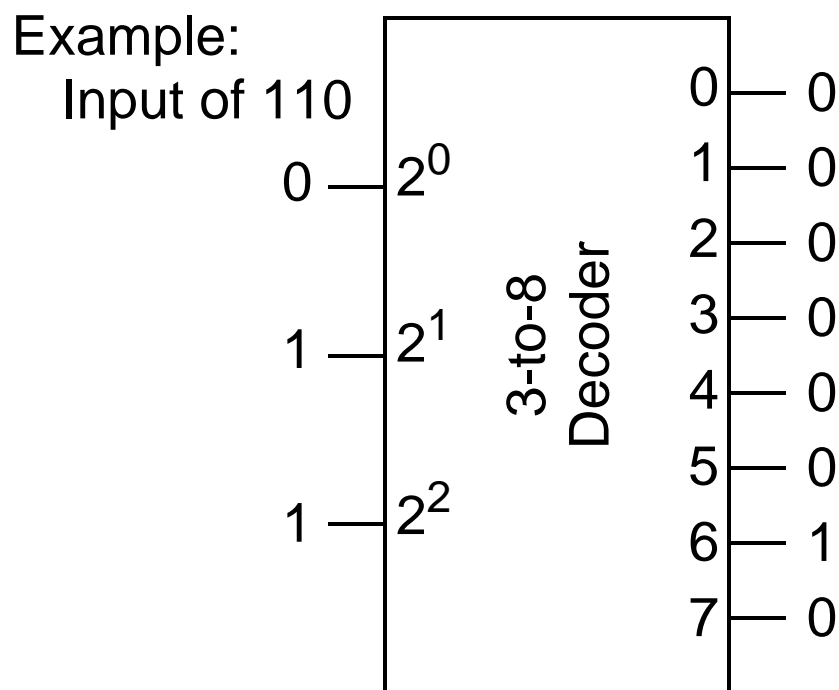 - Standard decoder is an n -to- m -line decoder, where $m \leq 2^n$.
- Example: 3-to-8-line decoder




- All outputs D_m are low except for the one corresponding to the binary value of the input $A_n \dots A_1 A_0$.

DECODERS

DECODERS WITH ENABLE

- Often, combinational logic building blocks will also have an enable line that turns on outputs or leaves them off.

3-to-8 Decoder
with Enable

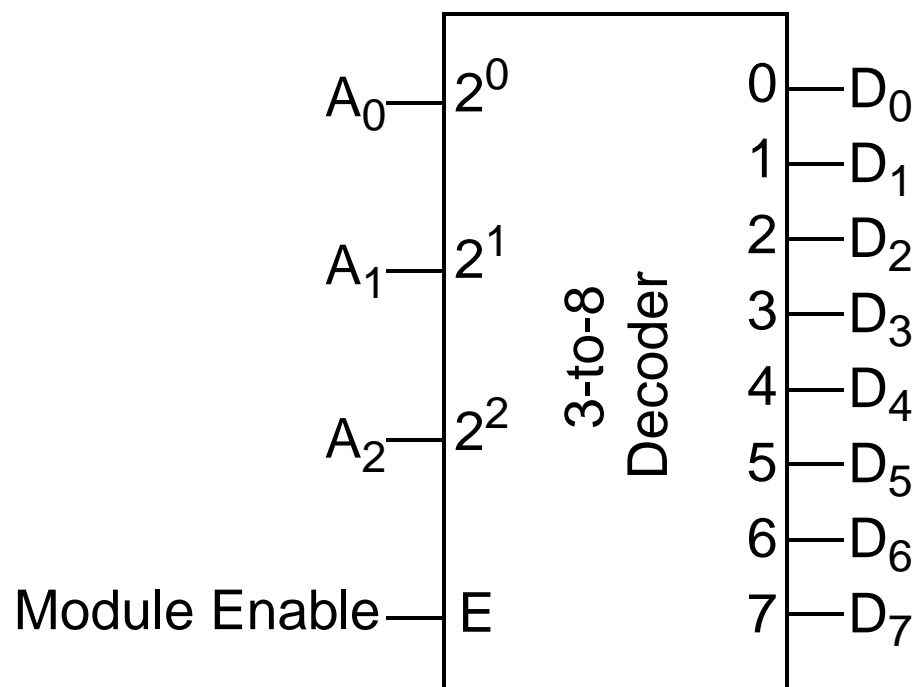

DECODERS

TRUTH TABLES



- Truth table for a **3-to-8-line decoder**:

Inputs				Outputs							
A_2	A_1	A_0	E	D_7	D_6	D_5	D_4	D_3	D_2	D_1	D_0
X	X	X	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0	0	0	0	1
0	0	1	1	0	0	0	0	0	0	1	0
0	1	0	1	0	0	0	0	0	1	0	0
0	1	1	1	0	0	0	0	1	0	0	0
1	0	0	1	0	0	0	1	0	0	0	0
1	0	1	1	0	0	1	0	0	0	0	0
1	1	0	1	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

DECODERS

IMPLEMENTATION

  - How can a decoder be implemented? Fill in the circuit!




DECODERS

DESIGNING WITH DECODERS

- Any Boolean function can be implemented using a **decoder** and **OR** gates by ORing together the function's **minterms**.

Inputs			Outputs	
A_2	A_1	A_0	F_1	F_2
0	0	0	0	0
0	0	1	1	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	1
1	1	0	0	0
1	1	1	1	0

 


DECODERS

DECODER NETWORKS

- We can also use multiple decoders to form a larger decoder.

 3-to-8 Decoder Implemented
with two 2-to-4 Decoders




A_2 used with enable input to control which decoder will output the 1.

A_1 and A_0 used to select which output on specific decoder will output 1.


ENCODERS

BASIC ENCODER

 - Standard binary encoder is an m -to- n -line encoder, where $m \leq 2^n$.
- Example: 8-to-3-line encoder



Example:
Input of 00010000

 

ENCODERS

ENCODER TRUTH TABLE

- Truth table for an **8-to-3-line encoder**:

Inputs								Outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

- Assumed that only one input is **1**. What happens if more than one is **1**?


ENCODERS

DESIGNING WITH ENCODERS

- DECODERS
- ENCODERS
 - BASIC ENCODER
 - TRUTH TABLE

- Encoders are useful when the occurrence of one of several disjoint events needs to be represented by an integer identifying the event.

Example: Wind direction encoder

 

ENCODERS

PRIORITY ENCODERS

- A priority encoder takes the input of 1 with the highest index and translates that index to the output.


Inputs								Outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	X	0	0	1
0	0	0	0	0	1	X	X	0	1	0
0	0	0	0	1	X	X	X	0	1	1
0	0	0	1	X	X	X	X	1	0	0
0	0	1	X	X	X	X	X	1	0	1
0	1	X	X	X	X	X	X	1	1	0
1	X	X	X	X	X	X	X	1	1	1

ENCODERS

DESIGN WITH P-ENCODER

- Priority encoders are useful when inputs have a predefined priority and we wish to select the input with the highest priority.

Example: Resolving interrupt requests

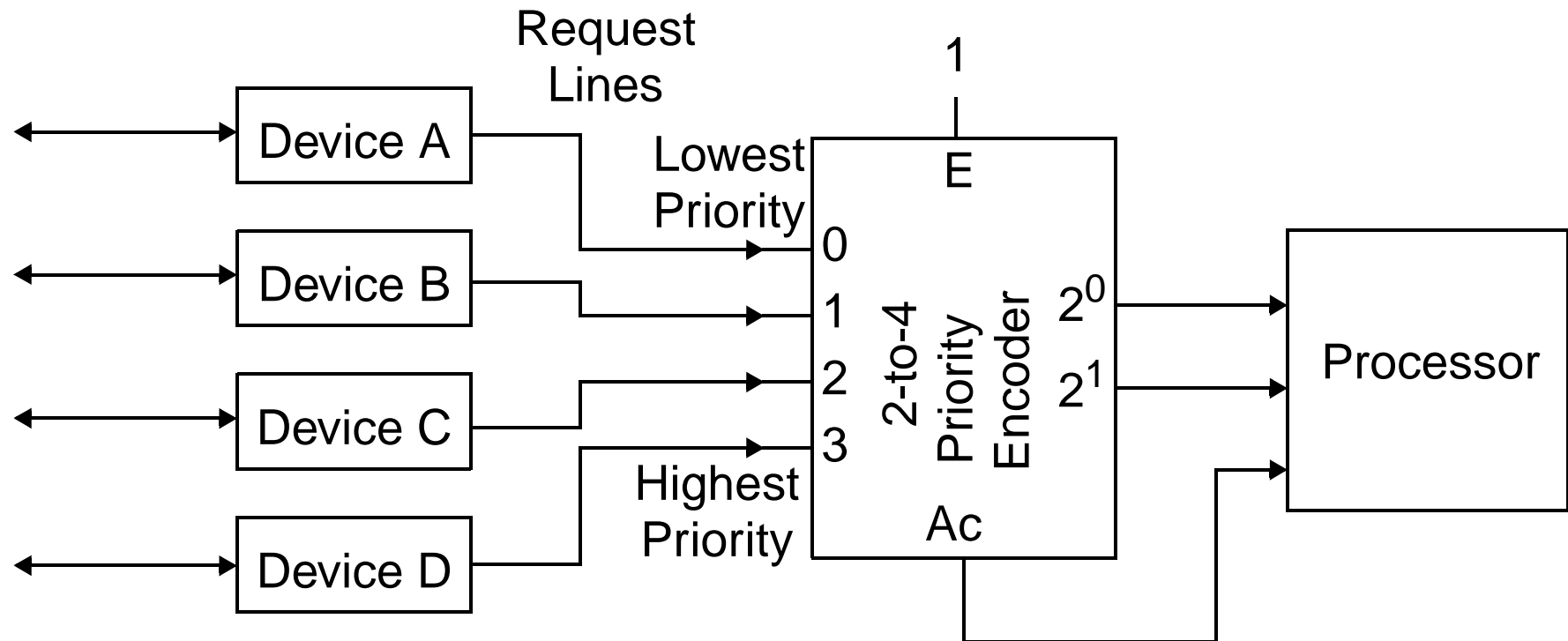


pp. 253-256 of Ercegovic, Lang and Moreno, "Introduction to Digital Systems", 1999.

MULTIPLEXERS

BASIC MULTIPLEXER (MUX)

 - Selects one of many inputs to be directed to an output.




		Inputs				Output
X	Y	A ₃	A ₂	A ₁	A ₀	F
0	0	X	X	X	0	A ₀ =0
0	1	X	X	0	X	A ₁ =0
1	0	X	0	X	X	A ₂ =0
1	1	0	X	X	X	A ₃ =0
0	0	X	X	X	1	A ₀ =1
0	1	X	X	1	X	A ₁ =1
1	0	X	1	X	X	A ₂ =1
1	1	1	X	X	X	A ₃ =1

MULTIPLEXERS

USING PASS GATES

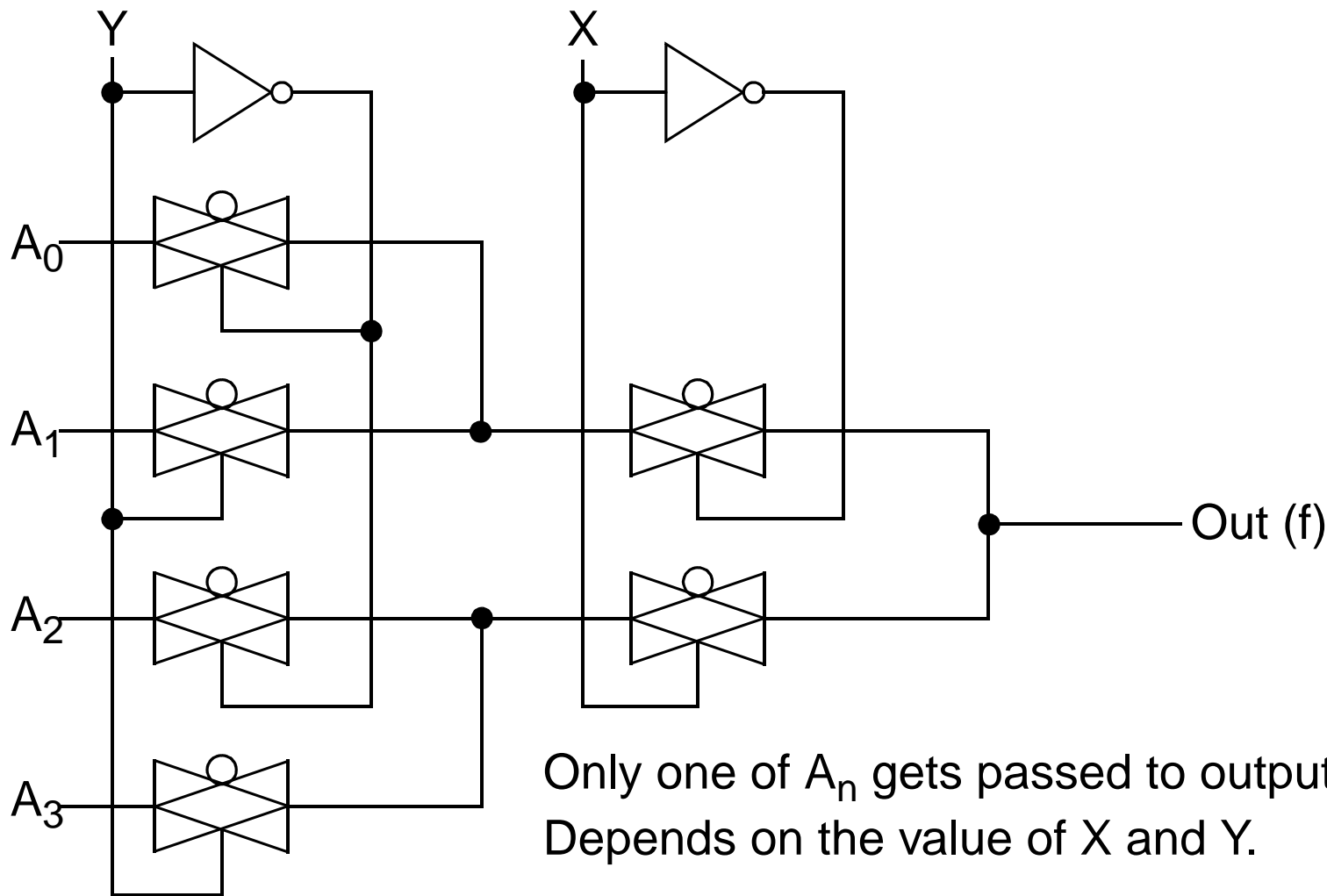- The **4x1 mux** can be implemented with **pass gates** as follows.



MULTIPLEXERS


DESIGN WITH MULTIPLEXERS

- Any Boolean function can be implemented by setting the inputs corresponding to the function and the selectors as the variables.

Example:

X	Y	Z	F_1
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1


Module Enable

 

DEMULTIPLEXERS

BASIC DEMULTIPLEXER

 - Takes one input and selects one of many outputs to direct the input.




Inputs			Outputs			
X	Y	W	D ₃	D ₂	D ₁	D ₀
0	0	0	0	0	0	W=0
0	1	0	0	0	W=0	0
1	0	0	0	W=0	0	0
1	1	0	W=0	0	0	0
0	0	1	0	0	0	W=1
0	1	1	0	0	W=1	0
1	0	1	0	W=1	0	0
1	1	1	W=1	0	0	0

DEMULTIPLEXERS

DESIGN W/ DEMULTIPLEXERS

- A demultiplexer is useful for routing an input to a desired location.


Example:

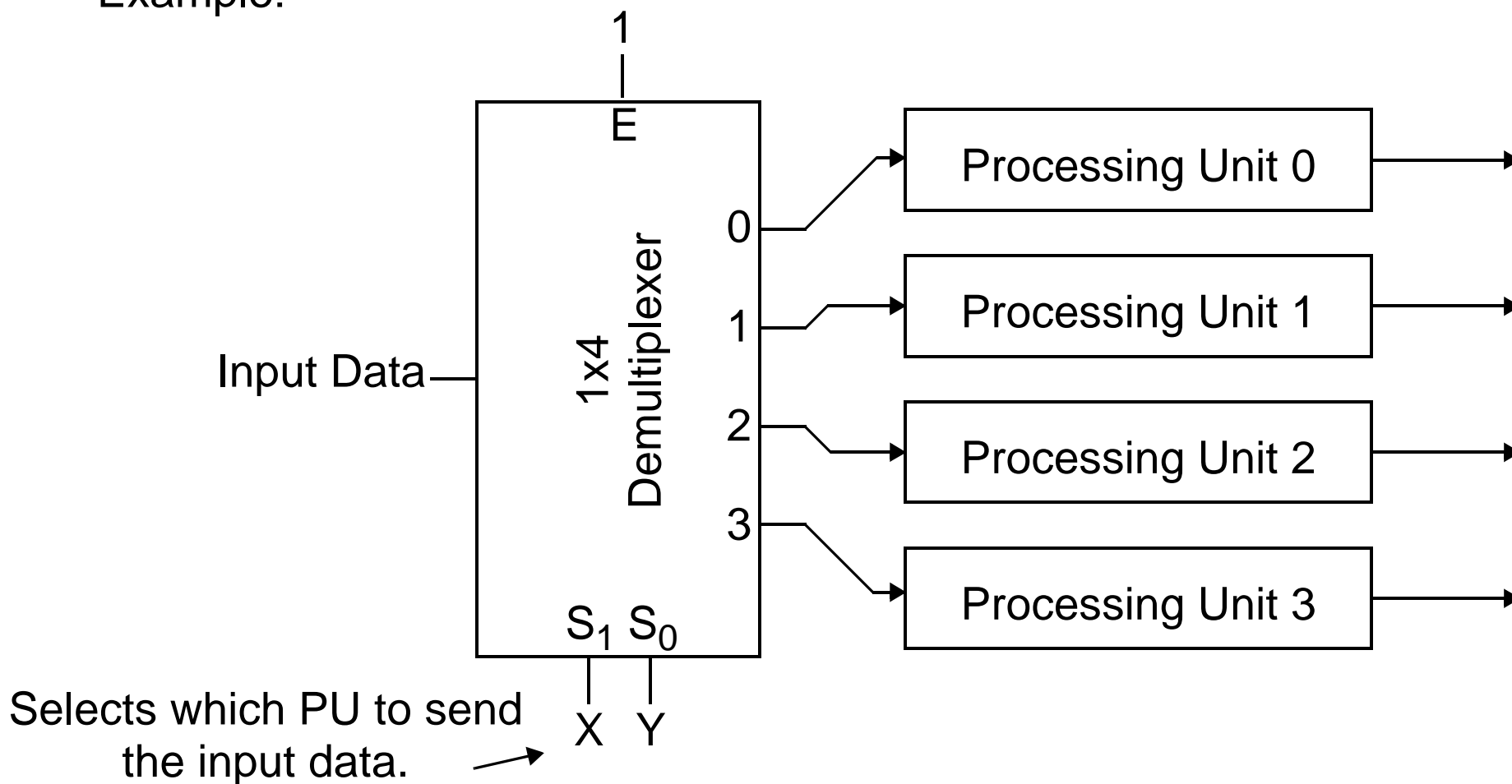

SHIFTERS

BASIC SHIFTER

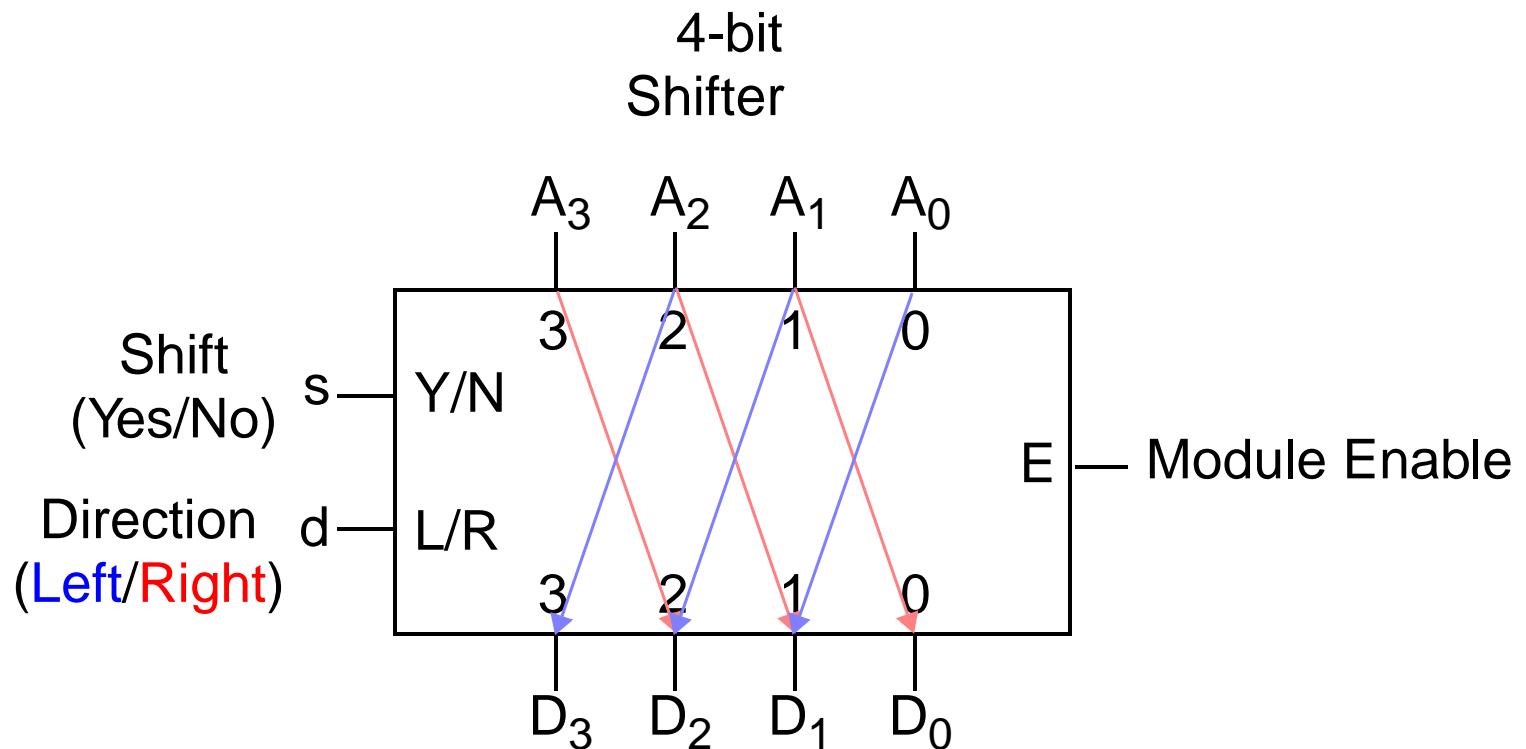
- A shifter takes a set of inputs and shifts it to the right or left.



SHIFTERS


COMMON SHIFTERS

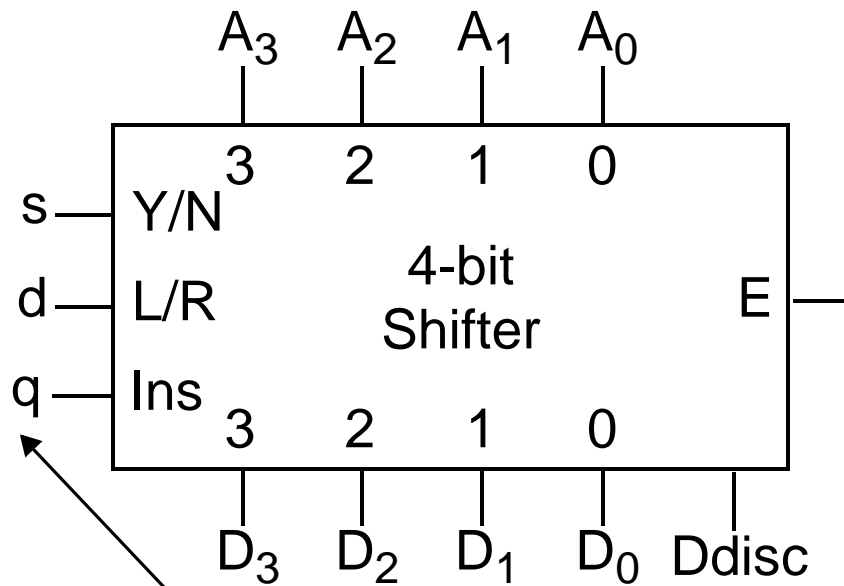- A whole variety of other shifters are possible such as



Value to insert into empty spot

Value discarded from shift

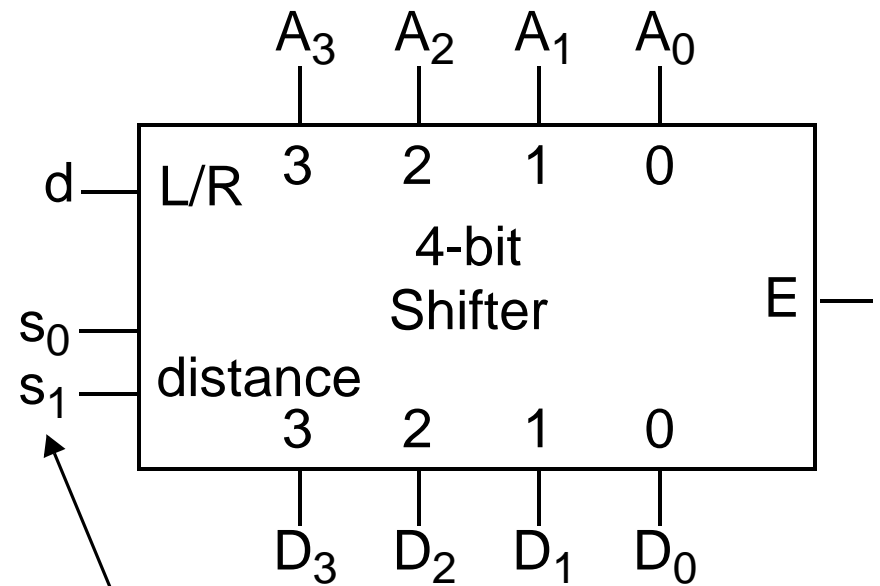


Distance (in binary) of how far to shift

ROTATORS

BASIC ROTATOR

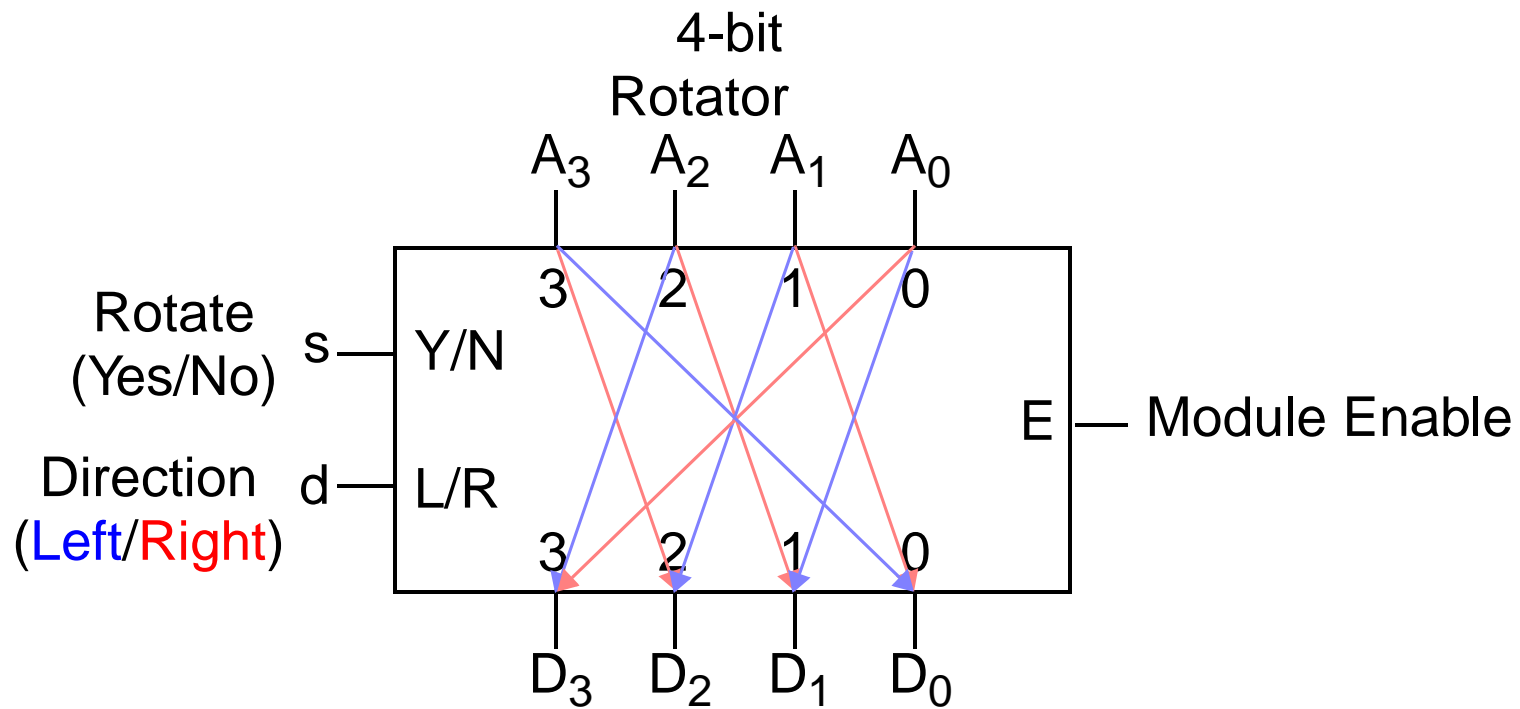
- A rotator takes a set of inputs and rotates it to the right or left.
- This is similar to a shifter except that instead of dropping the bit off of the end in the shifting, the normally discarded bit is taken and moved to fill the empty spot on the end.




ADDERS

HALF- AND FULL-ADDERS

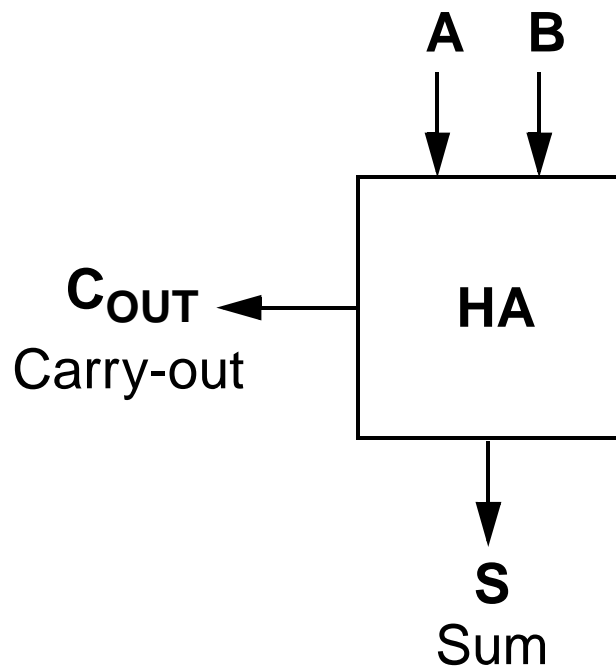- Two basic building blocks for arithmetic are half- and full-adders as depicted by the block diagrams below.



Half-adder

 

Full-adder

ADDERS


HALF-ADDER (HA)

- First of all, how do we add?
- 2's complement arithmetic allows us to add numbers normally.

Inputs		Sum	Carry-out
A	B	S	C _{OUT}
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = \bar{A}B + A\bar{B} = A \oplus B$$

$$C_{OUT} = AB$$

 

ADDERS

FULL-ADDER (FA) (1)

- Half-adder missed a possible carry-in. A full-adder (FA) includes this additional carry-in.

Inputs		Carry-in	Sum	Carry-out
A	B	C _{IN}	S	C _{OUT}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S = (A \oplus B) \oplus C_{IN}$$

$$C_{OUT} = AB + C_{IN}(A \oplus B)$$


ADDERS

FULL-ADDER (FA) (2)

- ADDERS
 - HALF- & FULL-ADDERS
 - HALF-ADDER (HA)
 - FULL-ADDER (FA)

$$S = (A \oplus B) \oplus C_{IN}$$

$$C_{OUT} = AB + C_{IN}(A \oplus B)$$

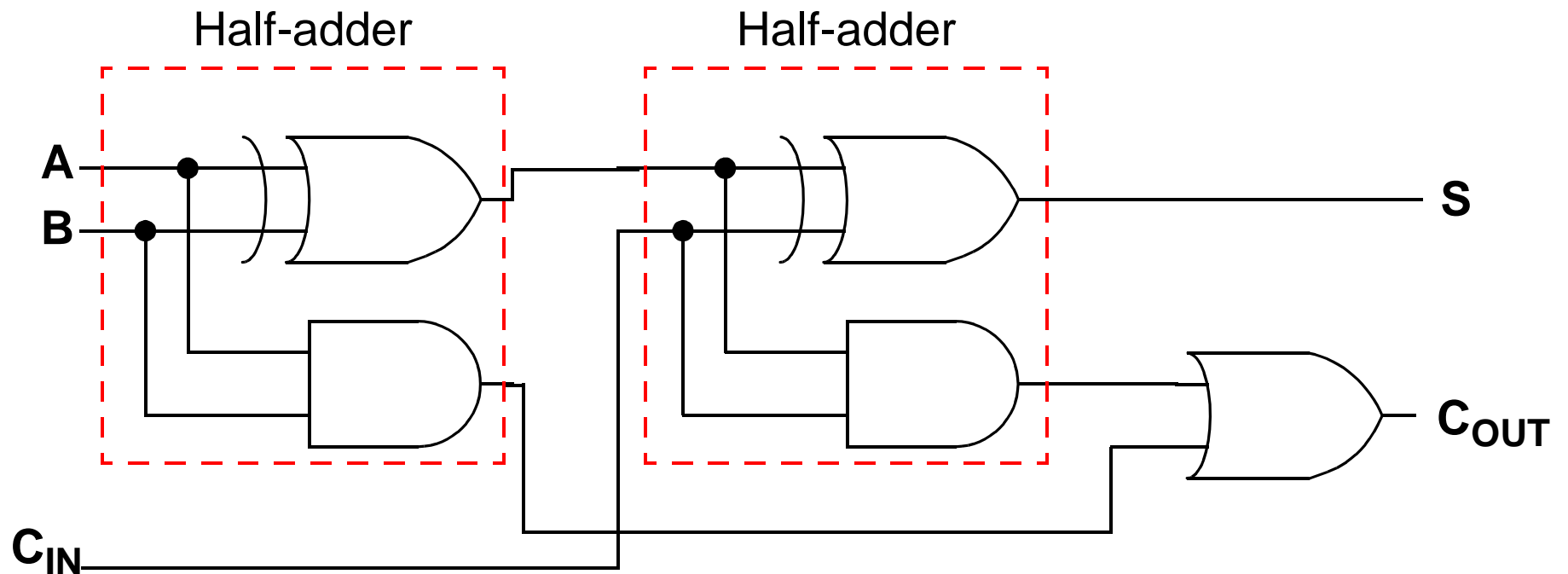


ADDERS

BINARY ADDITION

- ADDERS
 - HALF- & FULL-ADDERS
 - HALF-ADDER (HA)
 - FULL-ADDER (FA)

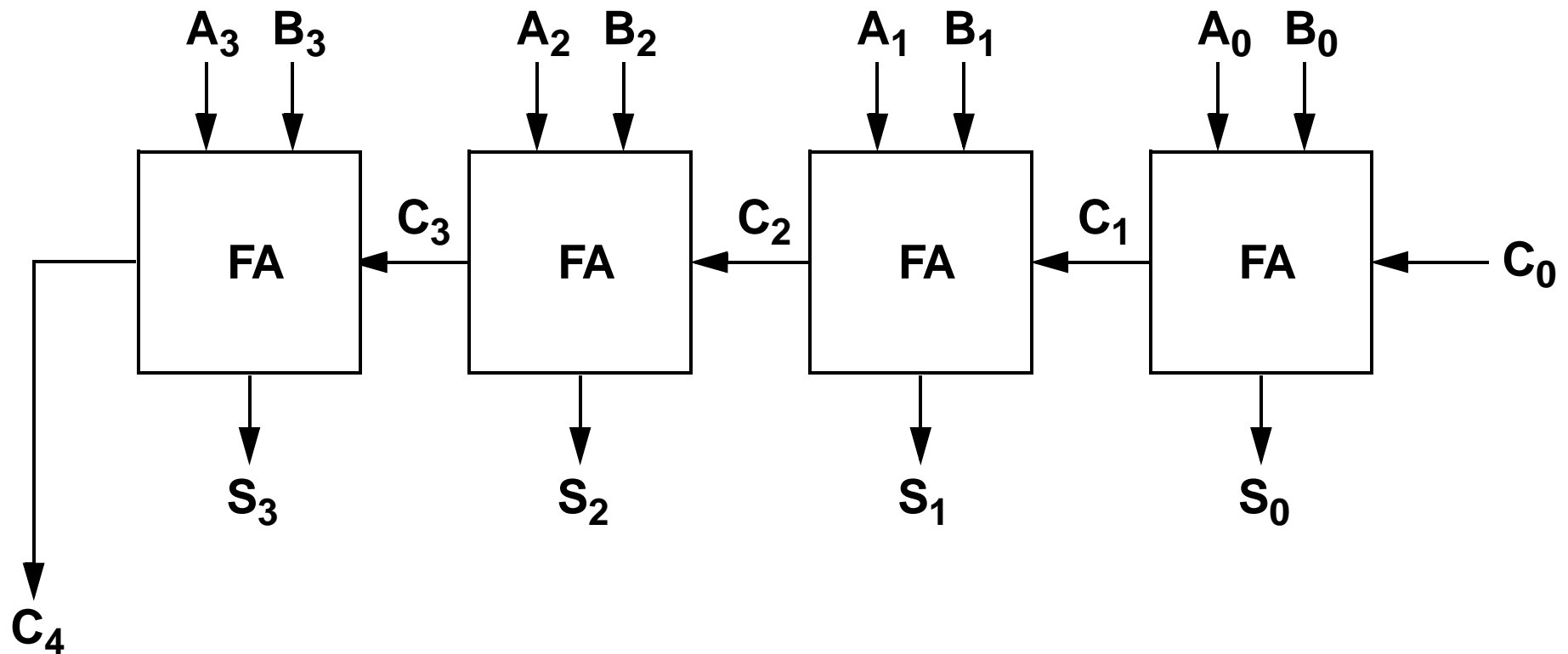
- A 4-bit binary adder can be formed with four full-adders as follows.



COMPARATORS

MAGNITUDE COMPARATOR

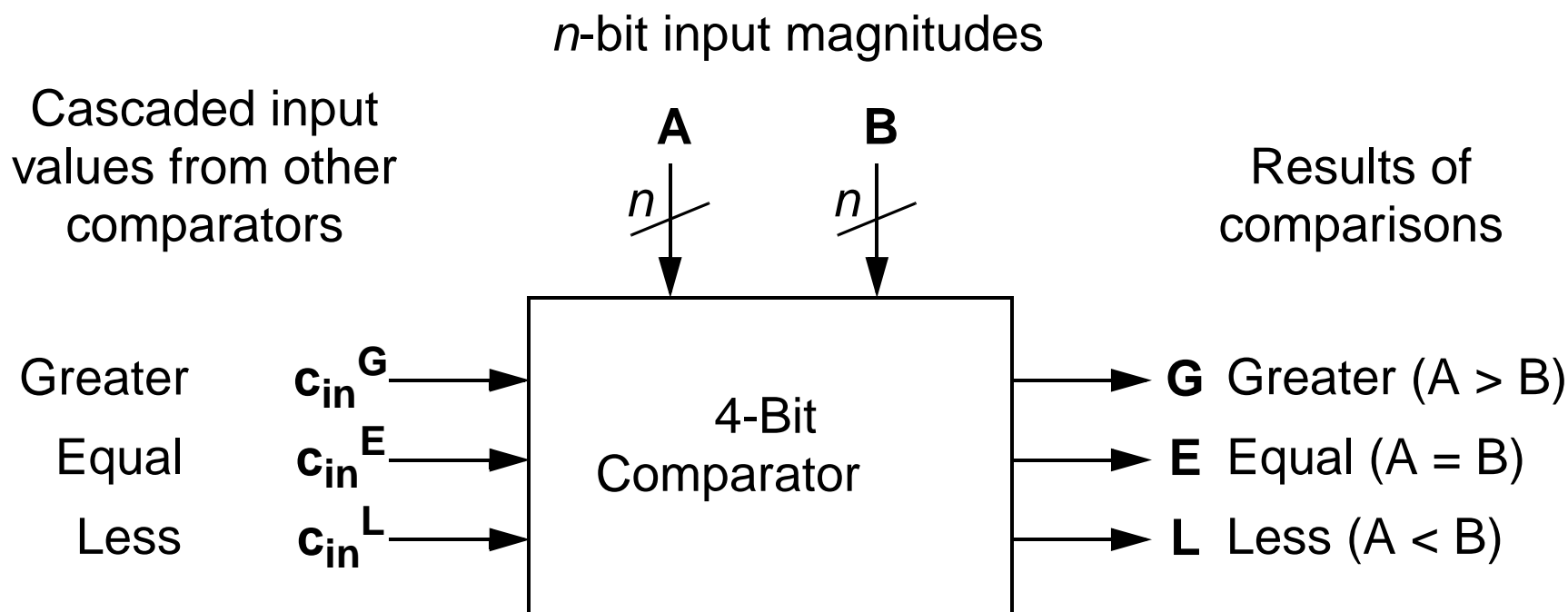- Given two n -bit magnitudes, A and B, a comparator indicates whether
 - $A = B$, $A > B$, or $A < B$



COMPARATORS

MAGNITUDE COMPARATOR

- The approach is to use the XNOR function (equivalence) on each of the n -bits as follows

$$x_i = \mathbf{A}_i \mathbf{B}_i + \overline{\mathbf{A}_i} \overline{\mathbf{B}_i} = \overline{\mathbf{A}_i \oplus \mathbf{B}_i}$$

- The Boolean functions for a 4-bit magnitude comparator is as follows
 - $(\mathbf{A} = \mathbf{B}) = x_3 x_2 x_1 x_0$
 - $(\mathbf{A} > \mathbf{B}) = \mathbf{A}_3 \overline{\mathbf{B}_3} + x_3 \mathbf{A}_2 \overline{\mathbf{B}_2} + x_3 x_2 \mathbf{A}_1 \overline{\mathbf{B}_1} + x_3 x_2 x_1 \mathbf{A}_0 \overline{\mathbf{B}_0}$
 - $(\mathbf{A} < \mathbf{B}) = \overline{\mathbf{A}_3} \mathbf{B}_3 + x_3 \overline{\mathbf{A}_2} \mathbf{B}_2 + x_3 x_2 \overline{\mathbf{A}_1} \mathbf{B}_1 + x_3 x_2 x_1 \overline{\mathbf{A}_0} \mathbf{B}_0$

Note: $\mathbf{A}_i \overline{\mathbf{B}_i}$ indicates whether $\mathbf{A}_i > \mathbf{B}_i$, $\overline{\mathbf{A}_i} \mathbf{B}_i$ indicates whether $\mathbf{A}_i < \mathbf{B}_i$, and x_i indicates whether $\mathbf{A}_i = \mathbf{B}_i$.


BUILDING BLOCKS

PARITY GENERATORS

- A parity generator/checker can detect a 1-bit error in a message.


To generate an even parity bit

$$P = X \oplus Y \oplus Z$$

 

To check a even parity bit

$$C = X \oplus Y \oplus Z \oplus P$$

 

Message			Even	
X	Y	Z	Parity Bit, P	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	0

If no errors detected, **C = 0**