

- 1.5 Given an op amp with $r_d \cong \infty$, $a = 10^4$ V/V, and $r_o \cong 0$, find (a) v_O if $v_P = 750.25$ mV and $v_N = 751.50$ mV, (b) v_N if $v_O = -5$ V and $v_P = 0$, (c) v_P if $v_N = v_O = 5$ V, and (d) v_N if $v_P = -v_O = 1$ V.
- 1.6 A 741 op amp drives a 1-k Ω load. Find the voltages across and the currents through r_d and r_o if $v_P = 1$ V and $v_O = 5$ V.

1.3 Basic op amp configurations

- 1.7 In the noninverting amplifier of Fig. 1.6a, let $R_1 = 100$ k Ω , $R_2 = 200$ k Ω , and $a = \infty$. (a) What is its closed-loop gain? How does its gain change if a third resistance $R_3 = 100$ k Ω is connected in series with R_1 ? In parallel with R_1 ? In series with R_2 ? In parallel with R_2 ? (b) Repeat (a) for the inverting amplifier of Fig. 1.10a.
- 1.8 (a) Design a noninverting amplifier whose gain is variable over the range 1 V/V $\leq A \leq 5$ V/V by means of a 100-k Ω pot. (b) Repeat (a) for 0.5 V/V $\leq A \leq 2$ V/V. *Hint:* To achieve $A \leq 1$ V/V, you need an input voltage divider.
- 1.9 (a) A noninverting amplifier is implemented with two 10-k Ω resistances having 5% tolerance. What is the range of possible values for the gain A ? How would you modify the circuit for the exact calibration of A ? (b) Repeat, but for the inverting amplifier.
- 1.10 In the inverting amplifier of Fig. 1.10a, let $v_I = 0.1$ V, $R_1 = 10$ k Ω , and $R_2 = 100$ k Ω . Find v_O and v_N if (a) $a = 10^2$ V/V, (b) $a = 10^4$ V/V, (c) $a = 10^6$ V/V. Comment on your findings.
- 1.11 (a) Design an inverting amplifier whose gain is variable over the range -10 V/V $\leq A \leq 0$ by means of a 100-k Ω pot. (b) Repeat, but for -10 V/V $\leq A \leq -1$ V/V. *Hint:* To prevent A from reaching zero, you must use a suitable resistor in series with the pot.
- 1.12 (a) A source $v_S = 2$ V with $R_s = 10$ k Ω is to drive a gain-of-five inverting amplifier implemented with $R_1 = 20$ k Ω and $R_2 = 100$ k Ω . Find the amplifier output voltage and verify that because of loading its magnitude is *less* than $2 \times 5 = 10$ V. (b) Find the value to which R_2 must be changed if we want to compensate for loading and obtain a full output magnitude of 10 V.
- 1.13 (a) A source $v_S = 10$ V is fed to a voltage divider implemented with $R_A = 120$ k Ω and $R_B = 30$ k Ω , and the voltage across R_B is fed, in turn, to a gain-of-five noninverting amplifier having $R_1 = 30$ k Ω and $R_2 = 120$ k Ω . Sketch the circuit, and predict the amplifier output voltage v_O . (b) Repeat (a) for a gain-of-five inverting amplifier having $R_1 = 30$ k Ω and $R_2 = 150$ k Ω . Compare and comment on the differences.
- 1.14 An inverting amplifier is implemented with $R_1 = 10$ k Ω , $R_2 = 20$ k Ω and an op amp with $r_d \cong \infty$, $a = 1$ V/mV, and $r_o \cong 0$. Sketch and label v_I , v_O , and v_N versus time if v_I is a 1-kHz sine wave with ± 5 -V peak values.

1.4 Ideal op amp circuit analysis

- 1.15 Find v_N , v_P , and v_O in the circuit of Fig. P1.15, as well as the power released by the 4-V source; devise a method to check your results.

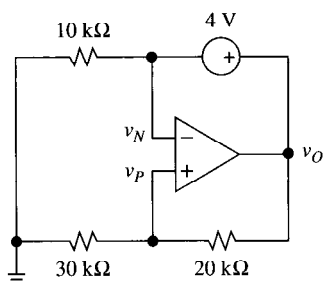


FIGURE P1.15

- 1.16 (a) Find v_N , v_P , and v_O in the circuit of Fig. P1.16. (b) Repeat (a) with a 5-k Ω resistance connected between A and B.

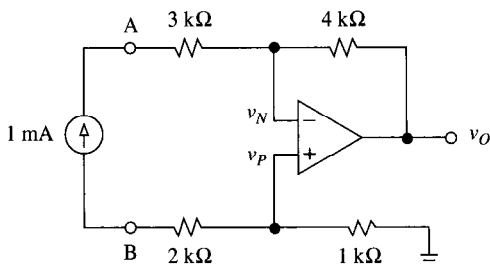


FIGURE P1.16

- 1.17 (a) Find v_N , v_P , and v_O in the circuit of Fig. P1.17 if $v_S = 9$ V. (b) Find the resistance R that, if connected between the inverting-input pin of the op amp and ground, causes v_O to double. Verify with PSpice.

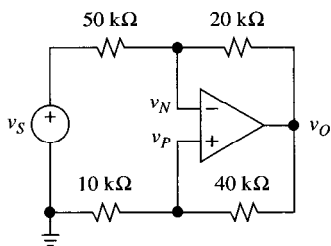


FIGURE P1.17

- 1.18 (a) Find v_N , v_P , and v_O in the circuit of Fig. P1.18. (b) Repeat (a) with a 40-k Ω resistance in parallel with the 0.3-mA source.

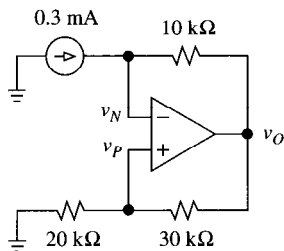


FIGURE P1.18

- 1.19** (a) Find v_N , v_P , and v_O in the circuit of Fig. P1.19 if $i_S = 1$ mA. (b) Find a resistance R that when connected in parallel with the 1-mA source will cause v_O to drop to half the value found in (a).

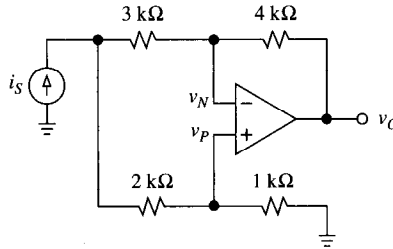


FIGURE P1.19

- 1.20** (a) If the current source of Fig. P1.16 is replaced by a voltage source v_S , find the magnitude and polarity of v_S so that $v_O = 10$ V. (b) If the wire connecting the 4-V source to node v_O in Fig. P1.15 is cut and a 5-kΩ resistance is inserted in series between the two, to what value must the source be changed to yield $v_O = 10$ V?
- 1.21** In the circuit of Fig. P1.21 the switch is designed to provide gain-polarity control. (a) Verify that $A = +1$ V/V when the switch is open, and $A = -R_2/R_1$ when the switch is closed, so that making $R_1 = R_2$ yields $A = \pm 1$ V/V. (b) To accommodate gains greater than unity, connect an additional resistance R_4 from the inverting-input pin of the op amp to ground. Derive separate expressions for A in terms of R_1 through R_4 with the switch open and with the switch closed. (c) Specify resistance values suitable for achieving $A = \pm 2$ V/V.

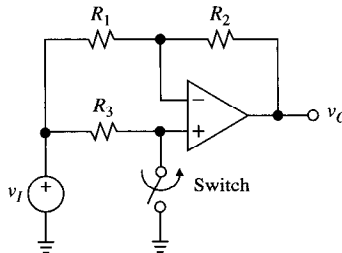


FIGURE P1.21

- 1.22** In the circuit of Fig. P1.22 the pot is used to control gain magnitude as well as polarity. (a) Letting k denote the fraction of R_3 between the wiper and ground, show that varying the wiper from bottom to top varies the gain over the range $-R_2/R_1 \leq A \leq 1$ V/V, so that making $R_1 = R_2$ yields -1 V/V $\leq A \leq +1$ V/V. (b) To accommodate gains greater than unity, connect an additional resistance R_4 from the op amp's inverting-input pin to ground. Derive an expression for A in terms of R_1 , R_2 , R_4 , and k . (c) Specify resistance values suitable for achieving -5 V/V $\leq A \leq +5$ V/V.

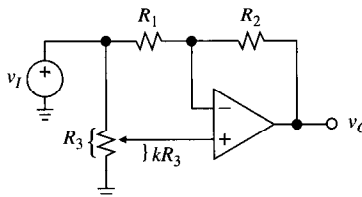


FIGURE P1.22

1.23 Consider the following statements about the input resistance R_i of the noninverting amplifier of Fig. 1.14a: (a) Since we are looking straight into the noninverting-input pin, which is an open circuit, we have $R_i = \infty$; (b) since the input pins are virtually shorted together, we have $R_i = 0 + (R_1 \parallel R_2) = R_1 \parallel R_2$; (c) since the noninverting-input pin is virtually shorted to the inverting-input pin, which is in turn a virtual-ground node, we have $R_i = 0 + 0 = 0$. Which statement is correct? How would you refute the other two?

1.24 (a) Show that the circuit of Fig. P1.24 has $R_i = \infty$ and $A = -(1 + R_3/R_4)R_1/R_2$. (b) Specify suitable components to make A variable over the range $-100 \text{ V/V} \leq A \leq 0$ by means of a 100-k Ω pot. Try minimizing the number of resistors you use.

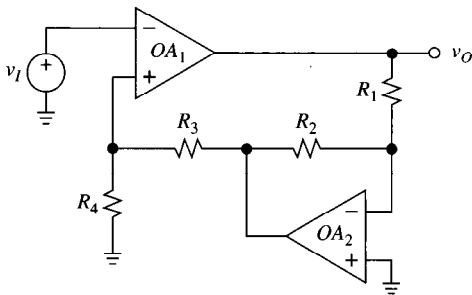


FIGURE P1.24

1.25 The audio panpot circuit of Fig. P1.25 is used to continuously vary the position of signal v_I between the left and the right stereo channels. (a) Discuss circuit operation. (b) Specify R_1 and R_2 so that $v_L/v_I = -1 \text{ V/V}$ when the wiper is fully down, $v_R/v_I = -1 \text{ V/V}$ when the wiper is fully up, and $v_L/v_I = v_R/v_I = -1/\sqrt{2}$ when the wiper is halfway.

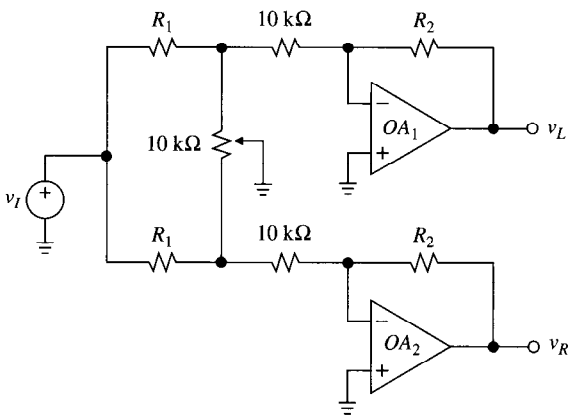


FIGURE P1.25

1.26 (a) Using standard 5% resistances in the kilohm range, design a circuit to yield $v_O = -100(4v_1 + 3v_2 + 2v_3 + v_4)$. (b) If $v_1 = 20 \text{ mV}$, $v_2 = -50 \text{ mV}$, and $v_4 = 100 \text{ mV}$, find v_3 for $v_O = 0 \text{ V}$.

1.27 (a) Using standard 5% resistances, design a circuit to give (a) $v_O = -10(v_I + 1 \text{ V})$; (b) $v_O = -v_I + V_O$, where V_O is variable over the range $-5 \text{ V} \leq V_O \leq +5 \text{ V}$ by means of a 100-k Ω pot. *Hint:* Connect the pot between the $\pm 15\text{-V}$ supplies and use the wiper voltage as one of the inputs to your circuit.

- 1.28** In the circuit of Fig. 1.17 let $R_1 = R_3 = R_4 = 10 \text{ k}\Omega$ and $R_2 = 30 \text{ k}\Omega$. (a) If $v_1 = 3 \text{ V}$, find v_2 for $v_O = 10 \text{ V}$. (b) If $v_2 = 6 \text{ V}$, find v_1 for $v_O = 0 \text{ V}$. (c) If $v_1 = 1 \text{ V}$, find the range of values for v_2 for which $-10 \text{ V} \leq v_O \leq +10 \text{ V}$.
- 1.29** You can readily verify that if we put the output in the form $v_O = A_2 v_2 - A_1 v_1$ in the circuit of Fig. 1.17, then $A_2 \leq A_1 + 1$. Applications requiring $A_2 \geq A_1 + 1$ can be accommodated by connecting an additional resistance R_5 from the node common to R_1 and R_2 to ground. (a) Sketch the modified circuit and derive a relationship between its output and inputs. (b) Specify standard resistances to achieve $v_O = 5(2v_2 - v_1)$. Try minimizing the number of resistors you use.
- 1.30** (a) In the difference amplifier of Fig. 1.17 let $R_1 = R_3 = 10 \text{ k}\Omega$ and $R_2 = R_4 = 100 \text{ k}\Omega$. Find v_O if $v_1 = 10 \cos 2\pi 60t - 0.5 \cos 2\pi 10^3t \text{ V}$, and $v_2 = 10 \cos 2\pi 60t + 0.5 \cos 2\pi 10^3t \text{ V}$. (b) Repeat if R_4 is changed to $101 \text{ k}\Omega$. Comment on your findings.
- 1.31** Show that if all resistances in Fig. P1.31 are equal, then $v_O = v_2 + v_4 + v_6 - v_1 - v_3 - v_5$.

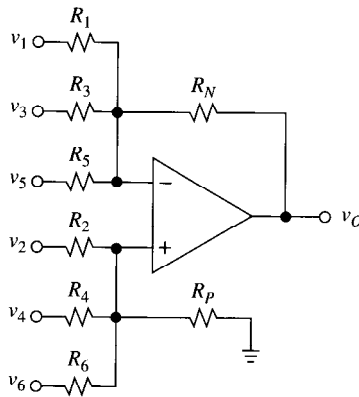


FIGURE P1.31

- 1.32** Using a topology of the type of Fig. P1.31, design a four-input amplifier such that $v_O = 4v_A - 3v_B + 2v_C - v_D$. Try minimizing the number of resistors you use.
- 1.33** Using just one op amp powered from $\pm 12\text{-V}$ regulated supplies, design a circuit to yield: (a) $v_O = 10v_I + 5 \text{ V}$; (b) $v_O = 10(v_2 - v_1) - 5 \text{ V}$.
- 1.34** Using just one op amp powered from $\pm 15\text{-V}$ supply voltages, design a circuit that accepts an ac input v_i and yields $v_O = v_i + 5 \text{ V}$, under the constraint that the resistance seen by the ac source be $100 \text{ k}\Omega$.
- 1.35** Design a two-input, two-output circuit that yields the sum and the difference of its inputs: $v_S = v_{I1} + v_{I2}$, and $v_D = v_{I1} - v_{I2}$. Try minimizing the component count.
- 1.36** Obtain a relationship between v_O and v_I if the differentiator of Fig. 1.18 includes also a resistance R_i in series with C . Discuss the extreme cases of v_I changing very slowly and very rapidly.
- 1.37** Obtain a relationship between v_O and v_I if the integrator of Fig. 1.19 includes also a resistance R_p in parallel with C . Discuss the extreme cases of v_I changing very rapidly and very slowly.

- 1.36** Obtain a relationship between v_O and v_I if the differentiator of Fig. 1.18 includes also a resistance R_s in series with C . Discuss the extreme cases of v_I changing very slowly and very rapidly.
- 1.37** Obtain a relationship between v_O and v_I if the integrator of Fig. 1.19 includes also a resistance R_p in parallel with C . Discuss the extreme cases of v_I changing very rapidly and very slowly.
- 1.38** In the differentiator of Fig. 1.18 let $C = 10 \text{ nF}$ and $R = 100 \text{ k}\Omega$, and let v_I be a periodic signal alternating between 0 V and 2 V with a frequency of 100 Hz. Sketch and label v_I and v_O versus time if v_I is (a) a sine wave; (b) a triangular wave.
- 1.39** In the integrator of Fig. 1.19 let $R = 100 \text{ k}\Omega$ and $C = 10 \text{ nF}$. Sketch and label $v_I(t)$ and $v_O(t)$ if (a) $v_I = 5 \sin 2\pi 100t \text{ V}$ and $v_O(0) = 0$; (b) $v_I = 5[u(t) - u(t - 2 \text{ ms})] \text{ V}$ and $v_O(0) = 5 \text{ V}$, where $u(t - t_0)$ is the unit step function defined as $u = 0$ for $t < t_0$, and $u = 1$ for $t > t_0$.
- 1.40** (a) In the integrator of Fig. 1.19 let $R = 10 \text{ k}\Omega$ and $C = 0.1 \text{ }\mu\text{F}$. Assuming that C is initially discharged, sketch and label $v_O(t)$ for $0 \leq t \leq 10 \text{ ms}$ if v_I is a 1-V step. (b) Repeat (a) with a 100-k Ω resistance connected in parallel with C .
- 1.41** If R_F in the summing amplifier of Fig. 1.15 is replaced by a capacitance C , the circuit becomes a *summing integrator*. (a) Derive a relationship between its output and its inputs. (b) Using a 10-nF capacitance, specify suitable resistances for $v_O(t) = v_O(0) - 10^3(\int_0^t v_1 d\xi + 2\int_0^t v_2 d\xi + 0.5\int_0^t v_3 d\xi)$.
- 1.42** Show that if the op amp of Fig. 1.20b has a finite gain a , then $R_{\text{eq}} = (-R_1 R / R_2) \times [1 + (1 + R_2 / R_1) / a] / [1 - (1 + R_1 / R_2) / a]$.
- 1.43** Find an expression for R_i in Fig. P1.43; discuss its behavior as R is varied over the range $0 \leq R \leq 2R_1$.

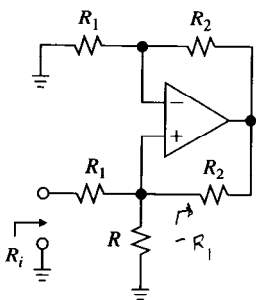



FIGURE P1.43

- 1.44** The circuit of Fig. P1.44 can be used to control the input resistance of the inverting amplifier based on OA_1 . (a) Show that $R_i = R_1 / (1 - R_1 / R_3)$. (b) Specify resistances suitable for achieving $A = -10 \text{ V/V}$ with $R_i = \infty$.

1.5 Negative feedback

- 1.45** A voltage amplifier has $a = 10^5 \text{ V/V}$ and $v_i = 10 \text{ mV}$. Find v_d , v_f , v_o , A , T , and the percentage deviation of A from A_{ideal} for $\beta = 10^{-3} \text{ V/V}$, 10^{-2} V/V , 10^{-1} V/V , and 1 V/V . Compare the various cases and comment.

FIGURE P1.44

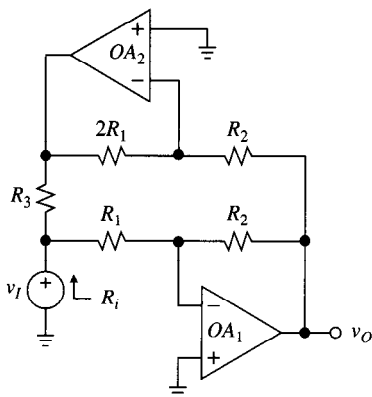

- 1.46** (a) Find the desensitivity factor of a negative-feedback system with $a = 10^3$ and $A = 10^2$. (b) Find A exactly via Eq. (1.40), and approximately via Eq. (1.49) if a drops by 10%. (c) Repeat (b) for a 50% drop in a ; compare with (b) and comment.
- 1.47** You are asked to design an amplifier with a gain A of 10^2 V/V that is accurate to within $\pm 0.1\%$, or $A = 10^2$ V/V $\pm 0.1\%$. All you have available are amplifier stages with $a = 10^4$ V/V $\pm 25\%$ each. Your amplifier can be implemented using a cascade of basic stages, each employing a suitable amount of negative feedback. What is the minimum number of stages required? What is the β of each stage?
- 1.48** The open-loop VTC of a certain amplifier can be approximated piecewise by five segments with symmetric breakpoints at $(v_D, v_O) = \pm(80 \mu\text{V}, 8 \text{ V})$, $\pm(280 \mu\text{V}, 12 \text{ V})$, and $\pm(530 \mu\text{V}, 13 \text{ V})$. (a) Sketch the above VTC; calculate and sketch the closed-loop VTC when the amplifier is placed in a feedback loop with $\beta = 0.5$ V/V. (b) Sketch v_I , v_O , and v_D versus time if v_I is a triangular wave with ± 5 -V peak values; comment on the waveform of v_D . *Hint:* $v_D(t)$ can be derived point by point from $v_O(t)$ using the open-loop VTC of (a).
- 1.49** A crude BJT power amplifier of the class B (push-pull) type exhibits the VTC of Fig. P1.49b. The dead band occurring for $-0.7 \text{ V} \leq v_1 \leq +0.7 \text{ V}$ causes a crossover distortion at the output that can be reduced by preceding the power stage with a preamplifier stage and then using negative feedback to reduce the dead band. This is shown in Fig. P1.49a for the case of a difference preamplifier with gain a_1 and $\beta = 1$ V/V. (a) Sketch and label the closed-loop VTC if $a_1 = 10^2$ V/V. (b) Sketch v_I , v_1 , and v_O versus time if v_I is a 100-Hz triangular wave with peak values of ± 1 V.
- 1.50** A certain audio power amplifier with a signal gain of 10 V/V is found to produce a 2-V peak-to-peak 120-Hz hum. We wish to reduce the output hum to less than 1 mV without changing the signal gain. To this end, we precede the power stage with a preamplifier stage with gain a_1 and then apply negative feedback around the composite amplifier. What are the required values of a_1 and β ?

1.6 Feedback in op amp circuits

- 1.51** A voltage follower is implemented with an op amp having $r_d = 1 \text{ M}\Omega$, $a = 1 \text{ V/mV}$, and $r_o = 1 \text{ k}\Omega$. (a) Find v_O if the follower is driven by a source $v_S = 10.000 \text{ V}$ with $R_S = 2 \text{ M}\Omega$. (b) Repeat (a) with a 1-k Ω output load.