

EXAMINATION NO. 2 - SOLUTIONS

(Average Score = 70/100)

Problem 1 - (25 points)

A CMOS op amp is shown. All W/L values of all transistors are $10\mu\text{m}/1\mu\text{m}$. Assume that $K_N' = 110\mu\text{A}/\text{V}^2$, $K_P' = 50\mu\text{A}/\text{V}^2$, $V_{TN} = 0.7\text{V}$, $V_{TP} = -0.7\text{V}$, $\lambda_N = 0.04\text{V}^{-1}$, and $\lambda_P = 0.05\text{V}^{-1}$. Find the low frequency differential voltage gain, v_{out}/v_{in} , the gainbandwidth, GB , the slew rate, SR , and the power dissipation, P_{diss} if $V_{DD} = 2\text{V}$.

Solution

The small-signal voltage gain can be expressed as,

$$\frac{v_{out}}{v_{in}} = g_{m1}R_{out} = g_{m2}R_{out}^*$$

where $R_{out} \approx [g_{m7}r_{ds7}(r_{ds4} \parallel r_{ds8})] \parallel [g_{m6}r_{ds6}(r_{ds2} \parallel r_{ds5})]$

Evaluating the small signal parameters,

$$g_{m1} = g_{m2} = \sqrt{2 \cdot 110 \cdot 10 \cdot 50} = 331.7\mu\text{S}, r_{ds1} = r_{ds2} = (25/50)\text{M}\Omega = 0.5\text{M}\Omega$$

$$g_{m6} = \sqrt{2 \cdot 50 \cdot 10 \cdot 100} = 316.2\mu\text{S}, r_{ds6} = (20/100)\text{M}\Omega = 0.2\text{M}\Omega$$

$$r_{ds5} = (20/150)\text{M}\Omega = 0.133\text{M}\Omega, r_{ds4} = (20/50)\text{M}\Omega = 0.4\text{M}\Omega$$

$$g_{m7} = \sqrt{2 \cdot 110 \cdot 10 \cdot 100} = 469\mu\text{S}, r_{ds7} = (25/100)\text{M}\Omega = 0.25\text{M}\Omega$$

$$r_{ds8} = (25/150)\text{M}\Omega = 0.167\text{M}\Omega$$

$$\begin{aligned} \therefore R_{out} &\approx [469 \cdot 0.25(0.4 \parallel 0.167)] \parallel [316.2 \cdot 0.2(0.5 \parallel 0.133)]\text{M}\Omega \\ &= (13.796 \parallel 6.644)\text{M}\Omega = 4.484\text{M}\Omega \end{aligned}$$

$$\frac{v_{out}}{v_{in}} = 331.7 \cdot 4.484 = \underline{1487 \text{ V/V}}$$

$$GB = \frac{g_{m1}}{C_L} = \frac{331.7 \times 10^{-6}}{5 \times 10^{-12}} = 66.33 \times 10^6 \rightarrow \underline{10.56\text{MHz}}$$

$$SR = \frac{100\mu\text{A}}{C_L} = \frac{100 \times 10^{-6}}{5 \times 10^{-12}} = \underline{20\text{V}/\mu\text{s}}$$

$$P_{diss} = 2(50\mu\text{A} + 50\mu\text{A} + 150\mu\text{A}) = \underline{500\mu\text{W}}$$

* This expression ignores the fact that about half the signal is lost due to the input resistances at the sources of M6 and M7 are at an r_{ds} level.

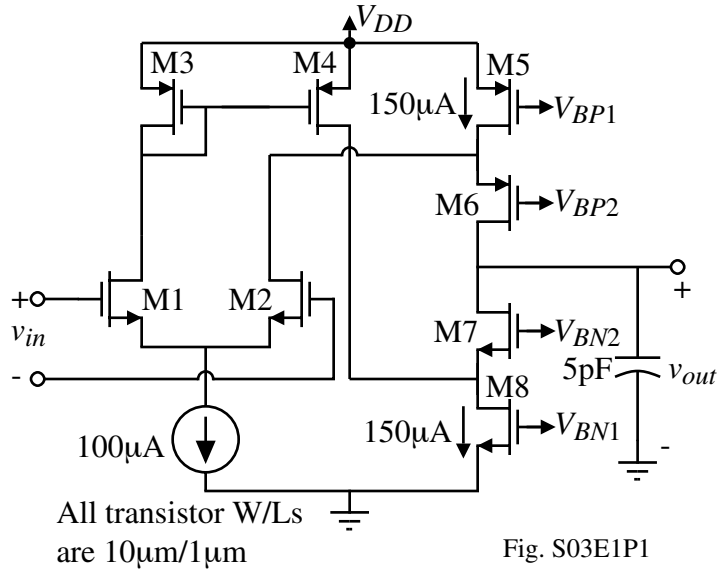


Fig. S03E1P1

Problem 2 - (25 points)

A two-stage, Miller compensated op amp has the following values: $g_{mI} = 100\mu\text{S}$, $g_{mII} = 1000\mu\text{S}$, $C_c = 2\text{pF}$, and $C_L = 10\text{pF}$.

- What value of nulling resistor, R_z , will cancel the output pole?
- If the output capacitance of the first stage is $C_I = 1\text{pF}$, what is the phase margin in part a.) if R_z is $5\text{k}\Omega$.
- If C_L is increased to 20pF and $R_z = 5\text{k}\Omega$, what is the new phase margin?

Solution

a.) The zero is given as $z = \frac{1}{C_c \left(\frac{1}{g_{mII}} - R_z \right)}$ and the output pole is $p_2 = -\frac{g_{mII}}{C_c}$. Equating

these two roots gives,

$$R_z = \frac{1}{g_{mII}} \left(\frac{C_L + C_c}{C_c} \right) = \frac{1}{1000\mu\text{S}} \left(\frac{12}{2} \right) = \underline{\underline{6\text{k}\Omega}}$$

b.) The pole due to R_z is

$$p_4 = -\frac{1}{R_z C_I} = -\frac{1}{5\text{k}\Omega \cdot 1\text{pF}} = -2 \times 10^8 \text{ rads/sec.}$$

Also, the GB is

$$GB = \frac{g_{mI}}{C_c} = \frac{100\mu\text{S}}{2\text{pF}} = 50 \times 10^6 \text{ rads/sec.}$$

The phase margin is,

$$PM = 180^\circ - 90^\circ - \tan^{-1} \left(\frac{GB}{|p_4|} \right) = 90^\circ - \tan^{-1} \left(\frac{50}{200} \right) = 90^\circ - 14^\circ = \underline{\underline{76^\circ}}$$

(You were intended to assume that z_1 still cancels p_2 . If you did assume this, the answer is 71.2° and you were given full credit.)

c.) The new phase margin is,

$$PM = 180^\circ - 90^\circ + \tan^{-1} \left(\frac{GB}{|p_2|} \right) - \tan^{-1} \left(\frac{2GB}{|p_2|} \right) - \tan^{-1} \left(\frac{GB}{|p_4|} \right)$$

$$z_1 = -\frac{g_{mII}}{C_L} = -\frac{1000\mu\text{S}}{10\text{pF}} = -100 \times 10^6 \text{ rads/sec.}$$

$$p_2 = -\frac{g_{mII}}{C_c} = -\frac{1000\mu\text{S}}{2\text{pF}} = -50 \times 10^6 \text{ rads/sec.}$$

$$\therefore PM = 90^\circ + \tan^{-1} \left(\frac{50}{50} \right) - \tan^{-1} \left(\frac{100}{50} \right) - \tan^{-1} \left(\frac{50}{200} \right) = 90^\circ + 43^\circ - 63.43^\circ - 14^\circ = \underline{\underline{57.52^\circ}}$$

(Again, you were intended to assume that z_1 is at the old value of p_2 . If you did assume this, the answer is 52.8° and you were given full credit.)

Problem 3 - (25 points)

For the CMOS op amp shown, assume the model parameters for the transistors are $K_N' = 110\mu\text{A}/\text{V}^2$, $K_P' = 50\mu\text{A}/\text{V}^2$, $V_{TN} = 0.7\text{V}$, $V_{TP} = -0.7\text{V}$, $\lambda_N = 0.04\text{V}^{-1}$, and $\lambda_P = 0.05\text{V}^{-1}$. Let all transistor lengths be $1\mu\text{m}$ and design the widths of every transistor and the dc currents I_5 and I_7 to satisfy the following specifications:


$$\text{Slew rate} = 10\text{V}/\mu\text{s}$$

$$+\text{ICMR} = 0.8\text{V}$$

$$-\text{ICMR} = 0\text{V}$$

$$\text{GB} = 10\text{MHz}$$

$$\text{Phase margin} = 60^\circ \quad (g_{mII} = 10g_{mI} \text{ and } V_{SG4} = V_{SG6})$$

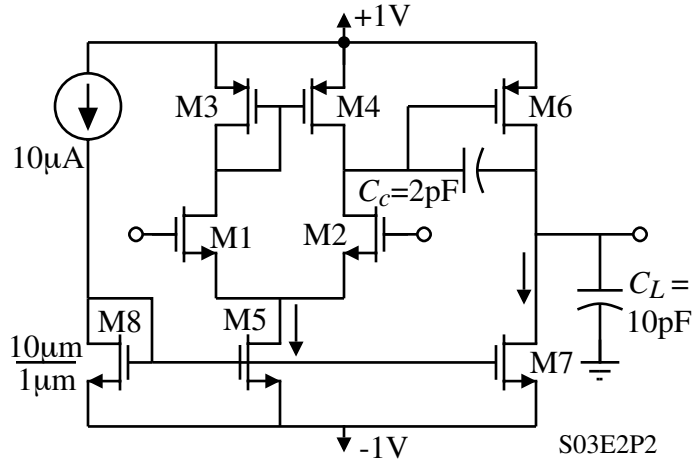Solution

$$\text{Slew rate} \rightarrow I_5 = SR \cdot C_L = 10\text{V}/\mu\text{s} \cdot 10\text{pF} = \underline{20\mu\text{A}} \rightarrow W_5 = 20\mu\text{m} \text{ (check } -\text{ICMR} \text{ later)}$$

$$+\text{ICMR} \rightarrow 0.8 = 1 - V_{SG3} + 0.7 \rightarrow V_{SG3} = 0.9 \rightarrow V_{SD3}(\text{sat}) = 0.2\text{V}$$

$$\frac{W_3}{L_3} = \frac{W_4}{L_4} = \frac{2I_3}{K_P(V_{SD3}(\text{sat}))^2} = \frac{2 \cdot 10}{50(0.2)^2} = 10 \rightarrow W_3 = W_4 = \underline{10\mu\text{m}}$$

$$\text{GB} \rightarrow \frac{g_{mI}}{C_c} = \text{GB} \rightarrow g_{mI} = \text{GB} \cdot C_c = 20\pi \times 10^6 \cdot 2 \times 10^{-12} = 40\pi \mu\text{S}$$

$$g_{mI} = \sqrt{2K_N \frac{W_1}{L_1} I_1} \rightarrow g_{mI}^2 = 2K_N \frac{W_1}{L_1} I_1 \rightarrow \frac{W_1}{L_1} = \frac{g_{mI}^2}{2K_N I_1} = \frac{(40\pi)^2}{2 \cdot 110 \cdot 10} = 7.17$$

$$W_1 = W_2 = \underline{7.17\mu\text{m}}$$

$$-\text{ICMR} \rightarrow 0 = V_{GS1} + V_{DS5}(\text{sat}) - 1 \rightarrow V_{DS5}(\text{sat}) = 1 - V_{GS1} = 1 - \sqrt{\frac{2I_1}{K_N(W_1/L_1)}} - V_{TN}$$

$$V_{DS5}(\text{sat}) = 1 - \sqrt{\frac{20}{110 \cdot 7.17}} + 0.7 = 1 - 0.859 = 0.141\text{V}$$

$$\frac{W_5}{L_5} = \frac{2I_5}{K_N(V_{DS5}(\text{sat}))^2} = \frac{2 \cdot 10}{110(0.141)^2} = 18.29 \rightarrow W_5 = 18.29\mu\text{m} \rightarrow W_5 = \underline{20\mu\text{m}}$$

$$60^\circ \text{ phase margin} \rightarrow g_{m6} = 10 g_{mI} = 400\pi \mu\text{S}$$

$$\text{Also, } g_{m4} = \sqrt{2 \cdot 50 \cdot 10 \cdot 10} = 100\mu\text{S} \rightarrow W_6 = \frac{400\pi}{100} \cdot 10 = 40\pi = \underline{125.66 \mu\text{m}}$$

$$I_6 = \frac{g_{m6}^2}{2K_P(W_6/L_6)} = \frac{(400\pi)^2}{100 \cdot 125.66} = \underline{125.66\mu\text{A}}$$

$$W_7 = W_5 \frac{I_6}{I_5} = 20 \frac{125.66}{20} = \underline{125.66\mu\text{m}}$$

Problem 4 - (25 points)

a) $RI_{C9} = V_T \ln(I_{C8}/I_{C9})$

$$I_{C8} = (20V - 1.4V) / 50k\Omega = 0.372mA$$

$$I_{C9} = 20\mu A \rightarrow R = 3.8k\Omega$$

b) $G_{mI} = \frac{g_{m4}}{1 + g_{m4}r_{e2}} = \frac{g_{m4}}{2} = 0.1923 \times 10^{-3} \frac{A}{V}$ note that: $r_{e2} = \frac{1}{g_{m2}} = \frac{1}{g_{m4}}$

$$R_I = r_{07} \parallel r_{04}(1 + g_{m4} \times r_{e2}) = r_{07} \parallel 2r_{04} = 5.65M\Omega \quad \text{because: } r_{07} = \frac{V_A}{I_7} = 13M\Omega \quad \text{and} \quad r_{04} = 5l$$

$$G_{mII} = \frac{g_{m14}}{1 + g_{m14}R_2} = 0.23 \times 10^{-3} \frac{A}{V} \quad \text{note that: } g_{m14} = \sqrt{2\mu C_{ox} \left(\frac{W}{L}\right)_{14} I_{M14}} = 0.424 \times 10^{-3} \frac{A}{V}$$

$$R_{II} = r_{ds14}(1 + g_{m14} \times R_2) \parallel r_{013}(1 + g_{m13} \times R_3) = 1.848M\Omega \parallel 1.13M\Omega = 0.7M\Omega$$

$$A_v = G_{mI} R_I G_{mII} R_{II} \cong 175,000$$

c) $GBW = \frac{G_{mI}}{C_C} \Rightarrow C_C = \frac{G_{mI}}{GBW} = 15.3pF$

d) $\Phi_M = 90^\circ - \tan^{-1}\left(\frac{2MHz}{p_2}\right) - \tan^{-1}\left(\frac{2MHz}{z}\right)$

$$p_2 = \frac{G_{mII}}{C_L} = \frac{0.23 \times 10^{-3}}{5 \times 10^{-12}} = 46 \times 10^6 \text{ rad/sec}$$

$$z = \frac{G_{mI}}{C_C} = \frac{0.23 \times 10^{-3}}{15.3 \times 10^{-12}} = 15.03 \times 10^6 \text{ rad/sec}$$

$$\Rightarrow \Phi_M = 90^\circ - \tan^{-1}\left(\frac{2 \times 2\pi}{46}\right) - \tan^{-1}\left(\frac{2 \times 2\pi}{15.03}\right) = 90^\circ - 15.27^\circ - 39.89^\circ = 34.83^\circ$$